

~~214~~

219

3

-: HAND WRITTEN NOTES:-
OF

ELECTRICAL ENGINEERING

①

-: SUBJECT:-

POWER ELECTRONICS

3

TOPICS

1. Power semiconductor devices - 25%
2. Phase controlled rectifiers - 35%
Application → DC drives
→ Charging batteries
→ Solar batteries
3. Inverters - 12%
4. Choppers - 12-15%
5. AC Voltage controllers & cycloconverters - 3 to 4%
6. Other applications - 7-10%
→ AC Drives
→ HVDC
→ SMPS

3

Power Electronics - deals with control & conversion of high power applications.

Power Semiconductor devices - should be capable to handle large magnitudes of power.

eg Power diode, SCR (PA), LASCR, GTO, ASCR, & RCT, TRIAC, DIAC, Power transistors (BJT, MOSFET, IGBT, $f \uparrow$)

Signal Electronics - deals with control of low power applications.

Signal Devices - handle low power & very high switching frequencies.

eg Signal diodes → Zener diode
→ LEDs
→ Varactor diode

Signal transistors → BJT
→ MOSFET
→ UJT etc.

* In the fabrication of semiconductor devices we must sacrifice one quality in order to improve the other quality.


eg If the device operates at very high switching frequency the power rating is reduced.

* A switch can be utilized in 4 different modes but all the devices need not operate in all the 4 modes.


* FOUR MODES OF A SWITCH (Ideal)

1. Forward Blocking Mode


(5)

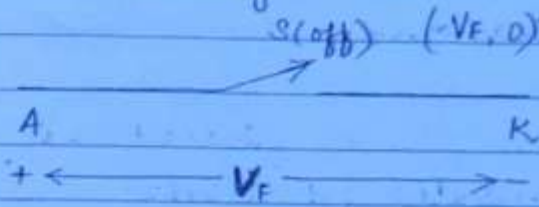



2. Forward Conduction Mode

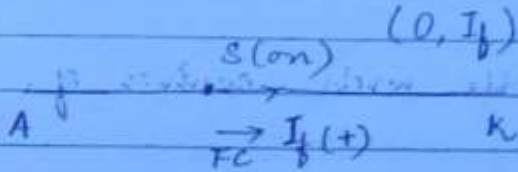

3. Reverse Blocking Mode

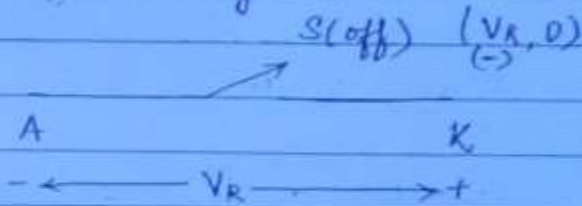

4. Reverse Conduction Mode

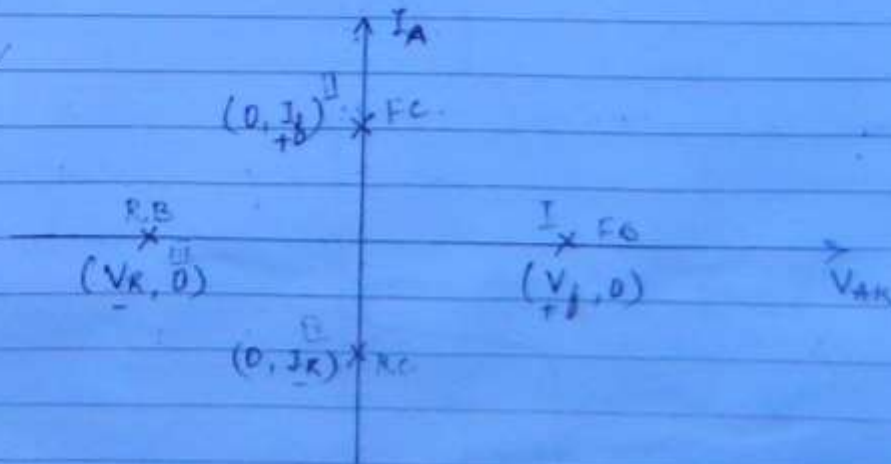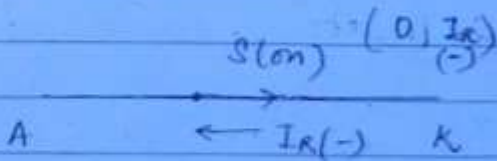


* TRIAC will support all four modes of operation.
 ∴ It is treated as an AC switch. (AC → AC)


Applications → AC voltage controller (6)

* SCR is a DC switch because it will not support reverse conduction.


POWER DIODE -

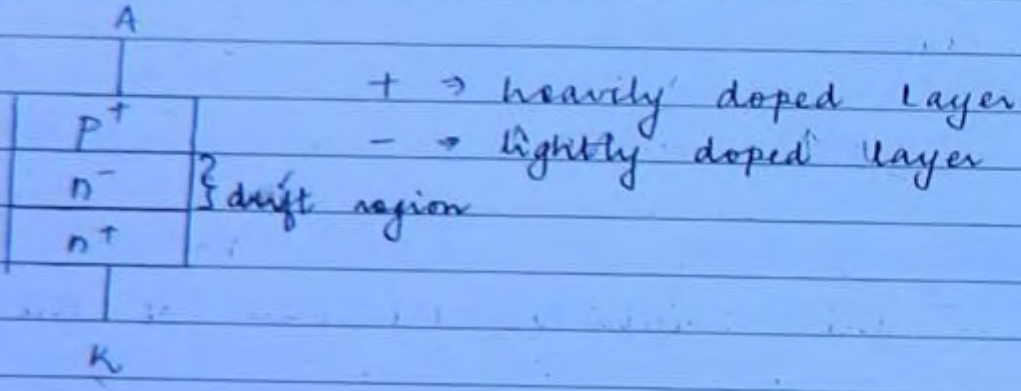


Signal Diode -

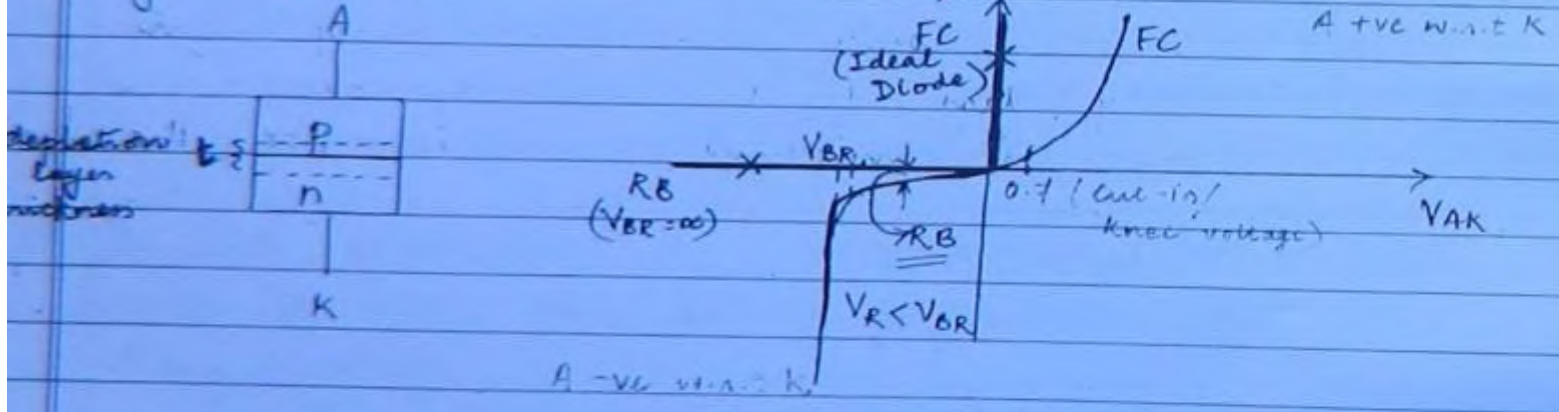

Power Diode -

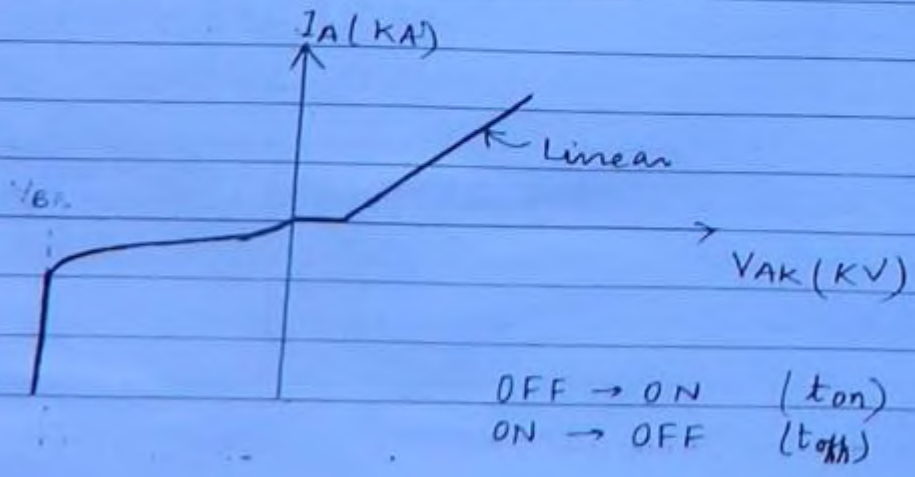

Significance of drift region -

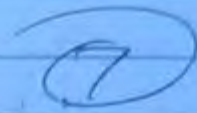


- * The thickness of the depletion layer decides the reverse blocking voltage capability.
- * The thickness of the depletion layer \uparrow due to the n^- region (depletion layer penetrates more deeper into the lightly doped layer to equilibrate the charge) this \uparrow the reverse blocking capability of the diode.

reverse bias \rightarrow $V_{R1} \uparrow$

REVERSE RECOVERY CHARACTERISTICS -

- * Explains the switching behaviour of the diode from ON time to OFF time.
- * When diode is conducting some excess is stored in the device. These excess charge carriers are mainly due to the minority carriers. When diode is switching from ON \rightarrow OFF, the excess charge carriers are still present in the device after anode current becomes 0.
- * In order to remove these excess charge carriers and acquire equilibrium state, recombination process takes place & hence reverse current flows in the device until all the excess charge carriers are removed from the device.
- * This process is known as Reverse Recovery Process & the transition time during this process is known as Reverse Recovery Time (t_{rr}).

8

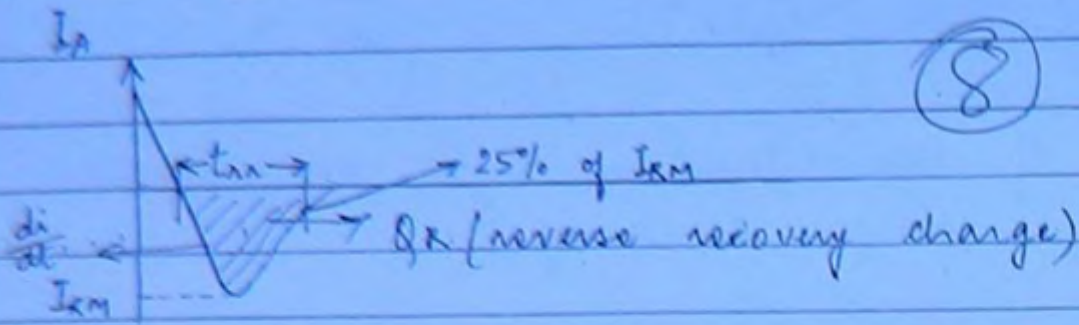

$t=0$

ON \rightarrow OFF

$t_{rr} \rightarrow (I_a=0) - t_0: (\downarrow I_a = 25\% I_m)$

$$I_m = \left[\frac{2Q_R \left(\frac{di}{dt} \right)}{t_{rr}} \right]^{1/2}$$

$$t_{rr} = \left[\frac{2Q_R}{\frac{di}{dt}} \right]^{1/2}$$

Q_R depends on I_a .

$$I_a \uparrow \Rightarrow Q_R \uparrow$$

$$\therefore I_m \uparrow \text{ f } \text{ thus } t_{rr} \uparrow$$

The t_{rr} decides the switching frequency of the diode.
 $t_{rr} \uparrow \Rightarrow f_s \downarrow$

Classification of Power Diodes based on Reverse Recovery Time (t_{rr}):

1. General Purpose Diode
2. Fast Recovery Diode
3. Schottky Diode

(Slow)

← (high speed) →

General Purpose Diodes

Fast Recovery Diode

Schottky Diode

9

1. $t_{rr} \rightarrow 25 \mu s$

$t_{rr} \rightarrow 5 \mu s$ (Less)

$t_{rr} \rightarrow$ nano secs

2. $I_{rating} \rightarrow 1A$ to several 1000's of A.

$I_{rating} \rightarrow 1A$ to several 100 of A.

$I_{rating} \rightarrow$ limited to 300 A.

$V_{rating} \rightarrow 50V$ to 5kV

$V_{rating} \rightarrow 50V$ to 3kV.

$V_{rating} = 100V$.

* In fast recovery diodes, the layers are doped with gold/platinum.

* Gold/platinum doping reduces the lifetime of charge carriers & increases the speed of recombination. This reduces the reverse recovery time.

* Used in choppers & inverters

* Schottky diode is a metal to semiconductor junction diode. Here the conduction is only due to majority carriers.

* Since there is no minority charge carriers the t_{rr} delay is very much reduced. \therefore it operates at very high switching frequency.

* Due to the absence of drift region, the thickness of depletion layer is reduced. \therefore it can block a small reverse voltage limited to 100V.

* Can be used in low power high switching frequency applications



eg Switch Mode Power Supply (SMPS)

* Used in uncontrolled rectifiers, free wheeling diodes for rectifiers.

* Diode is an uncontrolled device because there is no control terminal to decide its on/off state.

(10)


SCR -

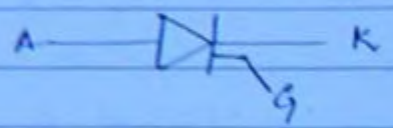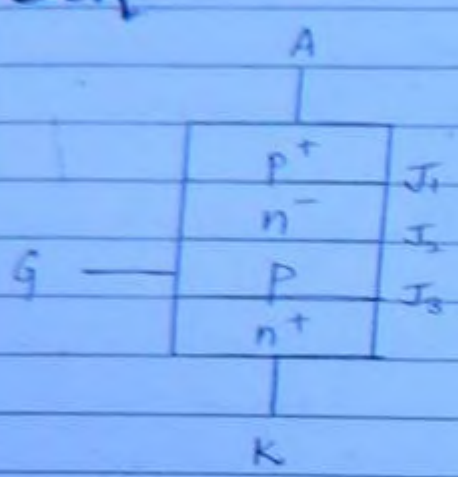

A, K \Rightarrow main terminals

G \Rightarrow control terminals
(on) there is no control of gate when SCR is ON.

Partially controlled device

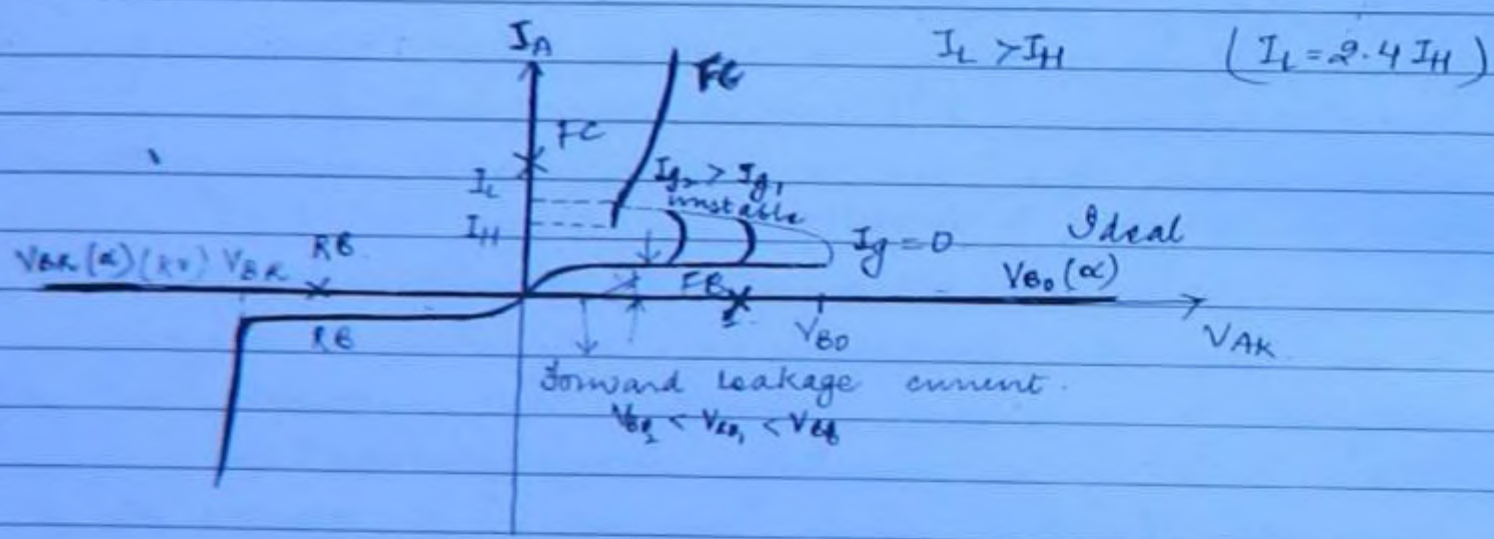

Forward Blocking Mode - A +ve w.r.t K

$J_1, J_3 \Rightarrow FB$

$J_2 = RB$


\therefore SCR \rightarrow OFF

Forward Conduction Mode

(forward breakdown voltage)
 $V_{AK} \uparrow \Rightarrow V_{BO}$ then breakdown occurs at J_2 \therefore SCR \rightarrow ON

(11)

Significance of gate signal -

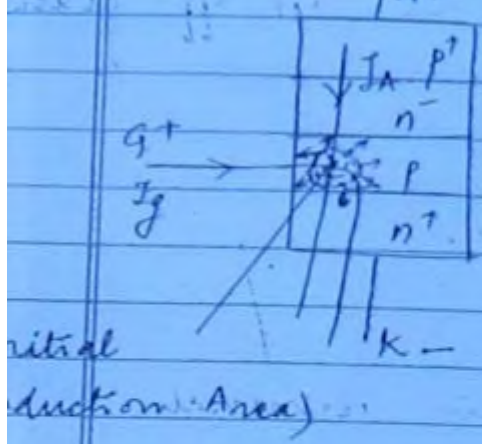

When gate signal is applied, charge gets accumulated in depletion region p. $I_A \uparrow$ and \uparrow the charge accumulation as it gets a conduction path. This leads to \uparrow of charge \uparrow thus breakdown of depletion region turning on the SCR.

If $I_G \uparrow \Rightarrow \frac{dI_G}{dt} \uparrow$ Initial conduction Area \uparrow

$\Rightarrow \frac{dI_A}{dt} \uparrow$ and lesser V_{TG} is used for breakdown - ie less V_{CO} .

Reverse Blocking Mode -

- A receives -ve w.r.t K
- $J_2 \Rightarrow FB$
- $J_1, J_3 \Rightarrow RB$
- SCR \rightarrow OFF


Significance of Latching Current -

Latching current is related to turn on process. When SCR is in the ON state, gate signal is removed to avoid the continuous gate power loss. If we remove the gate signal when $I_A < I_L$ then SCR fails to turn ON. i.e. We must maintain the gate pulse width until I_A reaches I_L just above certain minimum value (Latching current). When we remove gate signal, when $I_A > I_L$ then

SCR continuously SCR continues to be the ON state.

Q) What is the minimum gate pulse width required to turn on the SCR in the following circuit.

$$I_L = 100 \text{ mA}$$

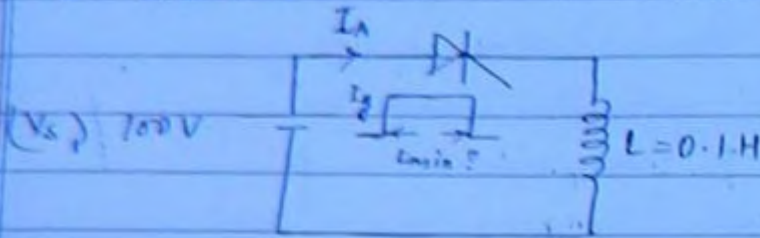

sol

$$V_s = L \frac{di_A}{dt}$$

$$\int di_A = \int \frac{V_s}{L} dt$$

$$I_A = \frac{V_s}{L} t \quad \Rightarrow \quad t_{\min} = \frac{I_A \times L}{V_s}$$

$$t_{\min} = \frac{I_L \times L}{V_s} = \frac{100 \times 10^{-3} \times 0.1}{100}$$

$$t_{\min} = 100 \mu\text{sec.}$$

** The minimum gate pulse width requirement to turn on the SCR depends on the load parameters.

eg. $L \uparrow \Rightarrow t_{\min} \uparrow$

of Load is $R = 20 \Omega$ $L = 0.1 \text{ H}$ in the prev ques.

$$V_s = L \frac{di_A}{dt} + R I_A$$

$$I_A = \frac{V_s}{R} (1 - e^{-t/\tau})$$

$$\tau = \frac{L}{R} = \frac{0.1}{20} = \frac{1}{200}$$

$$I_A = 5 (1 - e^{-200t})$$


$$I_L = 5 (1 - e^{-200 t_{\min}})$$

$$t_{\min} = 101 \mu\text{s}$$

Significance of Holding current -

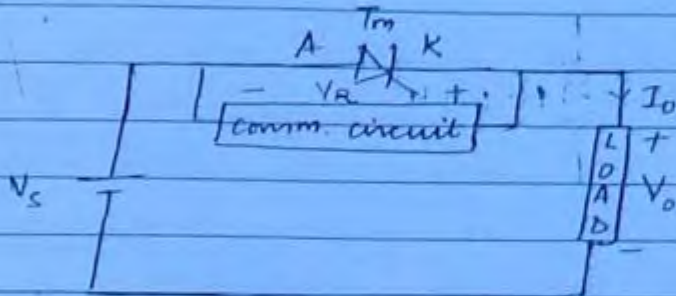(13)

Holding current is related to turn OFF process. Gate has no control to turn OFF SCR. In some cases we require commutation circuit to turn OFF SCR.



Comm ckt forces anode current to reduce below I_H . After that it applies reverse voltage to remove all charge carriers ~~from~~ ⁱⁿ the device.

* Procedure to turn OFF SCR using a commutation ckt -

Commutation circuit forces anode current to reduce below a certain minimum value I_H then it applies a reverse voltage across the SCR at least for a period of device turn off time or greater than that.

Circuit turn off time t_c

It is the time for which the comm circuit applies a reverse voltage across after the anode current becomes 0. It

Device turn off time t_q

It is the time taken to remove charge carriers present in the device provides the t_q .

will turn on' before applying gate (behaves as diode)

In successful commutation $t_c > t_q$ always.

If $t_c < t_q$ commutation fails (14)


Q what do you mean by commutation failure?

Ans If $t_c < t_q$ some excess charge carriers are still present in the device. For the next operation to turn on the SCR if A +ve w.r.t K, SCR will turn on before the gate signal is given. Here the SCR is losing forward blocking capability behaving as a diode. This is known as commutation failure.

To avoid this problem, the commutation circuit should apply reverse voltage across the SCR atleast for a period of t_q or greater than that

Holding current is the minimum I_a below which the SCR becomes off and regains the forward blocking capability if a reverse voltage is applied across SCR atleast for a period of t_q or more than that

Switching Characteristics of SCR -

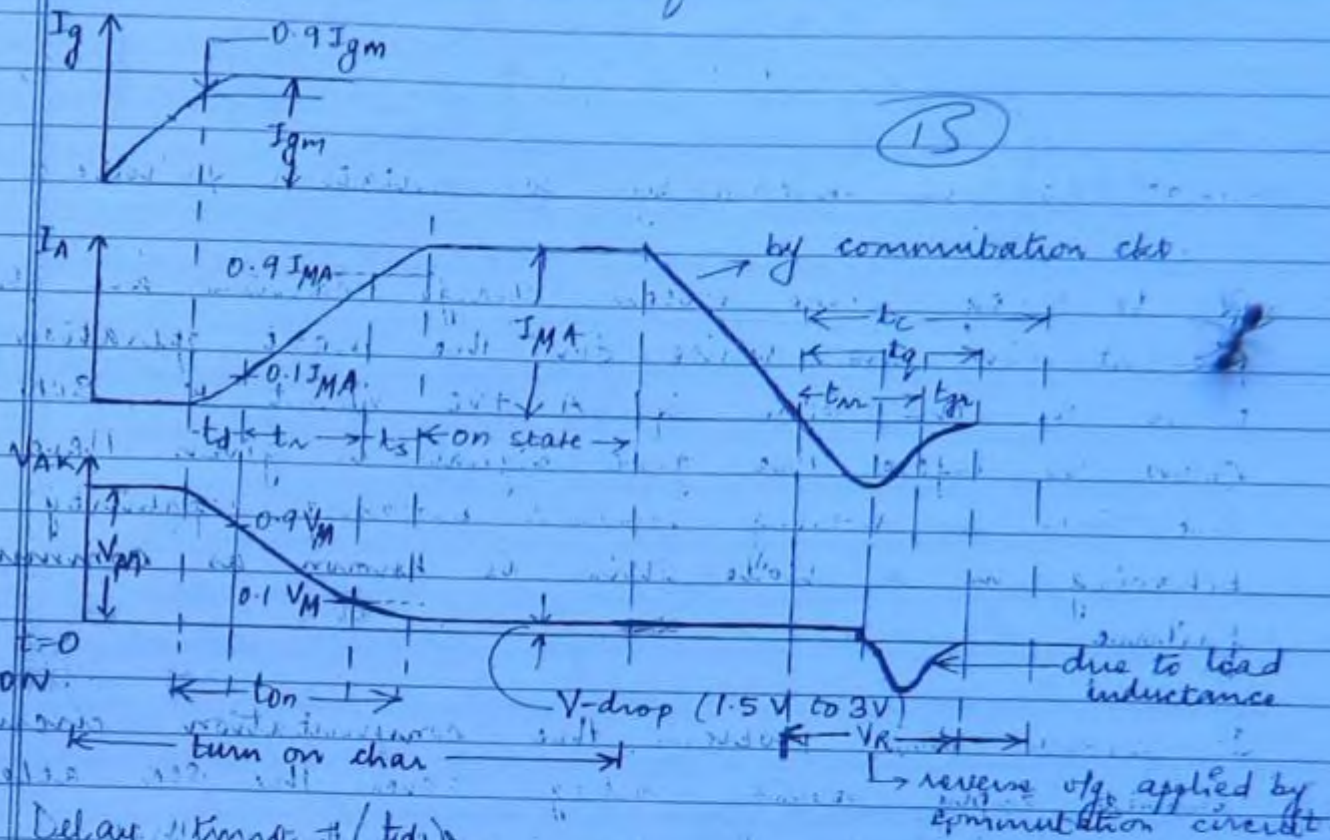

(15)

Delay time t_d (td)

depends on gate signal magnitude & dI_g/dt of gate signal magnitude.

Delay time \Rightarrow $0.9 I_{g_m}$ to $0.1 I_{M_A}$
 $0.9 I_{g_m}$ to $0.9 V_M$

Delay time depends on $\Rightarrow I_g \uparrow$ & $\frac{dI_g}{dt} \uparrow \Rightarrow t_d \rightarrow 0N$
 $\therefore t_{on} \downarrow$

\Rightarrow (initial conduction area) \uparrow
 $\frac{dI_a}{dt} \uparrow$ initial state
 $t_d \downarrow$

Rise time (t_r) $0.1 I_{MA}$ to $0.9 I_{MA}$
 $0.9 V_M$ to $0.1 V_M$

(16)

Rise time depends on Load parameters
of $L \uparrow \frac{di}{dt} \downarrow \therefore t_r \uparrow, t_{on} \uparrow$

Spread time (t_s) $0.9 I_{MA}$ to I_{MA}
 $0.1 V_M$ to (ON state V-drop)
(1.5 - 3V)

Reverse recovery time (t_{rr})

During t_{rr} the excess charge carriers present in the outer layers is reduced.

Gate recovery time (t_{gr})

During t_{gr} the excess charge carriers present in the inner layers near the gate junction is removed.

Device turn off time (t_q)
 $t_q = t_{rr} + t_{gr}$

The device turn off time is generally very much greater than turn on time. Therefore the device turn off time decides the switching characteristics of the SCR.

$t_q \rightarrow$ slow thyristors (converter grade thyristors)
 $t_q \rightarrow 50 \mu s$ to $200 \mu s$

\rightarrow Fast thyristors (inverter grade thyristors)
 $t_q \rightarrow 3 \mu s$ to $50 \mu s$


For successful commutation $t_c > t_q$

$$t_c = SF t_q$$

$SF > 1$ for successful comm.
(Safety factor)


TURN-ON / TRIGGERING METHODS OF SCR -

1. Forward voltage triggering -

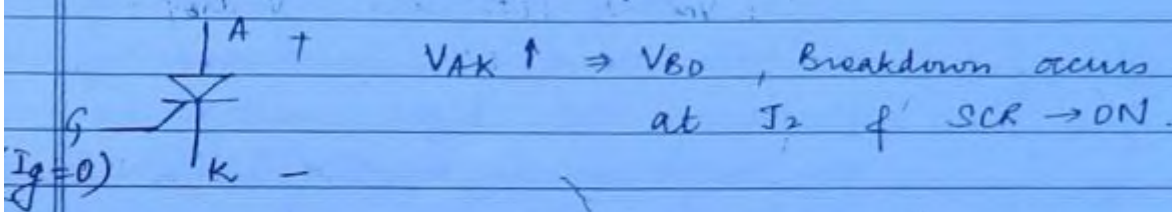

This method is generally not preferred because the SCR may get destroyed due to high power loss when triggered at high voltage.

2. $\frac{dv}{dt}$ triggering -

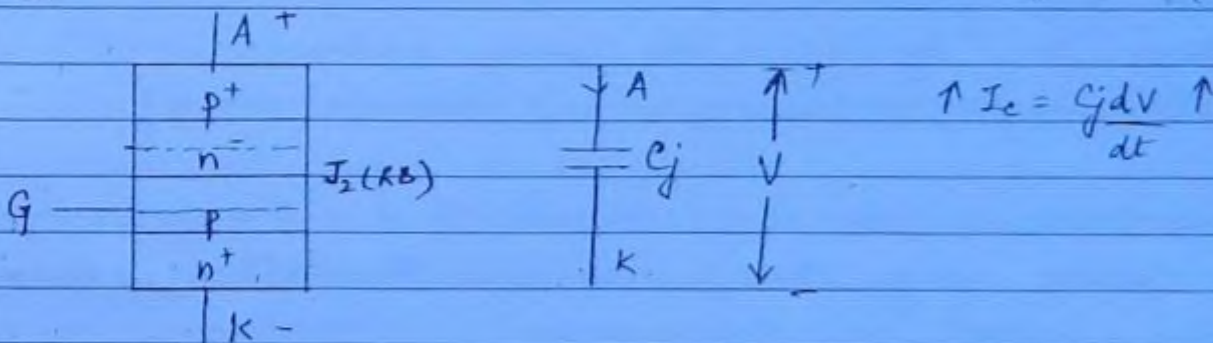


At high $\frac{dv}{dt}$ the charging current increases. If the increase in charging current is more than the latching current then SCR is turned on.

Critical $dv/dt \rightarrow$ Its the dv/dt at which SCR will turn on. At critical dv/dt charging current is equal to latching current $I_c = I_L$.

(18)

3. Light triggering -

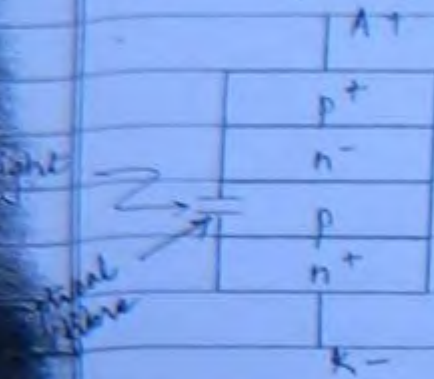

When light radiation is incident near the depletion layer then more number of e^- -hole pairs are produced by absorbing the light energy in the depletion layer, & this initiates the turn on process.

Application \rightarrow Used in LASCAs for HVDC applications.

Thermal triggering -

When temperature is increased near the reverse biased gate junction, then the device is initiated to turn on by e^- -hole pairs produced in depletion layer absorbing the thermal energy.


Semiconductors are very sensitive & the character of the device may change as the temperature changes, so this method is not used.

Gate triggering -

(a) Continuous Gate Triggering -

Continuous gate signal is applied until the SCR is expected to be in the ON state. This is not efficient triggering due to continuous gate power loss.

(b) Pulse gate signal -

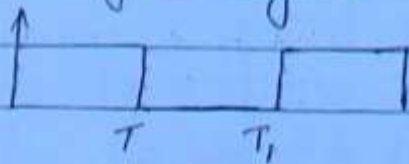

(79)


T = gate pulse width

$T > t_{min}$

T_1 → time period

$$D = \frac{T}{T_1} = \text{duty cycle}$$

(c) High frequency gate signal

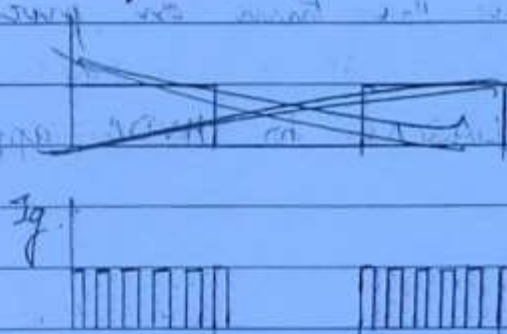



Adv

→ reduces the size of pulse transformer



provides electrical isolation b/w high power main circuit & low power gate firing circuit.

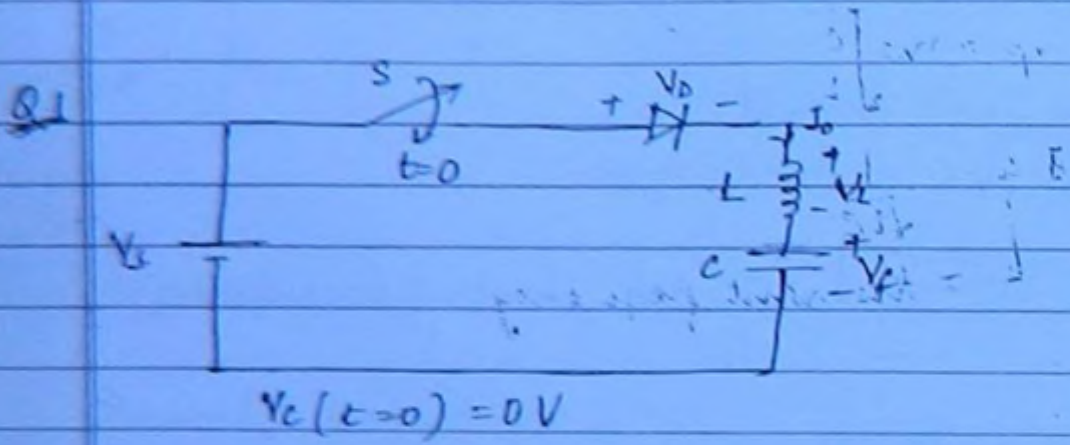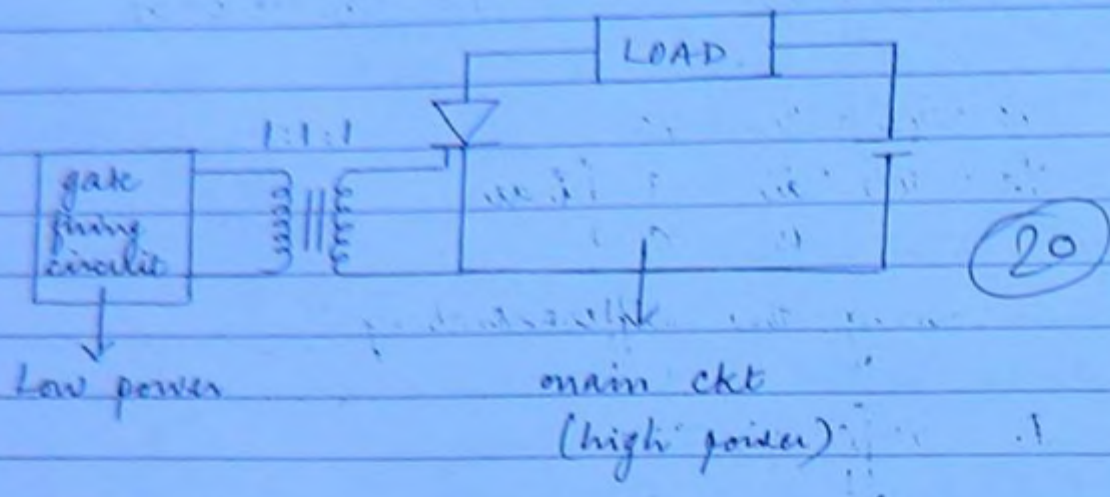→ we can trigger more than one SCR using a pulse transformer.



i) When switch is closed at $t=0$ then diode conducts for

- a) $\frac{\pi}{2} \sqrt{LC}$
- b) $\pi \sqrt{LC}$
- c) $\sqrt{3} \sqrt{LC}$
- d) $2\pi \sqrt{LC}$

ii) $V_C = ?$ when diode stops conducting

- a) V_s
- b) $2V_s$
- c) $-V_s$
- d) $-2V_s$

3d. i) $S \rightarrow ON (t=0)$ $R = D = FB$ (on at $t=0$)

$$V_s = V_D + V_L + V_C$$

$$V_s = 0 + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

(21)

on solving the differential eq.


$$I_o = V_s \sqrt{\frac{C}{L}} \sin \omega_0 t$$

$$I_o = I_p \sin \omega_0 t$$

where $I_p = V_s \sqrt{\frac{C}{L}}$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Resonant frequency

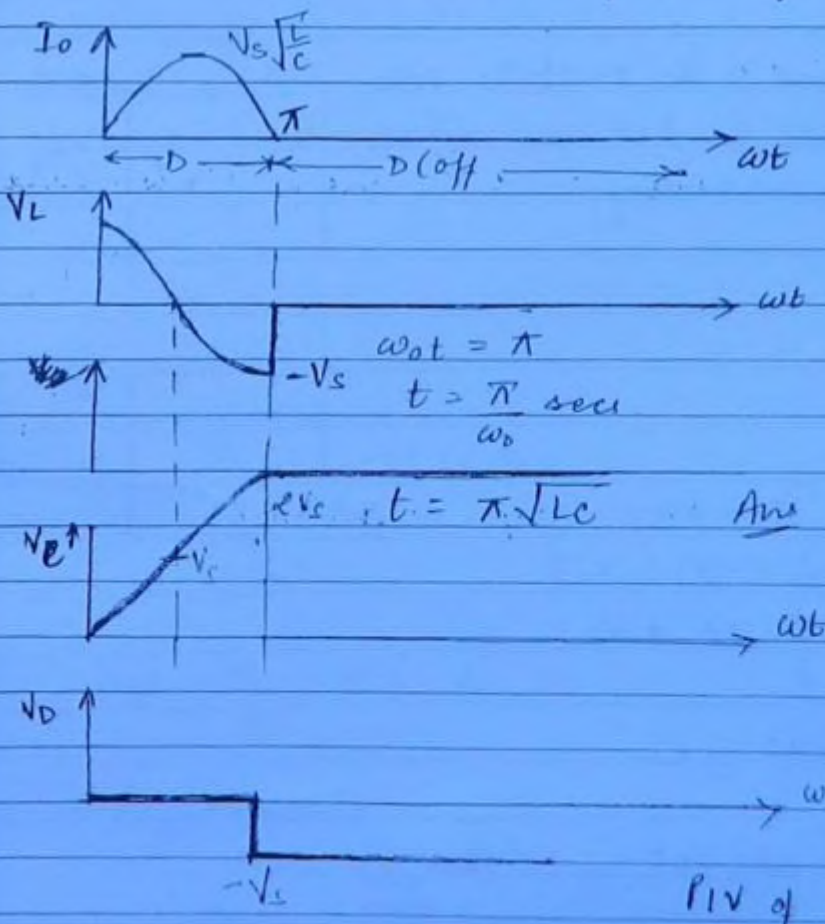

Ans (b)

PIV of diode = V_s

$$V_L = L \frac{dI}{dt}$$

$$= L \frac{d(I_p \sin \omega t)}{dt}$$

$$V_L = V_s \cos \omega t$$

$$V_C = V_s - V_L$$

$$= V_s - V_s \cos \omega t$$

$$V_C = V_s (1 - \cos \omega t)$$

$$-V_s + V_D + 0 + 2V_s = 0$$

$$V_D = -V_s$$

(22)

From 0 to 90°

$$\text{Source} \rightarrow \frac{1}{2} LI^2 + \frac{1}{2} CV^2$$

From 90 to 180°

$$\frac{1}{2} LI^2 \rightarrow \frac{1}{2} CV^2$$

2. In prev. ques assume $V_C(t=0) = V_0$ volts where $V_0 < V_s$.
 i) When switch is closed at $t=0$ sec. what's the cap. v/g (V_C) after the diode stops conducting.

a) $\frac{1}{2}(V_s + V_0)$

b) $\frac{1}{2}(V_s - V_0)$

c) $\frac{1}{2}V_s + V_0$

d) $\frac{1}{2}V_s - V_0$

$$S \rightarrow ON (t=0)$$

$$D = FB$$

$$V_s = 0 + L \frac{di}{dt} + \frac{1}{C} \int i dt + V_0$$

$$V_s - V_0 = L \frac{di}{dt} + \frac{1}{C} \int i dt$$

$$I_0 = (V_s - V_0) \sqrt{\frac{C}{L}} \sin \omega t$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$I_0 = I_p \sqrt{\frac{C}{L}} \sin \omega t$$

$$V_L = L \frac{d(I_p \sin \omega t)}{dt}$$


$$V_L = (V_s - V_o) \cos \omega t$$

$$V_c = V_s - V_L$$

$$= V_s - (V_s - V_o) \cos \omega t$$

$$V_c = V_s(1 - \cos \omega t) + V_o \cos \omega t$$


(23)

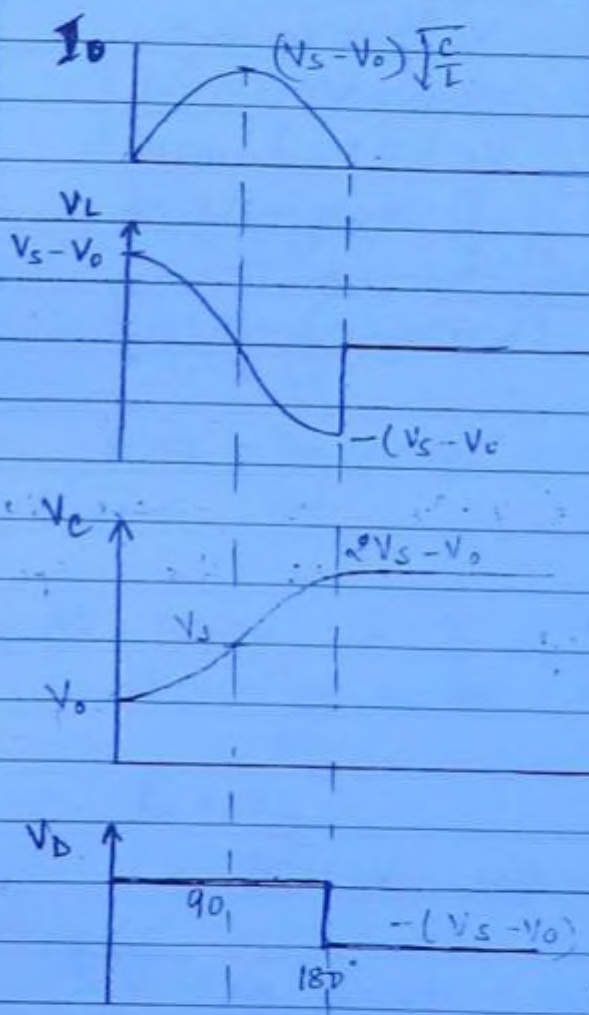

$$PIV = V_s - V_o$$

Ans $V_c = qV_s - V_o$

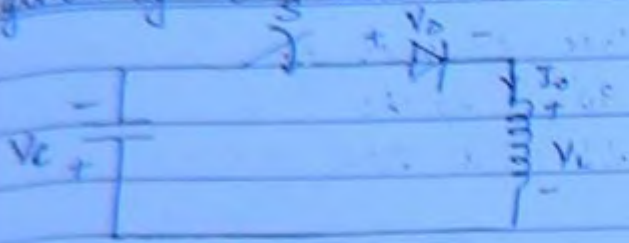then charging current of cap behaves as $i_p \sin \omega t$ given by $V_c = V_s \cos \omega t$.
 charging vol of cap behaves as V_c when i_D stops conducting



- a) $\frac{dV_s}{dt}$
- b) $-\frac{dV_s}{dt}$
- c) $-V_s$
- d) V_s

(24)

$V_c(t=0) = -V_s$

$V_c + V_D + V_L = 0$
 $V_L + (V_c - V_s) = 0$
 $V_s = V_L + V_c$

$V_L = L \frac{di}{dt} (I_p \sin \omega t)$

$V_s = L \frac{di}{dt} + \frac{1}{C} \int i dt$





$V_L = V_s \cos \omega t$

$I_p = V_s \sqrt{\frac{C}{L}} \sin \omega t$

$V_c = \frac{1}{C} \int i dt$

$V_c = -V_s \cos \omega t$

Ans ~~same as~~ $V_c = -V_s$ (a)

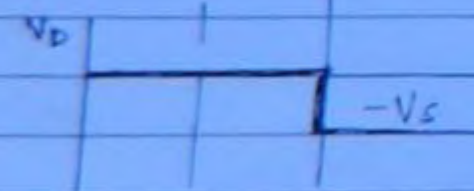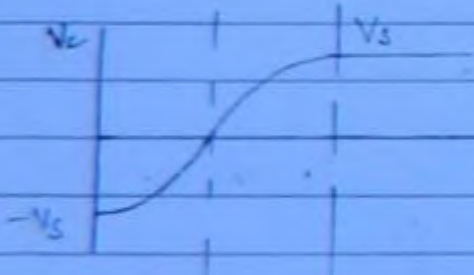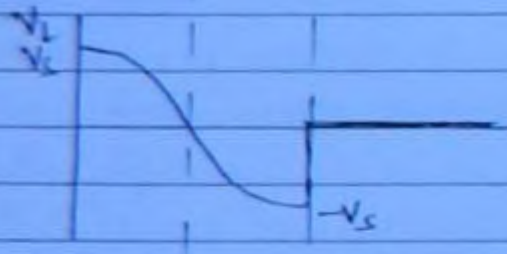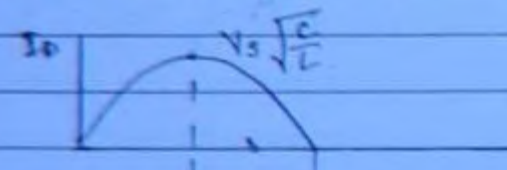


Ans $V_c = V_s$

PIV = V_s

* If $V_c(t=0) = V_s$ then cap vol reverses & $V_c = -V_s$

ATE
Q4

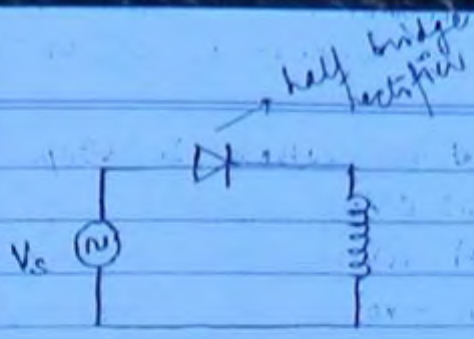

Diode conducts for
 a) 90° b) 180°
 c) 270° d) 360°

25

sol.

$$V_s = L \frac{di}{dt}$$

$$V_m \sin \omega t = L \frac{di}{dt}$$

$$\int di = \int \frac{V_m \sin \omega t}{L} dt$$

$$i = \frac{V_m}{\omega L} (\cos \omega t - 1)$$


$$i = -\frac{V_m}{\omega L} \cos \omega t + K$$

At $\omega t = 0$ $i = 0$

$$0 = -\frac{V_m}{\omega L} \cos 0 + K$$


$$K = \frac{V_m}{\omega L}$$
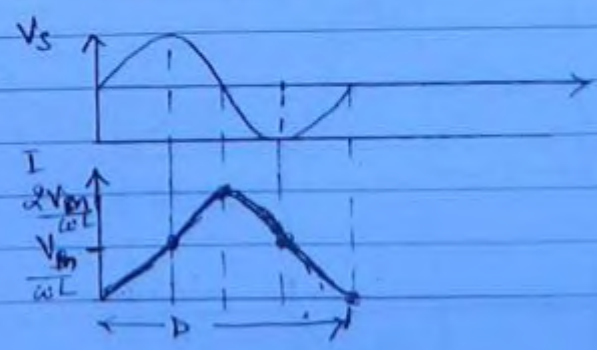
$$i = -\frac{V_m}{\omega L} \cos \omega t + \frac{V_m}{\omega L} = \frac{V_m}{\omega L} (1 - \cos \omega t)$$



Ans 360°

Q5

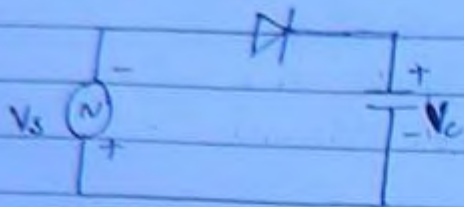

Diode conducts for

- a) 90°
- b) 180°
- c) 270°
- d) 360°

sol

$$V_c + V_s = 0$$

$$V_s = -V_c$$

$$V_m \sin \omega t = -\frac{1}{C} \int i dt$$

$$I = -V_m C \times \omega \times \cos \omega t$$

$$I = -V_m \omega C \cos \omega t$$

26

COMMUTATION TECHNIQUES -




1. Natural / Line Commutation -

If nature of supply supports commutation process its called natural commutation.

eg Rectifiers

AC vlg controllers

Step down cyclo converters

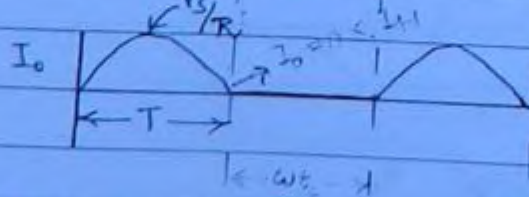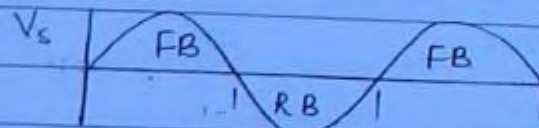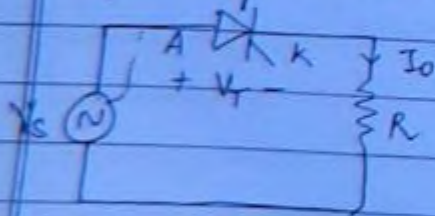


$$\omega t_c = \pi$$

$$t_c = \frac{\pi}{\omega} \text{ secs}$$

$T \rightarrow ON$

$$I_o = \frac{V_s}{R}$$

$$I_o = \frac{V_m \sin \omega t}{R}$$

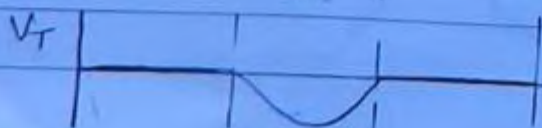

2 Forced commutation -

DC supply will not support the commutation process. We need a separate forced commutation circuit to turn off the SCR.

eg choppers
inverter



step up cycloconverter

(27)

a) Class A commutation circuits -

RLC should satisfy underdamped condition

$$R^2 < \frac{4L}{C}$$

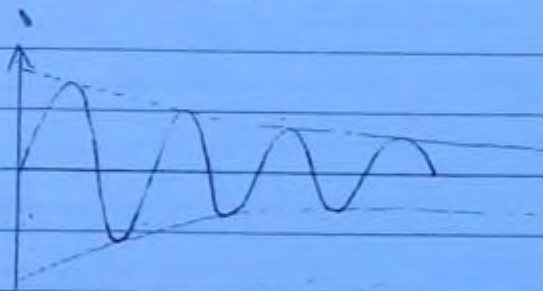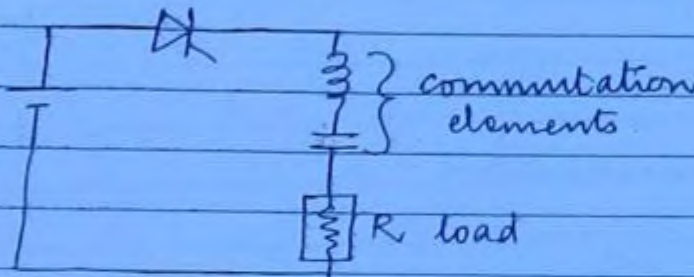


$$I = \frac{V_s}{\omega_n L} e^{-\delta t} \sin \omega_n t$$

$$\delta = \frac{R}{2L}$$

$$\omega_n = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

singing frequency

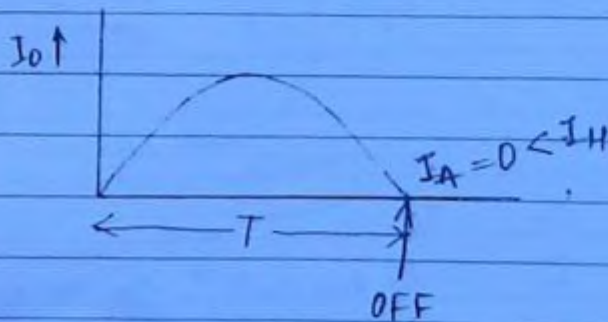

$$\omega_n t = \pi$$


$$t = \frac{\pi}{\omega_n}$$

conduction time of thyristor = $\frac{\pi}{\omega_n}$ sec.


Load commutation -

If the load elements support the commutation process then it is known as load commutation.

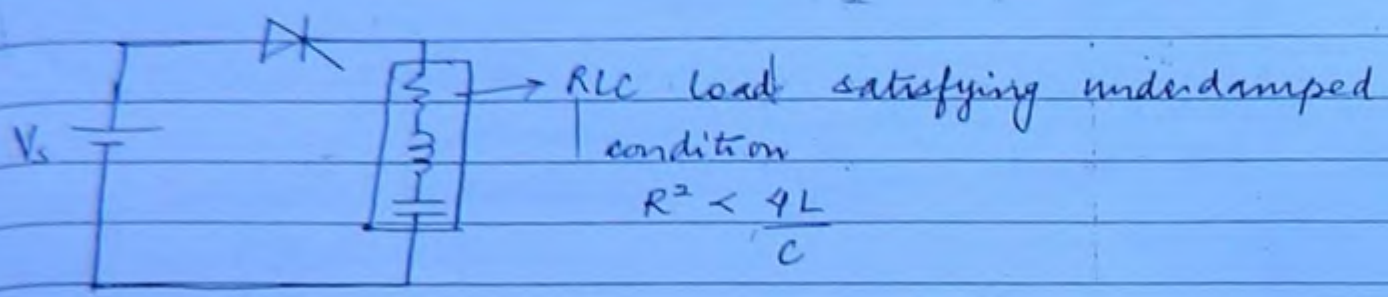eg If load is RLC load satisfying underdamped condition as shown in figure.



Class B - Current Commutation -

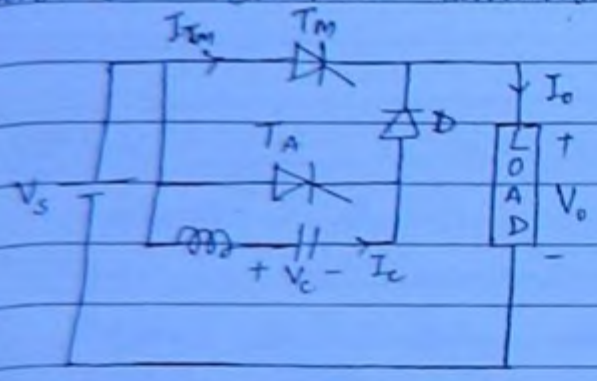


Assume $\rightarrow V_c(t=0) = V_s$
 $\rightarrow I_o = \text{constant}$
 (highly inductive load)
 $\rightarrow T_m \rightarrow \text{ON } (t < 0)$

① Mode

$T_A \rightarrow \text{ON } (t=0)$

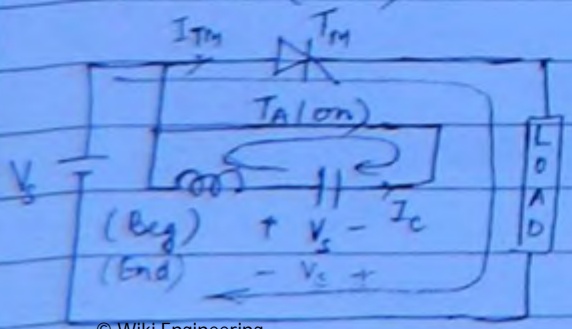
$I_{Tm} = I_o$
 $I_c = -I_p \sin \omega_0 t$ [∵ dirⁿ is opp to reference I_c]




$V_c = V_s \cos \omega_0 t$

End $\rightarrow V_c = -V_s$
 $I_c = 0$

(29)

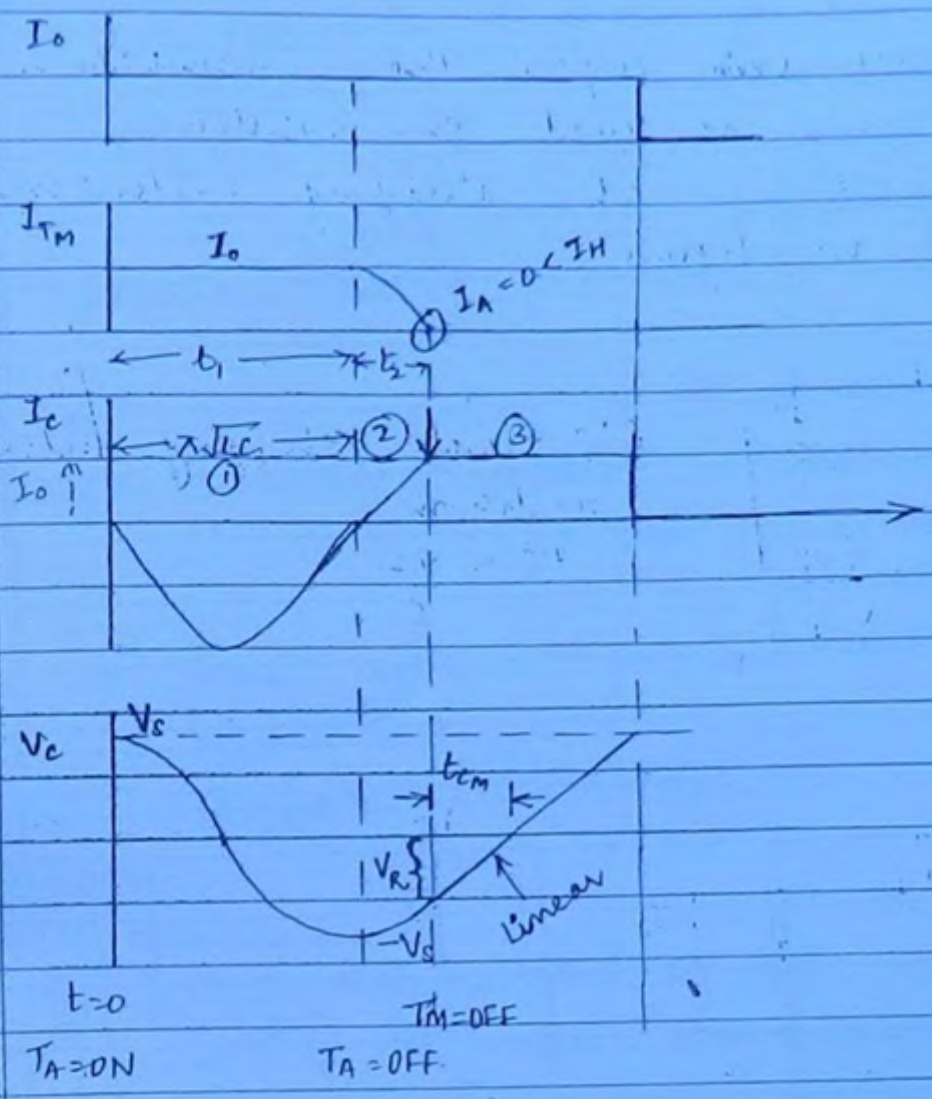

MODE

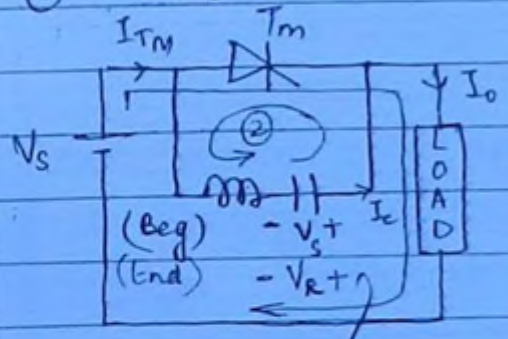

$$\downarrow I_{TM} = I_o - I_c \uparrow$$

GND \rightarrow when $I_c = I_o$ $I_{TM} = 0$
 $\therefore T_M \rightarrow$ OFF

for this also reference is the initial vlg V_c

$$I_p \sin(\omega_o t_2) = I_o$$

$$\omega_o t_2 = \sin^{-1} \frac{I_o}{I_p}$$

$$t_2 = \frac{\sqrt{LC} \sin^{-1} \frac{I_o}{I_p}}{f_p}$$

V_c at the end of mode ②

$$V_c = V_s \cos(\pi + \omega t_2)$$

$$V_c = -V_s \cos(\omega t_2)$$

$$V_c = -V_s \cos \left[\sin^{-1} \frac{I_o}{I_p} \right]$$



(150)

At the end of mode ②

V_R is the reverse voltage of cap.

$$V_R = V_s \cos \left[\sin^{-1} \frac{I_o}{I_p} \right]$$

③ MODE

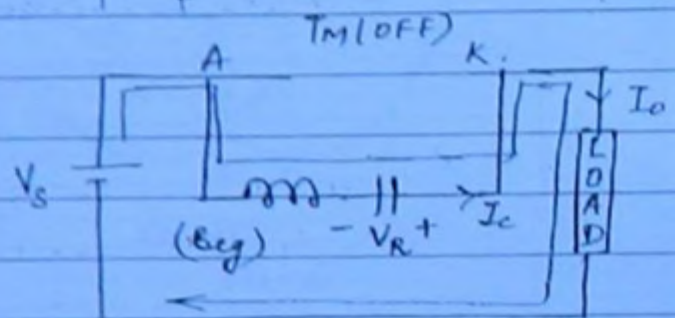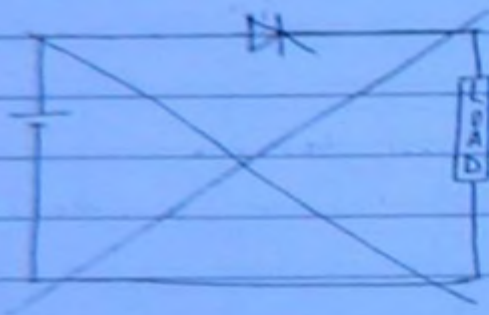

$$I_c = I_o$$

$$V_c = \frac{1}{C} \int i dt$$

$$V_c = \frac{I_o t}{C}$$

$$V_R = \frac{I_o t_{com}}{C}$$

$$t_{com} = \frac{V_R C}{I_o}$$

circuit turn off time
for main thyristor

* $(I_{T_M})_{\text{peak}} = I_0$

* $(I_{T_A})_{\text{peak}} = V_s \sqrt{\frac{C}{L}} \times I_p$ (31)

* conduction time of $T_A = \pi \sqrt{LC}$

* Min^m time required to turn OFF the main Thyristor after auxiliary thyristor is switched ON.
 $t = \pi \sqrt{LC}$ (for low values of load current I_0)

* Max^m time required to turn OFF T_M

$t = t_1 + t_2$

$= \pi \sqrt{LC} + \sqrt{LC} \sin^{-1} \left(\frac{I_0}{I_p} \right)$

from

* If $I_0 > I_p$, commutation is not possible.

∴ $I_0 \leq I_p$ to make commutation possible.


* $t_{CM} = \frac{CV_s}{I_0}$

* Max reverse v/g applied across the T_M when it is in off state is V_R .

$V_R = V_s \cos \left[\sin^{-1} \frac{I_0}{I_p} \right]$

If diode is not present, T_A has no control on commutation.

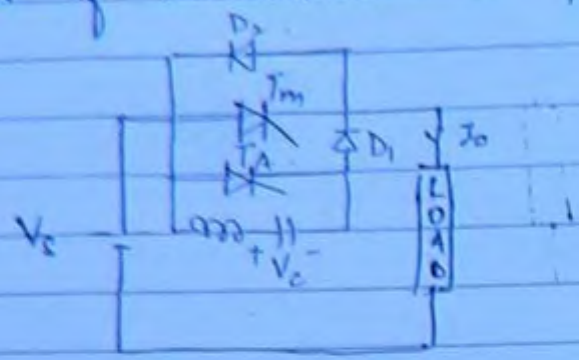
Check if commutation is possible. If possible, calculate the circuit turn-off time of T_M



(32)


End of mode 1 reverses polarity of $+V_c$ to $-V_c$. In mode 2, T_M is ON, D_2 reverse biases D_1 . D_1 is FB and D_2 is RB. so commutation is possible. D_1 is FB and D_2 is RB. so commutation is possible. D_1 is FB and D_2 is RB. so commutation is possible. D_1 is FB and D_2 is RB. so commutation is possible.

Mode (3)

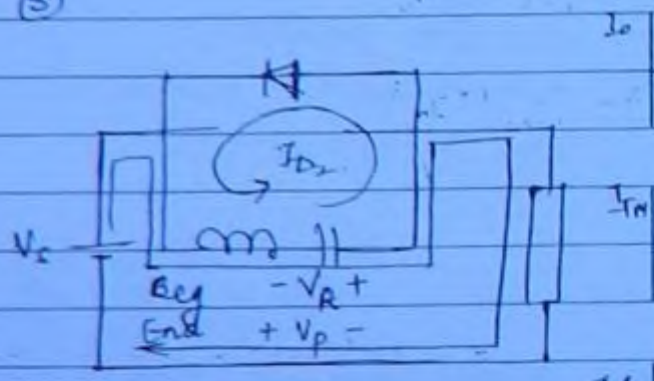


$$I_c = I_o + I_{D_2}$$


$$I_{D_2} = I_c - I_o$$

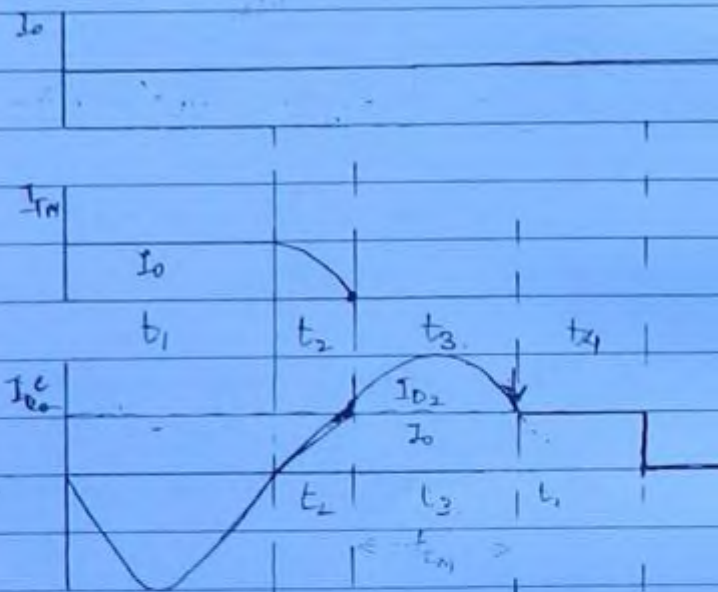

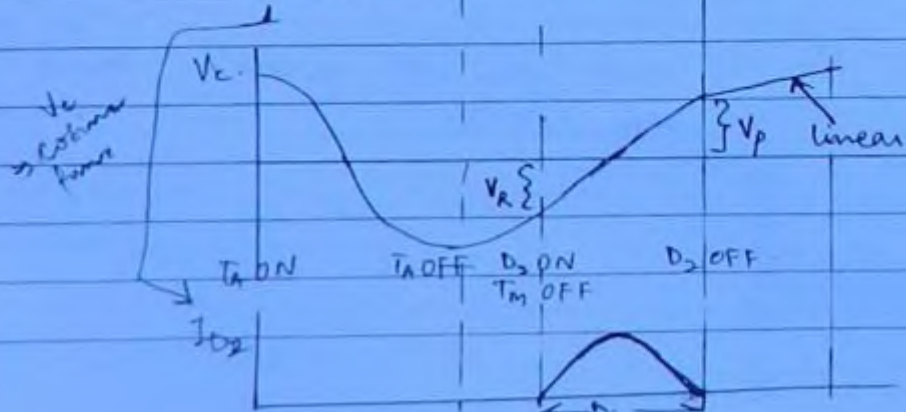END → when $I_c = I_o$
 $I_{D_2} = 0$
 $D_2 = \text{OFF}$



Mode (4)

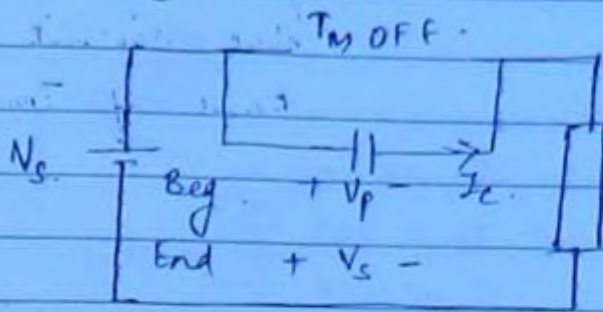

$$I_c = I_o$$

In mode (3) when D_2 is in the ON state, the voltage drop of D_2 applies reverse voltage across the main thyristor. The conduction time of D_2 is equal to the turn-off time of T_M .

$$t_{cm} = t_3 = \pi\sqrt{LC} - 2t_2$$


$$t_{cm} = \pi\sqrt{LC} - 2\sqrt{LC} \sin^{-1}\left(\frac{I_o}{I_p}\right)$$

Applications -

This type of commutation technique is used in step down chopper. It is also known as current commutation chopper.

(c) Class C - Complementary Commutation

(34)

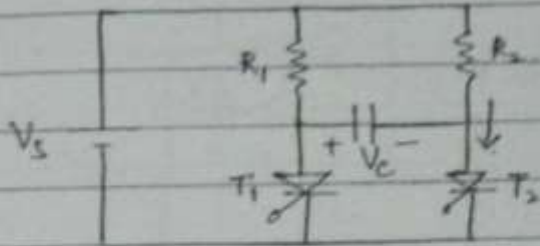


Assume

- $V_c(t=0) = V_c$
 - $T_2 \rightarrow ON$
 - $T_1 \rightarrow OFF$
- } (t < 0)

Mode (1)

At $t=0$, $T_1 \rightarrow ON$

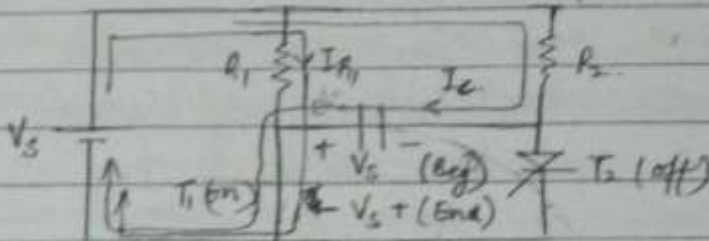

$$I_{T_1} = I_{R_1} + I_c$$

$$= \frac{V_s}{R_1} + K e^{-t/R_2 C}$$

initial current

$$I_{T_1} = \underbrace{\frac{V_s}{R_1}}_{\text{steady state current}} + \underbrace{\frac{2V_s}{R_2} e^{-t/R_2 C}}_{\text{transient current}}$$

steady state current

transient current

$$V_c = \frac{1}{C} \int i_c dt = \frac{1}{C} \int \frac{V_c}{R_2} e^{-t/R_2 C} dt$$

$$= \frac{2V_s}{R_2} e^{-t/R_2 C} - V_c \quad \text{by trial f. value form}$$

V_c graph

$$V_c = V_s (2e^{-t/R_2 C} - 1)$$

t_{c_2} = cut time off time of T_2 .



$$V_s (2e^{-t_{c_2}/R_2 C} - 1) = 0 \quad V_c$$

At $t = t_{c_2}$, $V_c = 0$

$$V_s [2e^{-t_{c_2}/R_2 C} - 1] = 0$$

$$t_{c_2} = R_2 C \ln 2$$


35

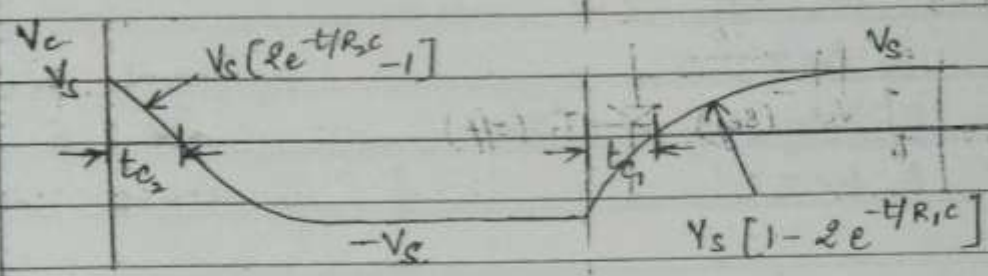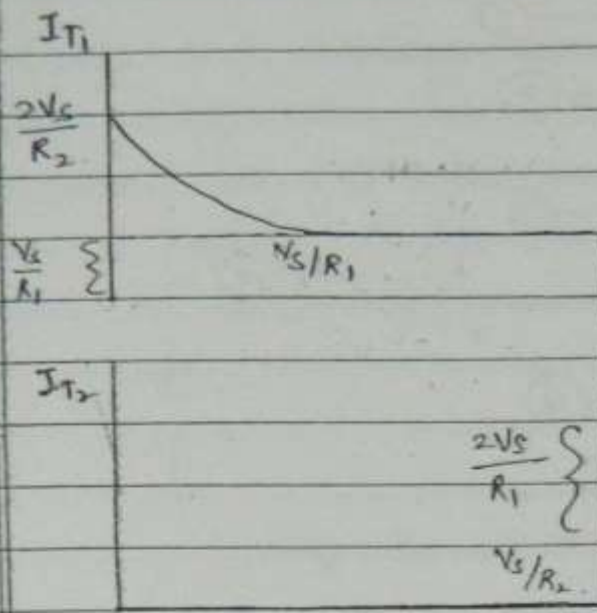

$t=0$
 $T_1 \rightarrow ON$ (1)
 $T_2 \rightarrow OFF$
 $t=t_2$ (2)
 $T_2 \rightarrow ON$

Mode (2)

At $t=t_2$, $T_2 \rightarrow ON$

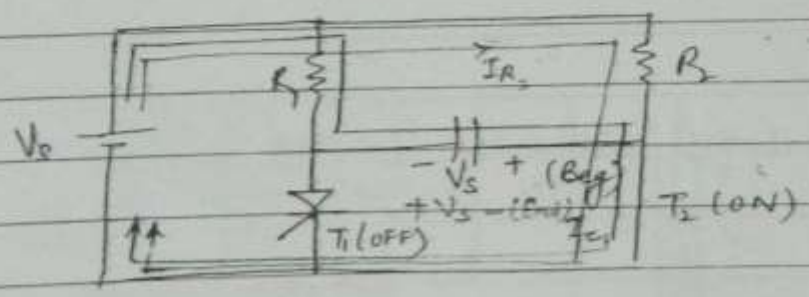

$$I_{T2} = I_{R2} + I_c$$

$$I_{T2} = \underbrace{V_s}_{\text{Steady state current}} + \underbrace{2 \frac{V_s}{R_1} e^{-t/R_1C}}_{\text{Transient current}}$$

$$t_{c1} = R_1 C \ln 2$$

* $t_{c2} = R_2 C \ln 2$ — (1)

* $t_{c1} = R_1 C \ln 2$ — (2)

* $(I_{T1})_{peak} = \frac{V_s}{R_1} + \frac{2V_s}{R_2}$ — (3)

(SF)

* $(I_{T2})_{peak} = \frac{V_s}{R_2} + \frac{2V_s}{R_1}$ — (4)

* Desired value of capacitance

from (1) $C = \frac{t_{c2}}{R_2 \ln 2}$

$C = \frac{(SF) t_{c2}}{R_2 \ln 2}$ — (5)

from (2) $C = \frac{(SF) t_{c1}}{R_1 \ln 2}$ — (6)

From eq (5) & (6) we get 2 different values for capacitance. We must consider the highest value of capacitance to make commutation possible.


Applications -

- Current source inverter (CSI)
- Parallel Inverter

(d) Class D - Voltage Commutation


Its used in step down choppers, i.e. its also known as voltage commutation chopper.

(39)

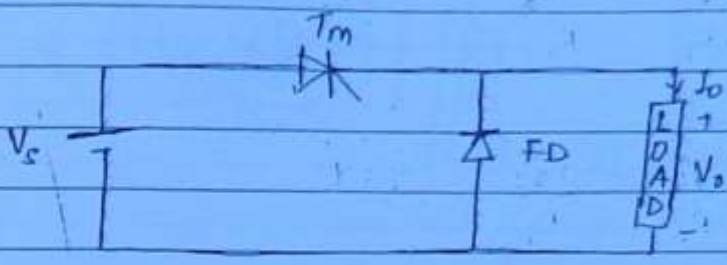

step down choppers.


without commutation circuit:

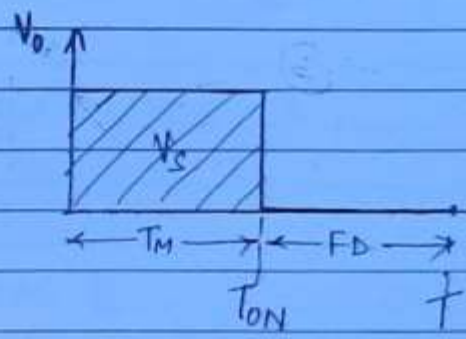

duty cycle $\alpha = \frac{T_{on}}{T}$

$V_o = \frac{\text{Area}}{\text{Time period}} = \frac{V_s T_{on}}{T}$

$V_o = \alpha V_s$

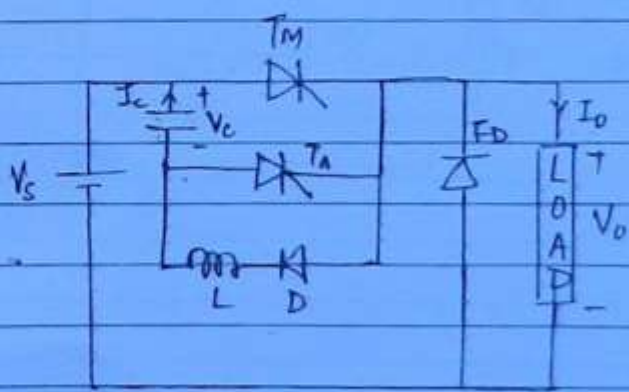


Assume


$\rightarrow V_c(t=0) = V_s$

\rightarrow Consider highly inductive load so that load current

$I_o = \text{constant}$

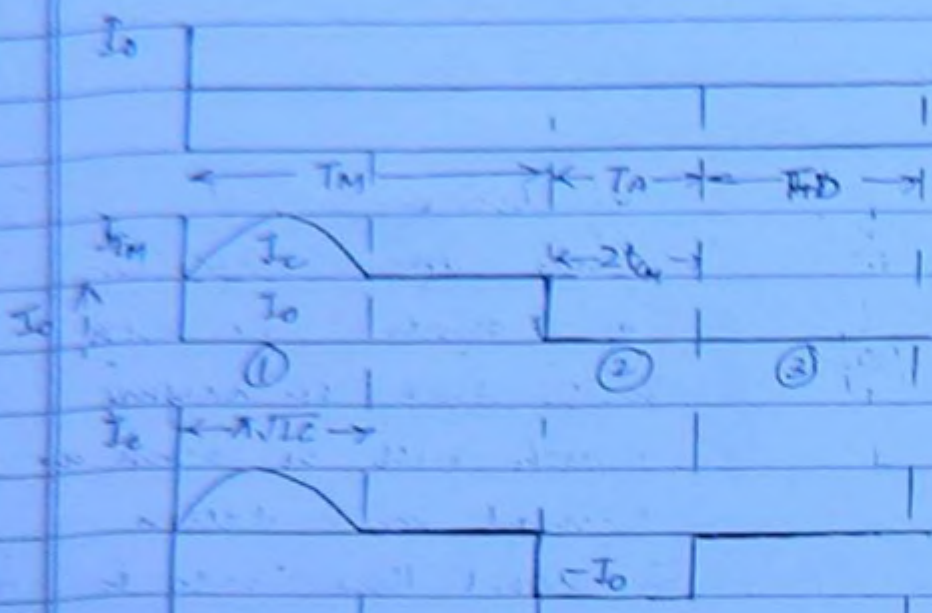

38

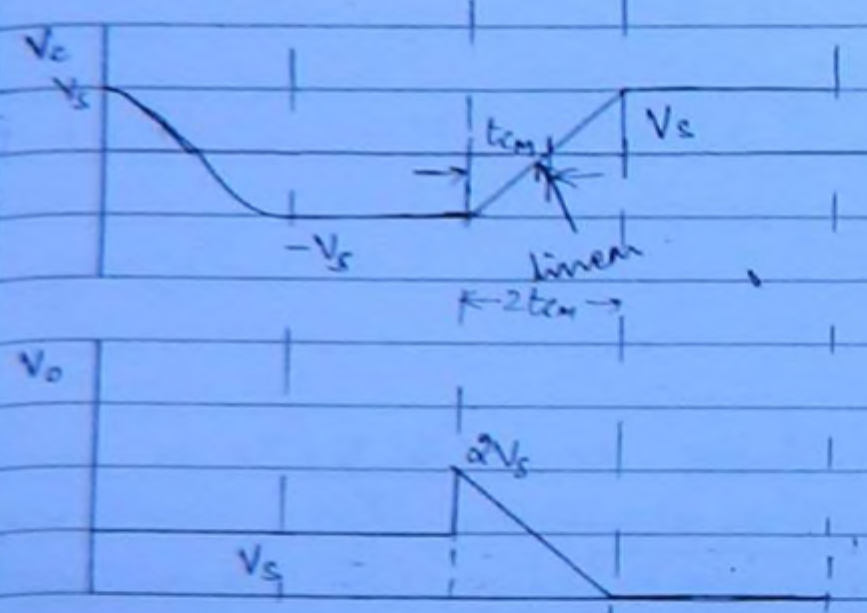


$t=0$ T_{ON} $T_A \rightarrow OFF$ T $\alpha = \frac{T_{ON}}{T}$
 $T_M \rightarrow ON$ $T_A \rightarrow ON$
 $T_M \rightarrow OFF$

Mode (1)

At $t=0$ $T_M \rightarrow ON$

(39)

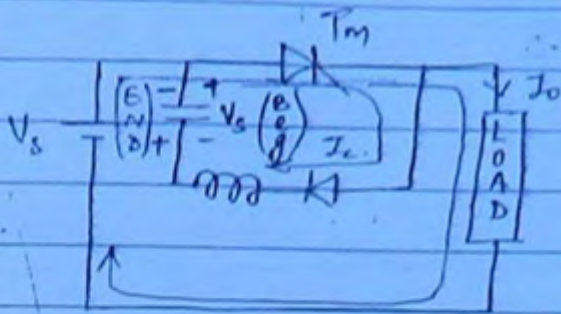

(*) If diode is not, there, after completion of mode 1 capacitor will start discharging which will be same as current commutation. To avoid this Diode is present.

$$I_{T_M} = I_o + I_c$$

$$I_c = I_p \sin \omega t$$


$$V_c = V_s \cos \omega t$$

End $\rightarrow V_c = -V_s$

$$I_c = 0$$

Mode (2)

At $t=T_{ON}$ $T_A \rightarrow ON$

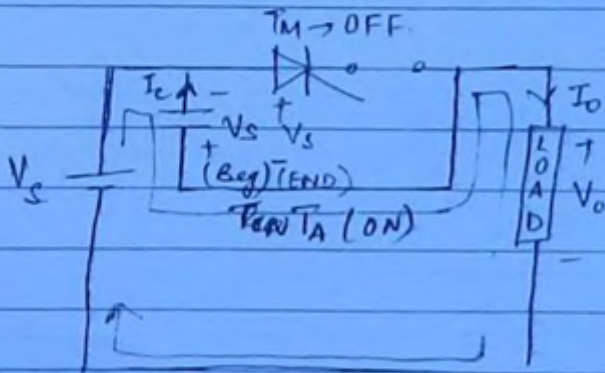

$$I_c = -I_o$$

$$V_c = -V_s$$

$$V_o = -2V_s$$


End $\rightarrow V_c = V_s$

$$V_o = 0$$

$$I_c = 0$$

$$T_A \rightarrow OFF$$

Mode (3)

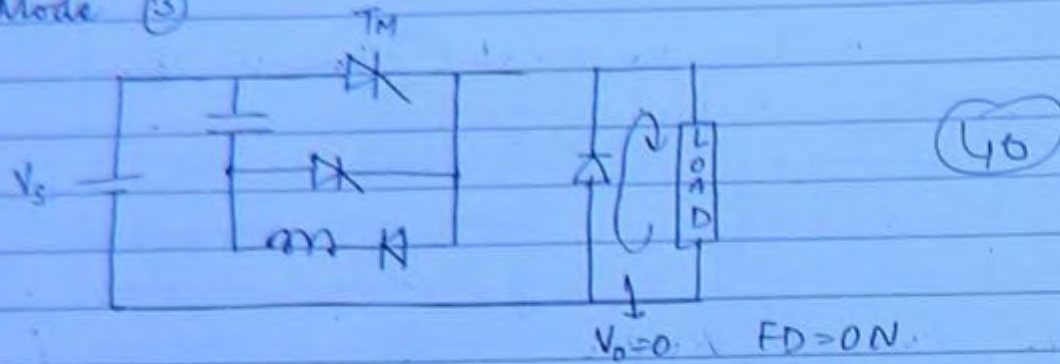

$$(I_{TM})_{peak} = I_o + V_s \sqrt{\frac{C}{L}}$$

$$(I_{TA})_{peak} = I_o$$

Without completion of the 1st mode we cannot turn off the TM i.e. the min^m turn ON time of the thyristor is $\pi\sqrt{LC}$ sec.

(This is because the polarities will not change before the completion of 1st mode)

Min^m duty cycle of the chopper

$$\alpha = \frac{(T_{on})_{min}}{T} = \pi\sqrt{LC} f$$

Circuit turn off time of TM

$$V_c = \int i dt \Rightarrow V_c = I_o t \quad (\text{linear})$$

$$V_s = \frac{I_o t_{cm}}{C} \Rightarrow t_{cm} = \frac{C V_s}{I_o}$$

Conduction time of TA = αt_{cm}

Commutation interval = time taken to disconnect the load from the source once TM is off.

$$= 2t_{r-1}$$

* PIV of FD is $2V_s$
since its RB by the load, (when its off)
so max vlg at load is $2V_s$

(41)

* PIV of $T_M = V_s$

* Average value of voltage
$$V_o = \frac{V_s T_{ON} + \frac{1}{2} \times 2t_{cm} \cdot 2V_s}{T}$$

$$V_o = V_s \left[\frac{T_{ON} + 2t_{cm}}{T} \right] = \frac{V_s (T_{ON})_{eff}}{T}$$


* Effective turn-on time of chopper
i.e. $(T_{ON})_{effective}$

$$T_{(effective)} = T_{ON} + 2t_{cm}$$

* Minimum possible average voltage of chopper
is

$$(V_o)_{min} = V_s \left[\frac{\pi \sqrt{LC} + 2t_{cm}}{T} \right]$$

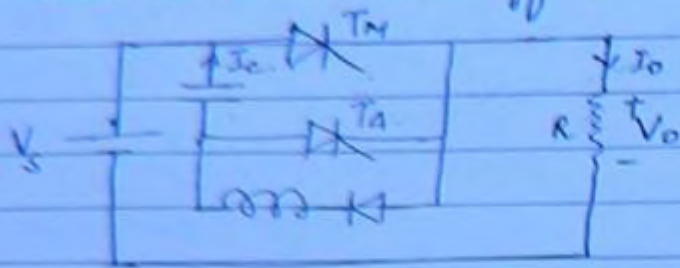Find the circuit turn off time of the main thyristor



(42)

Mode 1 is same as prev. case

Mode 2 \rightarrow is not same as $I_o \neq$ const due to R load.
(which forms RC ckt with cap C)

$$I_c = -I_o = -\frac{2V_s}{R} e^{-t'/RC}$$

$$I_o = \frac{2V_s}{R} e^{-t'/RC}$$

At $t' = 0$

$$I_o = \frac{2V_s}{R}$$

f load current is exponentially reducing.

$$I_c = -\frac{2V_s}{R} e^{-t'/RC}$$

current \downarrow
exponentially


\uparrow
Vc also.

$$V_c = V_s [1 - 2e^{-t/RC}]$$

At $t = t_{com}$ $V_c = 0$

$$t_{com} = RC \ln 2$$

(103)

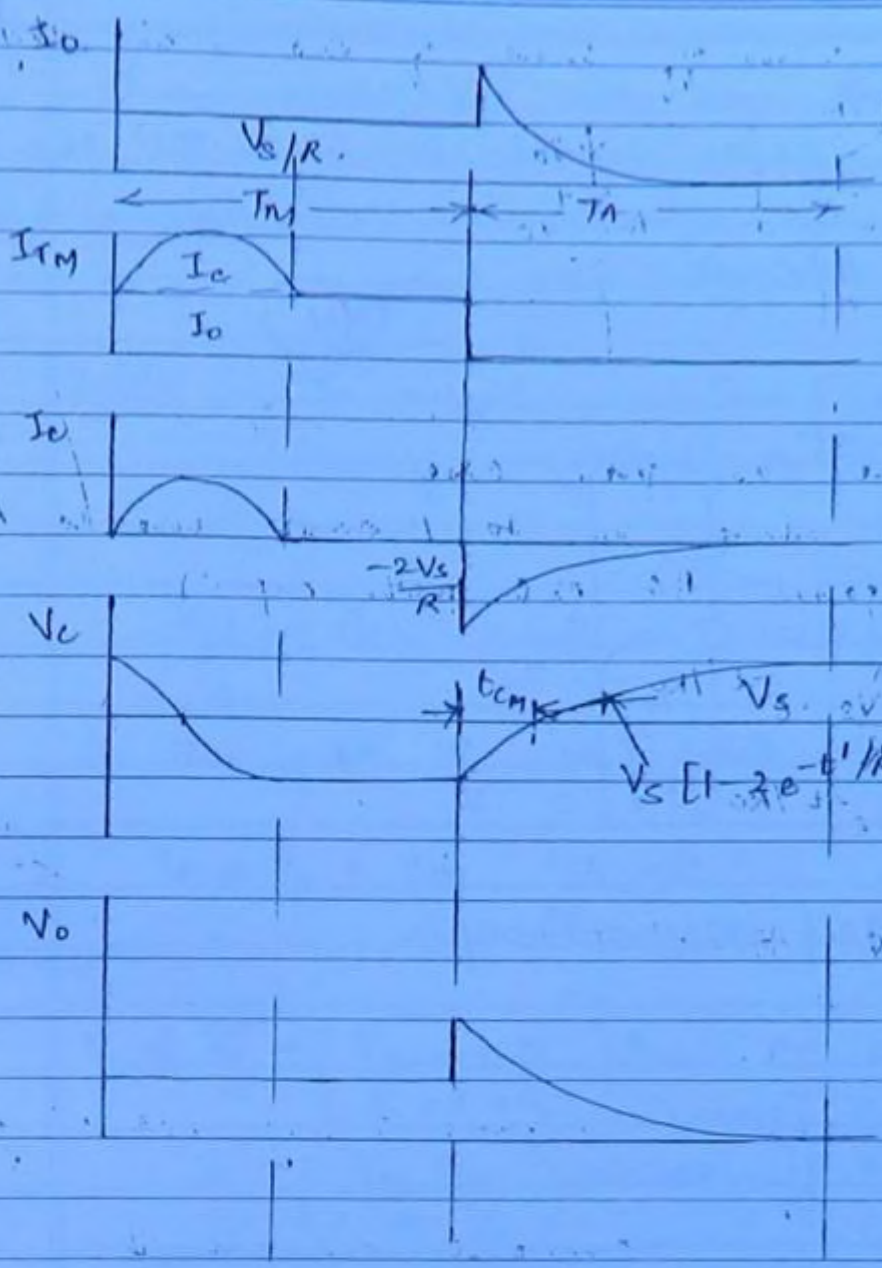


FIRING CIRCUITS

gives the required gate signal to turn ON the SCR.

! Resistance firing circuit -

(44)

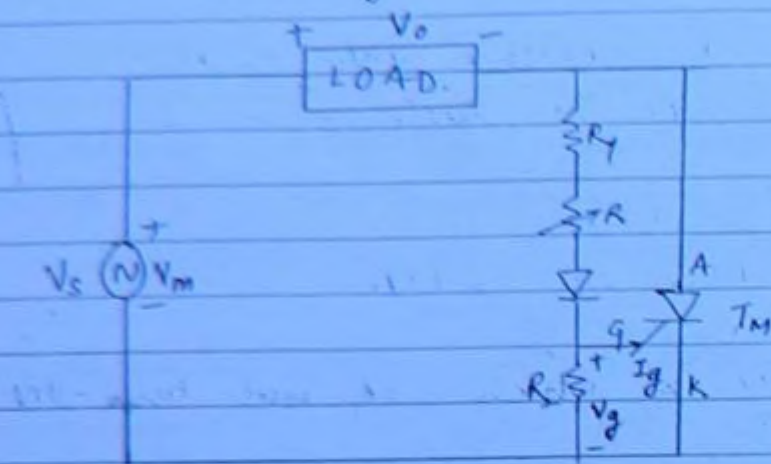

Main ckt : 1ϕ Half Wave Rectifier

Gate specifications \rightarrow

$$I_{g \min} \leq I_g \leq I_{g \max}$$

$$V_{g \min} \leq V_g \leq V_{g \max}$$

R_1 \rightarrow To limit gate current I_g within max^m value ($I_{g \max}$)

For worst condition.

$$\text{Maximum gate current} = \frac{V_m}{R_1} \leq I_{g \max}$$

$$\therefore R_1 \geq \frac{V_m}{I_{g \max}}$$

R_2 \rightarrow To limit gate vlg V_g within max^m value ($V_{g \max}$)

For worst condition.

$$\text{Maximum gate vlg} = \left(\frac{V_m}{R_1 + R_2} \right) R_2 \leq V_{g \max}$$

From above eqⁿ we can design value of R_2 .

Variable R → To change the timing of gate signal i.e. α

(45)

Diode → To avoid negative gate signal during negative cycle of source.

V_{gt} → Gate turn on voltage.

At the gate V_g at which SCR will turn-ON

i.e. at $V_g = V_{gt}$ SCR → ON
($\omega t = \alpha$)

$$V_g = \left(\frac{V_m \sin \omega t}{R_1 + R + R_2} \right) R_2$$

$$V_g = \left(\frac{V_m R_2}{R_1 + R + R_2} \right) \sin \omega t$$

FF → $V_g = V_{gm} \sin \omega t$ where $V_{gm} = \frac{V_m R_2}{R_1 + R + R_2}$

$$V_g = 0$$

→ $T_{on} = 0$

At $V_g = V_{gt}$ SCR → ON

$$V_{gm} \sin \alpha = V_{gt}$$

$$\alpha = \sin^{-1} \frac{V_{gt}}{V_{gm}}$$

↑ R $V_{gm} \downarrow \alpha \uparrow$

for example

(I) $R = R_a$
 $\alpha = \alpha_a$

$$V_{gma} = \frac{V_m R_2}{R_1 + R_a + R_2}$$


$$V_{g_a} = V_{gma} \sin \omega t$$

II $\uparrow R = R_b$
 $\alpha = \alpha_b$

$$V_{gmb} < V_{gma}$$

$$V_{g_b} = V_{gmb} \sin \omega t$$

(4b)

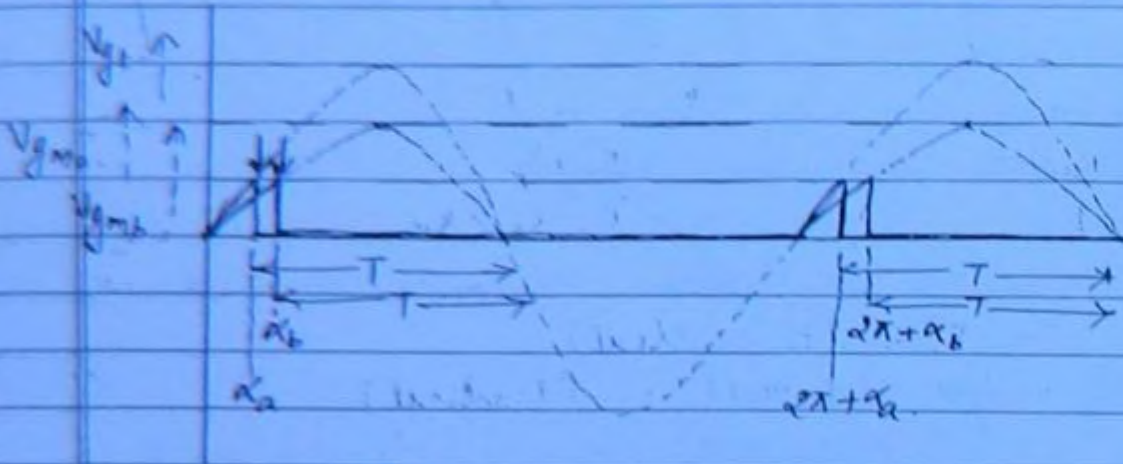


$\uparrow R \quad V_{gm} \downarrow \therefore \alpha \uparrow$


Limitation of R firing circuit.


The maximum firing angle is limited to 90°

3 RC firing circuit -

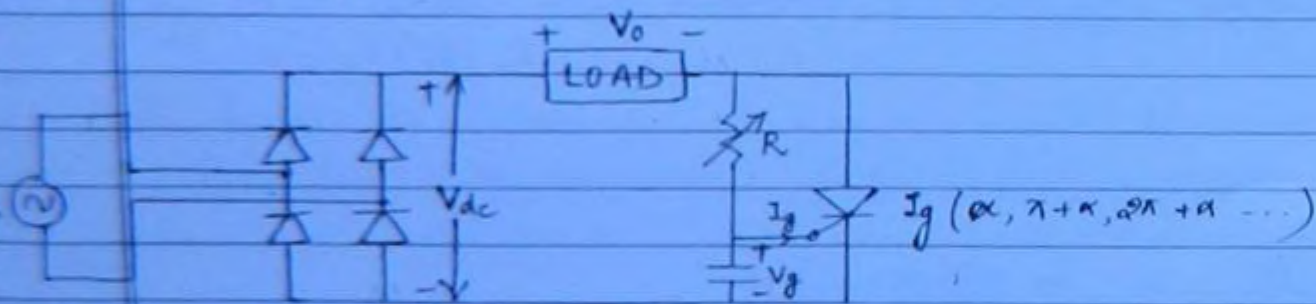

Main circuit: Full wave Rectifier

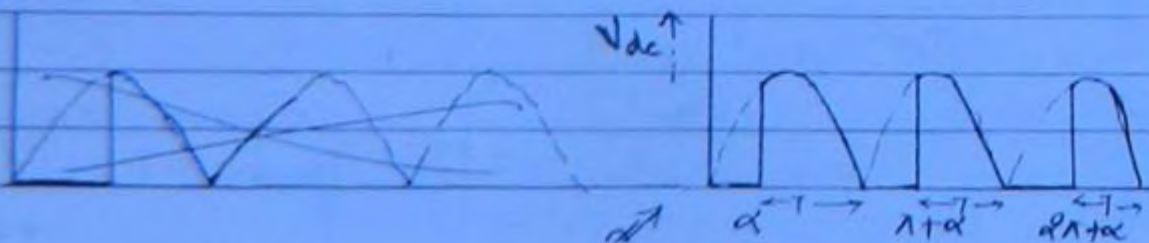

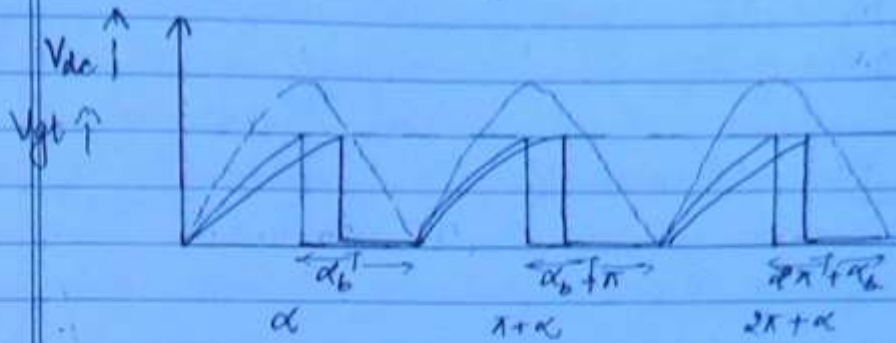

(17)

$$I = R = R_a$$

$$T = R_{ac}$$

$$V_{g_a} \uparrow$$


$$T = R_{bc}$$

$$R = R_b > R_a$$

$$0 < \alpha < 180^\circ \text{ (Ideal)}$$

$$(5 \text{ to } 7^\circ) \leq \alpha \leq (165 \text{ to } 175^\circ) \text{ (Practical)}$$

VJT firing circuit -

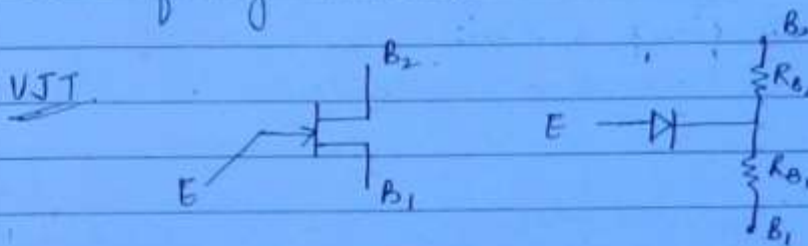


$B_1, B_2 \rightarrow$ Base terminals

$R_{B1}, R_{B2} \rightarrow$ Base resistances

$E \rightarrow$ Emitter terminal

When diode is ON
VJT ON

When diode is OFF
VJT OFF

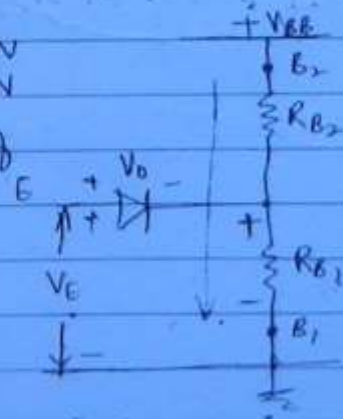

$$V_{R_{B1}} = \left(\frac{R_{B1}}{R_{B1} + R_{B2}} \right) V_{EB}$$

$$V_{R_{B1}} = \eta V_{EB}$$

$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$$

Intrinsic stand off ratio

$$V_E = V_{R_E} + V_D$$

$$= \eta V_{BB} + V_D$$

$$\boxed{\uparrow V_E \Rightarrow V_p}$$

then UJT \rightarrow ON

(when $\uparrow V_E$ reaches V_p UJT \rightarrow ON)

$$V_p = \eta V_{BB} + V_D$$

peak point voltage

OFF to ON state

When UJT is switching from the base resistance R_{B1} starts decreasing i.e. UJT exhibits negative resistance behaviour. This reduces emitter V_E .



$$\boxed{V_E \downarrow \Rightarrow V_v}$$

\rightarrow UJT OFF

(when $\downarrow V_E$ reaches V_v UJT \rightarrow OFF)



Valley voltage

UJT working as Relaxation Oscillator -

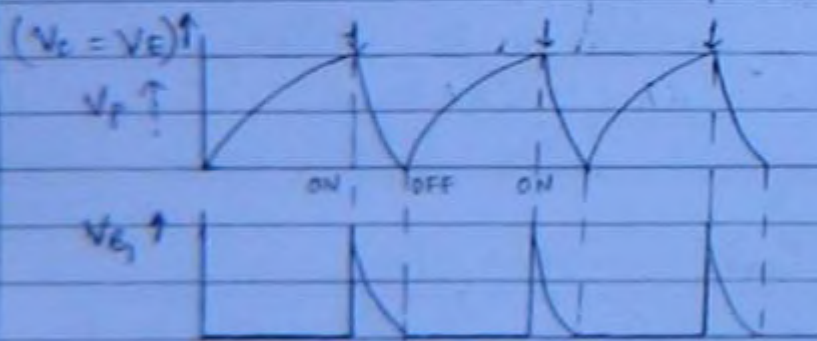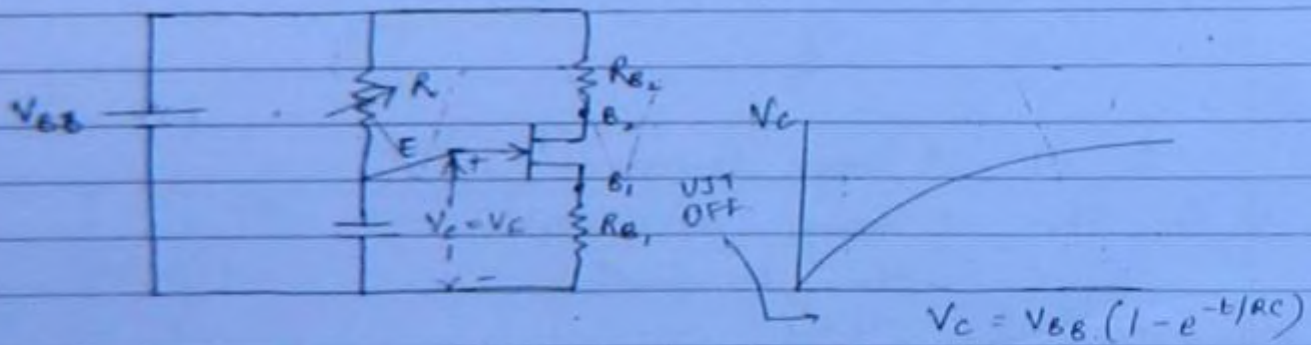


Synchronized UJT firing circuit - (49)

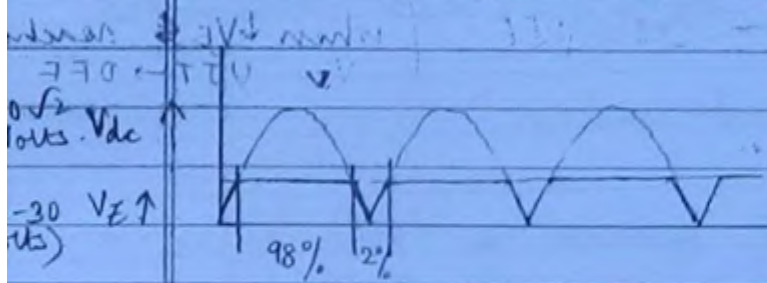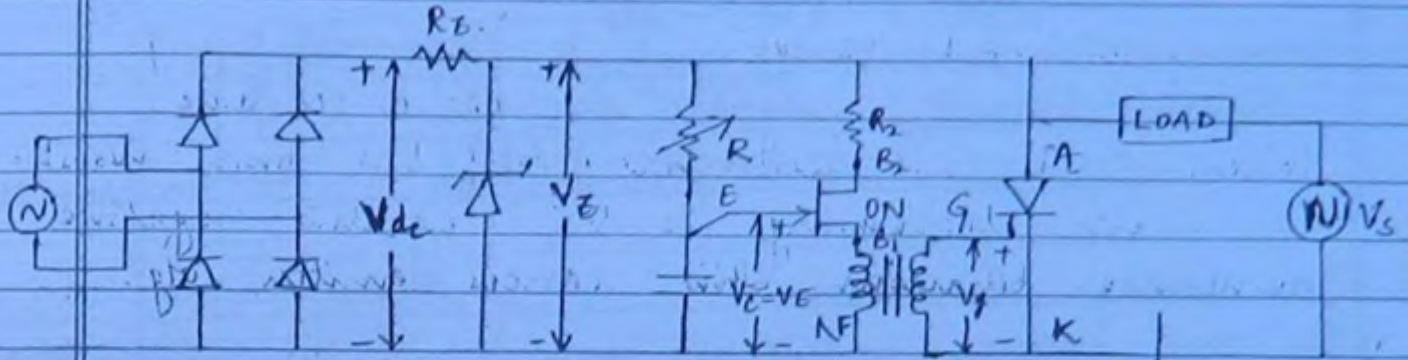We must synchronise the firing circuit with the main circuit in order to match the timing of gate pulse in both the circuits. Here we must use same power supply in the main & firing circuits for the purpose of synchronisation.



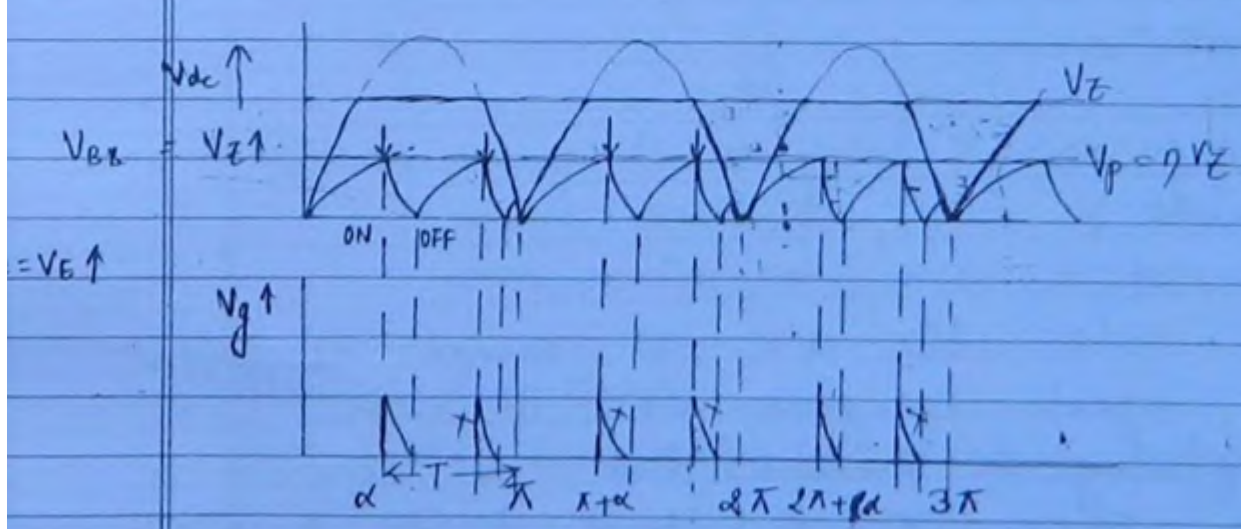main circuit
Half wave rectifier
 $I_g(\alpha, 2\pi + \alpha, \dots)$




PROTECTION OF THYRISTORS -

1 Over Current Protection -

50

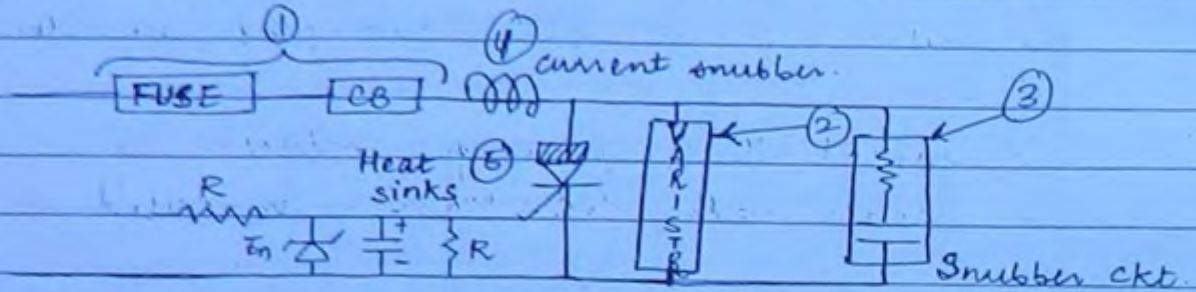For over current protection, we must connect fuse or circuit breaker in series with the SCR.




2 Over Voltage Protection -

For over voltage protection, varistors are connected across the SCR.

Varistors \rightarrow Non-linear resistor

All metal oxide resistors behave as non-linear R.

3 dV/dt Protection -

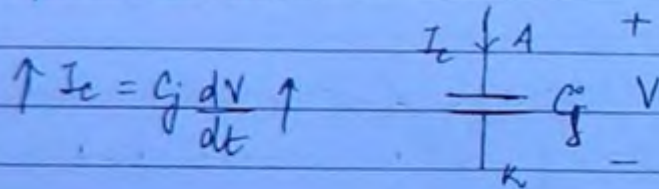

At high dV/dt the SCR is turned ON before the gate signal is given. This is known as false triggering. To prevent this a capacitor is connected across SCR to limit dV/dt . A resistor is connected in series with the C, to reduce the discharge current magnitude. This is called Snubber circuit.

4 di/dt Protection

(57)

When $di/dt >$ (spread velocity of charge carriers) the charge accumulation increases cumulatively in a small conduction area & leads to the formation of hot spots damaging the device.

To prevent this, a large inductor is connected in series with the SCR. This is called current snubber.



Initial conduction area \uparrow


(*) di/dt capability of thyristor can be improved by:

i) \rightarrow by increasing I_g or
 \rightarrow by increasing $\frac{dI_g}{dt}$

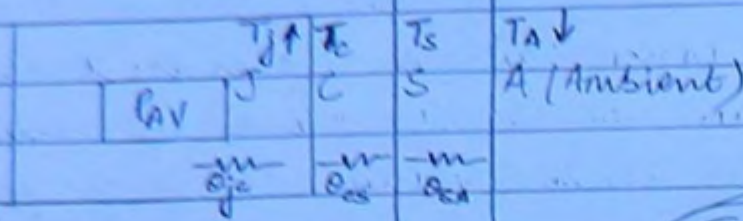
ii) \rightarrow by using Centre Gated Thyristor.
(initial conduction area is increased when centre gated SCR is preferred)

5 Thermal Protection -

Heat sinks are used for thermal protection.



(52)

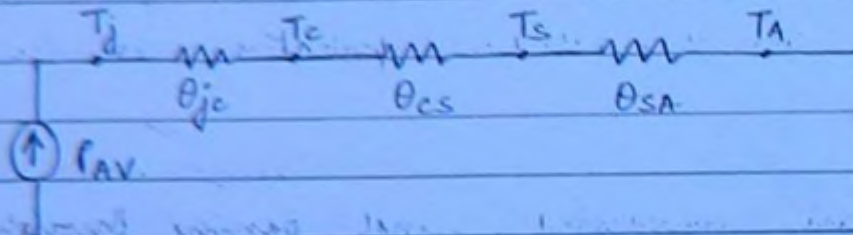

$$P_{AV} = \frac{T_j - T_c}{\theta_{jc}} = \frac{T_c - T_s}{\theta_{cs}} = \frac{T_s - T_A}{\theta_{sa}} = \frac{T_j - T_s}{\theta_{jc} + \theta_{cs}} = \frac{T_c - T_A}{\theta_{cs} + \theta_{sa}} = \frac{T_j - T_A}{\theta_{jc} + \theta_{cs} + \theta_{sa}}$$

* Rating of SCR is $\propto \sqrt{P_{AV}} \propto \sqrt{\frac{T_j - T_A}{\theta_{ja}}}$

* Rating of SCR is decided by cooling methods in the heat sink. Lesser the ambient temperature (T_A) higher the rating of the SCR.

6 Gate Protection. -

(53)

a) Over Current Protection

A resistance is connected in series with the gate to limit the gate current within the permissible value.

b) Over Voltage Protection

Zener diode is connected across gate cathode terminals for overvoltage protection in the gate.

c) Protection against noise signals -

Noise is an unwanted signal passing through the gate terminal. It will false turn ON the SCR.

To prevent it, connect a parallel RC across gate cathode terminals, to protect the SCR against noise signals.

CWB chapter 1

Q1 (b)

$$T_j = 125^\circ\text{C}$$
$$T_s = 70^\circ$$
$$\theta_{jc} = 0.16$$
$$\theta_{cs} = 0.08$$

$$P_{AV1} = \frac{T_j - T_s}{\theta_{jc} + \theta_{cs}} = \frac{125 - 70}{0.16 + 0.08} = 229.167 \text{ W}$$


$$P_{AV2} = \frac{125 - 60}{0.16 + 0.08} = 270.83 \text{ W}$$

$$\% \text{ Increase in Rating of SCR} = \frac{\sqrt{PAV_2} - \sqrt{PAV_1}}{\sqrt{PAV_1}} \times 100$$

$$= \frac{\sqrt{270.83} - \sqrt{229.16}}{\sqrt{229.16}} \times 100$$

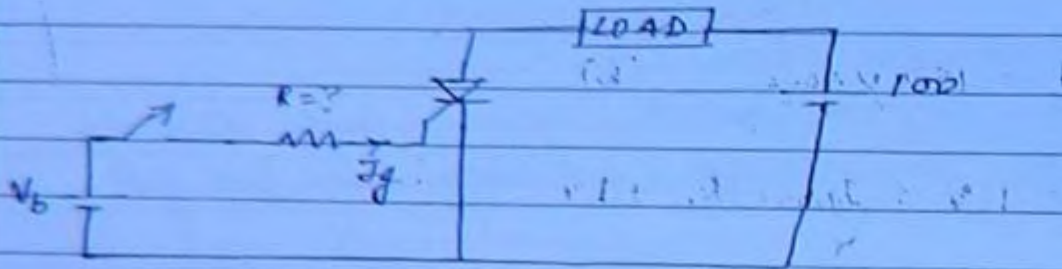(54)

$$\% \text{ Increase in Rating} = 8.7\%$$



$$V_b = 12 \text{ V}$$

$$I_{g \text{ min}} = 100 \text{ mA}$$

For worst condition


$$\text{Minimum possible } I_g = \frac{12 - 4}{R}$$

$$\frac{12 - 4}{R} \geq 10 \text{ mA}$$

$$R \leq 800 \Omega \quad (d)$$

$$C = \frac{S F \times t_q}{R \ln 2} = \frac{2 \times 50 \times 10^{-6}}{50 \times \ln 2} = 2.88 \mu\text{F} \quad (a)$$
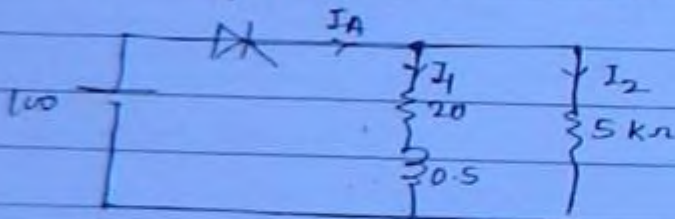
$$T_{on} = 5 \mu\text{sec} \quad I_L = 50 \text{ mA} \quad I_H = 40 \text{ mA}$$



$$I_A = I_1 + I_2$$

$$= \frac{V_s (1 - e^{-t/T_1})}{R_1} + \frac{V_s}{R_2}$$

$$T_1 = \frac{L_1}{R_1} = \frac{0.5}{20} = \frac{1}{40}$$

$$I_A = \frac{100}{20} (1 - e^{-40t}) + \frac{100}{5 \times 10^3}$$

$$I_A = 5(1 - e^{-40t}) + (20 \times 10^{-3})$$

↓
till I_L

(5)

$$50 \times 10^{-3} = 5(1 - e^{-40t}) + (20 \times 10^{-3})$$

$$\frac{30 \times 10^{-3}}{5} = 1 - e^{-40t}$$

$$t = 150 \mu\text{secs.} \quad (b)$$

$$9V = 1V + I_{gmax} R + 1V$$

$$I_{gmax} = 150 \text{ mA}$$

$$R \geq 46.67 \Omega$$

$$9V = 1V + I_{gmin} R + 1V$$

$$I_{gmin} = 100 \text{ mA}$$

$$R \leq 70 \Omega$$

$$46.6 \leq R \leq 70$$

$$\text{Ans } 47 \Omega \quad (c)$$

Q8. Volt sec rating of pulse transformer
= $10V \times t_{gpw}$

(gate pulse width)

$$t_{gpw} > t_{min}$$

$$I_A = \frac{200}{1} (1 - e^{-t/T})$$

$$\frac{L}{R} = 150 \times 10^{-3} = 0.15$$

$$I_A = 200 (1 - e^{-t/0.15})$$


$$I_L \rightarrow 150 \text{ mA} = 200 (1 - e^{-t/0.15})$$

$$t_{min} = 187 \mu\text{s}$$

$$t_{gpw} > 187 \mu\text{s}$$

Ans (d)

10. GTO (Gate Turn OFF Thyristor)

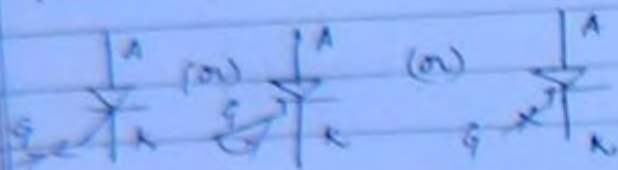


(58)

To turn ON $\rightarrow + I_g$ (When A +ve w.r.t. K)

To turn OFF $\rightarrow - I_g$ (When $I_{gN} \rightarrow 20-25\% [I_{TA}], [I_{MA}]$)

The V-I characteristics of GTO for conventional thyristor (SCR) are similar.

Switching Characteristics of GTO

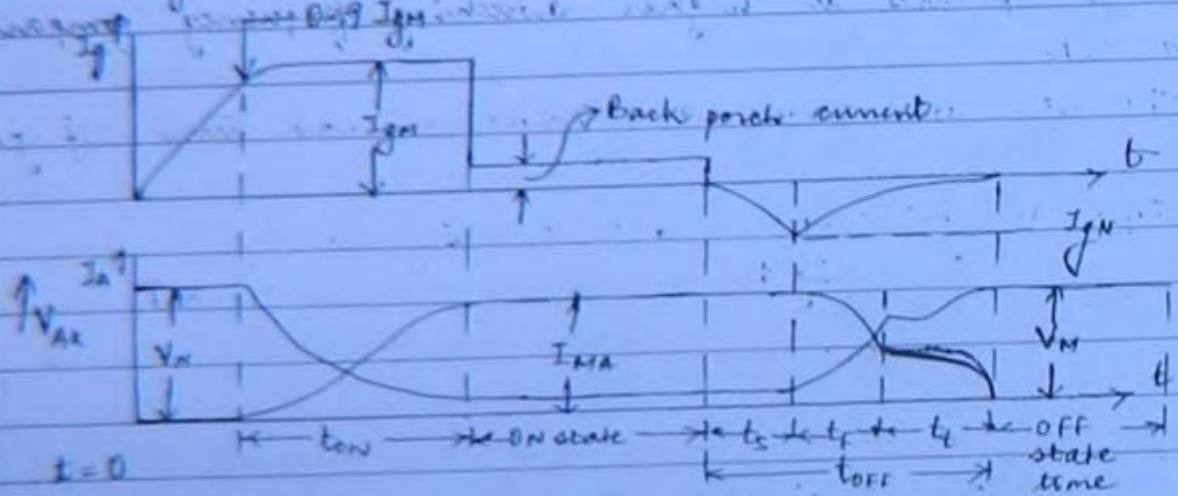

OFF \rightarrow ON
turn ON char.

During storage time the stored charge carriers are removed from the device

$$t_s = \text{storage time}$$

During fall time rate of reduction of anode current is fast
 $t_f = \text{fall time}$

* During tail time rate of reduction of anode current is slow.

t_t = tail time

(57)

Compare GTO with conventional thyristor (SCR)

1. I_L & I_H are higher in GTO.
2. On state v_g drop is higher in GTO.
3. Gate signal requirement is higher in GTO.
4. Reverse v_g blocking capability is lesser than forward v_g blocking capability in GTO.
5. GTO is more efficient & compact compared to SCR.
6. GTO has fast turn on & faster turn off.
∴ it operates at higher switching frequency compared to SCR.
7. GTO has low turn-on gain & low turn-off gain.

$$\downarrow \text{turn-on gain} = \frac{I_{MA}}{(+I_g) \uparrow}$$

$$\downarrow \text{turn-off gain} = \frac{I_{MA}}{-I_{gNT} \uparrow}$$

Applications -


* In inverters & choppers we can replace the SCR by using a GTO to avoid commutation circuit.

ASCR (Asymmetrical SCR)

It's a special thyristor with reduced reverse vlg blocking capability.

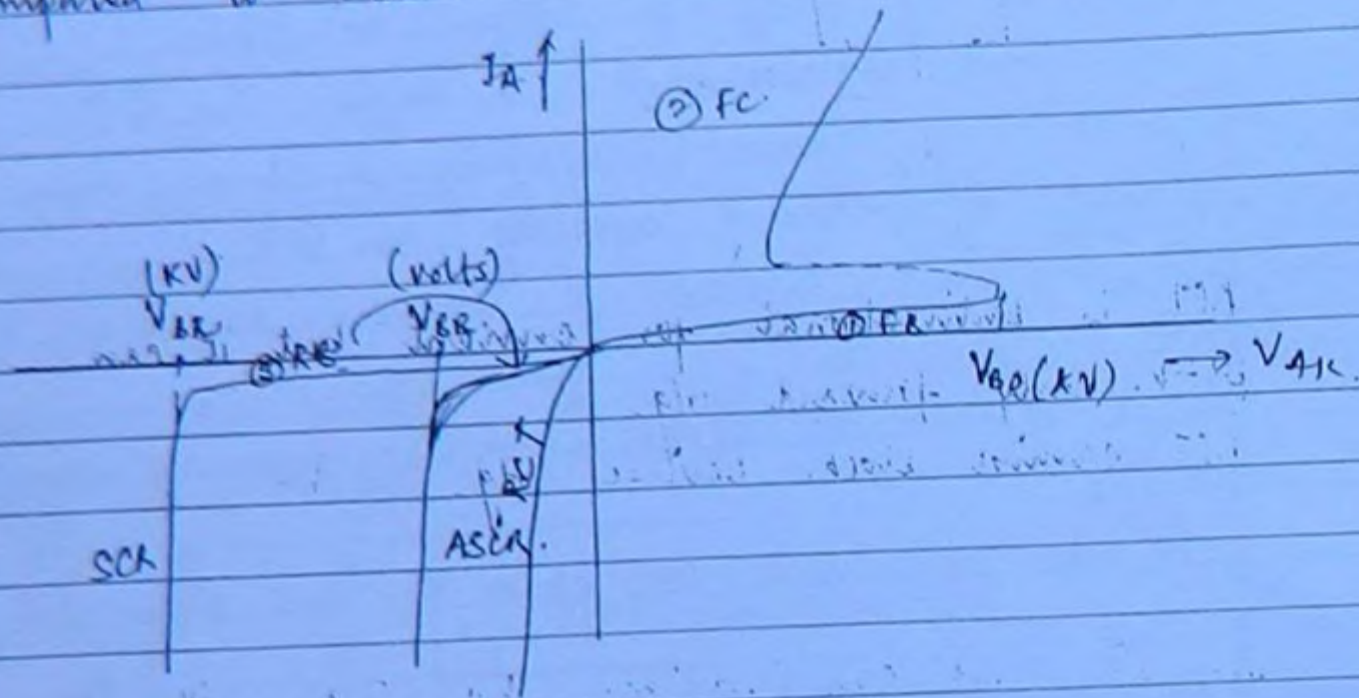(58)

ASCR has fast turn-on & turn off times.
∴ it operates at higher switching frequency as compared to SCR.




Applications -

In vlg source inverters (VSI) we can replace the SCR by ASCR.

RCT (Reverse Conducting Thyristor)

An antiparallel diode is inbuilt across the SCR within the same structure.

(59)

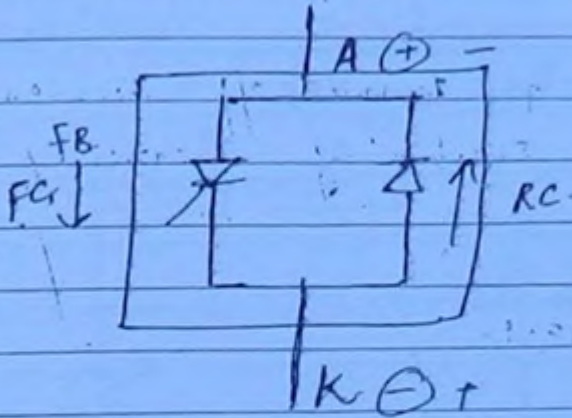



RCT is bidirectional for current but it can block only forward vlg.
RCT cannot block reverse vlg.

Applications -

In VSI, we can replace the SCR with an antiparallel diode by RCT.

TRIAC -

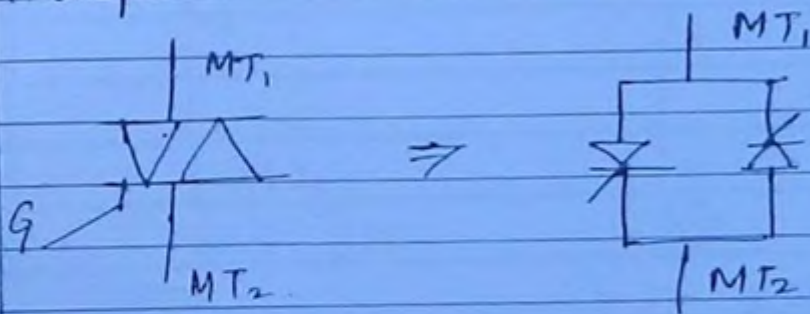

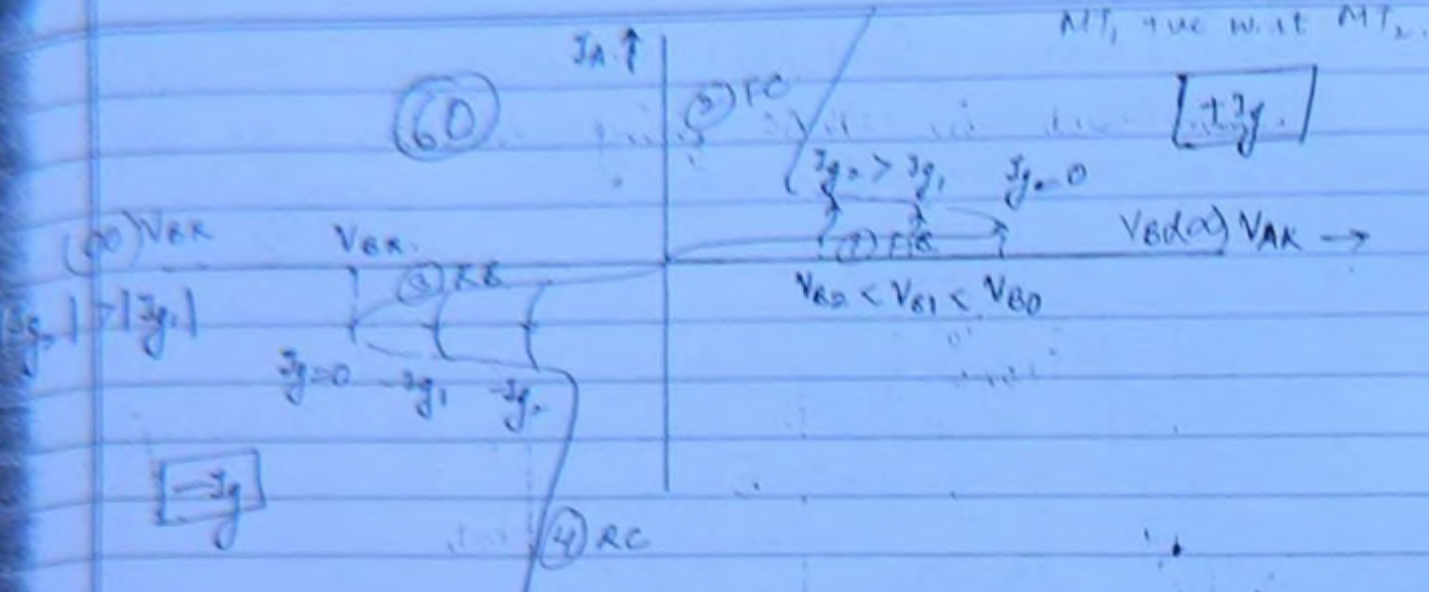

$MT_1 -ve w.r.t MT_2$



Applications -

used in AC v/f controllers as AC switch

Limitations of Triac -

Can AC v/f controllers, its used only for resistive loads and low inductive loads. Its not preferred for high inductive loads with high time constant.

DIAC

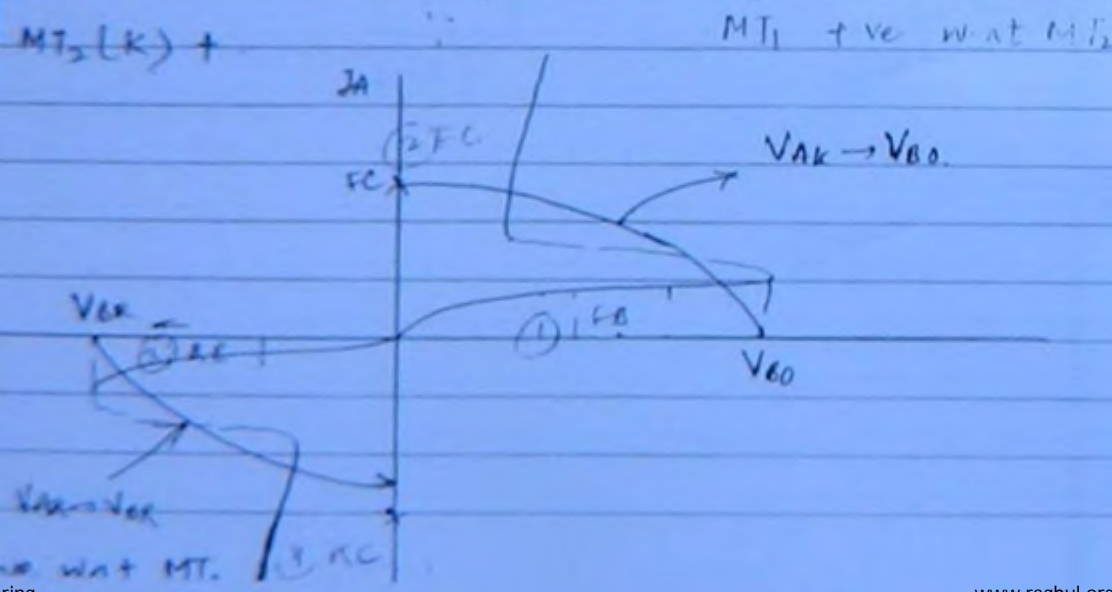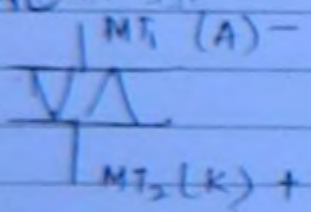


Applications -

main used in TRIAC firing circuit.


(6)

TRIAC firing circuit using DIAC

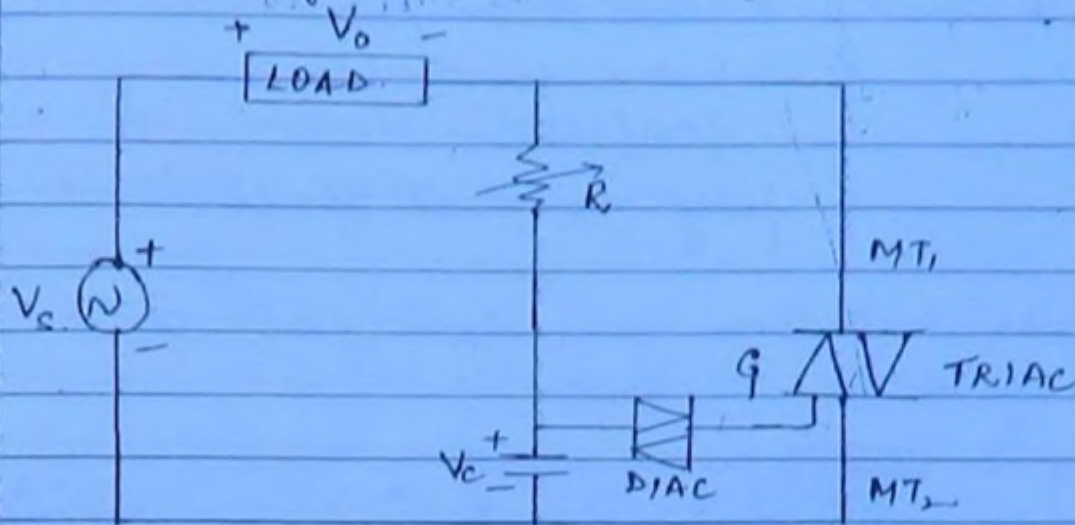

different DA and applications etc DA and basic


main ck \rightarrow AC vlg controller.

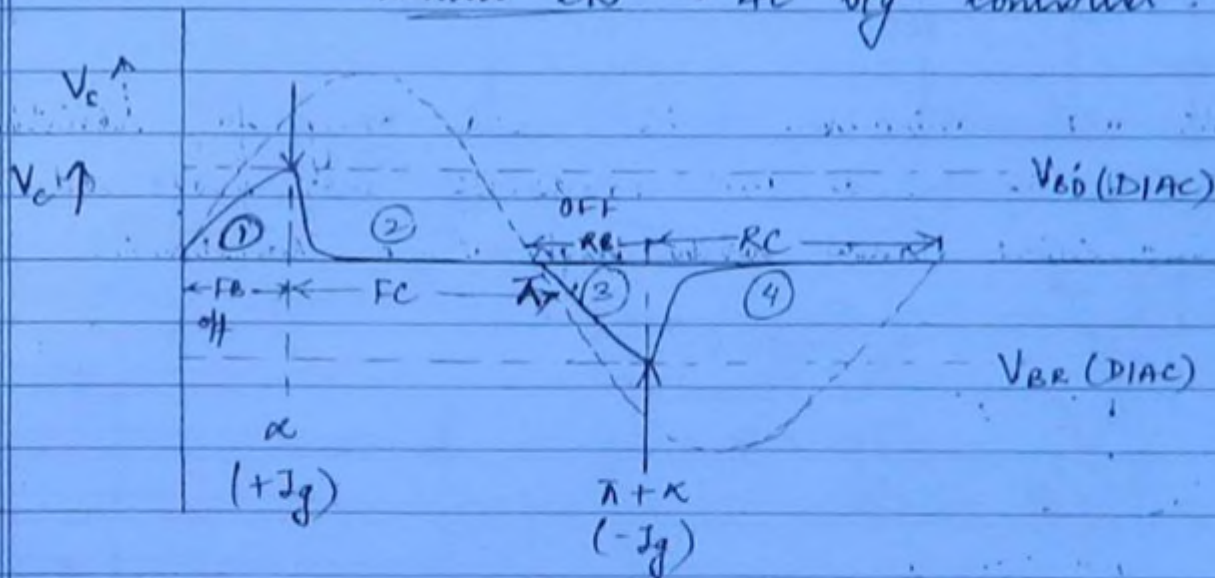

POWER TRANSISTORS -

(62)

POWER BJT

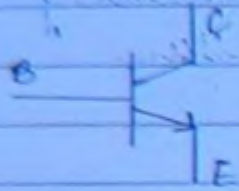



C, E \Rightarrow Major terminals

B \Rightarrow Control terminal

(ON/OFF)

\therefore fully controlled device

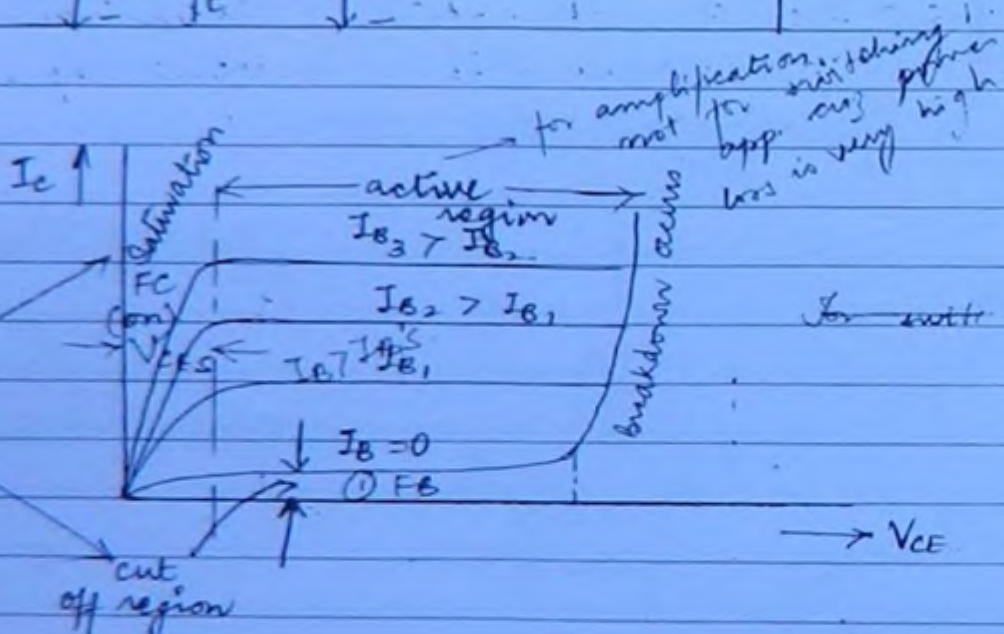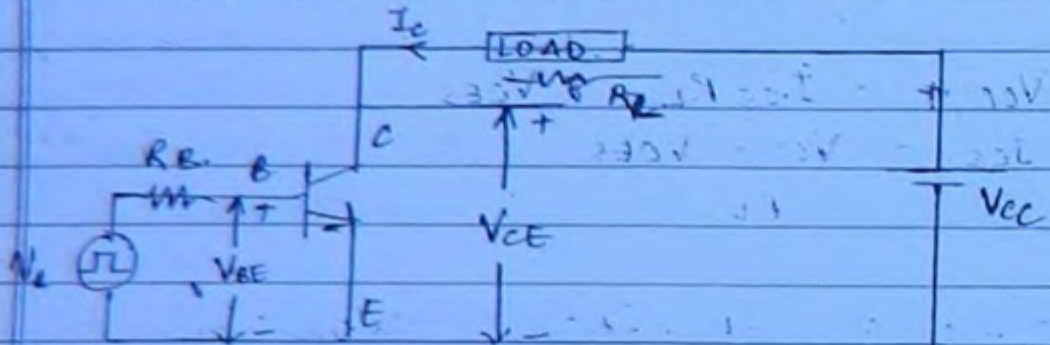* Here we require continuous gate signal (base) to maintain the device in ON state.



$I_{B(sat)}$ \rightarrow min^m base current required to drive the transistor into saturation.

* For switching applications in PE, the transistor should be operated in the cut-off region for OFF state & saturation region for ON state. Active region is not preferred for switching applications. It's only preferred in amplifiers.

(63)

Consider transistor in Saturation region


$\beta = \beta_{DC}$

$V_{CE} = V_{CES}$
 $I_C = I_{CS}$

KVL $\rightarrow V_{CC} = I_{CS} R_L + V_{CES}$
 $I_{CS} = \frac{V_{CC} - V_{CES}}{R_L}$

$I_{BS} = \frac{I_{CS}}{\beta} \left\{ \begin{array}{l} I_B > I_{BS} \rightarrow \text{saturation} \\ I_B < I_{BS} \rightarrow \text{active region} \end{array} \right.$

Switching Characteristics of BJT -

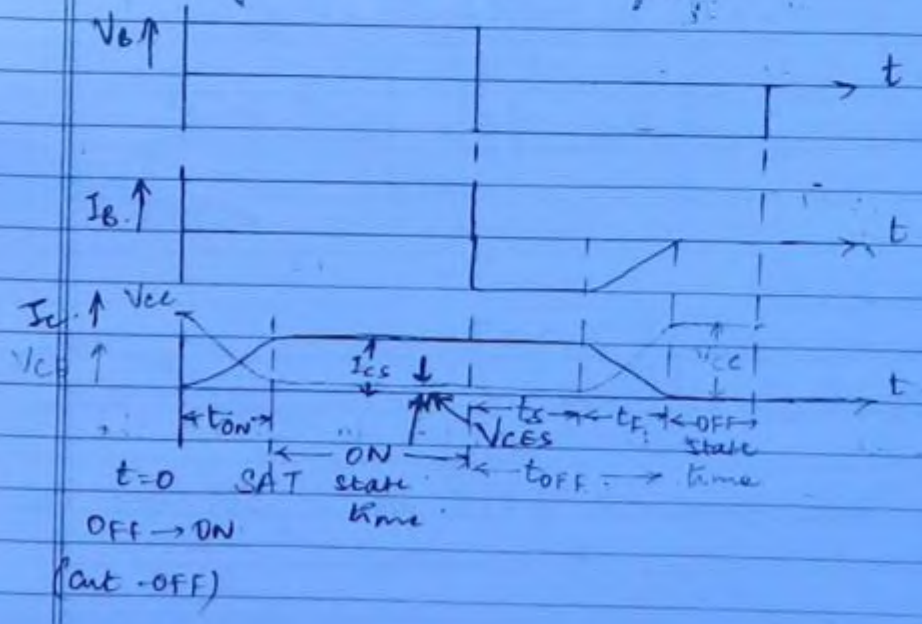


As during storage time, stored charges present in the base region is removed. (64)

Instantaneous power loss during t_{on} process $P(t) = V_{CE}(t) I_c(t)$

Energy lost during turn-on process $= \int_0^{t_{on}} P(t) dt$

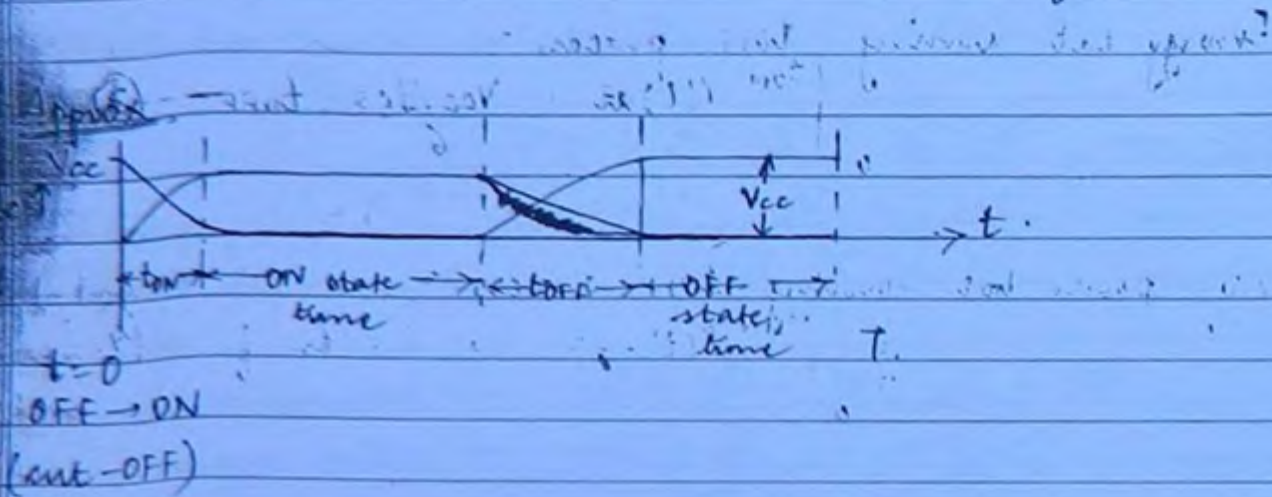Avg power lost during turn-on process $= \frac{1}{T} \int_0^{t_{on}} P(t) dt$



t_{on} process
 $I_c = \left(\frac{I_{cs}}{t_{on}} \right) t$

$V_{CE} = \left(\frac{-V_{cc}}{t_{on}} \right) t + V_{cc}$

t_{off} process
 $I_c = \left(\frac{-I_{cs}}{t_{off}} \right) t + I_{cs}$

$V_{CE} = \left(\frac{V_{cc}}{t_{off}} \right) t$

$P(t) = V_{CE}(t) I_c(t)$
 $= \left[\left(\frac{-V_{cc}}{t_{on}} t \right) + V_{cc} \right] \left[\left(\frac{I_{cs}}{t_{on}} \right) t \right]$

Energy lost during t_{on} process $= \int_0^{t_{on}} P(t) dt = \frac{V_{cc} \cdot I_{cs} \cdot t_{on}}{6}$ (1)

Aug power lost during ton process = $\frac{1}{T_0} \int_0^{t_{on}} P(t) dt$

(6.5) = $\frac{V_{cc} I_{cs} t_{on} f}{6}$ - (2)

Instantaneous power loss during toff process

$P(t) = V_{CE}(t) \cdot I_c(t)$
 $= \left(\frac{V_{cc}}{t_{off}} t \right) \left(-\frac{I_{cs}}{t_{off}} t + I_{cs} \right)$


Energy lost during toff process =


$\int_0^{t_{on}} P(t) dt = \frac{V_{cc} \cdot I_{cs} \cdot t_{off}}{6}$ - (3)

Aug power lost during toff process =

$\frac{1}{T_0} \int_0^{t_{on}} P(t) \cdot dt = \frac{V_{cc} I_{cs} t_{off} f}{6}$ - (4)

2 POWER MOSFET -

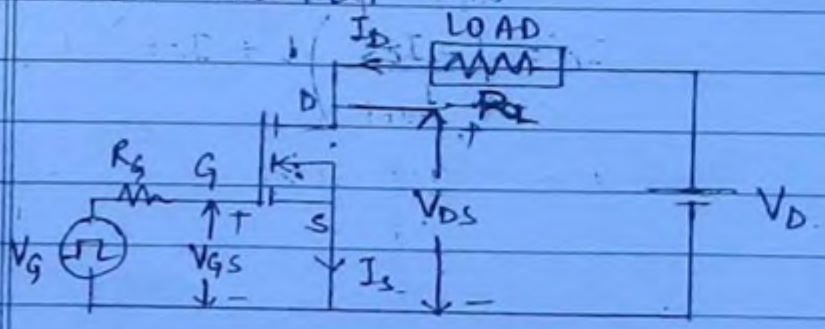

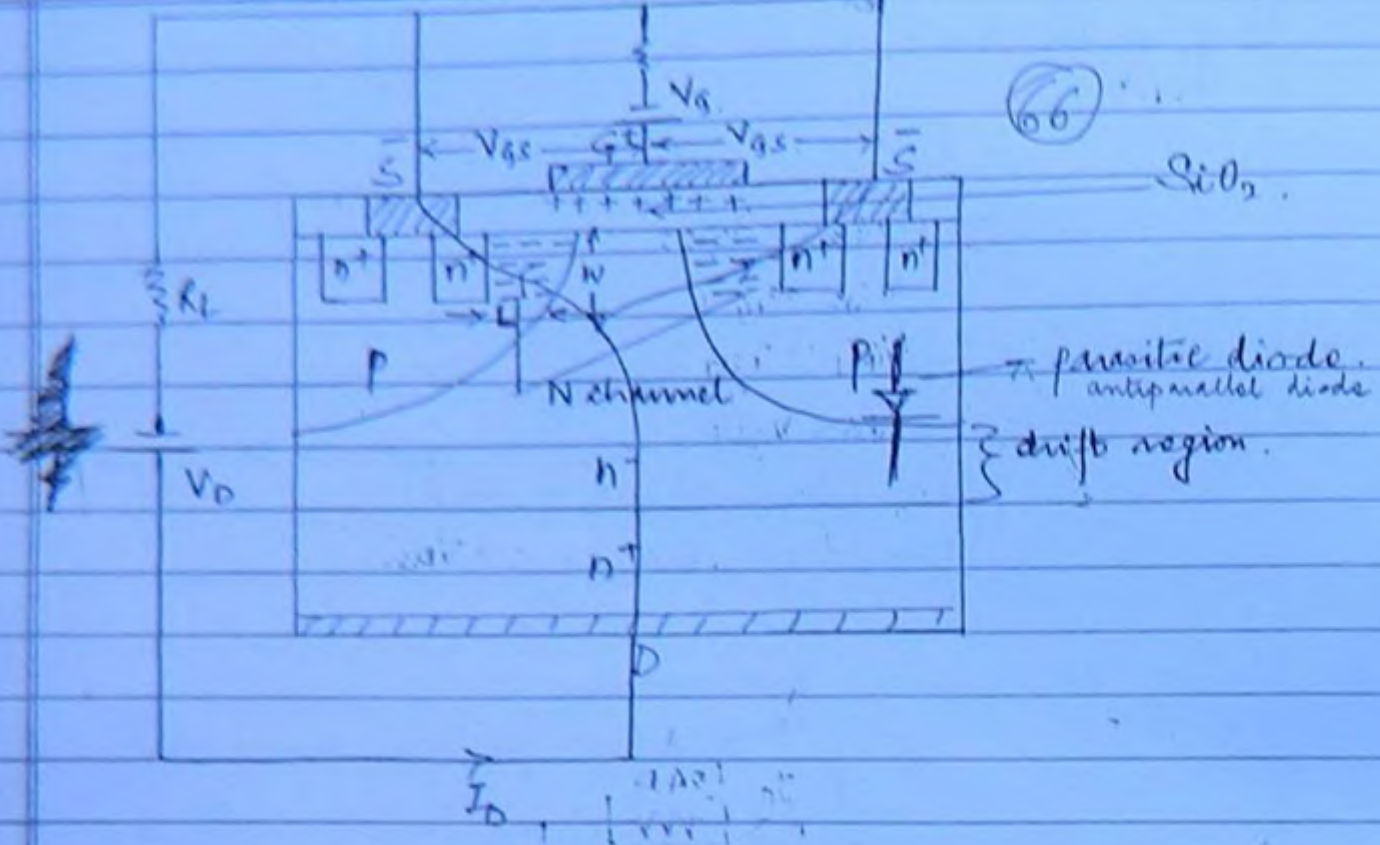

Here n is n and p is p

② The MOSFET starts conducting only after the formation of N-channel when positive gate signal is given. Here the conduction is only due to majority carriers, since there is no charge carrier f .
 The reverse & recovery time delay is very much reduced. Hence Mosfet operates at high switching frequency.

$$V_{GS} \uparrow \therefore W \uparrow \therefore R_{ch} \downarrow \therefore I_D \uparrow$$


$$V_{GS} \uparrow, I_D \uparrow$$

$$I_D \uparrow, I_C \uparrow$$


$$\text{channel resistance } \downarrow R_{ch} \propto \frac{L}{W \uparrow}$$

$$V_{GS} \uparrow, W \uparrow$$

(67)

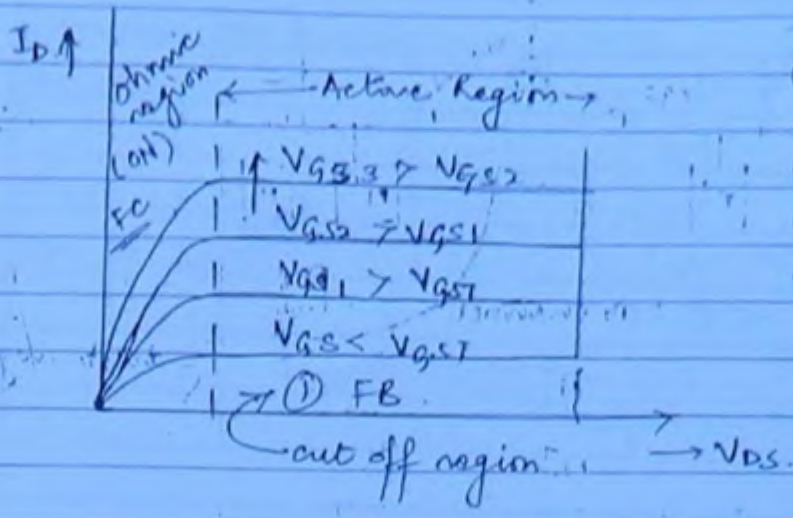



3 IGBT -

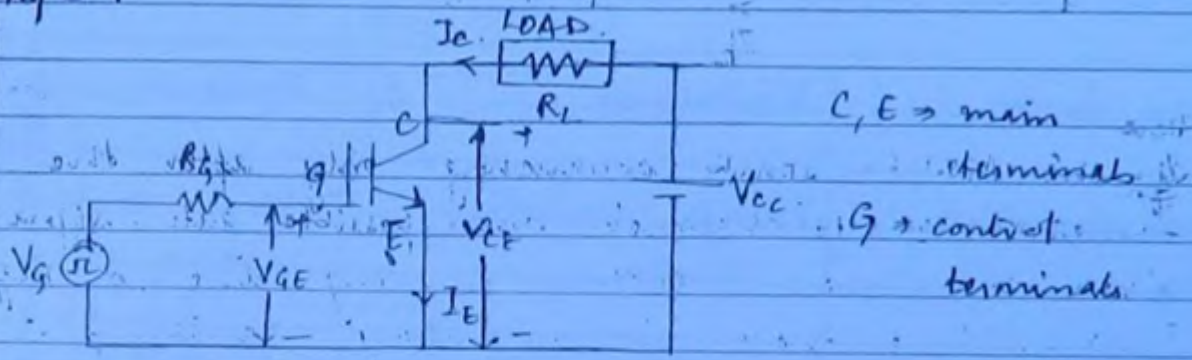

IGBT is a hybrid device that gives the advantages of both MOSFET & BJT.

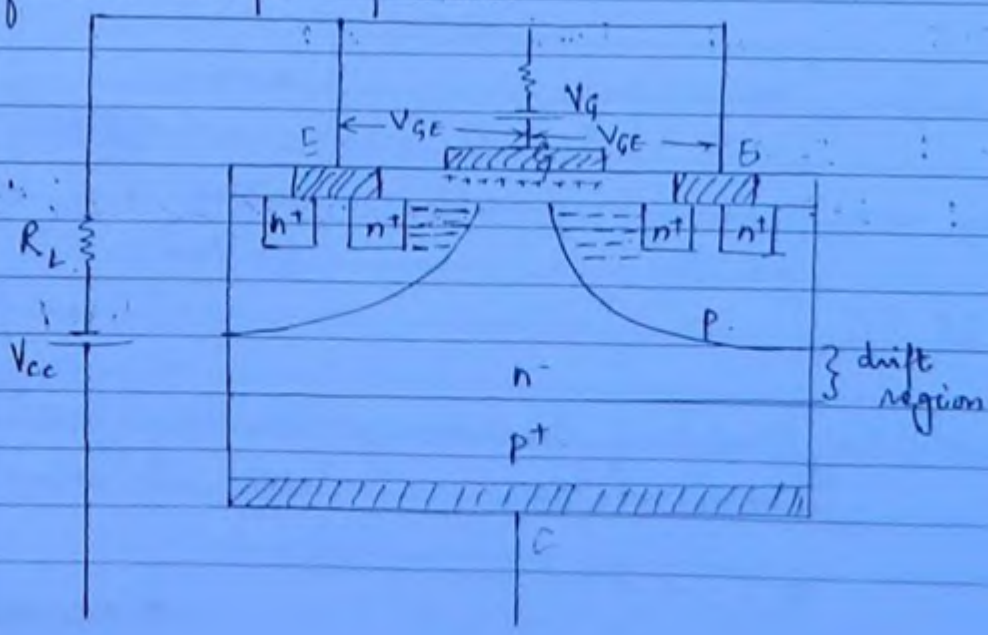IGBT switching is like MOSFET construction like BJT.



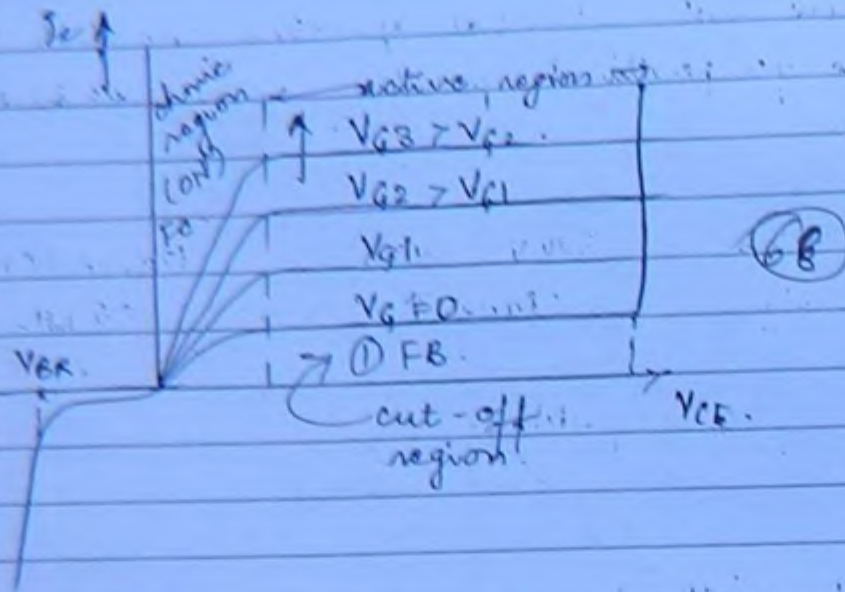

| POWER BJT | POWER MOSFET | IGBT |
|---|------------------------------------|------------------------------------|
| 1. Bipolar device | Unipolar | Bipolar |
| 2. Current controlled device | Voltage controlled device | Voltage controlled device |
| 3. Low i/p impedance | high i/p impedance | high i/p impedance |
| 4. on state v/d drop & conduction loss is less | more | less |
| 5. Switching loss higher | less low | less low |
| 6. ^{DISADV} Negative Temp co-eff for R_{on} Temp \uparrow R_{on} \downarrow $I \uparrow$ $P \uparrow$ | Positive Temp co-eff for R_{on} | Positive Temp co-eff for R_{on} |
| \therefore Secondary Breakdown occurs | Secondary Breakdown will not occur | Secondary Breakdown will not occur |

7. BJTs are not advisable for parallel operation. Parallel operation is possible. Parallel operation is possible.

69

Ratings 8.

1200V, 800A
10-20 KHz

500V, 140A
1 MHz ↑


1200V, 500A
50 KHz

App


SMPS.

chapter 1 CWB

1 (b)

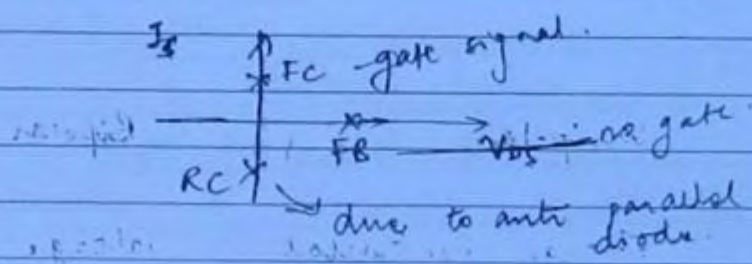

3

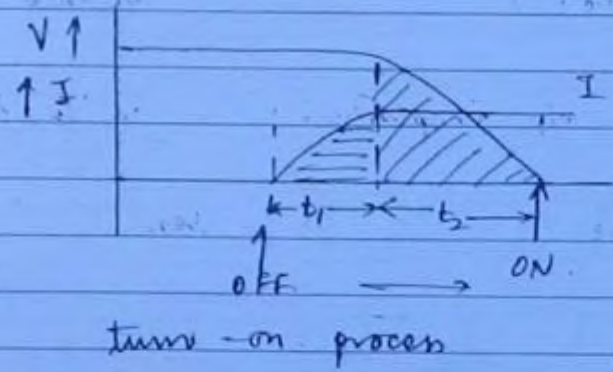


Energy lost during $t_1 = V \int_0^{t_1} I dt$

$= V \cdot \frac{1}{2} I t_1 = \frac{1}{2} V I t_1$

Energy lost during $t_2 = I \left(\int_0^{t_2} V dt \right) = I \cdot \frac{1}{2} V t_2 = \frac{1}{2} V I t_2$

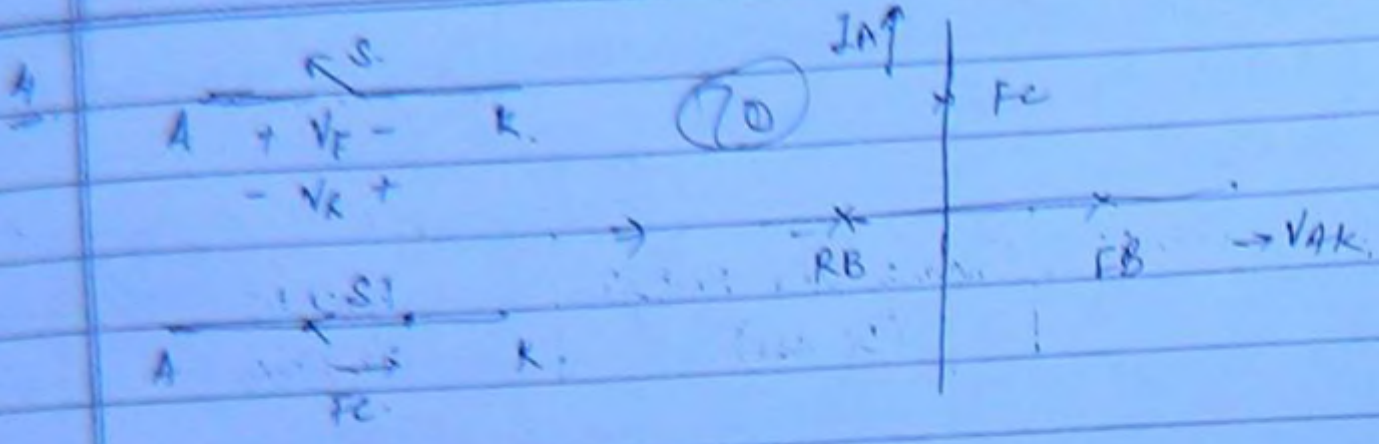
Total = $\frac{1}{2} V I (t_1 + t_2)$ (a)



Ans (c)

In common emitter configuration, the input signal is applied to the base terminal and the output is taken from the collector terminal. The emitter terminal is connected to ground.

17



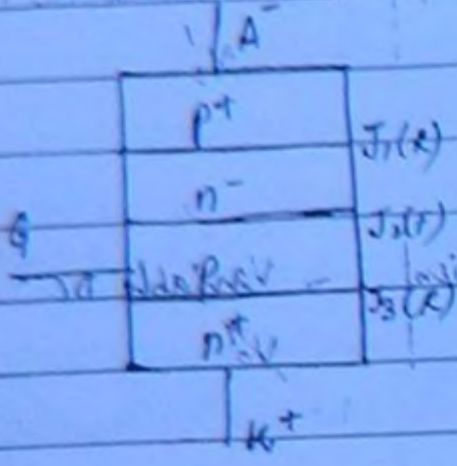


In common base configuration, the input signal is applied to the emitter terminal and the output is taken from the collector terminal. The base terminal is connected to ground.

$P \uparrow$ temp \uparrow $J_c \uparrow$


RECTIFIERS

(7)

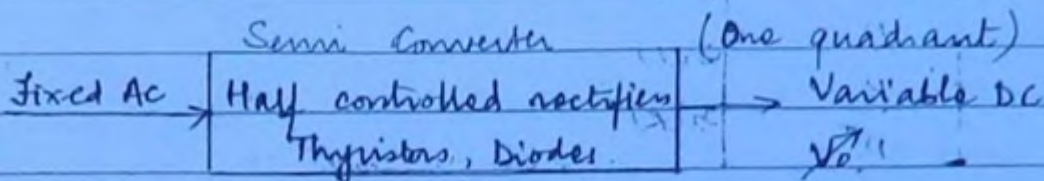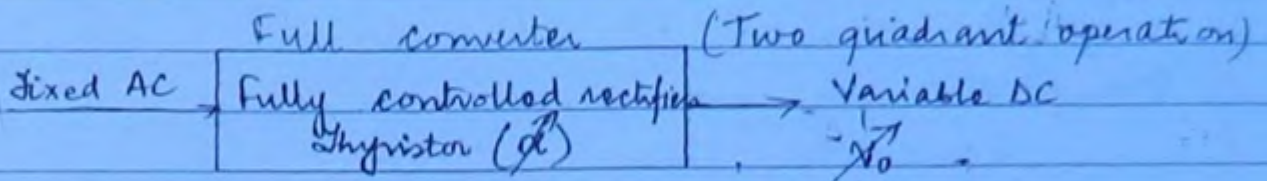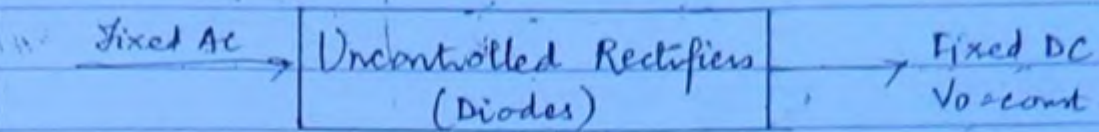


Classification of Converters based on pulse number (m)


1 One pulse converter

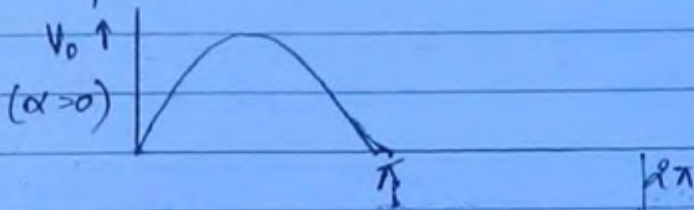

2 Two pulse converter

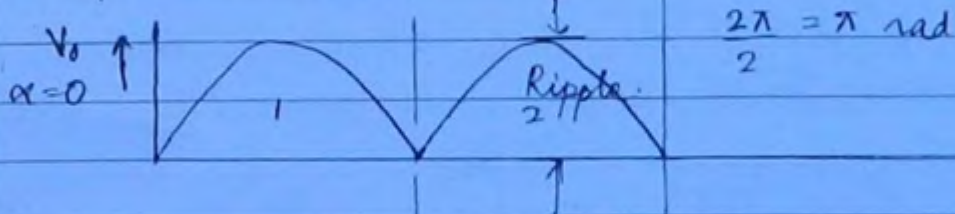

3 Three pulse converter

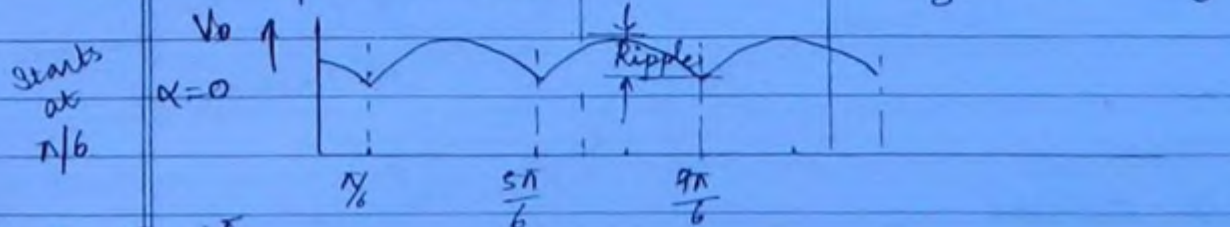


Starts at $\frac{\pi}{6}$

$$\text{so } \frac{\pi}{6} + \frac{4\pi}{6} = \frac{5\pi}{6}$$

Output ripple frequency = $f_0 = m f_s$
 peak to peak

4 6 pulse converter.

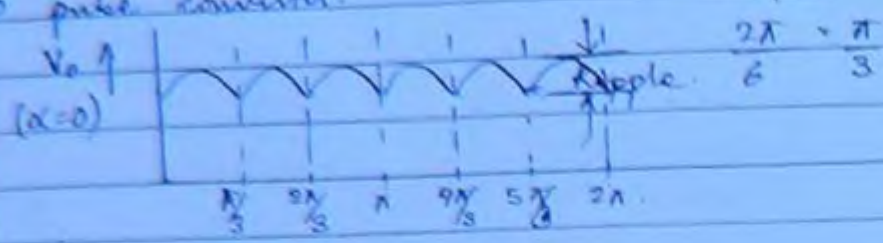

$f_0 = 6 f_s$

$m \uparrow$ ripple \downarrow & harmonics \downarrow

That's why we classify converters based on pulse number.


Applications

Performance of a DC motor fed with converters -
 for R loads (eg heater) harmonics are also useful so take V_{o1} not V_o .

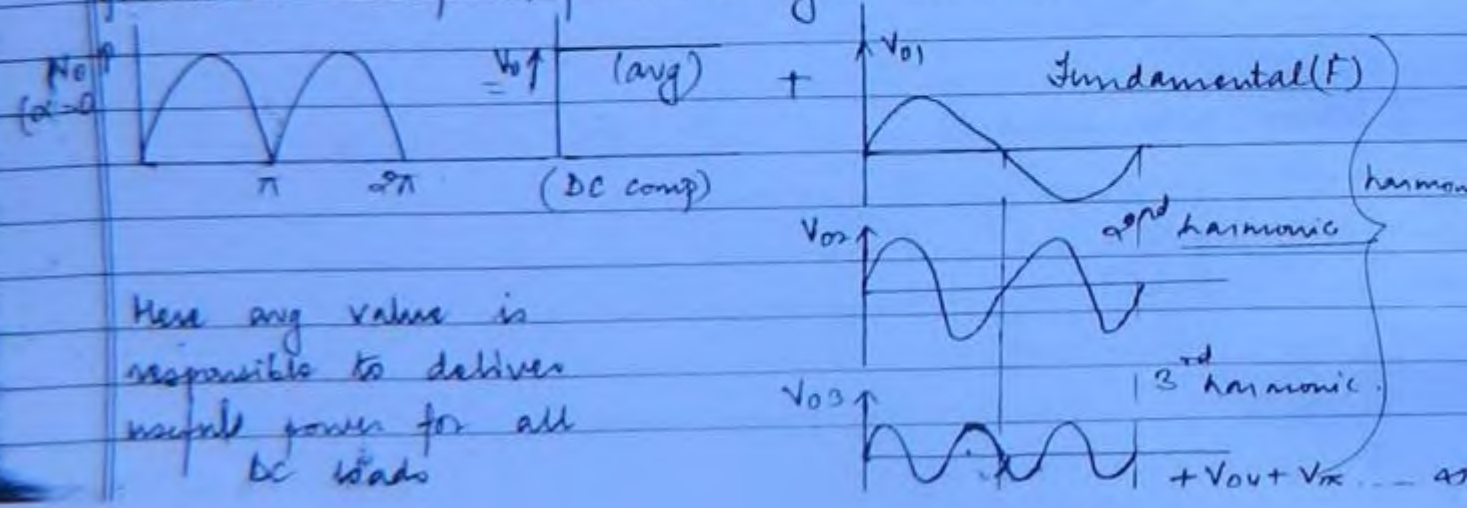1. Harmonics will overheat machine windings
 i.e we cannot utilize the m/c to its full capacity.
 i.e we must derate the m/c when fed with converters.
2. Harmonics produce pulsating torque in the motor & hence smooth rotation is not possible.

Harmonic Analysis on DC side of converter (V_o)

Output vlg waveform of a two pulse converter is distorted with harmonics. To find harmonic content present in waveform, fourier analysis is done.



Here avg value is responsible to deliver useful power for all DC loads

$$V_o = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

73

$$V_o = a_0 + \sum_{n=1}^{\infty} C_n \sin(n\omega t + \phi_n)$$

↑
avg. where $C_n = \sqrt{a_n^2 + b_n^2}$
(DC comp)

$$V_{or} = \sqrt{V_o^2 + (V_{o1})_{rms}^2 + (V_{o2})_{rms}^2 + (V_{o3})_{rms}^2 + \dots}$$

↑ ↑
RMS avg

Squaring both sides

$$V_{or}^2 = V_o^2 + (V_{o1})_{rms}^2 + (V_{o2})_{rms}^2 + (V_{o3})_{rms}^2 + \dots$$

$$\sqrt{V_{or}^2 - V_o^2} = \sqrt{(V_{o1})_{rms}^2 + (V_{o2})_{rms}^2 + (V_{o3})_{rms}^2 + \dots}$$

RMS value of harmonics

VRF = Voltage Ripple Factor

→ Its the measure of harmonics on DC side of converter.

$$VRF = \frac{\sqrt{V_{or}^2 - V_o^2}}{V_o} = \sqrt{\left(\frac{V_{or}}{V_o}\right)^2 - 1} = \sqrt{FF^2 - 1}$$

FF = form factor
= $\frac{rms}{avg}$

VRF = $\sqrt{FF^2 - 1}$

Quality of perfect DC -

1. $V_o = V_{av}$ (74)
avg rms.
2. $FF = 1$
3. $V_{RF} = 0$
i.e. no harmonics. no ripple.

without harmonics $FF = 1$
with harmonics $FF > 1$
 $FF \downarrow$ approaching unity
 \Rightarrow smoothness of waveform is improved towards DC.

• Form Factor \rightarrow gives the information of shape of the waveform.

Harmonic analysis on AC side of converter -

- * Consider an inverter. Output vlg waveform of inverter is not perfect AC. Its distorted with harmonics
- * For all AC loads, fundamental is responsible to deliver useful power

$$V_{or} = \sqrt{V_o^2 + (V_{o1})_{rms}^2 + (V_{o2})_{rms}^2 + (V_{o3})_{rms}^2 + \dots}$$

\uparrow \uparrow
RMS avg

$$\sqrt{V_{or}^2 - (V_{o1})_{rms}^2} = \sqrt{V_o^2 + (V_{o2})_{rms}^2 + \dots}$$

[THD]


~~Total Harmonic Distortion~~ \rightarrow Method of harmonics on AC side of the converter.

$$THD = \frac{\sqrt{V_{or}^2 - V_{o1}^2}}{V_{o1}}$$

Distortion Factor (g) $\rightarrow g = \frac{(V_{o1})_{rms}}{V_{or}}$

(75)

w/o harmonics $g = 1$

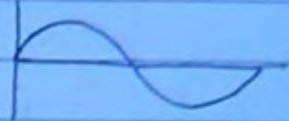

with harmonics $g < 1$ [$\because (V_{o1})_{rms} < V_{or}$]


As $g \uparrow$ & approaches unity, smoothness of waveform is improved towards AC.


Qualities of perfect AC

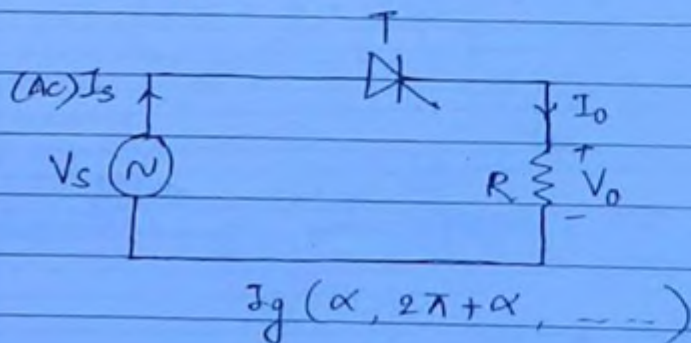1. $V_{or} = (V_{o1})_{rms}$
2. $g = 1$
3. $THD = \left(\frac{1}{g^2} - 1 \right)^{1/2}$

for perfect AC, $THD = 0$
 \Rightarrow no harmonics.

1 ϕ Half Wave Rectifier (one pulse converter)



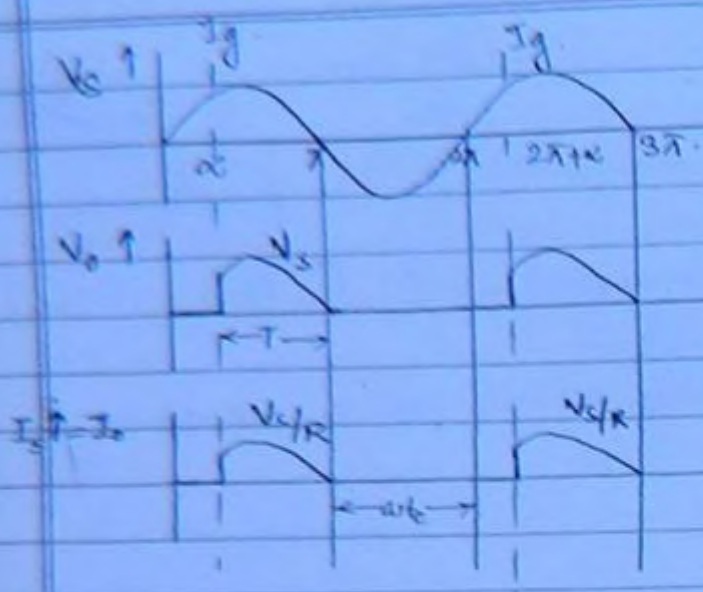

$$\omega t_c = \pi$$

$$t_c = \frac{\pi}{\omega}$$

$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$(I_s)_{avg} = I_o = \frac{V_o}{R} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

DC comp

Disadvantages -

- = Source current contains DC component & saturates the supply transformer core.

$$V_{rms} = V_{or} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$\Rightarrow V_{or} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \left(\frac{1 - \cos 2\omega t}{2} \right) d(\omega t) \right\}^{1/2}$$

$$\Rightarrow V_{or} = \frac{V_m}{2\sqrt{\pi}} \left\{ (\omega t)_{\alpha}^{\pi} - \frac{1}{2} (\sin 2\omega t)_{\alpha}^{\pi} \right\}^{1/2}$$

$$\sin \alpha = \frac{1}{\sqrt{2}}$$

$$V_{or} = \frac{V_m}{\sqrt{2}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}}$$

(77)

$$P_{in} = V_{sr} I_{sr} \cos \phi$$

$$P_o = V_{or} I_{or}$$

$$P_{in} = P_o$$

$$\cos \phi = \frac{V_{or} I_{or}}{V_{sr} I_{sr}}$$

$$\boxed{PF = \frac{V_{or}}{V_{sr}}}$$

$$PF = \frac{1}{\sqrt{2}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}}$$


Power Factor depends on -

1. Firing angle - As $\alpha \uparrow$ PF \downarrow
2. PF also depends on the harmonics i.e. it depends on the shape of the source current waveform.

$$\boxed{PF = g \times FDF}$$

\boxed{FDF} = fundamental displacement factor

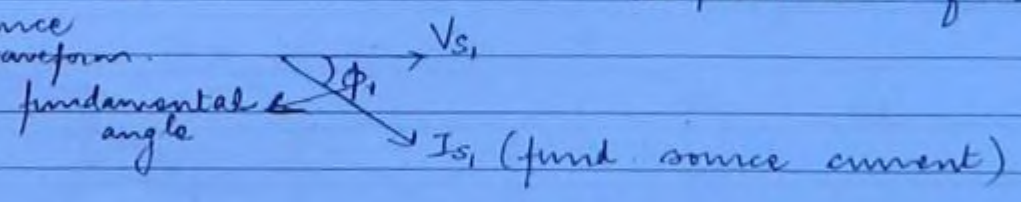distortion factor for source current waveform



$$FDF = \cos \phi_1$$

$$P_{in} = V_{s1} I_{s1} (\text{PF}) = V_{s1} I_{s1} (\text{D.F.})$$

$$\text{PF} = \frac{I_{s1} (\text{D.F.})}{I_{s2}}$$

(78)

$$\text{PF} = g (\text{D.F.}) \quad g = \frac{I_{s1}}{I_{s2}}$$

3. PF also depends on load parameters.


Drawbacks of PE converters -

1. The converter inject harmonics into the supply system (or utility system) & reduce the quality of supply line. To rectify this problem, we must use AC filters on AC side of converter.

2. The converter draws reactive power from supply line for its operation. We must compensate the reactive power required for converter operation by using reactive power source on the AC side of the converter.

(II) 1 ϕ Half Wave Rectifier \rightarrow RL load.

(1) α to π $T \rightarrow$ ON

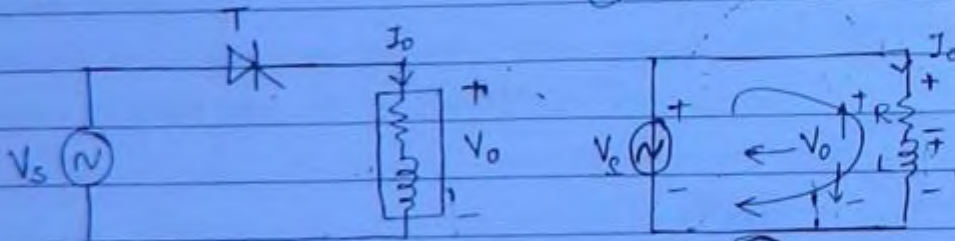

(P+)

$$P_{source} \rightarrow P_{load}$$

$$= \frac{(I^2 R + \frac{1}{2} L I^2)}{2}$$

L stores energy.

$$V_m \sin \omega t = Ri + L \frac{di}{dt}$$

$$I_o = I_{steady} + I_{transient}$$

(79)

$$I_{steady} = \frac{V_m \sin(\omega t - \phi)}{|Z|}$$

$$\text{where } |Z| = \sqrt{R^2 + (\omega L)^2}$$

$$\phi = \tan^{-1} \frac{\omega L}{R}$$

$$I_{transient} = K e^{-t/\tau}$$

$$I_o = I_{steady} + I_{transient}$$


$$I_o = \frac{V_m \sin(\omega t - \phi)}{|Z|} + K e^{-t/\tau}$$


$$\text{At } \omega t = \alpha \quad I_o = 0$$

$$t = \alpha \quad \tau = \frac{L}{R}$$

$$0 = \frac{V_m \sin(\omega t - \phi)}{|Z|} + K e^{-R\alpha/\omega L}$$


$$K = -\frac{V_m \sin(\alpha - \phi)}{|Z|} e^{R\alpha/\omega L}$$

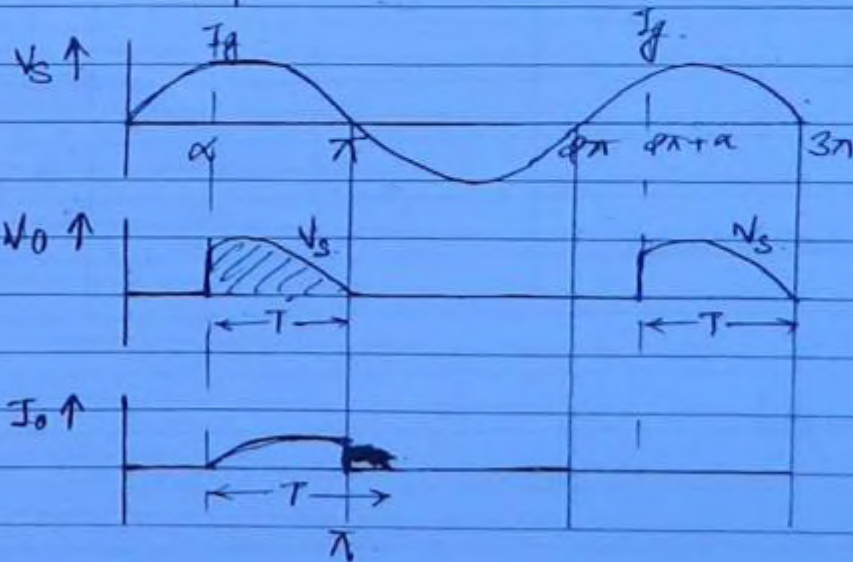

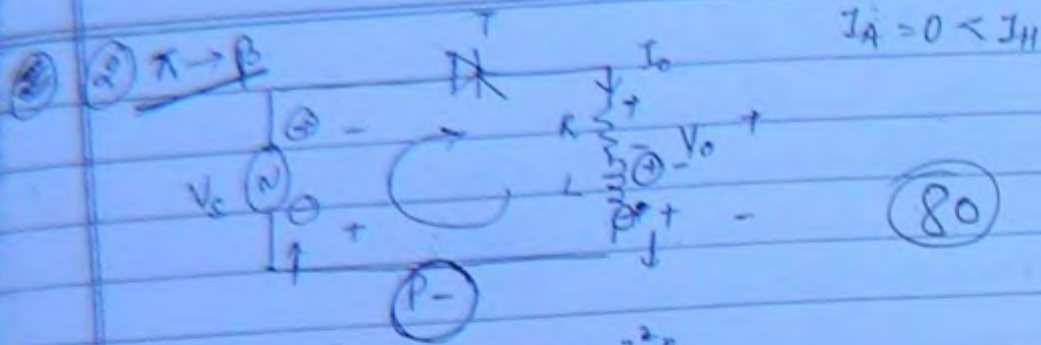

1 $L I^2 \rightarrow \text{source} + I^2 R$
 2

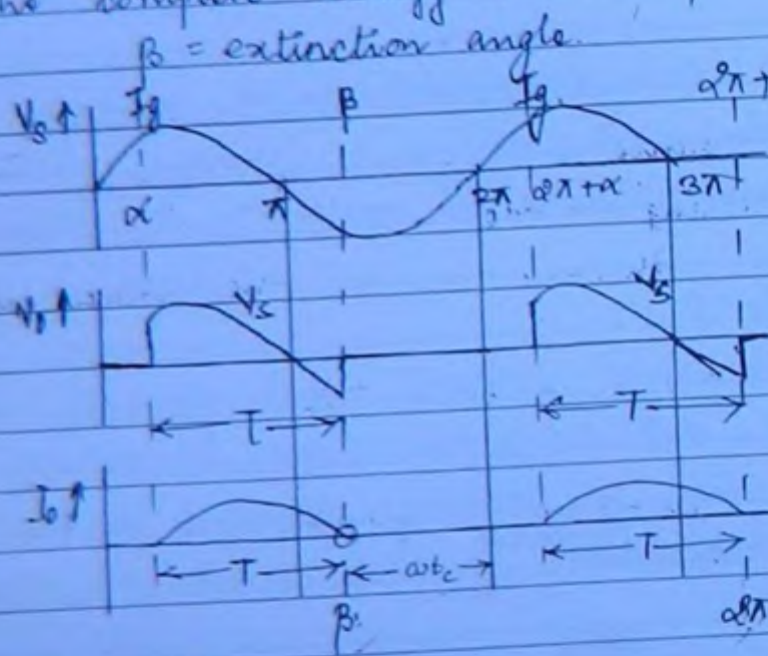⇒ The inductance energy maintains conduction of thyristor even in the -ve cycle until it releases the complete energy at $\omega t = \beta$.



At $\omega t = \pi$ reverse voltage is applied across SCR but it'll still conduct, SCR doesn't get turned OFF until $I_a = 0$.
 L does not accept sudden change in i .
 I_a continues to flow till β → the point where L loses its energy completely.

$$\omega t_c = 2\pi - \beta$$

$$t_c = \frac{2\pi - \beta}{\omega}$$

$$V_0 = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \, d(\omega t)$$


$$V_0 = \frac{V_m}{2\pi} [\cos \alpha - \cos \beta]$$

$$V_{or} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{2\sqrt{\pi}} \left[(\beta - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right]$$

(81)

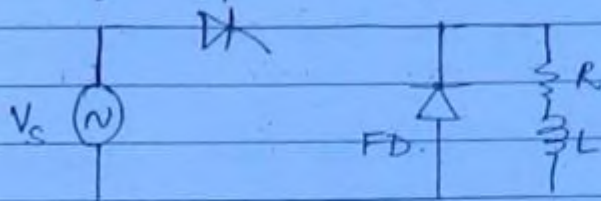(III) 1- ϕ Half Wave Rectifier \rightarrow RL load with FD.




① mode is same.

② ~~FD~~ freewheeling mode.

During free wheeling action, -ve spikes are removed.

L releases energy through $I^2 R$ \rightarrow takes more time $\beta \uparrow$

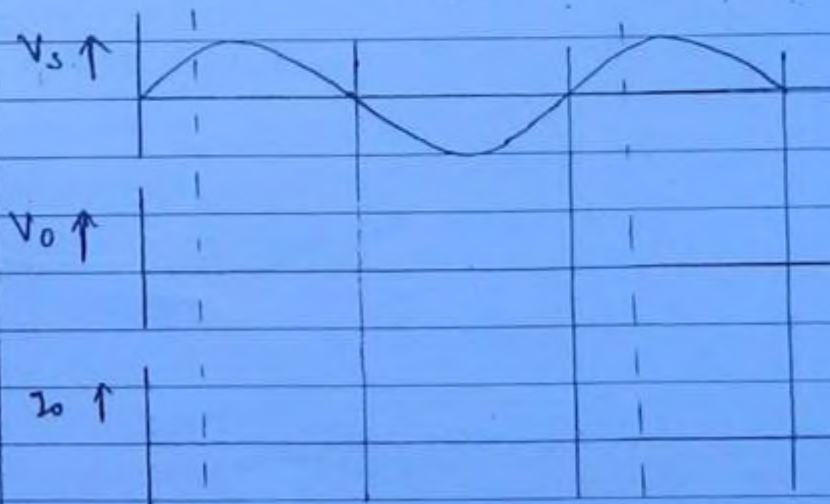smoothness improves $g \uparrow$ $PF \uparrow$




Advantages of FD -

(82)

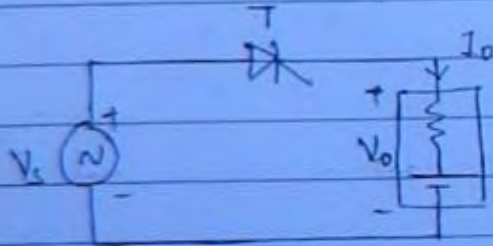1. PF is improved
2. no spikes in load vlg is improved & this ↑ avg vlg.
3. Smoothness of output current waveform is improved as $\beta \uparrow$.
4. ∴ the overall performance of the converter is improved with FD.
5. There will be freewheeling action in semiconverter ∴ PF is better in semiconverter as compared to full converter.
6. ∴ performance of semiconverter is superior to full converter.

2-12

IV 1- ϕ Half Wave Rectifier - charging a battery (RE load)



$$\text{At } \omega t = \theta_1$$

$$V_s = E$$

$$V_m \sin \theta_1 = E$$

$$\alpha_{\min} = \theta_1 = \sin^{-1} \left(\frac{E}{V_m} \right)$$


$$\alpha_{\max} = \theta_2 = \pi - \theta_1$$

$$\theta_1 \leq \alpha \leq \theta_2$$

$$I_g(\alpha, 2\pi + \alpha, \dots)$$

$$T \rightarrow \text{ON} \Rightarrow V_o = V_s \Rightarrow V_s = I_o R + E$$
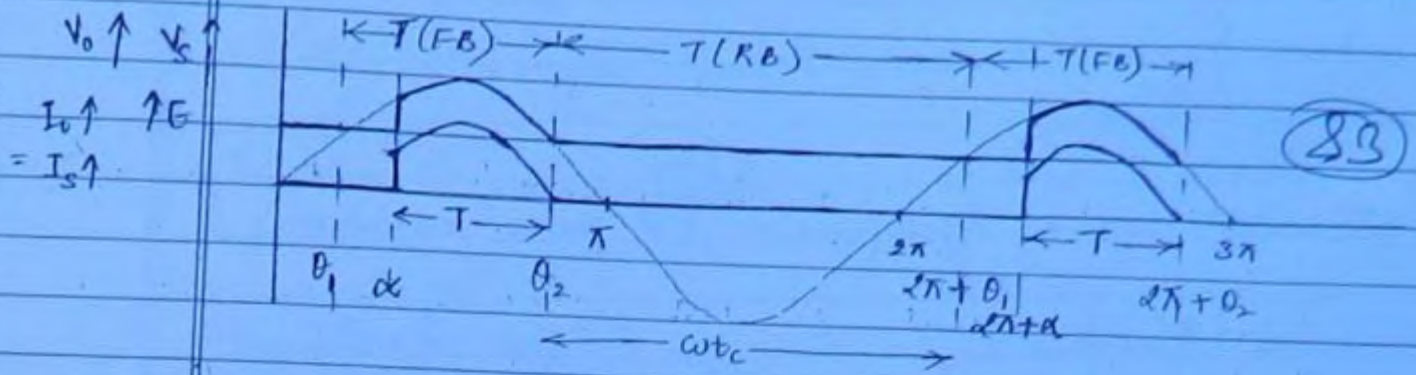
$$I_o = \frac{V_s - E}{R} = \frac{V_m \sin \omega t - E}{R}$$



$$\omega t_c = (2\pi + \theta_1) - \theta_2$$

$$= (2\pi + \theta_1) - (\pi - \theta_2)$$

$$t_c = \frac{\pi + 2\theta_1}{\omega}$$

$$PIV = V_m + E$$

$$V_o = \frac{1}{2\pi} \left[\int_{\alpha}^{\theta_2} V_m \sin \omega t d(\omega t) + \int_{\theta_2}^{2\pi + \alpha} E d(\omega t) \right]$$

$$V_o = \frac{1}{2\pi} \left[V_m (\cos \alpha - \cos \theta_2) + E (2\pi + \alpha - \theta_2) \right]$$

radians

* Avg charging current of the battery

$$I_o = \frac{1}{2\pi} \int_{\alpha}^{\theta_2} \frac{V_m \sin \omega t - E}{R} d(\omega t)$$

$$I_o = \frac{1}{2\pi R} \left[V_m (\cos \alpha - \cos \theta_2) - E (\theta_2 - \alpha) \right]$$

radians

$$P_{in} = V_{s_r} I_{s_r} (PF)$$

$$P_o = I_o^2 R + E I_o$$

$$PF = \frac{I_o^2 R + E I_o}{V_{s_r} I_{s_r}}$$

$$PF = \frac{I_o^2 R + E I_o}{V_{s_r} I_{s_r}}$$


$$I_{O_{avg}} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\pi} \left(\frac{V_m \sin \omega t - E}{R} \right)^2 d(\omega t) \right\}^{1/2}$$

(84)

1- ϕ Full Wave Rectifiers - (2 pulse converter)

Midpoint Rectifiers -

where transformer is required

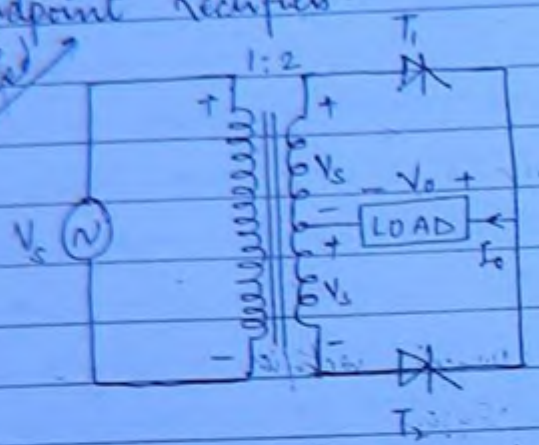


$T_1 \rightarrow ON$
 $V_o = V_s$
 $I_o = V_s/R$

$T_2 \rightarrow ON$
 $V_o = -V_s$
 $I_o = -V_s/R$

+ T_1 (FB) $I_g(\alpha, 2\pi + \alpha \dots)$
 - T_2 (FB) $I_g(\pi + \alpha, 3\pi + \alpha \dots)$

Bridge Rectifiers -

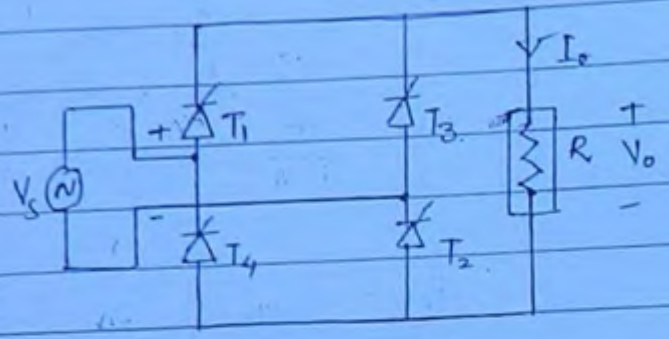


+ $T_1 T_2$ (FB) $I_g(\alpha, 2\pi + \alpha \dots)$
 - $T_3 T_4$ (FB) $I_g(\pi + \alpha, 3\pi + \alpha \dots)$

$T_1 T_2 \rightarrow ON$

$V_o = V_s$
 $I_o = V_s/R$

$T_3 T_4 \rightarrow ON$

$V_o = -V_s$
 $I_o = -V_s/R$

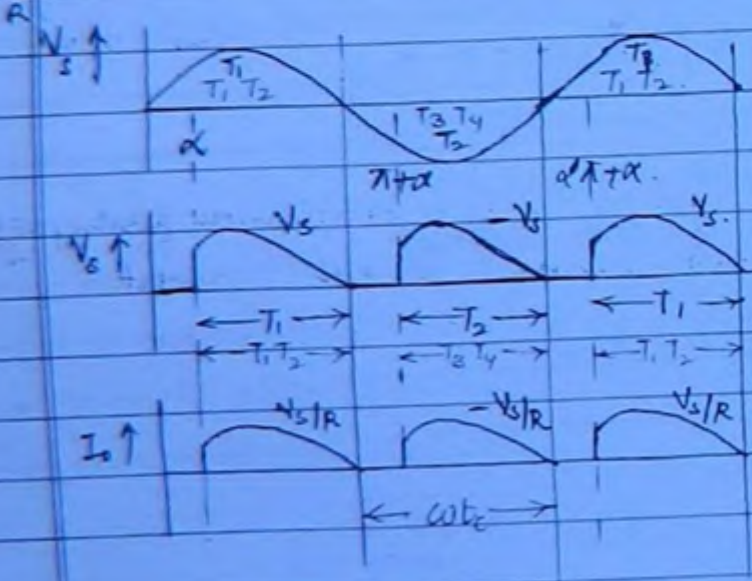

$$\omega t_c = \pi$$

$$t_c = \frac{\pi}{\omega} \text{ secs}$$

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

(85)

$$V_{or} = \left\{ \frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2}\pi} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$PIV = 2V_m \rightarrow \text{In mid-point rectifier}$$


$$PIV = V_m \rightarrow \text{bridge rectifier}$$

Advantages of Bridge Rectifier -


1. PIV of thyristor in bridge rectifier is half that of mid-point rectifier.
2. If same thyristors with same specifications (same v/f & current ratings) are same in both converters then power handled by bridge rectifier is double that of mid-point rectifier.

1- ϕ Full Wave Rectifiers (R-L Load) (Full converter)

Discontinuous conduction.

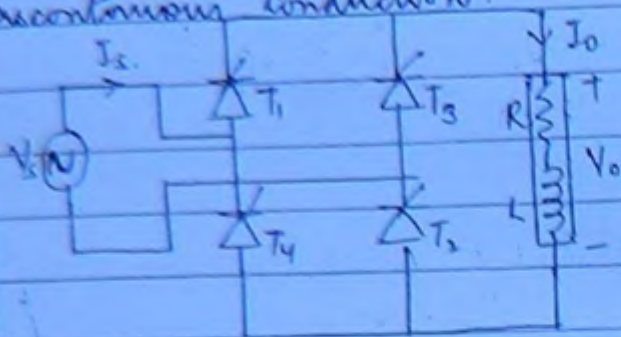

(86)

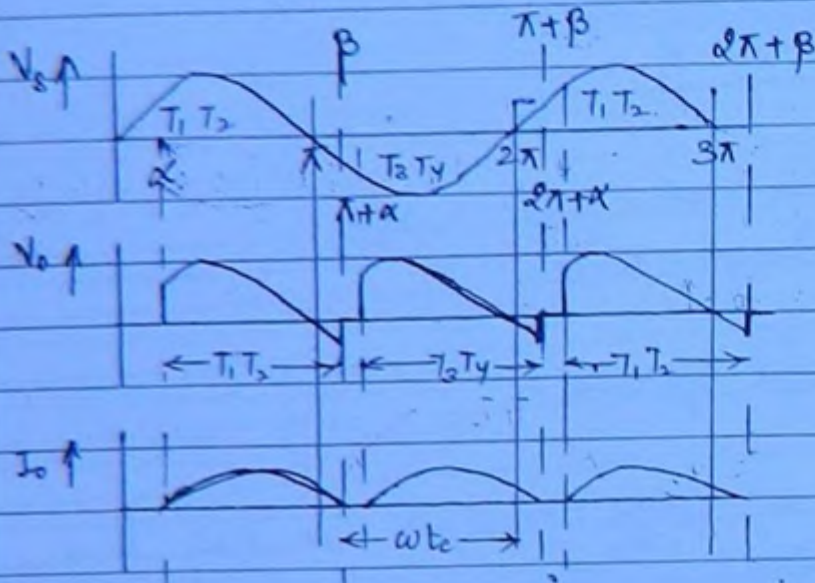

$$\omega t_c = 2\pi - \beta$$

$$t_c = \frac{2\pi - \beta}{\omega}$$

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \, d(\omega t)$$

$$V_o = \frac{V_m}{\pi} (\cos \alpha - \cos \beta)$$

$$V_{or} = \left\{ \frac{1}{\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2\pi}} \left[(\beta - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right]^{1/2}$$

Reasons for Discontinuous Conduction -

1. $L \downarrow$ [Time constant $T \downarrow = \frac{L}{R}$] or $R \uparrow$
 $T \downarrow \therefore \beta \downarrow$ [$\beta < (\pi + \alpha)$]

(87)

2. $\alpha \uparrow$ (High value of firing angle) — less energy is stored in inductor.


3. $I_o \downarrow \rightarrow E = \frac{1}{2} I_o^2 L$ not sufficient energy.

RL Load Continuous Conduction

1. $L \uparrow$ [$\uparrow T = \uparrow \frac{L}{R}$] 2. $\uparrow T \Rightarrow \uparrow \beta$ [$\beta > (\pi + \alpha)$]


2. $\alpha \downarrow$

3. $I_o \uparrow$

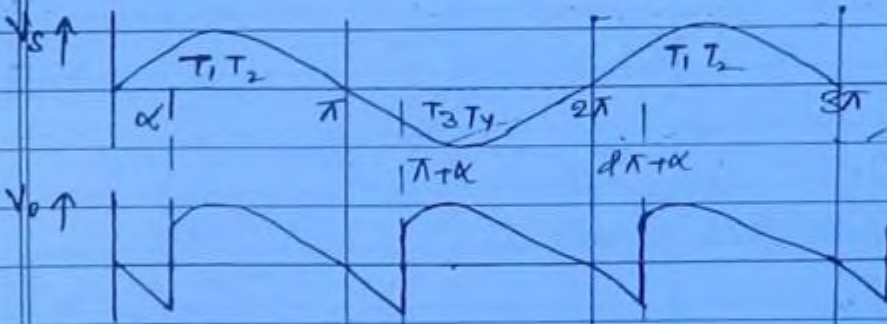

$T_1 = T_3$
 $T_2 = T_4$

for highly inductive load

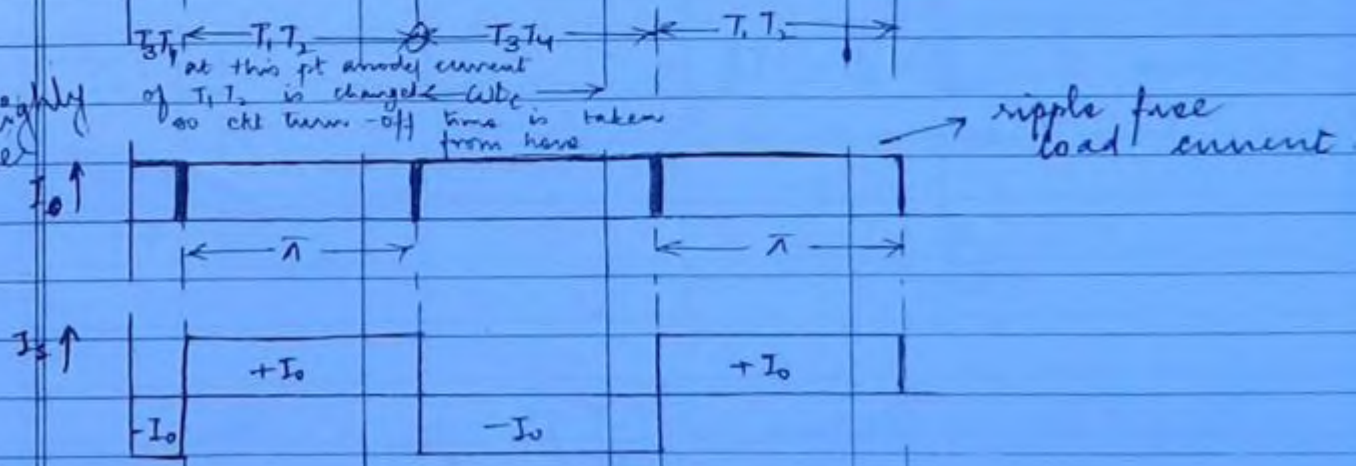

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, d(\omega t)$$

$$V_o = \frac{2V_m \cos \alpha}{\pi}$$

(88)

$$V_{or} = \left\{ \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2}}$$

→ Squaring V_s or V_o waveform gives same waveform so their rms values are equal.
Hence Rms value of $V_s = \frac{V_m}{\sqrt{2}}$.

$$\omega t_c = 2\pi - (\pi + \alpha)$$

$$t_c = \frac{\pi - \alpha}{\omega}$$

so is that of V_o .

$$T_1, T_2 \rightarrow ON$$

$$I_s = I_o$$

$$T_2, T_4 \rightarrow ON$$

$$I_s = -I_o$$

Assume highly inductive load -

Conduction Angle of = π rad [for every 2π rad]
each thyristor

$$(I_o)_{avg} = \frac{1}{2\pi} \int_{\alpha}^{\pi+\alpha} I_o \, d(\omega t) = \frac{I_o}{2}$$

$$= I_o \left(\frac{\pi}{2\pi} \right)$$

$$(I_T)_{avg} = \frac{I_o}{2}$$

$$(I_T)_{rms} = I_o \left(\frac{\pi}{2\pi} \right)^{1/2} = \frac{I_o}{\sqrt{2}}$$


Qo

$$I_{or} = I_o$$

1- ϕ Half Controlled Rectifier - (Semi Converter)


89

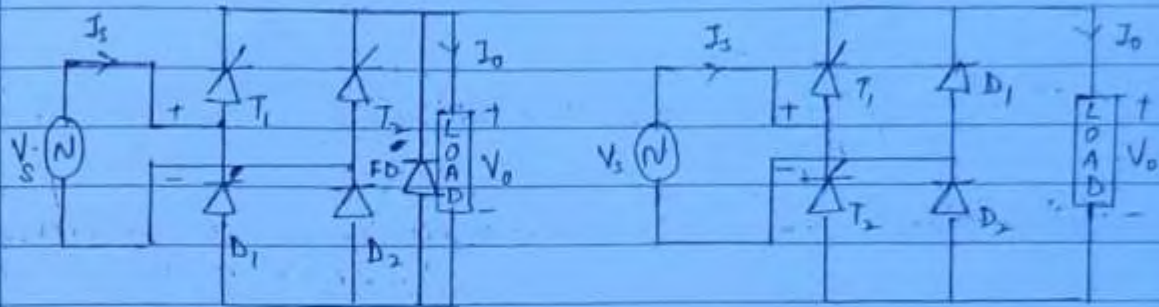Symmetrical Connection - Asymmetrical Connection -




+ T_1, D_2 (F)
- T_2, D_1 (F)

+ T_1, D_2 (F)
- T_2, D_1 (F)

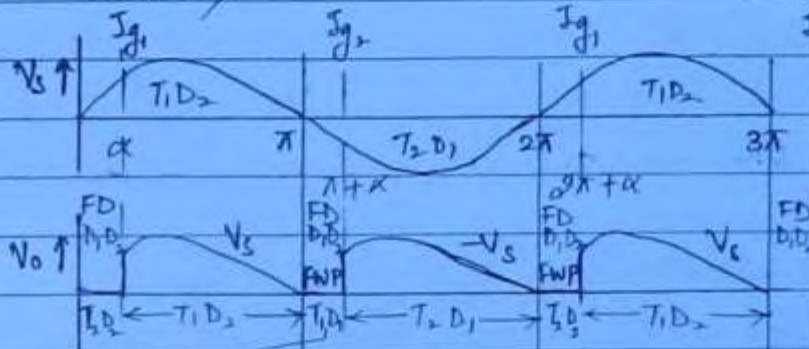

Due to freewheeling diode -ve spikes are removed. Thus the V_o becomes same as that of a load in full converter.

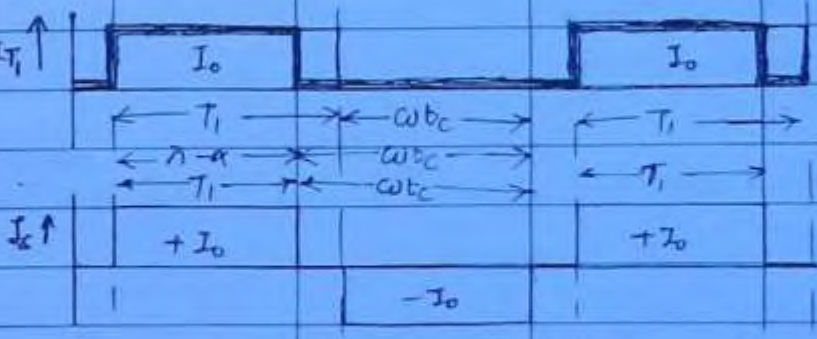FWP
Free wheeling period (that's why no need of separate FD)
load current $I_o = 0$



For resistive load waveform remains same for full converter & semi converter

Assume highly inductive load -

(90)

π to $\pi + \alpha$ $T_1, D_1 \rightarrow ON$

FWP $V_o = 0$

FWP $I_o = 0$

$T_1, D_2 \rightarrow ON$ $I_s = I_o$

$T_2, D_1 \rightarrow ON$ $I_s = -I_o$

if $\omega t_c = \alpha$ $\omega t_c = \alpha - (\pi + \alpha)$

$\omega t_c = \alpha - \pi$

| |
|----------------------|
| $t_c = \pi - \alpha$ |
| ω |

| |
|-------------|
| $t_c = \pi$ |
| ω |

* In symmetrical connection there is a possibility of S.C across the supply when the incoming thyristor starts conducting before the outgoing thyristor stops conducting. Here the problem is severe, because before the incoming thyristor starts conducting, the free wheeling action is through outgoing thyristor because of which S.C period is more.

* To rectify this problem we must use a separate FD.

Symmetrical connection with FD.

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t)$$

$$V_o = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$V_{or} = \left\{ \frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

91

Assume highly inductive load -

Conduction angle each thyristor = $(\pi - \alpha)$ rad [for every 2π rad]

$$= \frac{\pi - \alpha}{2\pi}$$

Conduction angle of FD = α rad [for every π rad]

$$= \frac{\alpha}{\pi}$$

$$(I_T)_{avg} = I_o \frac{(\pi - \alpha)}{2\pi}$$

$$(I_{FD})_{avg} = I_o \left(\frac{\alpha}{\pi} \right)$$



$$(I_T)_{rms} = I_o \left(\frac{\pi - \alpha}{2\pi} \right)^{1/2}$$

$$(I_{FD})_{rms} = I_o \left(\frac{\alpha}{\pi} \right)^{1/2}$$

$$I_{or} = I_o \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}$$

1 ϕ Full Converter - Charging a Battery

Q2

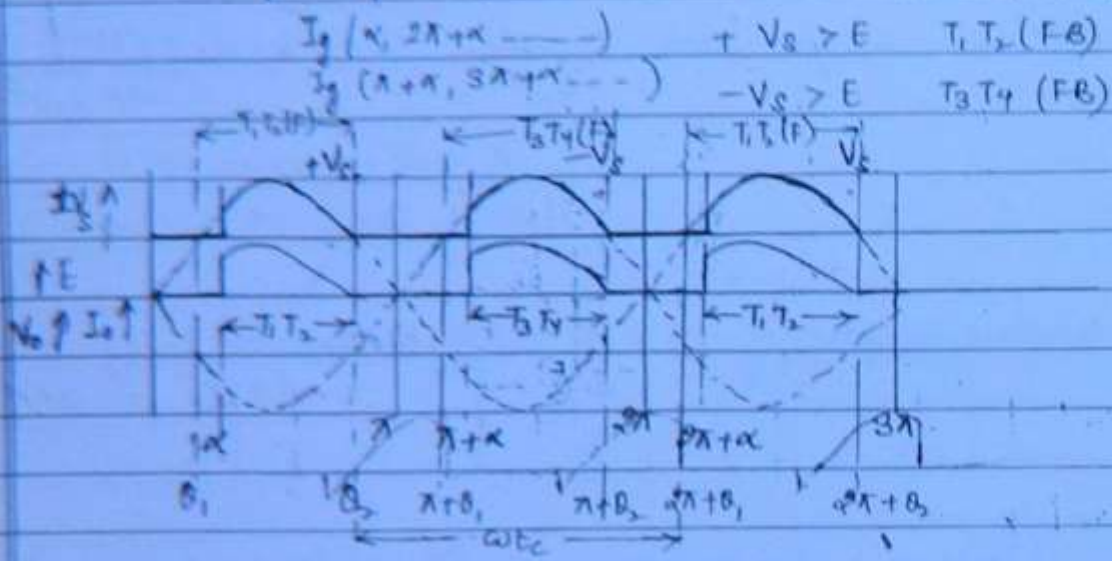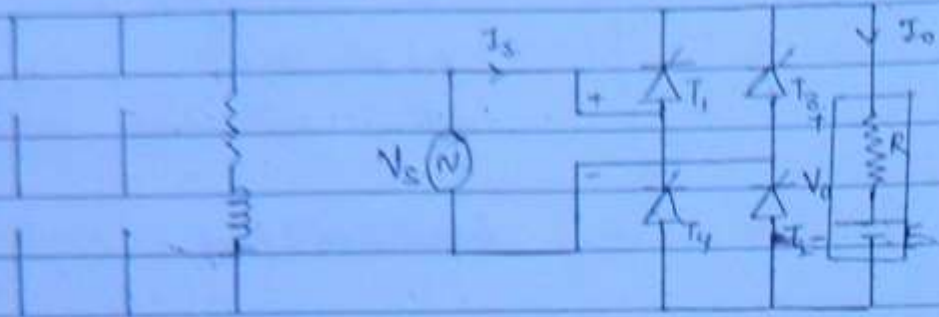

$T_1 T_2 \rightarrow ON$
 $V_o = V_s$
 $I_o = \frac{V_s - E}{R}$

$\theta_1 = \sin^{-1} \frac{E}{V_m}$
 $\theta_2 = \pi - \theta_1$

$$I_o = \frac{V_m \sin \omega t - E}{R}$$

$\omega t_c = (2\pi + \theta_1) - \theta_2$
 $= (2\pi + \theta_1) - (\pi - \theta_1)$

$$t_c = \frac{\pi + 2\theta_1}{\omega}$$

$$V_o = \frac{1}{\pi} \left[\int_{\alpha}^{\theta_2} V_m \sin \omega t d(\omega t) + \int_{\theta_2}^{\pi + \alpha} E d(\omega t) \right]$$


$$V_o = \frac{1}{\pi} \left[V_m (\cos \alpha - \cos \theta_2) + E (\pi + \alpha - \theta_2) \right]$$

Q3


$$I_0 = \frac{1}{\pi} \int_{\alpha}^{\theta_2} \left(\frac{V_m \sin \omega t - E}{R} \right) d(\omega t)$$

$$I_0 = \frac{1}{\pi R} \left[V_m (\cos \alpha - \cos \theta_2) - E(\theta_2 - \alpha) \right]$$


1 ϕ Full Converter - DC Motor (RLE Load)

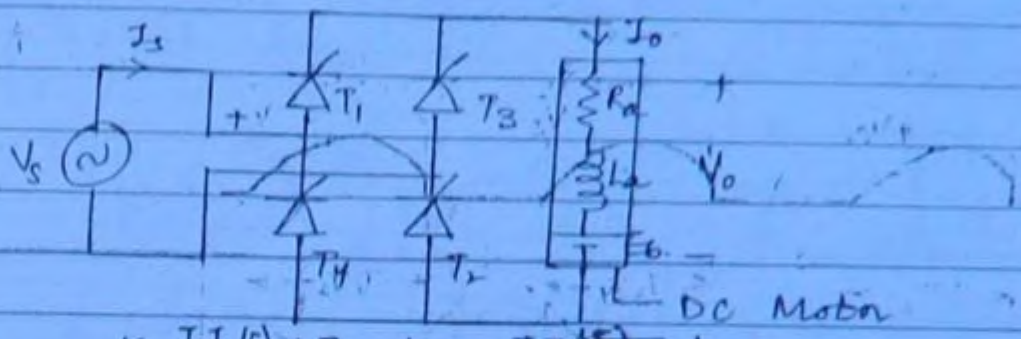

$\beta < \pi$

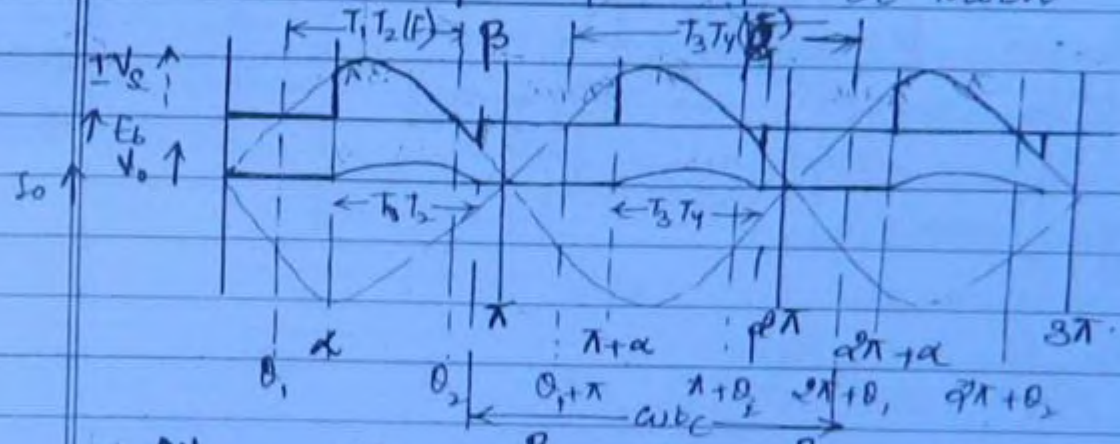

$\beta > \pi$

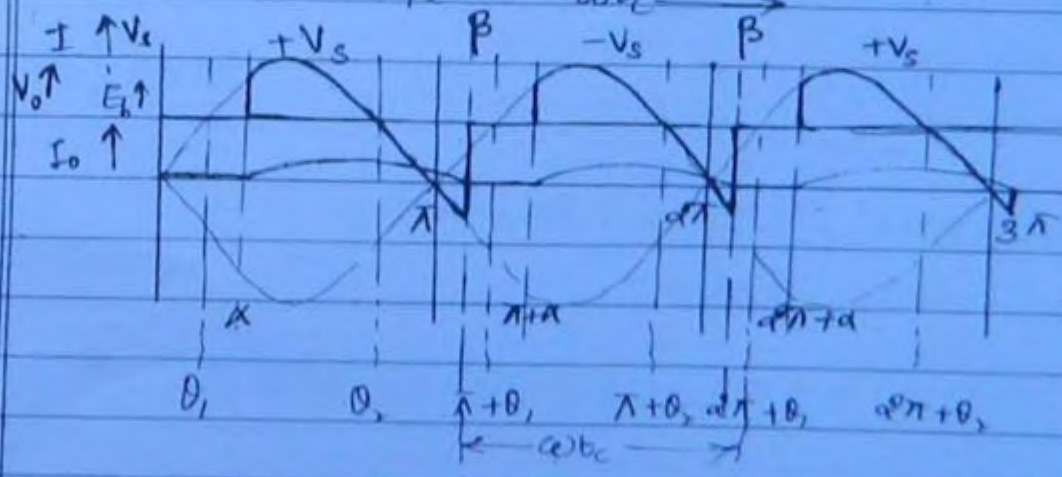

$$\omega t_c = (\alpha + \theta_1) - \beta$$

$$\downarrow t_c = \frac{\alpha + \theta_1 - \beta}{\omega}$$

(94)

For continuous conduction waveform remains same for RL & RLE load. \therefore

$$V_o = \frac{1}{\pi} \left[\int_{\alpha}^{\beta} V_m \sin \omega t d(\omega t) + \int_{\beta}^{\pi + \alpha} E_b d(\omega t) \right]$$

$$V_o = \frac{1}{\pi} \left[V_m (\cos \alpha - \cos \beta) + E_b (\pi + \alpha - \beta) \right]$$

For continuous conduction +


$$V_o = \frac{\alpha V_m \cos \alpha}{\pi} \rightarrow \text{RL / RLE}$$

$$I_o = \frac{V_o}{R} \rightarrow \text{RL}$$


$$I_o = \frac{V_o - E_b}{R_a} \rightarrow \text{RLE}$$

1 φ Semiconductor - DC Motor (RLE load)


(95)

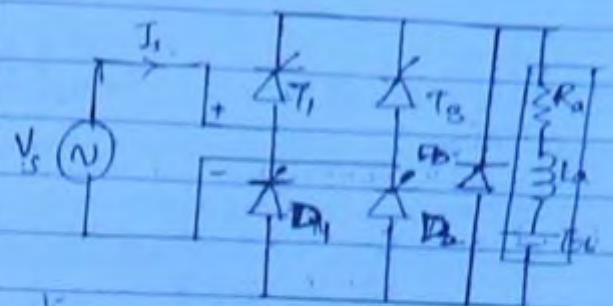

$\beta < \pi$
FD will not conduct

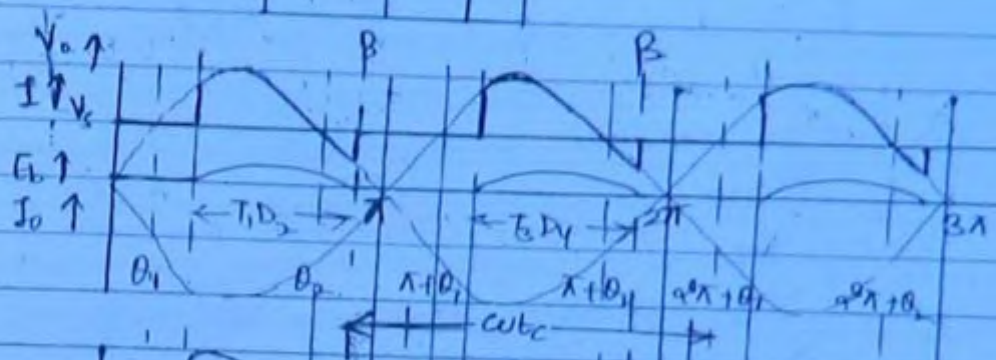

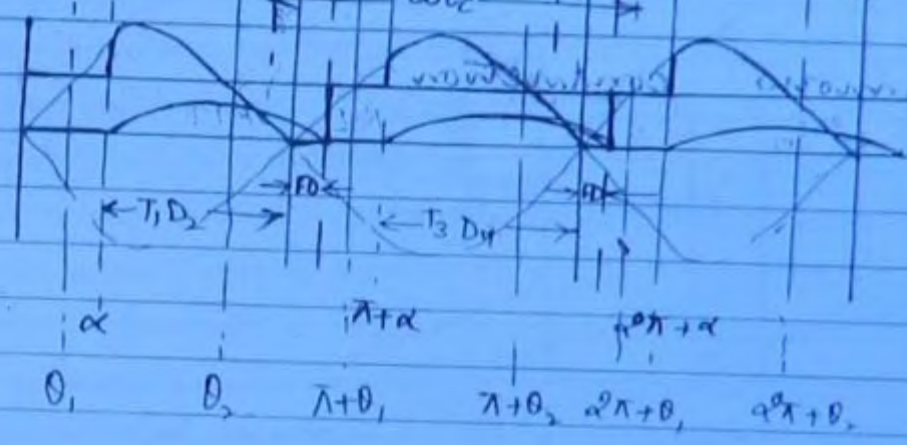$\beta > \pi$
conduction of FD = $(\beta - \pi)$ rad



For $\beta > \pi$

$$V_0 = \frac{1}{\pi} \left[\int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t) + \int_{\beta}^{\pi + \alpha} E_b \, d(\omega t) \right]$$

$$V_0 = \frac{1}{\pi} \left[V_m (1 + \cos \alpha) + E_b (\pi + \alpha - \beta) \right]$$


For continuous conduction waveform remains same for RL & RLE load.

Back emf will not affect the avg value

$$V_0 = \frac{V_m}{\pi} (1 + \cos \alpha)$$

Performance of 1 ϕ Full Converter -

96

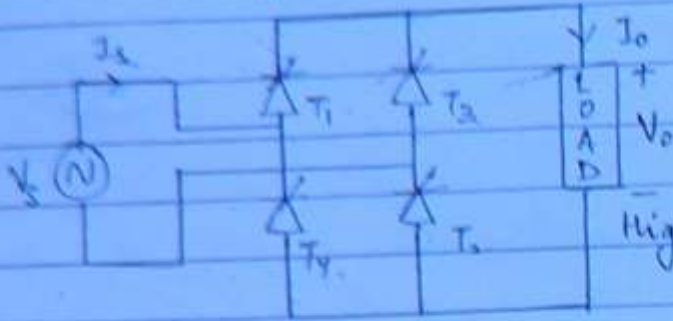


Highly inductive load
(RL, RLE)

$$V_o = \frac{\alpha V_m \cos \alpha}{\pi}$$

$$V_{os} = \frac{V_m}{\sqrt{2}}$$

$$I_{s1} = I_o$$

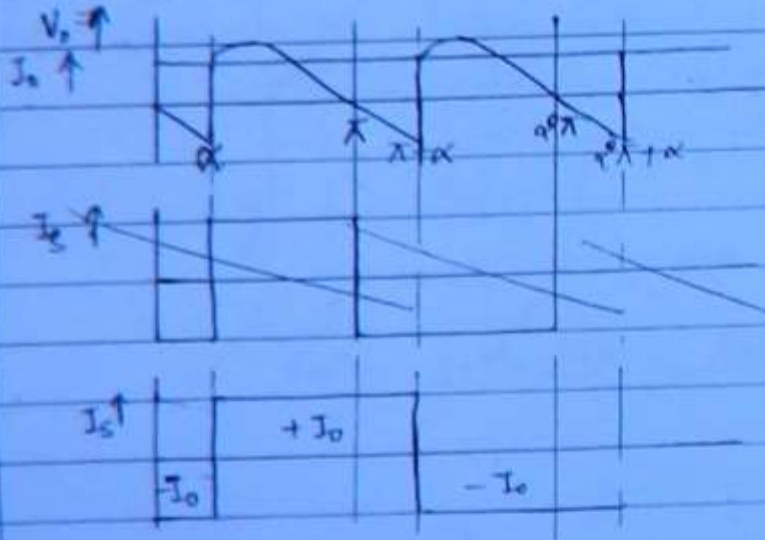

Harmonic Analysis on AC side of converter for source current (I_s)

$$I_s = \sum_{n=1,3,5,\dots}^{\infty} \frac{4I_o \sin(n\omega t + \phi_n)}{n\pi} = \frac{4I_o \sin(\omega t - \alpha)}{\pi} + \frac{4I_o \sin(3\omega t - 3\alpha)}{3\pi} + \frac{4I_o \sin(5\omega t - 5\alpha)}{5\pi} \dots$$

$$\phi_n = -n\alpha$$

\hookrightarrow n^{th} harmonic displacement angle

$$I_{an} = \frac{4I_0}{n\pi} \sin(n\omega t + \phi_n)$$

$$(I_{an})_{rms} = \frac{2\sqrt{2} I_0}{n\pi}$$

(1)

$$(I_{a1})_{rms} = \frac{2\sqrt{2} I_0}{\pi} \quad \text{--- (1)}$$

$$FDF = \cos \phi_1$$

$$FDF = \cos(-\alpha) = \cos \alpha \quad \text{--- (2)}$$

$$g = \frac{(I_{a1})_{rms}}{I_{a1}} \Rightarrow \frac{2\sqrt{2} I_0}{\pi} \cdot \frac{1}{I_0}$$

$$g = \frac{2\sqrt{2}}{\pi} \quad \text{--- (3)}$$



$$PF = g (FDF)$$

$$PF = \frac{2\sqrt{2}}{\pi} \cos \alpha \quad \text{--- (4)}$$

$$THD = \left(\frac{1}{g^2} - 1 \right)^{1/2}$$

$$THD = \left(\frac{\pi^2}{8} - 1 \right)^{1/2} = 0.4834$$

$$THD = 48.34\% \quad \text{--- (5)}$$

avg delivered
useful power

avg delivered
useful power.

Active power -

$$P = V_{s,r} I_{s,r} \cos \alpha = V_o I_o \quad \text{--- (6)}$$
$$= \left(\frac{V_m}{\sqrt{2}} \right) \left(\frac{2\sqrt{2} I_o}{\pi} \right) \cos \alpha$$

(98)

$$P = \frac{\pi}{\pi} V_m \cos \alpha, I_o = V_o I_o$$

Reactive Power -

$$Q = V_{s,r} I_{s,r} \sin \alpha = V_o I_o \tan \alpha \quad \text{--- (7)}$$
$$= V_{s,r} I_{s,r} \cos \alpha \cdot \frac{\sin \alpha}{\cos \alpha}$$

$$Q = P \tan \alpha$$

Harmonics on DC side of converter - (V_o)

$$V_{RF} = \sqrt{FF^2 - 1}$$

$$FF = \frac{V_{o,r}}{V_o} = \frac{V_m / \sqrt{2}}{\frac{\pi V_m \cos \alpha}{\pi}} = \frac{\pi \cos \alpha}{\pi \sqrt{2}}$$

$$V_{RF} = \sqrt{\frac{\pi^2}{8 \cos^2 \alpha} - 1}$$

When $0 < \alpha < 90$


$\alpha \uparrow$ ripple \uparrow harmonics \uparrow

When $90 \leq \alpha < 180$

$\alpha \uparrow$ ripple \downarrow harmonics \downarrow

Performance of 1 ϕ Semi Converter -


(99)

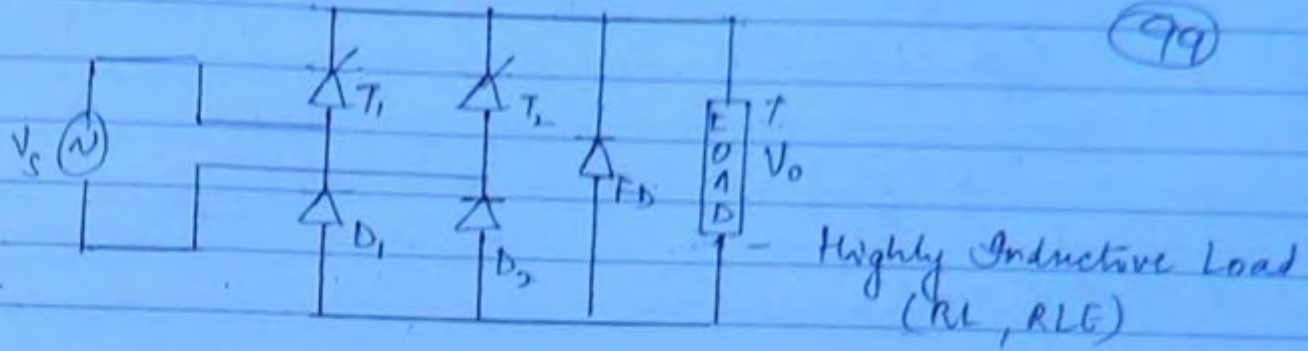

$$V_s = V_m \sin \omega t \quad V_{s1} = \frac{V_m}{\sqrt{2}}$$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$
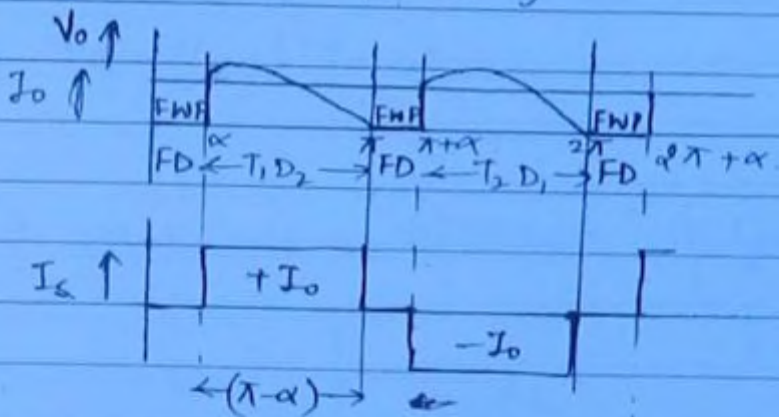
$$I_{s1} = I_o \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}$$



Harmonic Analysis of I_s on Ac side of Converter (I_s)

$$I_s = \sum_{n=1,3,5}^{\infty} \frac{4I_o \cos n\alpha}{n\pi} \sin(n\omega t + \phi_n)$$

where $\phi_n = \frac{-n\alpha}{2}$

$$(I_{s1})_{rms} = \frac{2\sqrt{2} I_o \cos \alpha}{\pi}$$

$$(I_{s1})_{rms} = \frac{2\sqrt{2} I_o \cos \alpha}{\pi} \quad \text{--- (1)}$$

$$\text{FDF} = \frac{\cos \alpha}{2} \quad \text{--- (2)}$$

$$g = \frac{I_{s1}}{I_{s1}} = \frac{\frac{\alpha \sqrt{2}}{\pi} I_0 \cos \alpha / 2}{I_0 \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}} \quad \text{--- (100)}$$

$$g = \frac{\alpha \sqrt{2} \cos \alpha}{2 \sqrt{\pi (\pi - \alpha)}} \quad \text{--- (3)}$$

$$\text{PF} = g (\text{FDF})$$

$$\text{PF} = \frac{\frac{\alpha \sqrt{2} \cos \alpha}{2} \sqrt{2} (1 + \cos \alpha)}{\sqrt{\pi (\pi - \alpha)} \sqrt{\pi (\pi - \alpha)}} \quad \text{--- (4)}$$

$$\text{THD} = \left(\frac{1}{g^2} - 1 \right)^{1/2}$$

$$\text{THD} = \left[\frac{\pi (\pi - \alpha) - 1}{8 \cos^2 \alpha} \right]^{1/2} \quad \text{--- (5)}$$

Active Power -

$$P = \frac{V_{s1} I_{s1} \cos \alpha}{2} = V_0 I_0 \quad \text{--- (6)}$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{2 \sqrt{2}}{\pi} I_0 \cos \alpha \cdot \frac{\cos \alpha}{2}$$

$$= \frac{V_m}{\pi} (1 + \cos \alpha) I_0$$

$$P = V_0 I_0$$

Reactive Power -

$$Q = V_{sr} I_{sr} \sin \frac{\alpha}{2} = V_o I_o \tan \frac{\alpha}{2} \quad \text{--- (7)}$$

$$Q = P \tan \frac{\alpha}{2}$$

(10)

Harmonics on DC side of converter (V_o)


$$V_{RF} = \sqrt{FF^2 - 1}$$

$$FF = \frac{V_{or}}{V_o}$$


$$V_{or} = \frac{V_m}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

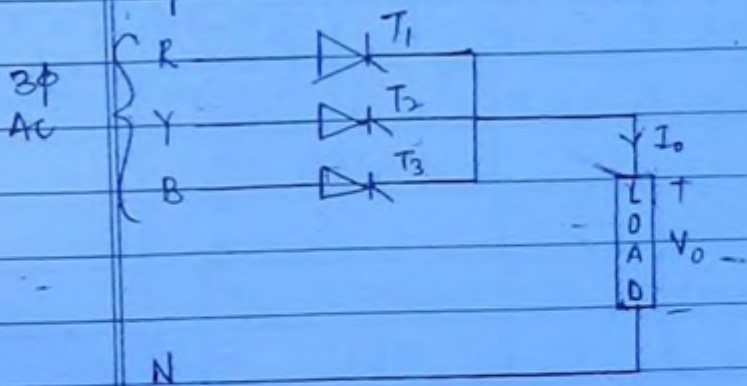3 ϕ HALF WAVE RECTIFIER (3 pulse converter)



RYB phase sequence

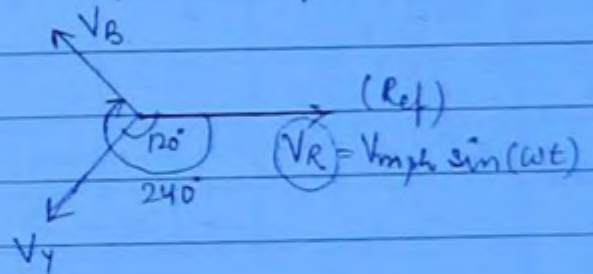


$$I_L = I_{ph} = I_T$$



$$V_{ML} = \sqrt{3} V_{m\phi}$$

from cross over point of thyristor

(102)

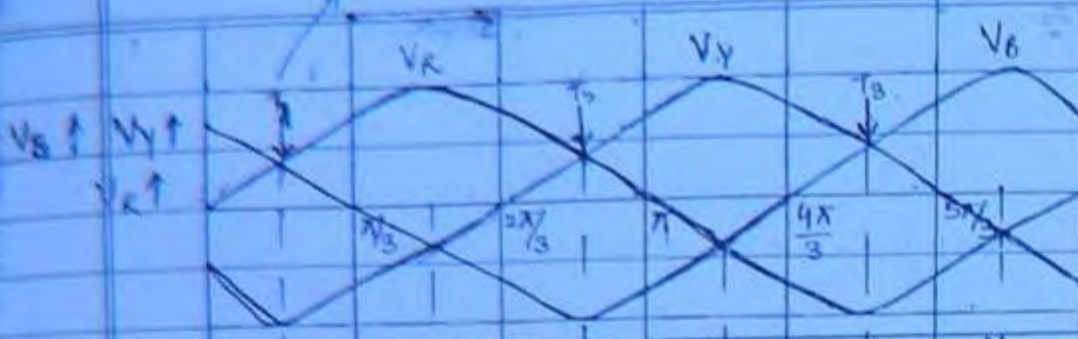

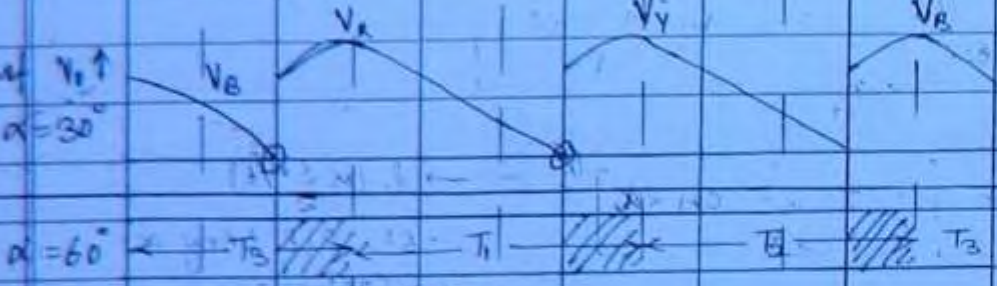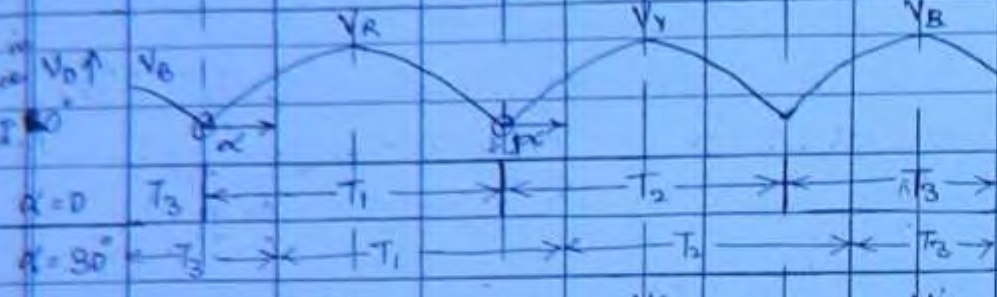Always output voltage is taken the max of v_g (in which ever phase it might be)



FD $\rightarrow (\alpha - \pi/6)$


For π load, upper limit remains π only as it is independent of α . Even if $\alpha \uparrow$ from 60° to 61° - the spikes are removed at π only.

max of v_g available in the device is obtained

am of $V_o \uparrow$

$\alpha = 60^\circ$
R Load
RL RLE with FD
 $T \rightarrow \frac{\pi - (\alpha - \pi)}{3 + 6}$
 $T = \frac{5\pi - \alpha}{6}$

Highly inductive w/o FD $I_R \uparrow$

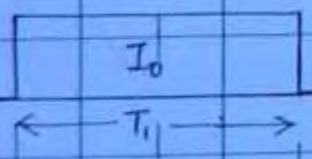

for L load -ve spikes occur.

I $\alpha \leq \frac{\pi}{6}$ \Rightarrow continuous conduction for R load

$$V_o = \frac{1}{2\pi/3} \int_{\alpha+\pi/6}^{\alpha+5\pi/6} V_{m\phi} \sin \omega t d(\omega t)$$

(103)

$$V_o = \frac{3\sqrt{3} V_{m\phi}}{2\pi} \cos \alpha = \frac{3V_{mL}}{2\pi} \cos \alpha$$

$\rightarrow R (\alpha \leq \pi/6)$
 $\rightarrow RL, RLE$
(any α)
Continuous

$$V_{or} = \left\{ \frac{1}{2\pi/3} \int_{\alpha+\pi/6}^{\alpha+5\pi/6} V_{m\phi}^2 \sin^2 \omega t d(\omega t) \right\}^{1/2}$$

$$V_{or} = V_{mL} \left[\frac{1}{6} + \frac{\sqrt{3} \cos 2\alpha}{8\pi} \right]^{1/2}$$

$\rightarrow R (\alpha \leq \pi/6)$
 $\rightarrow RL, RLE$ (Any α)
Continuous

II $\alpha > \frac{\pi}{6}$ \Rightarrow discontinuous conduction for R load.

$$V_o = \frac{1}{2\pi/3} \int_{\alpha+\pi/6}^{\pi} V_{m\phi} \sin \omega t d(\omega t)$$

$$V_o = \frac{3V_{m\phi}}{2\pi} \left[\frac{1 + \cos(\alpha + \pi)}{6} \right]$$

$\rightarrow R (\alpha > \pi/6)$
 $\rightarrow RL, RLE$ with FD ($\alpha > \pi/6$)

$$V_{or} = \left\{ \frac{1}{2\pi/3} \int_{\alpha+\pi/6}^{\pi} V_{m\phi}^2 \sin^2 \omega t d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_{mL}}{2\sqrt{\pi}} \left[\left(\frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \frac{\sin(2\alpha + \pi)}{3} \right]^{1/2}$$

$\rightarrow R (\alpha > \pi/6)$
 $\rightarrow RL, RLE$ with FD ($\alpha > \pi/6$)

Assume highly Inductive Load with FD -

I $\alpha \leq \frac{\pi}{6}$ FD will not conduct

(104)

∴ Conduction angle of each thyristor = $\frac{2\pi}{3}$ i.e. 120°
[for every 2π rad.]

$$V_o \times (I_T)_{avg} = I_o \left(\frac{2\pi/3}{2\pi} \right) = \frac{I_o}{3}$$

$$(I_L = I_{ph} = I_T)_{avg} = \frac{I_o}{3}$$

$$(I_L = I_{ph} = I_T)_{rms} = \frac{I_o}{\sqrt{3}}$$

II $\alpha > \frac{\pi}{6}$ Conduction angle of FD = $\left(\frac{\alpha - \pi}{6} \right)$ for every $2\pi/3$ radians.

Conduction angle of each thyristor = $\left(\frac{5\pi - \alpha}{6} \right)$ for every 2π radians

$$(I_L = I_{ph} = I_T)_{avg} = I_o \left[\frac{(5\pi/6 - \alpha)}{2\pi} \right]$$

$$(I_L = I_{ph} = I_T)_{rms} = I_o \left[\frac{(5\pi/6 - \alpha)}{2\pi} \right]^{1/2}$$

$$(I_{FD})_{avg} = I_o \left[\frac{(\alpha - \pi/6)}{2\pi/3} \right]$$

$$(I_{FD})_{rms} = I_o \left[\frac{(\alpha - \pi/6)}{2\pi/3} \right]^{1/2}$$

Assume highly Inductive Load without FB -

Any α

(105)

Conduction angle of each thyristor = $\frac{2\pi}{3}$ [for every 2π rad]

$$(I_T = I_{ph} = I_f)_{avg} = I_o \cdot \left(\frac{2\pi/3}{2\pi} \right) = \frac{I_o}{3}$$

$$(I_T = I_{ph} = I_T)_{rms} = \frac{I_o}{\sqrt{3}}$$

$$\rightarrow (I_s)_{avg} = \frac{I_o}{3} \text{ (DC comp)}$$

Drawback

The source current contains DC component & saturates the ~~trans~~ supply transformer core

RATINGS OF SCR -

1. $(I_T)_{RMS}$ Rating (RMS Rating of ON state current) provided by manufacturer

$(I_T)_{RMS}$ Rating $\geq (I_T)_{rms}$ value of in a converter

eg

$$1-\phi \text{ full conv } (I_T)_{rms} = \frac{I_o}{\sqrt{2}}$$

$$1-\phi \text{ semi conv } (I_T)_{rms} = I_o \left(\frac{\pi - \alpha}{2\pi} \right)^{1/2}$$

$$3 \text{ phase } (I_T)_{rms} = \frac{I_o}{\sqrt{3}}$$

e. (I_{TAV}) Rating [Average ON state current rating]

$$(I_{TAV})_{\text{Rating}} = (I_T)_{\text{RMS}} \text{ Rating}$$

(106)


FF = form factor of ^{thyristor} current waveform in a converter

depends on shape of waveform.

CWB chapter 1

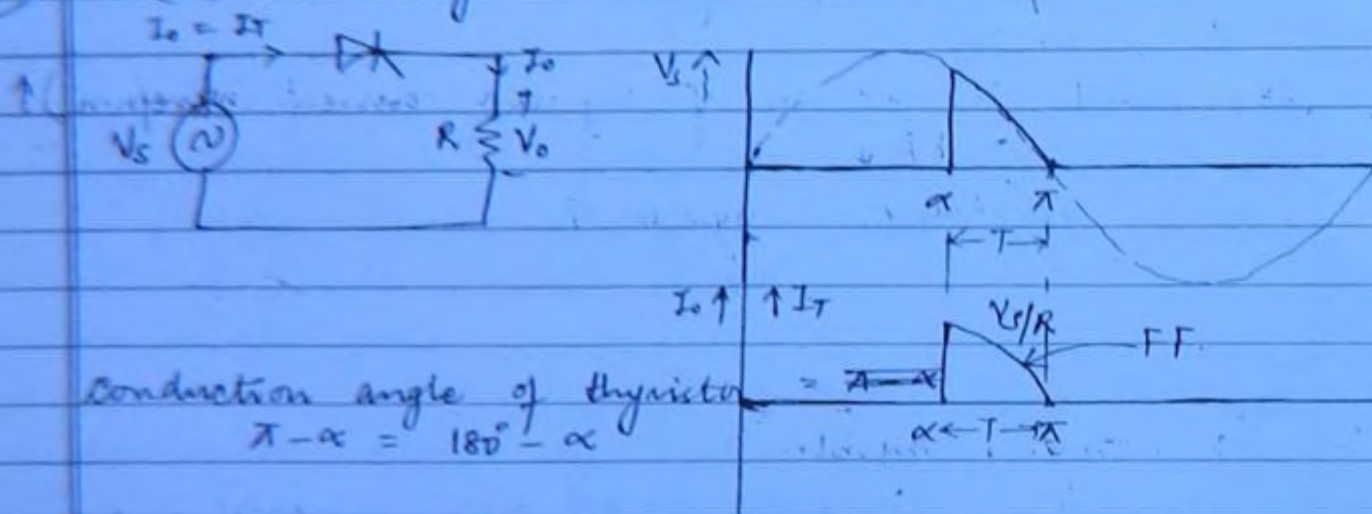(20)

$$(I_T)_{\text{RMS}} \text{ Rating} = 35 \text{ A}$$



$$\text{Given } 180^\circ - \alpha = 30^\circ$$

$$\alpha = 150^\circ$$

$$FF = \frac{(I_T)_{\text{RMS}}}{(I_T)_{\text{avg}}} = \frac{I_{O_{\text{RMS}}}}{I_o} = \frac{V_{O_{\text{RMS}}}/R}{V_o/R} = \frac{V_{O_{\text{RMS}}}}{V_o}$$

$$FF = \frac{V_m}{\sqrt{\pi}} \cdot \left[\frac{\pi - \alpha}{2} + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$\frac{V_m}{\sqrt{\pi}} [1 + \cos \alpha]$$

$$= \sqrt{\pi} \left[\left(\frac{\pi}{6} \right) + \frac{1}{2} \sin \frac{300^\circ}{3} \right]^{1/2} = 3.98$$

$$[1 + \cos 150^\circ]$$

$$I_{TAV} = \frac{(I_T)_{rms} \text{ Rating}}{FF} = \frac{35}{3.98} = 8.79 \text{ A} \quad (d)$$

(107)

Avg rating depends on -

Conduction angle of thyristor

As conduction angle $\uparrow \Rightarrow$ (smoothness of I_T waveform) \uparrow
 $\Rightarrow FF \downarrow$

Thus avg rating of thyristor \uparrow

Load parameters

eg. $L \uparrow \Rightarrow$ (smoothness of thyristor current waveform) \uparrow
 $\Rightarrow FF \downarrow$
 (I_{TAV}) Rating of thyristor \uparrow

(I^2t rating of thyristor)

provided by manufacturer - to select a proper fuse for the thyristor

I^2t rating of thyristor $\leq I^2t$ rating of fuse

Surge current Rating of Thyristor

i) n cycle surge current rating - (I_{sn})

It's the surge current that the SCR can withstand for n cycles at the most

$$\therefore (I_{sn})^2 \cdot n \cdot \frac{T}{2} \leq I^2t \text{ rating}$$

(ii) one cycle surge current rating (I_{sr}):
It is the surge current that the SCR can withstand for one cycle.

$$(I_{s1})^2 \cdot \frac{T}{2} = (I_{sn})^2 \cdot \frac{T}{2}$$

$$I_{sr} = \sqrt{n} I_{s1}$$

(iii) Sub-cycle surge current rating ($I_{s/n}$):

It is the surge current that the SCR can withstand for $1/n$ th period of a cycle.

$$(I_{s/n})^2 \cdot \frac{T}{n} = (I_{s1})^2 \cdot \frac{T}{2}$$

$$I_{s/n} = \sqrt{n} I_{s1}$$

(iv) Half cycle surge current.
 $I_{s/2} = \sqrt{2} I_{s1}$

CWB chapter 1

(19) $I_{s/n} = 3000$

$$I_{s1} = \frac{3000}{\sqrt{2}} = 2121.32 \text{ A} \quad (b)$$

(21) (c)

CWB chapter 2

(2) (b) -ve spikes are removed.


(109)

(3) Half wave rectifier

PIV depends on secondary not on primary

$$V_s = 50 \text{ PIV (rms)} \therefore V_m = 50\sqrt{2}$$
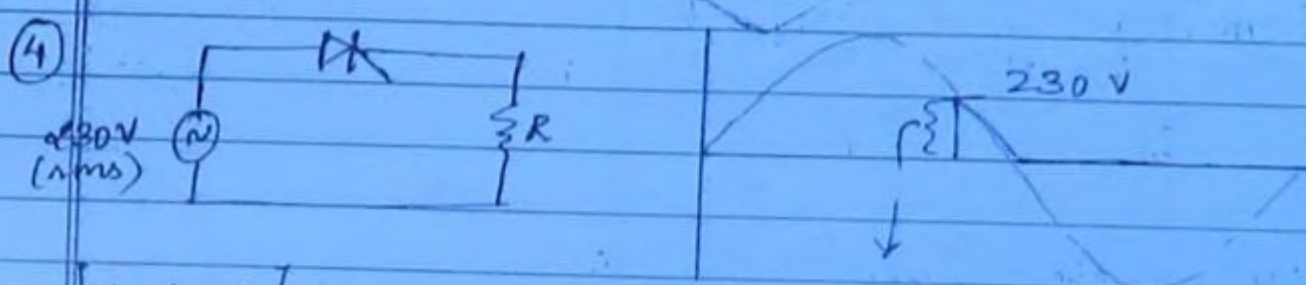
$$\begin{aligned} \text{PIV} &= 2V_m = 50\sqrt{2} (2) \\ &= 100\sqrt{2} \text{ (A)} \end{aligned}$$



$$V_o (\text{wt})_{\text{peak}} = 230 \text{ V}$$

$$\begin{aligned} V_m \sin \alpha &= 230^\circ \\ 230\sqrt{2} \sin \alpha &= 230^\circ \\ \sin \alpha &= \frac{1}{\sqrt{2}} \end{aligned}$$


$$\begin{aligned} V_o \text{ for } \alpha \leq 90^\circ \\ V_m &= 230\sqrt{2} \quad \times \end{aligned}$$

So $\alpha > 90^\circ$


$$\alpha = \cancel{45^\circ}, 135^\circ$$

↓
Ans (b)

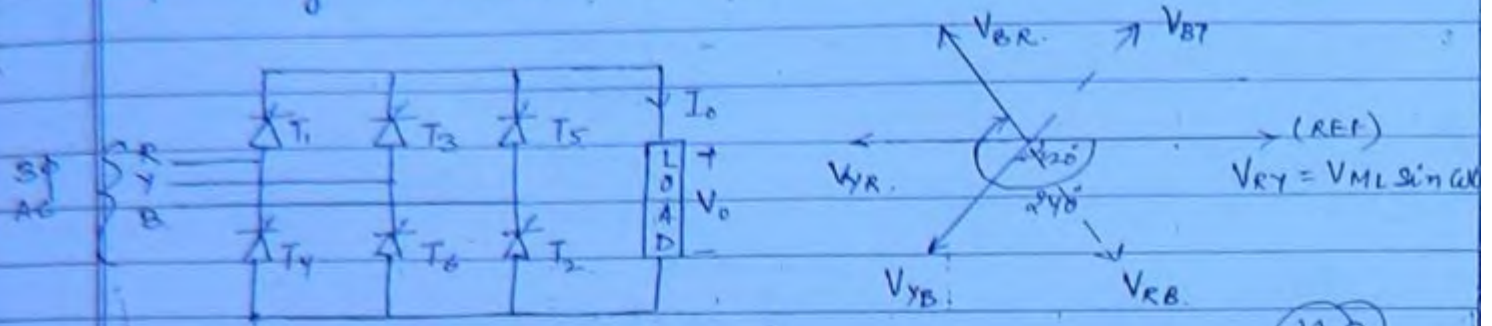3φ Fully Controlled Rectifier (6 pulse Converter)




110

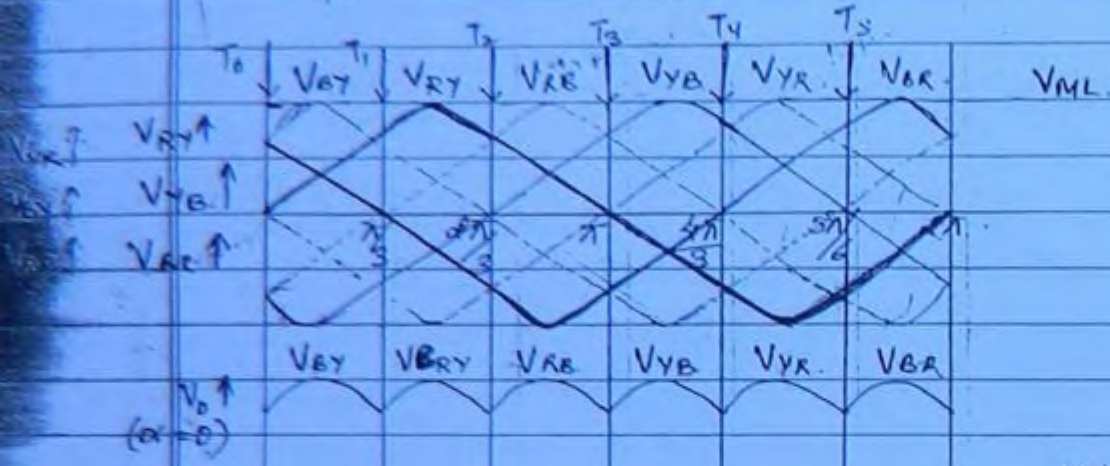


| | | | | | | |
|---------------------|---|-------|-------|-------|-------|-------|
| $\alpha = 0^\circ$ | + | T_5 | T_1 | T_3 | T_2 | T_4 |
| | - | T_6 | T_2 | T_4 | T_1 | T_3 |
| $\alpha = 60^\circ$ | + | T_5 | T_1 | T_3 | T_2 | T_4 |
| | - | T_6 | T_2 | T_4 | T_1 | T_3 |

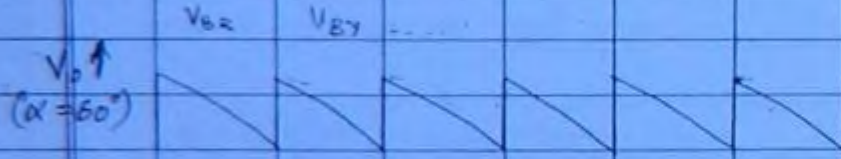Count α from crossover pt.
 + T_1, T_3, T_5 } seq. remains same.
 - T_4, T_6, T_2 }



| | | | | | | |
|---------------------|---|-------|-------|-------|-------|-------|
| $\alpha = 90^\circ$ | + | T_5 | T_1 | T_3 | T_2 | T_4 |
| | - | T_6 | T_2 | T_4 | T_1 | T_3 |

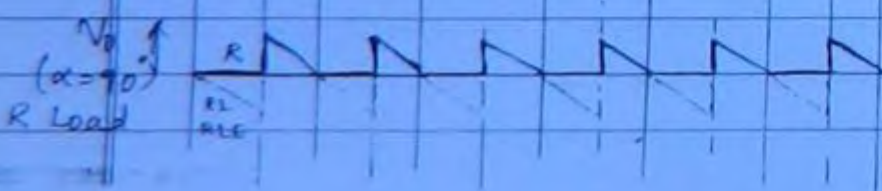

$\alpha \leq \pi/3 \rightarrow$ continuous conduction for R load

$$V_o = \frac{1}{\pi/3} \int_{\alpha}^{\alpha + \pi/3} V_{ML} \sin \omega t \, d(\omega t)$$

| | |
|---|---|
| $V_o = \frac{3V_{ML} \cos \alpha}{\pi}$ | $\rightarrow R (\alpha \leq \pi/3)$ |
| | $\rightarrow RL, RLE$ (Any α) continuous |

(112)

$$V_{OR} = \left\{ \frac{1}{\pi/3} \int_{\alpha}^{\alpha + \pi/3} V_{ML}^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$= \left[\frac{3}{2\pi} V_{ML} \left\{ \frac{\pi}{3} + \frac{1}{2} \left[\sin \left(\frac{2\alpha + 2\pi}{3} \right) - \sin \left(\frac{2\alpha + 4\pi}{3} \right) \right] \right\} \right]^{1/2}$$

$\alpha > \pi/3 \rightarrow$ discontinuous conduction for R load -

$$V_o = \frac{1}{\pi/3} \int_{\alpha}^{\pi} V_{ML} \sin \omega t \, d\omega t$$

| | |
|---|----------------------------------|
| $V_o = \frac{3V_{ML}}{\pi} \left[1 + \cos \left(\alpha + \frac{\pi}{3} \right) \right]$ | $\rightarrow R (\alpha > \pi/3)$ |
|---|----------------------------------|

$$V_{OR} = \left\{ \frac{1}{\pi/3} \int_{\alpha}^{\pi} V_{ML}^2 \sin^2 \omega t \, d\omega t \right\}^{1/2}$$

$$= \left[\frac{3}{2\pi} V_{ML} \left\{ \left(\frac{2\pi - \alpha}{3} \right) + \frac{1}{2} \sin \left(\frac{2\alpha + 2\pi}{3} \right) \right\} \right]^{1/2} \rightarrow R (\alpha > \pi/3)$$

Assume highly inductive load - (RL, RLE)

Conduction angle of each thyristor = $\frac{2\pi}{3}$ (for every $\frac{2\pi}{3}$ rad)

$$(I_T)_{avg} = I_o \left(\frac{2\pi/3}{2\pi} \right) = \frac{I_o}{3}$$

(13)

$$(I_T)_{rms} = \frac{I_o}{\sqrt{3}}$$

$$(I_R)_{rms} = I_o \left(\frac{2\pi/3}{\pi} \right)^{1/2}$$

$$I_{RR} = (I_R)_{rms} = I_o \sqrt{\frac{2}{3}}$$

Harmonic Analysis on AC side of converter for source current (I_s) waveform.

$$I_s = \sum_{n=1,3,5}^{\infty} \frac{4I_o \sin n\pi}{n\pi} \sin(n\omega t + \phi_n)$$

$n = 6k \pm 1$

Since $\sin \frac{3\pi}{3} = 0$ so 3rd harmonic & multiples of 3 harmonics (triple harmonics) are absent. So are even harmonics.

NOTE: Even if triple harmonics are absent

$$\phi_n = -n\alpha \quad \phi_1 = -\alpha$$

$$(I_{sn})_{rms} = \frac{2\sqrt{2}}{n\pi} I_o \sin n\pi$$

$$(I_{s1})_{rms} = \frac{2\sqrt{2}}{\pi} I_o \sin \pi$$

$$(I_{s1})_{rms} = \frac{\sqrt{6}}{\pi} I_0 \quad \text{--- (1)}$$

$$FDF = \cos \phi_1$$

$$FDF = \cos \alpha \quad \text{--- (2)}$$

$$g = \frac{(I_{s1})_{rms}}{I_{sA}} = \frac{\frac{\sqrt{6}}{\pi} I_0}{I_0 \sqrt{\frac{2}{3}}}$$

174

$$g = \frac{3}{\pi} \quad \text{--- (3)}$$

$$THD = \left(\frac{1}{g^2} - 1 \right)^{1/2} = \left(\frac{\pi^2}{9} - 1 \right)^{1/2}$$

$$THD = 31\% \quad \text{--- (4)}$$

$m \uparrow$ THD \downarrow \therefore harmonics \downarrow

$$PF = g (FDF)$$

$$PF = \frac{3}{\pi} \cos \alpha \quad \text{--- (5)}$$

$$\text{Active power } P = \sqrt{3} V_{sA} I_{s1} \cos \alpha \quad \text{--- (6)}$$

$$= \sqrt{3} V_{ML} \frac{\sqrt{6}}{\pi} I_0 \cos \alpha$$

$$= \frac{3 V_{ML}}{\pi} \cos \alpha \cdot I_0 = V_0 I_0$$

$$\text{Reactive power } \Rightarrow Q = \sqrt{3} V_{sA} I_{s1} \sin \alpha = V_0 I_0 \tan \alpha \quad \text{--- (7)}$$

$$= P \tan \alpha$$

To find t_c & PIV across thyristor we need to plot V_T .

(115)

$$T_1 \rightarrow ON \quad V_T = 0$$

$$T_3 \rightarrow ON \quad V_T = V_{e1}$$

$$T_5 \rightarrow ON \quad V_T = V_{e3}$$

$$\omega t_c = \frac{4\pi}{3} \quad t_c = \frac{4\pi}{3\omega} \text{ sec.}$$

I) $\alpha < 60^\circ$

$$\alpha + \omega t_c = \frac{4\pi}{3}$$

$$\omega t_c = \frac{4\pi}{3} - \alpha$$

$$t_c = \frac{4\pi - \alpha}{3\omega}$$


II) $\alpha \geq 60^\circ$

$$\alpha + \omega t_c = \pi$$

$$\omega t_c = \pi - \alpha$$

$$t_c = \frac{\pi - \alpha}{\omega} \text{ sec.}$$

3 pulse converter -

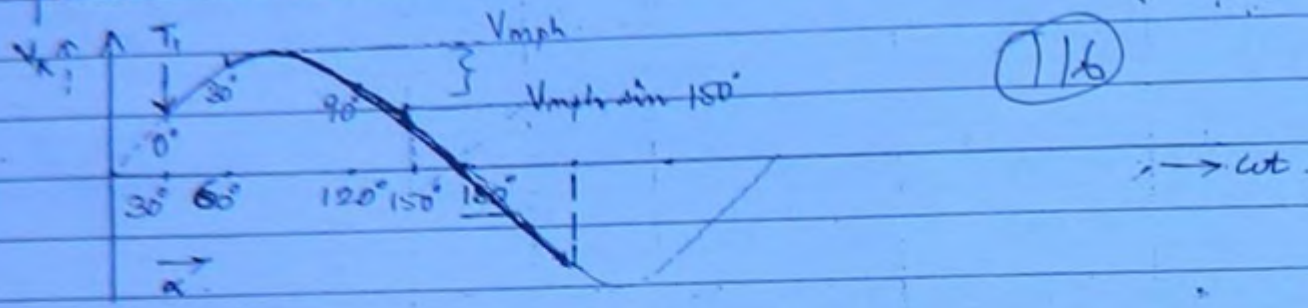


$$\alpha = \omega t - 30^\circ$$

$$\text{Length of pulse} = \frac{2\pi}{3} = 120^\circ$$

- | | |
|--------------------------------|------------------|
| $0 \leq \alpha \leq 150^\circ$ | → R load |
| $0 \leq \alpha \leq 180^\circ$ | → Inductive Load |

3 pulse converter

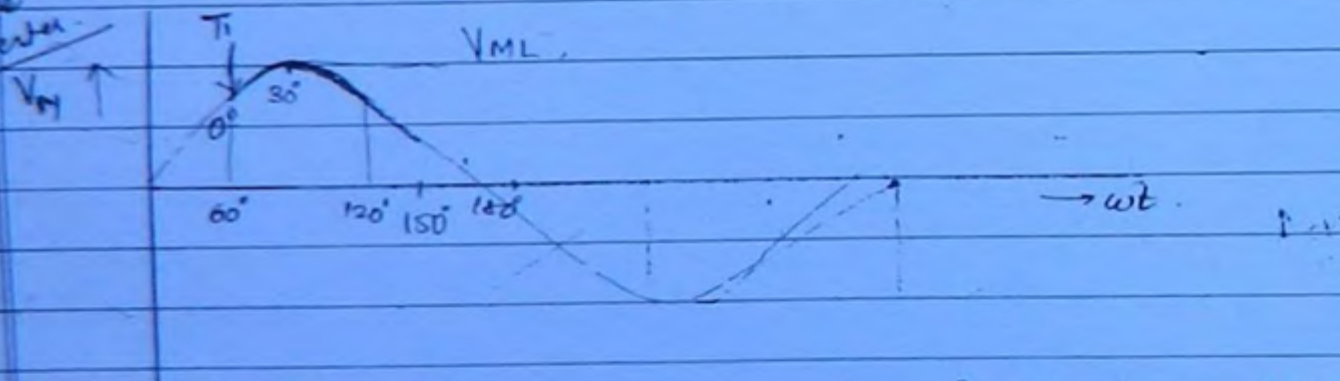

$$\alpha = \omega t - 60^\circ$$

$$\text{Length of pulse} = \frac{\pi}{3} = 60^\circ$$

for R load → $0 \leq \alpha \leq 150^\circ$

RL, RLE load → $0 \leq \alpha \leq 180^\circ$








CWB chapter 2


① $\frac{\text{Peak to peak vlg ripple}}{\text{peak of dc voltage}} = \frac{V_{ML} - V_{ML} \sin 150^\circ}{V_{ML}}$

$$= 1 - \sin 150^\circ$$

$$= 0.5 \quad (A)$$

3φ Half Controlled Rectifier

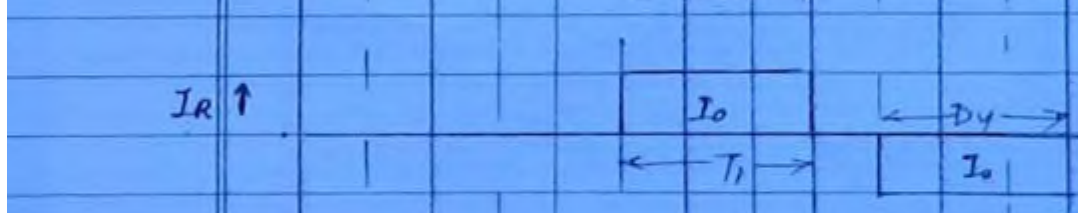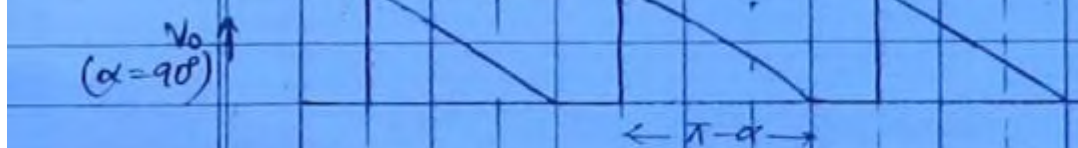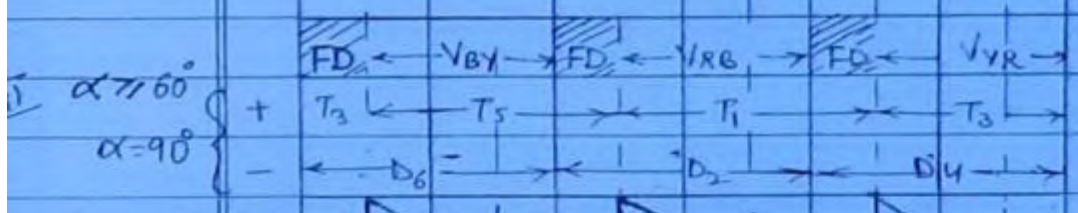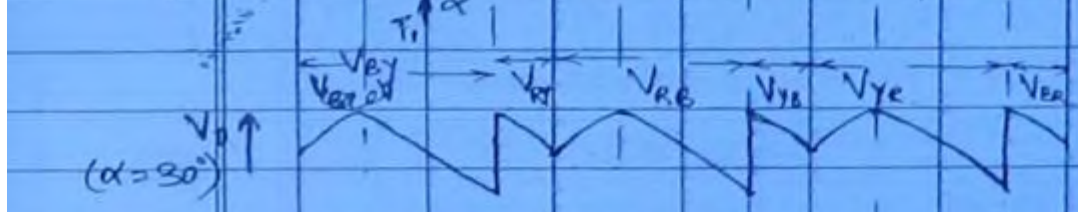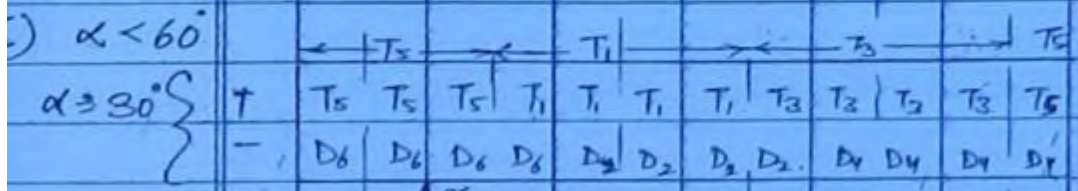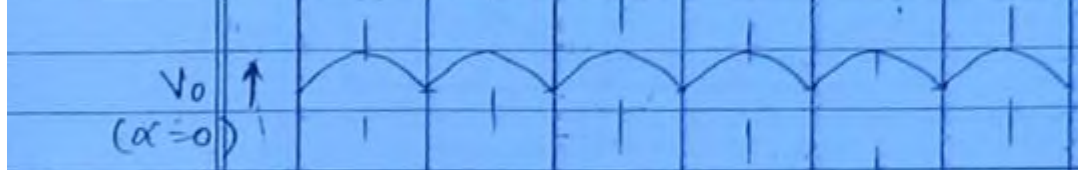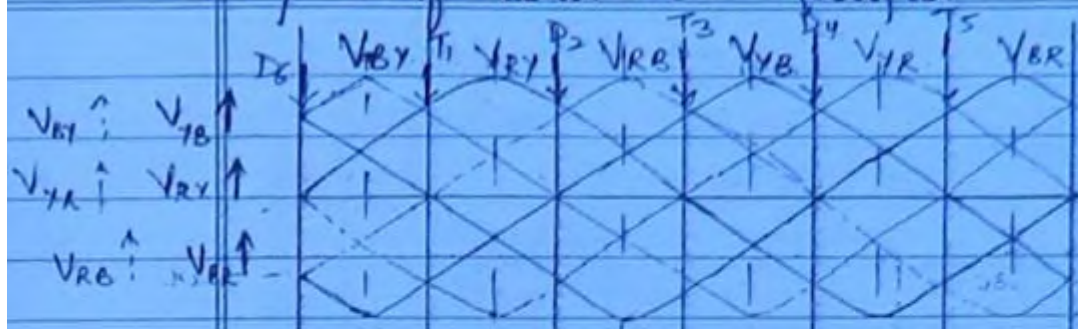


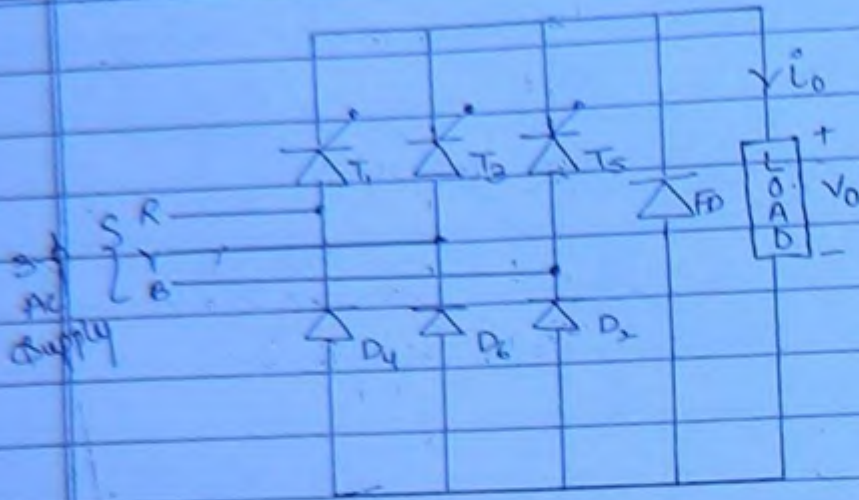

+ T_1, T_3, T_5
 - D_4, D_6, D_2

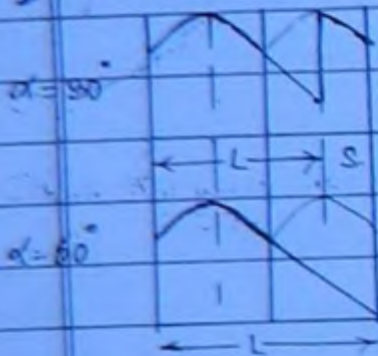(115)

Short method - 1 mark
 I $\alpha < 60^\circ$ FD will not conduct.



$$\rightarrow S = 60 - \alpha$$

$$= 60 - 60$$

$$= 0$$

Take $V_o (\alpha = 0)$ as ref
 Long pulse $= 60 + \alpha$
 Short pulse length $= 60 - \alpha$

(*) $\alpha < 60^\circ \Rightarrow 6$ pulse IES
 $\alpha \geq 60^\circ \Rightarrow 3$ pulse.

For $\alpha < 60^\circ$ FD will not conduct.


for $\alpha \geq 60^\circ$

conduction period of FD $= \left(\alpha - \frac{\pi}{3} \right)$ radians

conduction period of thyristor $= \frac{2\pi}{3} - \left(\alpha - \frac{\pi}{3} \right)$

$$= \pi - \alpha$$

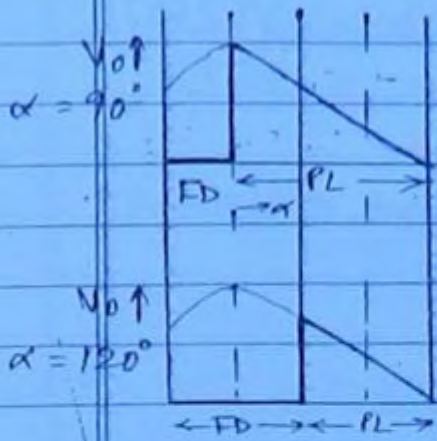\therefore Length of pulse $= \pi - \alpha$



(119)

Take V_0 ($\alpha = 60^\circ$) as ref

$$FD \rightarrow \alpha - \pi/3$$

$$\text{Pulse length} = \pi - \alpha$$

As $\alpha \uparrow$ Free wheeling \uparrow
Pulse length \downarrow

Assume Highly Inductive Load

$\alpha \leq 60^\circ$ FD will not conduct

Conduction angle of FD = $(\alpha - \pi/3)$

Conduction angle of thyristor = $\frac{2\pi}{3}$ rad (for every 2π radians)

$$(I_T)_{avg} = I_0 \left(\frac{2\pi/3}{2\pi} \right) = \frac{I_0}{3}$$

$$(I_T)_{rms} = \frac{I_0}{\sqrt{3}}$$

$$I_{sA} = I_0 \sqrt{\frac{2}{3}}$$

$\alpha > 60^\circ$ FD will conduct

Conduction angle of FD = $\alpha - \frac{\pi}{3}$ (for every $\frac{2\pi}{3}$ rad)

Conduction angle of thyristor = $\pi - \alpha$ (for every 2π rad)

$$(I_T)_{avg} = I_0 \left(\frac{\pi - \alpha}{2\pi} \right)$$

$$(I_T)_{rms} = I_0 \left(\frac{\pi - \alpha}{2\pi} \right)^{1/2}$$

$$I_{sA} = I_0 \left(\frac{\pi - \alpha}{2\pi} \right)^{1/2}$$

$$V_o = \frac{3V_{ML}}{\pi} (1 + \cos \alpha)$$

(12a)


Representation of semi-converter.



$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha) \rightarrow 1\phi$$

$$V_o = \frac{3V_{ML}}{\pi} (1 + \cos \alpha) \rightarrow 3\phi$$


Representation of full converter.

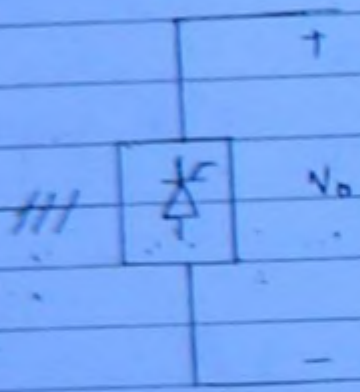

APPLICATIONS -

DC Drives -

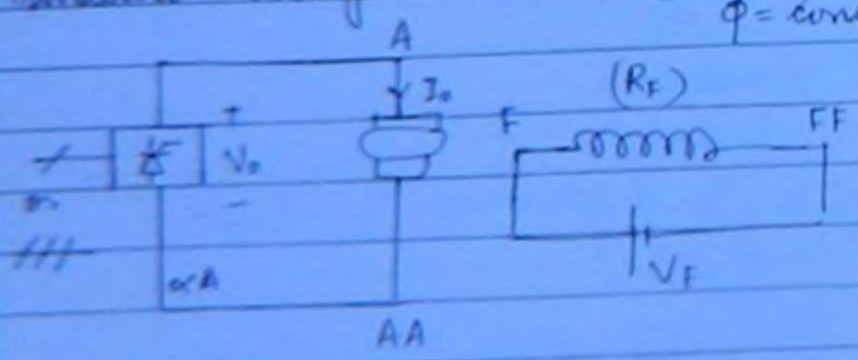1. Armature Voltage Control ($\omega < \omega_n$)
 $\phi = \text{const}$



$$1\phi \quad V_o = \alpha V_m \cos \alpha$$

$$E_b \propto \phi N$$

$$E \propto N \quad (\phi = \text{const})$$

$$E = KN$$

→ EMF const. (V/rpm)
or Motor const

$$E = K\omega$$

→ EMF const (V.sec)/rad
or Motor const

$$T_a \propto \phi I_a$$

$$T_a \propto I_a \quad (\phi = \text{const})$$

$$T_a = K I_a$$

$$\rightarrow I_a = T_a / K$$

→ Motor const $\text{NM/A} = (\text{V.sec})/\text{rad}$
or Torque const

$$\omega = \frac{2\pi N}{60}$$

$$N \rightarrow \text{rpm}$$

$$\omega \rightarrow \text{rad/sec}$$

For Motoring Mode

$$V_o = E_b + I_a R_a$$

$$V_o = K\omega + I_a R_a$$


$$\omega = \frac{V_o - I_a R_a}{K}$$

$$\omega = \frac{V_o}{K} - \frac{R_a I_a}{K}$$

$$\alpha_A \uparrow \quad V_o \downarrow \quad \therefore \omega \downarrow \quad (\omega \propto \omega_s)$$

(II) Field Control Method ($\omega > \omega_n$)

(122)

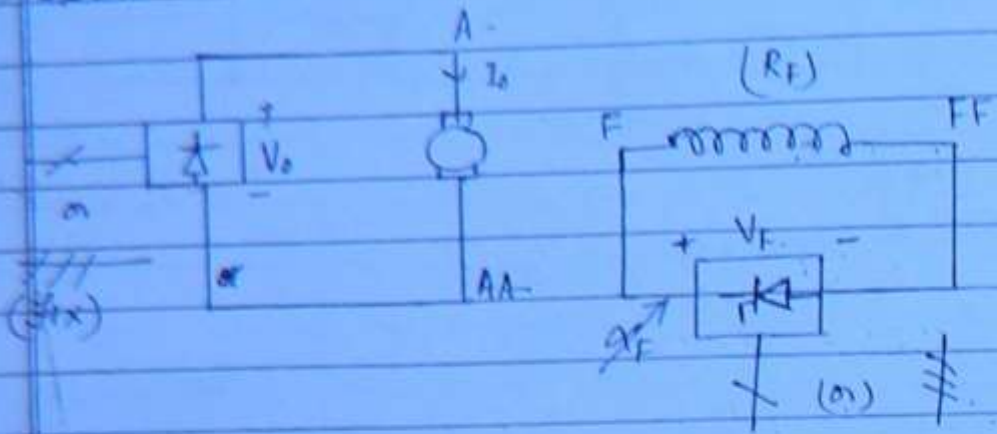

$$1\phi \quad V_F = \frac{\alpha V_m}{\pi} \cos \alpha_F$$

$$I_{F1} = \frac{V_F}{R_F}$$

$$3\phi \quad V_F = \frac{3V_{ML}}{\pi} \cos \alpha_F$$

$$\phi \propto I_F$$

$$\phi = K_F I_F$$

$$E_b \propto \phi N \propto (K_F I_F) N$$

$$E_b = K_1 (K_F I_F) N$$

$$E = \underbrace{K_1}_{\text{EMF const}} I_F N$$

→ EMF const $\frac{V}{\text{rpm} \cdot A}$
or Motor const

$$E = \underbrace{K_1}_{\text{EMF const}} I_F \omega$$

→ EMF const $\frac{V \cdot \text{sec}}{\text{rad} \cdot A}$
or Motor const

$$T_a \propto \phi I_a$$

$$T_a = K I_F I_a$$

$$T_a = \underbrace{K I_F}_{\text{Motor const}} I_a \quad \rightarrow I_a = \frac{T_a}{K I_F}$$

→ Motor const $\frac{V \cdot \text{sec}}{\text{rad} \cdot A}$
or Torque const

$$\omega = \frac{a' \pi N}{60}$$

(123)

for Motoring Mode

$$V_o = E_b + I_o R_a$$

$$V_o = K I_f \omega + I_o R_a$$

$$\omega = \frac{V_o - I_o R_a}{K I_f}$$


$$\omega \rightarrow \frac{V_o - R_a T_a}{K I_f} \quad (K I_f)^2$$

$$\alpha_f \uparrow \quad V_f \downarrow \Rightarrow I_f \downarrow \Rightarrow \omega_o > \omega_n$$

for Motoring Mode \Rightarrow Torque developed is in same dirⁿ as speed

Current enters at +ve terminal of back emf, so that electrical effect absorbed is transformed in mech. energy.

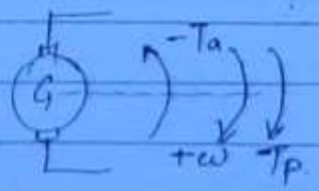for Generating Mode \Rightarrow Torque developed of speed in opp dirⁿ



(125)



Rectification Mode -

- can be used for motoring mode of a DC m/c.
- can also be used to charge a battery.

Inversion Mode

- can be used for regenerative braking of DC m/c.
- solar energy stored in the form of DC can be given to the AC side of utility system where the converter is operating in (inversion) mode.

Full converter feeding DC m/c -

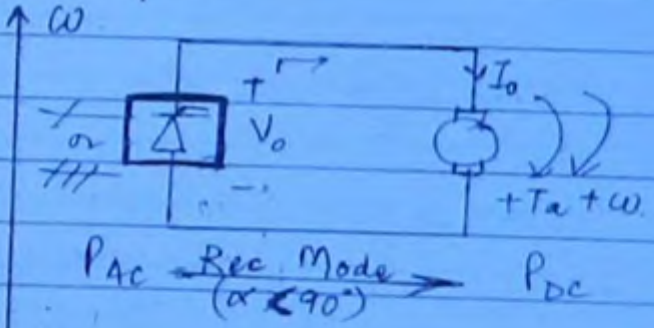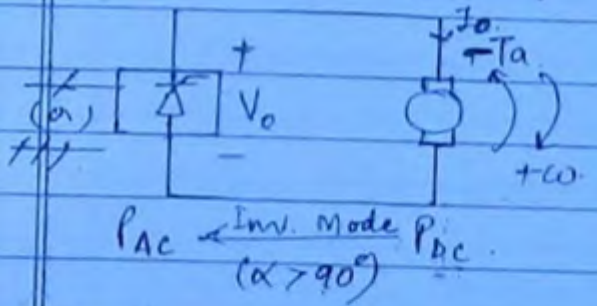

Since ← Braking Energy (regenerative braking)

$\alpha < 90^\circ$ $V_o + E_b + \omega \cdot I_a + \dots$
 $I_a + \dots$
 $T_a \rightarrow \phi I_a$

Converter will support the inversion if $\alpha > 90^\circ$
 Load supports inversion if emf is having ability to deliver power.

Converter will support the rectification if $\alpha < 90^\circ$
 Load supports rectification if emf is having ability to absorb the power.

$$V_o = -E_b + I_o R_a$$

126

$$V_o = E_b + I_o R_a$$

$$\omega = \frac{\alpha^2 V_m}{\pi K} \cos \alpha - \frac{R_a T_a}{K^2} \rightarrow 1\phi$$

$$\omega = \frac{3V_m}{\pi K} \cos \alpha - \frac{R_a T_a}{K^2} \rightarrow 3\phi$$

$$T_a + \omega T \therefore (P+) \quad (\phi +)$$

Quadrant Operation of Semi Converter.
Supports

DUAL CONVERTER (Four Quadrant Operation)


(127)

i) Non-Circulating Current Type -

In non-circulating current type dual converter, if one converter is in the ON state then other converter is in the OFF state.

Advantage -

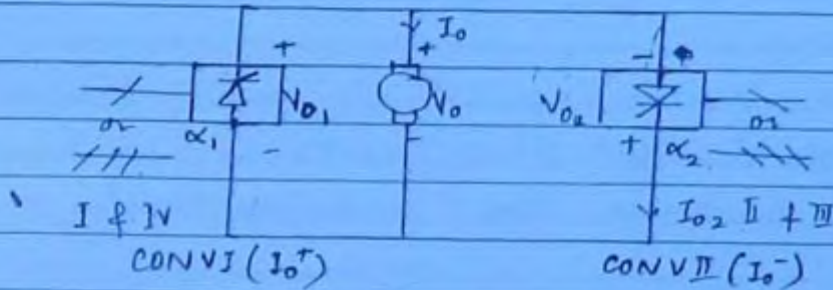There is no circulating current b/w the converters.



1φ, $V_{01} = \frac{2V_m \cos \alpha_1}{\pi}$

1φ, $V_{02} = \frac{2V_m \cos \alpha_2}{\pi}$

3φ, $V_{01} = \frac{3V_{ML} \cos \alpha_1}{\pi}$

3φ, $V_{02} = \frac{3V_{ML} \cos \alpha_2}{\pi}$

CONV I → OFF, CONV II → ON

CONV I → ON, CONV II → OFF


$\alpha_2 > 90^\circ$

$\alpha_1 < 90^\circ$

$V_{02} = -V_0 +$


$V_{01} +, V_0 +, E_b +, \omega +$

RB

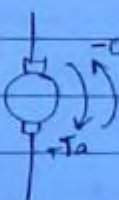

$T_a \rightarrow \phi I_0 \therefore T_a +$
 $E_b \rightarrow \phi \omega \therefore E_b +$

$I_a +, T_a +$

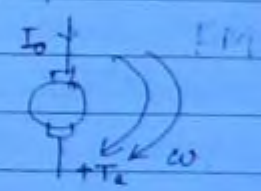


CONV I → OFF, CONV II → ON

CONV I → ON, CONV II → OFF

$\alpha_2 < 90^\circ$

CONV I → ON, CONV II → OFF

CONV I → OFF, CONV II → ON

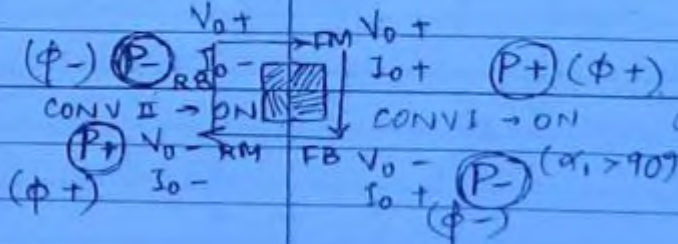


RM


$V_{02} +, V_0 - E_b - \omega -$

$V_{01} -, V_0 -$

$I_0 -, T_a -$

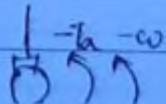

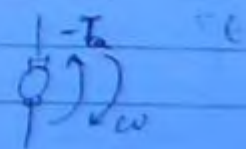$T_a \rightarrow \phi I_a \therefore T_a = -ve$



Disadvantage -

- It gives slow speed response if the reversal of armature current is not smooth during switching transition of the converter.



We must provide commutation delay time (Δt_d) to the outgoing converter before the incoming converter is switched ON to avoid high circulating current during switching transitions of converter. This commutation delay time is responsible for slow speed response.


ii) Circulating Current Type -

Here, both the converters are simultaneously in the ON state.

Disadvantage -

There will be circulating current b/w the converters & hence responsible for additional power loss.

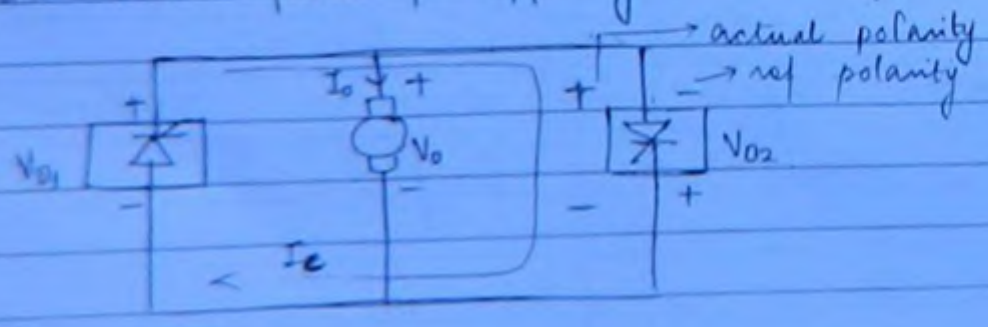Circulating current is due to the vlg difference b/w the two converters. We can reduce the circulating current if the output vlg of the converters are equal & opposing each other.



$I_c \downarrow \Rightarrow V_{o1} = -V_{o2} \quad \alpha_1 + \alpha_2 = 180^\circ$


$\frac{2V_m}{\pi} \cos \alpha_1 = -\frac{2V_m}{\pi} \cos \alpha_2$

129

$\cos \alpha_1 + \cos \alpha_2 = 0$
 $\alpha_2 = 180 - \alpha_1$
 $\alpha_1 + \alpha_2 = 180^\circ$

Even after maintaining $\alpha_1 + \alpha_2 = 180^\circ$, still there is some circulating current due to the instantaneous vlg difference b/w the converters

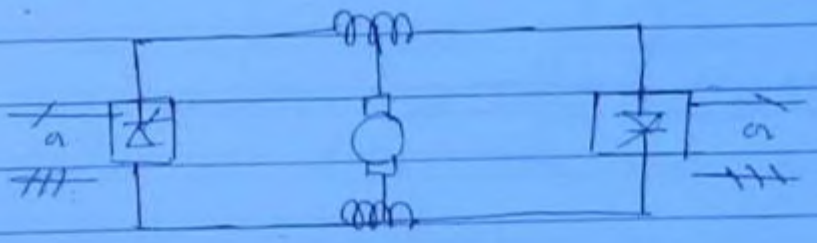* To reduce this circulating current, we must connect a reactor core ~~reactive power~~ b/w the converters as shown.




* In order to satisfy the relation $\alpha_1 + \alpha_2 = 180^\circ$ if one converter is operating in rectification mode then other converter must work in inversion mode

Advantage -



It gives high speed response if the reversal of armature current is smooth during switching transition of converters.

Effects of Source Inductance (L_s) on one Pulse Converter

(136)

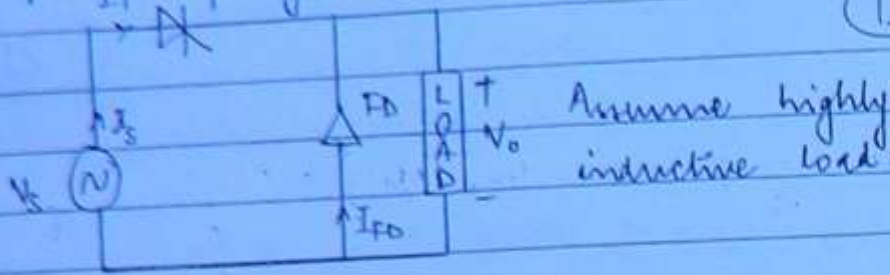

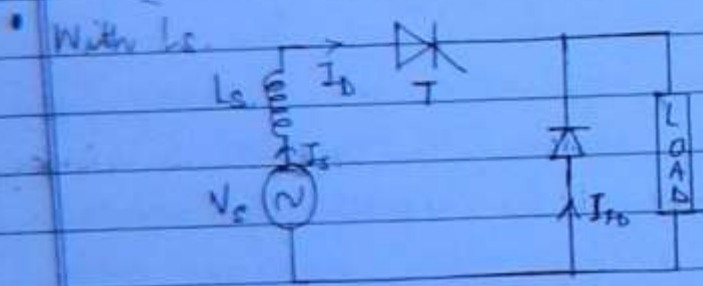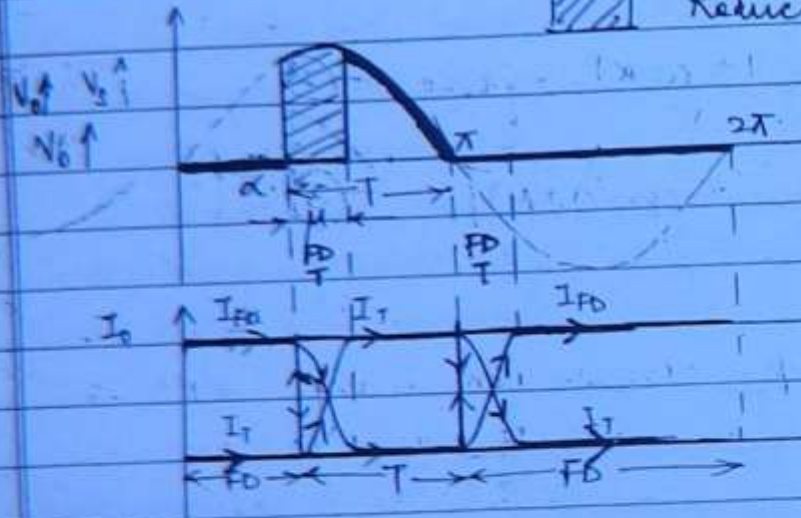Without L_s - $\rightarrow V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$
 Reduction in v_o due to L_s .



$\mu = \text{overlap period}$

During overlap period both T & FD are ~~on~~ exchanging load current thus $v_o = 0$

During Overlap \Rightarrow FD & T \rightarrow ON $V_o = 0$
 $V_s = L_s \frac{dI_o}{dt}$

$$\frac{V_m [\cos \alpha - \cos (\alpha + \mu)]}{2} = \frac{\omega L_s I_o}{2}$$

$$(131)$$

divide to give
avg. reduction
in vlg.

$$\Delta V_{do} = \frac{V_m [\cos \alpha - \cos (\alpha + \mu)]}{2\pi} = \frac{\omega L_s I_o}{2\pi} = f L_s I_o \quad \text{--- (1)}$$

ΔV_{do} = Avg reduction in V_o due to L_s .

$$V_o = \frac{V_m (1 + \cos \alpha)}{2\pi} - f L_s I_o \quad \text{--- (2)}$$

$$V_o = \frac{V_m [1 + \cos (\alpha + \mu)]}{2\pi} \quad \text{--- (3)}$$

* * Overlap angle μ depends on firing angle α but avg reduction in vlg due to source inductance i.e. ΔV_{do} does not depend on firing angle α .


* Avg reduction in vlg due to source inductance depends upon frequency, L_s & I_o

* If $f \uparrow$ or $L_s \uparrow$ or $I_o \uparrow$ w/o changing V_s & α then μ also \uparrow .

If $V_s \uparrow$ w/o changing f , L_s , I_o & α then $\mu \downarrow$ due to \uparrow in V_s height of pulse \uparrow . I_o maintain same area ΔV_{do} the width \downarrow . Thus $\mu \downarrow$


Effect of Source Inductance for Two Pulse Converter.

(132)

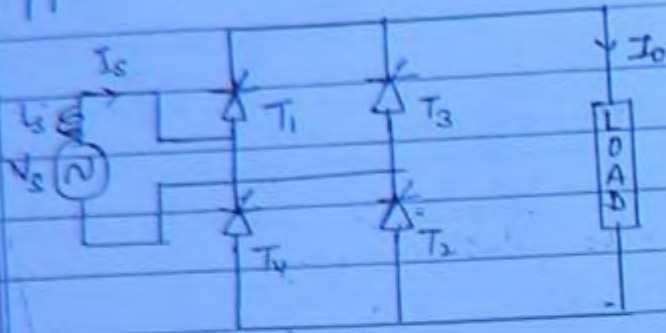

$$V_{do} = \frac{2V_m}{\pi} \quad (\text{max dc o/p v/g})$$

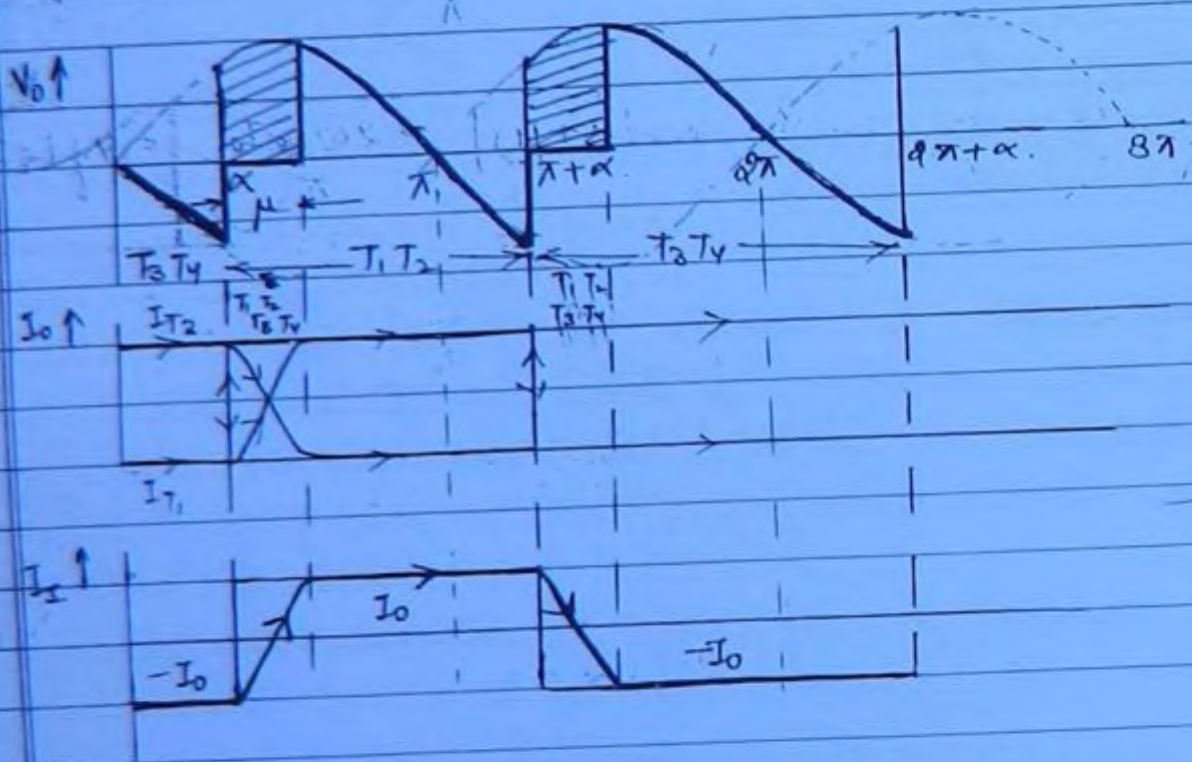Without \$L_s \rightarrow V_o = V_{do} \cos \alpha\$



$T_1, T_2 \rightarrow ON \quad I_{T1} = I_{T2} = I_o$
 $T_3, T_4 \rightarrow ON \quad I_{T3} = I_{T4} = I_o$

with \$L_s\$.

During the overlap period \$v_g\$ is 0 as all thyristors are conducting.

During μ T_1, T_2 & $T_3, T_4 \rightarrow ON$ $\therefore V_0 = 0$

(133)

$$V_0 = L_s \frac{dI_s}{dt}$$

$$\int_{\alpha}^{\alpha+\mu} V_m \sin \omega t \, d(\omega t) = \omega L_s \int_{-I_0}^{+I_0} dI_s$$

Wrong P.E.

$$\frac{V_m [\cos \alpha - \cos(\alpha + \mu)]}{\pi} = \frac{2\omega L_s I_0}{\pi}$$

$$\Delta V_{do} = \frac{V_m [\cos \alpha - \cos(\alpha + \mu)]}{\pi} = \frac{2\omega L_s I_0}{\pi} = 4f L_s I_0 \quad \text{--- (1)}$$

$$V_{do} = \frac{V_m \cdot 2}{\pi} \Rightarrow \frac{V_{do}}{2} = \frac{V_m}{\pi}$$

$$\Delta V_{do} = V_{do} [\cos \alpha - \cos(\alpha + \mu)] = \frac{2\omega L_s I_0}{\pi}$$

$$V_0 = V_{do} \cos \alpha - 4f L_s I_0 \quad \text{--- (2)}$$

$$V_0 = \frac{V_{do}}{2} [\cos \alpha + \cos(\alpha + \mu)] \quad \text{--- (3)}$$

From (1)

$$V_m [\cos \alpha - \cos(\alpha + \mu)] = 2\omega L_s I_0$$

$$I_0 = \frac{V_m}{2\omega L_s} [\cos \alpha - \cos(\alpha + \mu)]$$

$$I_0 = \cos \alpha - \cos(\alpha + \mu) \quad \text{--- (4)}$$

Inductive Voltage Regulation -

Measure of reduction in v_g due to the source inductance.

$$\Delta V_{do} = \frac{N_{do}}{2} [\cos \alpha - \cos(\alpha + \mu)]$$

$$= \frac{V_{do}}{2} [\cos \alpha - \cos(\alpha + \mu)]$$

ΔV_{do} does not depend on α .

At $\alpha = 0$ let $\mu = \mu_0$

$$\text{Inductive V/g Reg} = \frac{\cos 0 - \cos(0 + \mu_0)}{2}$$

$$= \frac{1 - \cos \mu_0}{2}$$

Effect of L_s on the performance of converter -

* Reduces avg output v_g of the converter

* It limits the range of α

$$\alpha_{max} = 180 - (\omega t_g + \mu_0)$$

t_g = device turn off time

Disadv

$$\text{PF} = \cos\left(\frac{\alpha + \mu}{2}\right)$$

due to L_s

Adv

* $g \uparrow$ = gives smoothness of waveform towards sine wave,


so $g \uparrow$ waveform approaches towards sine wave

\therefore with L_s , $g \uparrow$ THD \downarrow

hence \downarrow on AC side of converter.

Here the \uparrow in g value is dominating the \downarrow in PDF . i.e. the PF is slightly \uparrow (135)

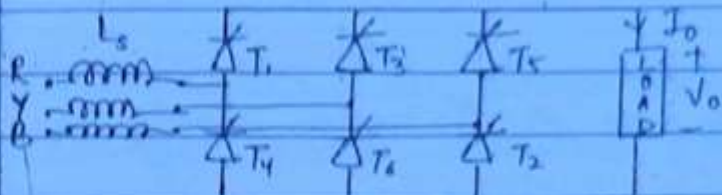
Effect of Source Inductance \rightarrow 6 pulse converter.



Without L_s

With L_s

Reduction in V_o due to L_s

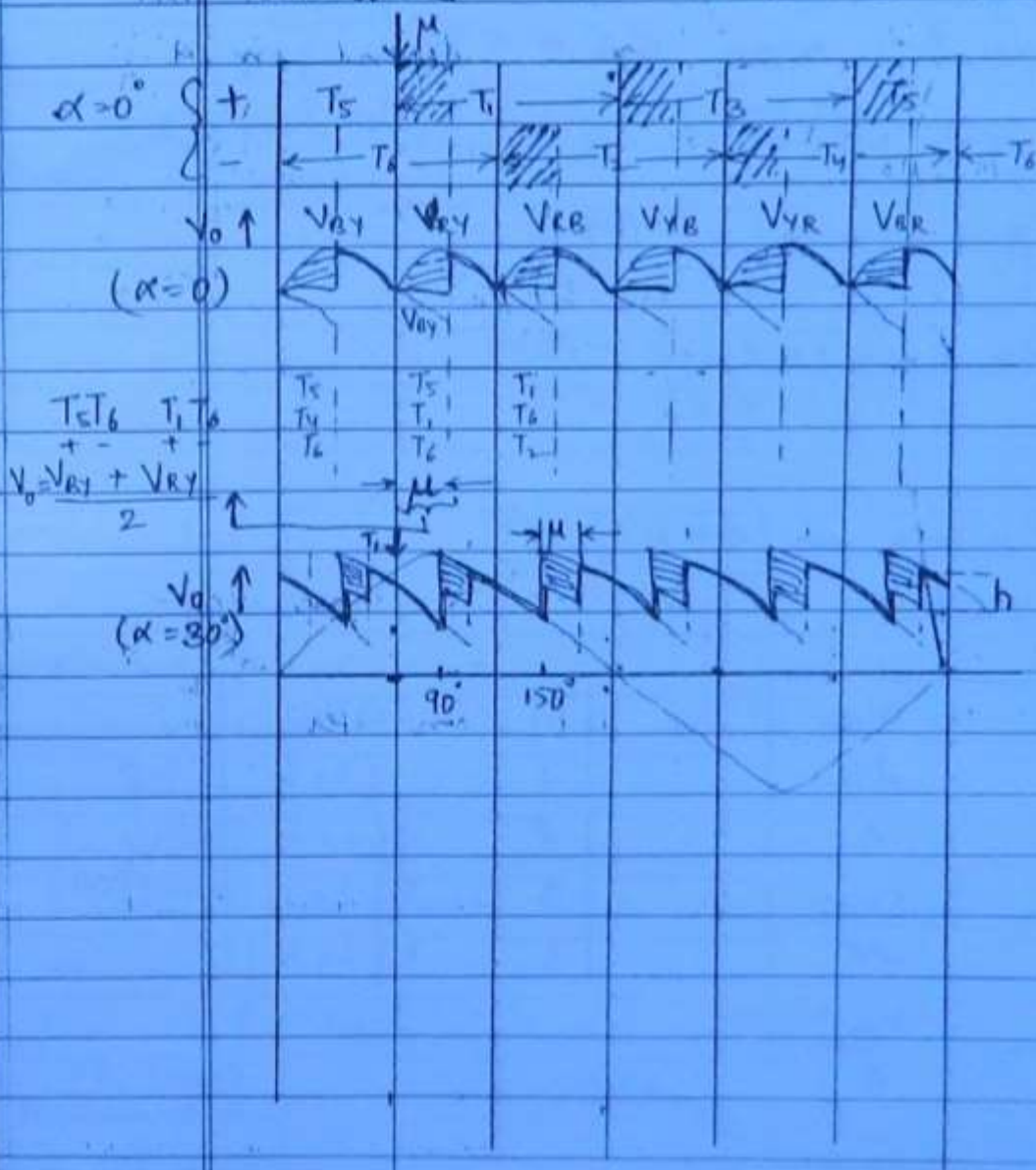

$\alpha \uparrow$ ripple \uparrow $h \uparrow$
 $\therefore \mu \downarrow$ to maintain same area
 [max ripple \rightarrow at 90°]
 [min μ \rightarrow at 90°]

$$\Delta V_{do} = \frac{V_{do}}{2} (\cos \alpha - \cos(\alpha + \mu)) = 6fL_s I_o \quad \text{--- (1)}$$

(136)

* We get minimum μ at $\alpha = 90^\circ$ cuz we get maximum ripple.

* We get maximum μ at $\alpha = 0^\circ$ cuz ripple is minimum

⇒ When other parameters are ~~at~~ ^{held} constant
 $\mu \downarrow$ ripple \uparrow when $0 \leq \alpha \leq 90^\circ$

* for $\alpha > 90^\circ$ $\alpha \uparrow \mu \uparrow$ --- ~~at~~ ^{held} constant


$$V_o = V_{do} \cos \alpha - 6fL_s I_o \quad \text{--- (2)}$$

$$V_o = \frac{V_{do}}{2} [\cos \alpha + \cos(\alpha + \mu)] \quad \text{--- (3)}$$

$$I_o = \frac{V_{ML}}{2\omega L_s} [\cos \alpha - \cos(\alpha + \mu)] \quad \text{--- (4)}$$

| | |
|---|-----------------------|
| m | V_{do} |
| 2 | $2V_M$ |
| | π |
| 3 | $3V_{ML}$ |
| | 2π |
| 6 | $\frac{3V_{ML}}{\pi}$ |

| | |
|---|-----------------|
| m | ΔV_{do} |
| 1 | $fL_s I_o$ |
| 2 | $4fL_s I_o$ |
| 3 | $8fL_s I_o$ |
| 6 | $6fL_s I_o$ |

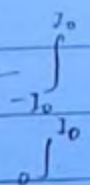

INVERTERS

137


Fixed DC \rightarrow Variable AC
(No f_o)

Classification of Inverters -

- \rightarrow Voltage Source Inverters (VSI) \rightarrow i waveform depends on load, vlg waveform is independent of load
- \rightarrow Current Source Inverters (CSI) \rightarrow app of VSI

VSI


a) 1ϕ Half Bridge Inverter -

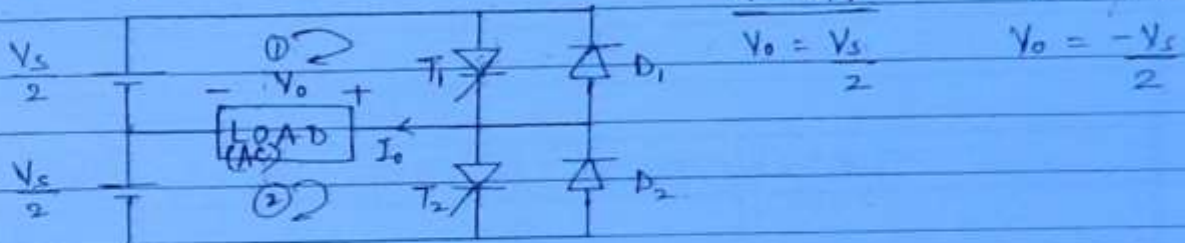

$I_g \uparrow$


$I_g \uparrow$

$V_o \uparrow$
(Any Load)

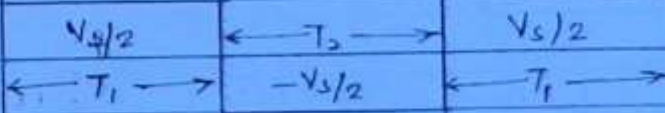

$I_o \uparrow$

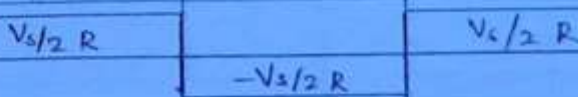(R Load)
Feedback diodes
will not conduct



\rightarrow Forced commutation is required

$$V_o = \sum_{n=1,3,5,\dots} \frac{4}{n\pi} \left(\frac{V_s}{2} \right) \sin n\omega t$$

138

$$\rightarrow V_o = \sum_{n=1,3,5,\dots} \frac{2V_s}{n\pi} \sin n\omega t$$

$$\rightarrow V_{o(n)} = \frac{2V_s \sin n\omega t}{n\pi}$$


$$(V_{o(n)})_{rms} = \frac{\sqrt{2} V_s}{n\pi}$$

$$(V_{o(1)})_{rms} = \frac{\sqrt{2} V_s}{\pi}$$

$$g = \frac{(V_{o(1)})_{rms}}{V_{o(n)}} = \frac{\frac{\sqrt{2} V_s}{\pi}}{\frac{V_s}{2}} = \frac{2\sqrt{2}}{\pi}$$

$$THD = 48.34\%$$

b) 1φ Full Bridge Inverter

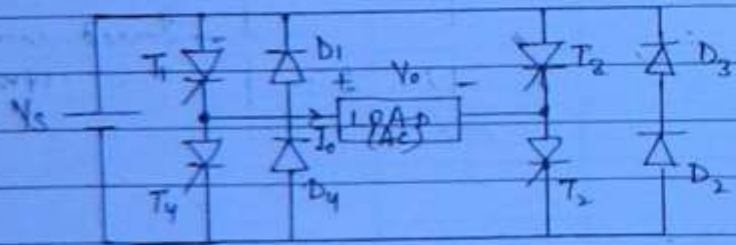

$T_1, T_2 \rightarrow ON$ $T_3, T_4 \rightarrow ON$
 $V_o = V_s$ $V_o = -V_s$

| | | | |
|--------------------------|-----------------------------------|-----------------------------------|-----------------------------------|
| $I_g, I_g \uparrow$ | | | |
| $I_g, I_g \uparrow$ | | | |
| Chng Load $V_o \uparrow$ | V_c | $\leftarrow T_3, T_4 \rightarrow$ | V_c |
| | $\leftarrow T_1, T_2 \rightarrow$ | $-V_c$ | $\leftarrow T_1, T_2 \rightarrow$ |

$$V_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s \sin n\omega t}{n\pi}$$

$$V_{on} = \frac{4V_s \sin n\omega t}{n\pi}$$


$$(V_{on})_{rms} = \frac{2\sqrt{2}}{n\pi} V_s$$

$$(V_{o1})_{rms} = \frac{2\sqrt{2}}{\pi} V_s$$

$$g = \frac{(V_{o1})_{rms}}{V_{on}} = \frac{2\sqrt{2} V_s}{\pi V_s} = \frac{2\sqrt{2}}{\pi}$$

THD = 48.34%

1 ϕ Half Bridge Inverter (Various Loads)

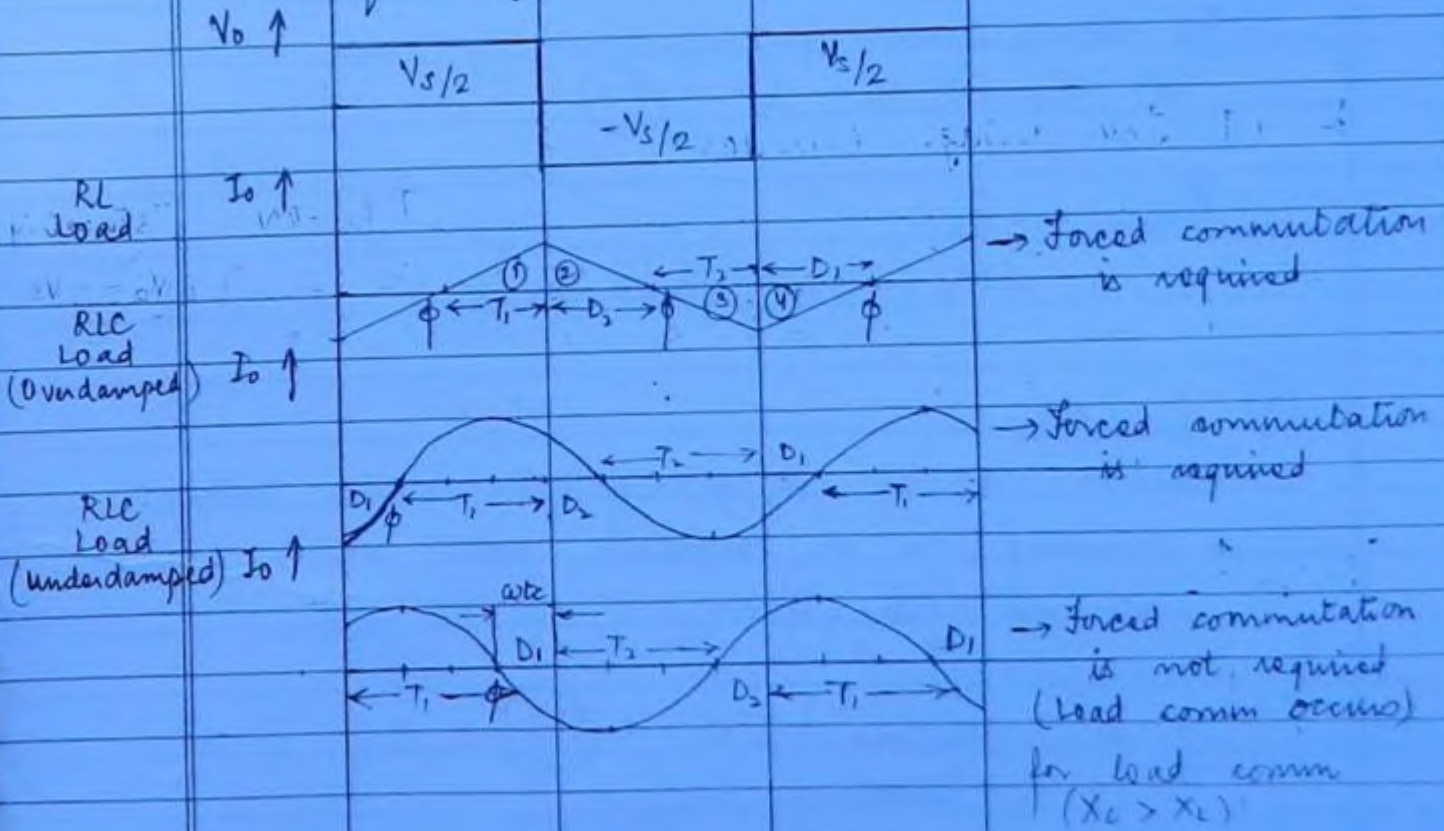

switching logic for 1-quadrant converter


- ① $T \rightarrow ON$ $P \oplus$
- ② $D \rightarrow ON$ $P \ominus$
- ③ $(T, D) \rightarrow ON$ $V_o \oplus$
- ④ $(T, D) \rightarrow ON$ $V_o \ominus$

classmate
Date _____
Page _____

I RL Load -

After reaching steady state
to lag V by $\phi = \tan^{-1} \frac{\omega L}{R}$

140
V

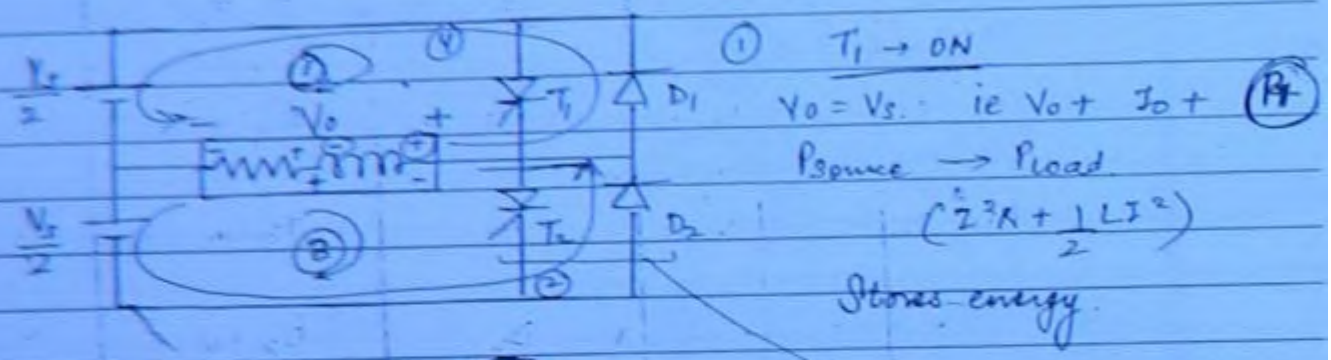

① $T_1 \rightarrow ON$
 $V_o = V_s$ i.e. $V_o + I_o R + \frac{1}{2} L I_o^2$ $(P+)$
 $P_{source} \rightarrow P_{load}$
 $(I^2 R + \frac{1}{2} L I^2)$
 Stores energy.

② $D_2 \rightarrow ON$ $(P-)$
 $\frac{1}{2} L I^2 \rightarrow source + I^2 R$
 T (Releasing Energy)

of antiparallel devices cannot be ON at the same time. eg. D_2 when ON provides RB to T_2 so T_2 is OFF

③ $T_2 \rightarrow ON$
 (D_2 releases reverse polarity thus T_2 starts conducting)
 $V_o = -V_s$ i.e. $V_o - I_o R - \frac{1}{2} L I_o^2$ $(P+)$

$P_{source} \rightarrow P_{load}$
 $(I^2 R + \frac{1}{2} L I^2)$ Stores Energy

④ $D_1 \rightarrow ON$
 Inductor reduces its polarity to release energy searching for a favourable path which is achieved from D_1

$\frac{1}{2} L I^2 \rightarrow source + I^2 R$ $(P-)$
 (Releasing Energy)

* Forced commutation is required for RL load.

Switching Logic Table

Page 141

| | | Device (ON) | | | |
|------------------|-------|------------------|------------|-------------|--|
| V_o | I_o | P | 1/2 Bridge | Full Bridge | |
| T_1^+ D_1 | + | T_1^+ T_2 | T_1 | T_1, T_2 | |
| T_1^+ D_1 | - | D_1^- D_2 | D_1 | D_1, D_2 | |
| T_2^- D_2 | - | T_1^+ T_2 | T_2 | T_3, T_4 | |
| T_2^- D_2 | + | D_1^- D_2 | D_2 | D_3, D_4 | |

for all leading loads it starts with T

for all lagging loads it starts with D

II RLC (Overdamped)

$$X_L > X_C$$

$$I_o \text{ lags } V_o \text{ by } \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

III RLC (Underdamped)

$$X_C > X_L$$

$$I_o \text{ lags } V_o \text{ by } \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$\text{or } I_o \text{ leads } V_o \text{ by } \phi = \tan^{-1} \left(\frac{X_C - X_L}{R} \right)$$

$$\cot \phi = \phi$$

$$\tan \phi = \frac{1}{\phi} \tan^{-1} \left(\frac{X_C - X_L}{R} \right)$$

→ If $t_c < t_d$ then load commutation fails
 (∴ forced commutation is required)

→ 4 for full bridge

$$V_{on} = \frac{2V_s}{n\pi} \sin n\omega t \quad (\text{Any Load})$$

(142)

Consider an RLC load

$$I_{on} = \frac{V_{on}}{Z_n}$$

$$Z_n = R + j(X_{Ln} - X_{Cn})$$

$$X_{Ln} = n\omega L \quad X_{Cn} = \frac{1}{n\omega C}$$

\downarrow
 n^{th} harmonic inductive impedance \downarrow $n\omega C$
 n^{th} harmonic capacitive impedance

$$Z_n = |Z_n| \angle \phi_n$$

$$|Z_n| = \sqrt{R^2 + (X_{Ln} - X_{Cn})^2}$$

$$\phi_n = \tan^{-1} \left(\frac{X_{Ln} - X_{Cn}}{R} \right)$$

\downarrow
 n^{th} harmonic impedance angle
 (or) displacement angle.

$$I_{on} = \frac{V_{on}}{Z_n} = \frac{V_{on}}{|Z_n| \angle \phi_n} = \frac{V_{on}}{|Z_n|} \angle -\phi_n$$

→ 4 for full bridge

$$I_{on} = \frac{2V_s}{n\pi |Z_n|} \sin(n\omega t - \phi_n) \quad \rightarrow \text{for RLC load.}$$

eg for pure inductive load

$$|Z_n| = n\omega L$$

$$\phi_n = 90^\circ$$


$$I_{on} = \frac{2V_s}{n\pi} \sin(n\omega t - 90^\circ) \Rightarrow I_{on} \propto \frac{1}{n}$$

If n^{th} harmonic is inv. prop. to n^2 shape


3φ VSI

143


a) 180°
MODE

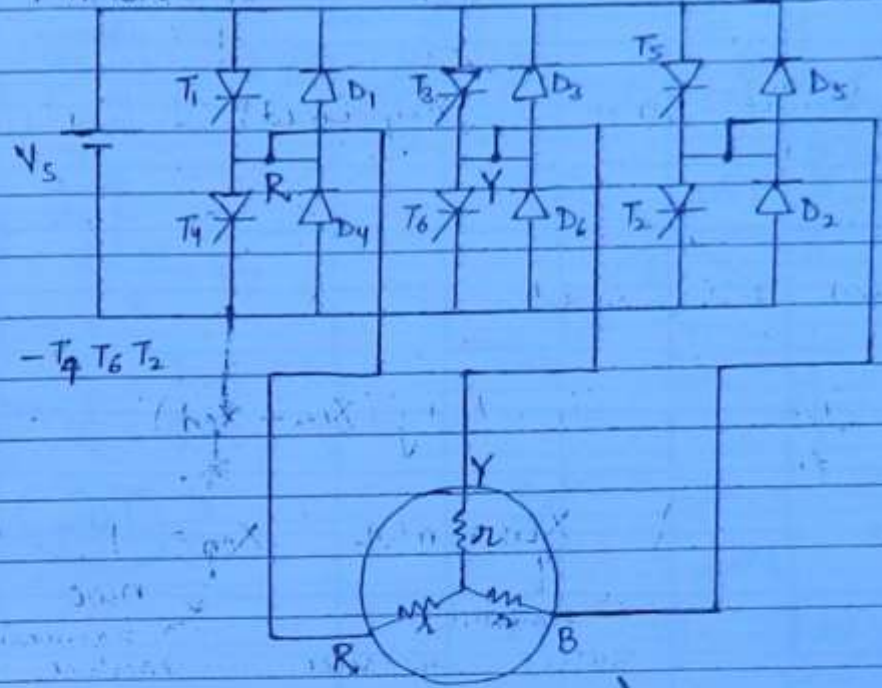



3φ Y connected R_L Load

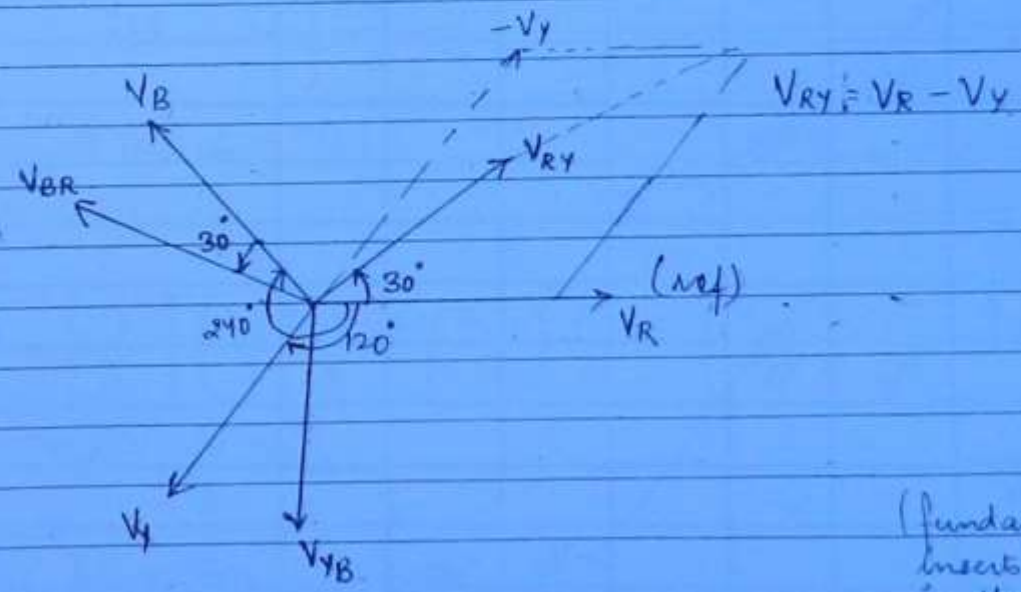

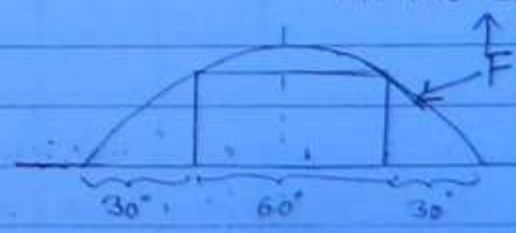
(fundamental
insert the pulse
in the centre)





Switching pattern is forming diagonally

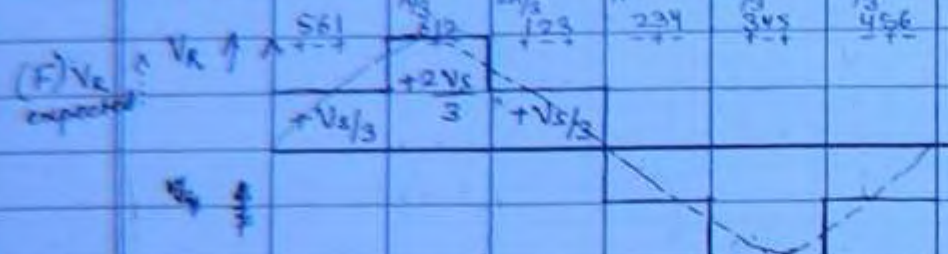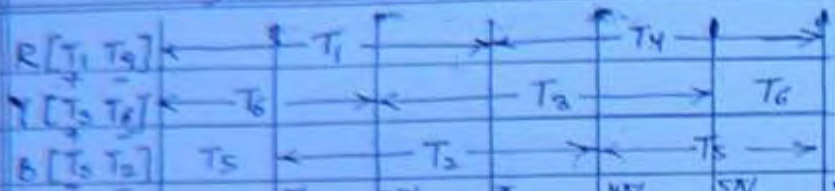

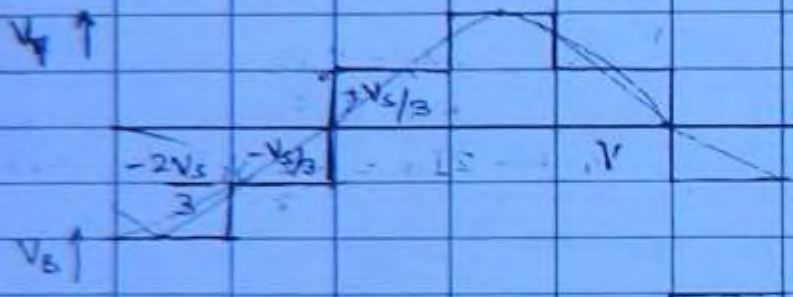561
+ - +
↓
this -ve share current of 2 +ve phases
so its double
ie Y & V of I
are double of R & B.
since its -ve
its polarity is -ve
so $5 \rightarrow B \rightarrow +\frac{V_s}{3}$
 $6 \rightarrow Y \rightarrow -\frac{2V_s}{3}$
 $1 \rightarrow R \rightarrow +\frac{V_s}{3}$




(144)

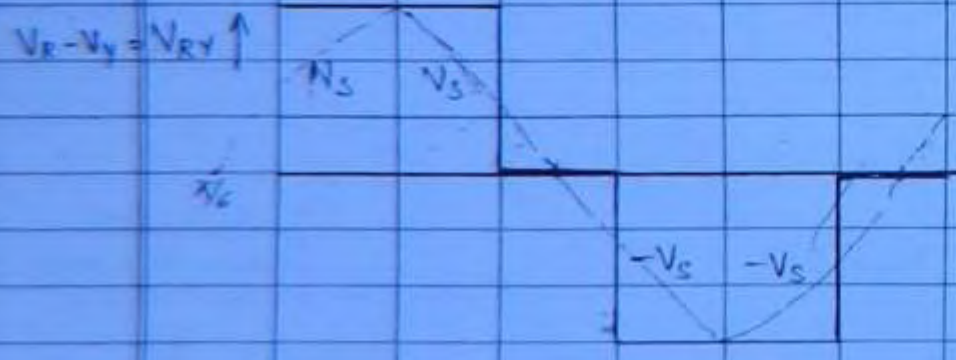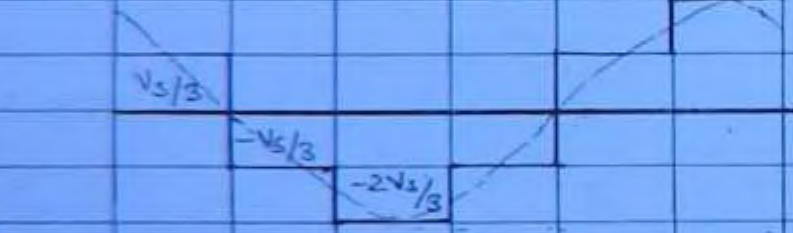


The waveforms are same for any load Δ connected or
A Δ / DC motor, induction motor etc
as V_s i.e. waveform is independent of load

$0 \text{ to } \frac{\pi}{3}$

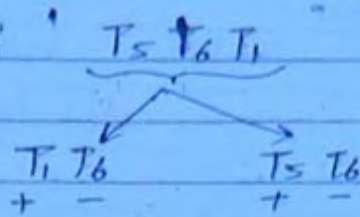

(145)

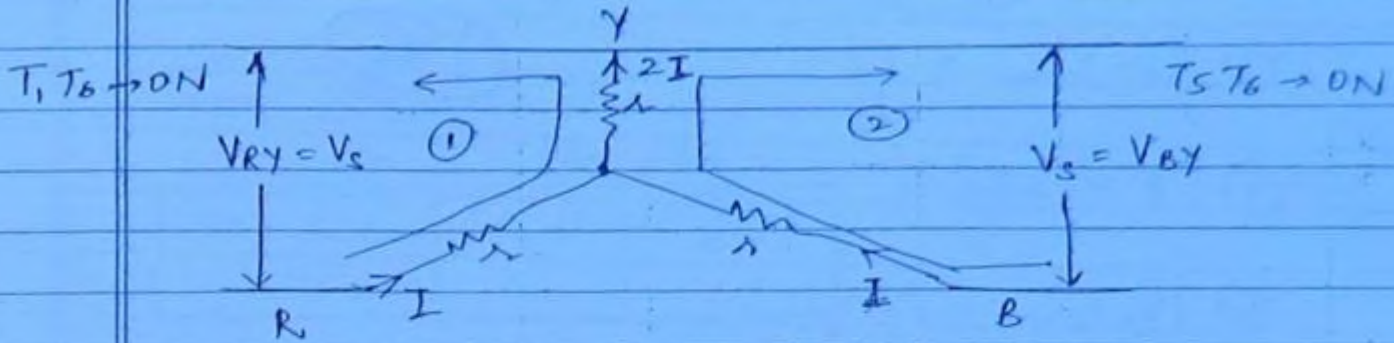

$$V_s = I\alpha + 2I\alpha$$

$$V_R = +I\alpha = +\frac{V_s}{3}$$

$$V_s = 3I\alpha$$

$$I\alpha = \frac{V_s}{3}$$

$$V_Y = -2I\alpha = -\frac{2}{3}V_s$$

$$V_B = +I\alpha = +\frac{V_s}{3}$$

$$V_{RY} = V_s \left(\frac{2\pi/3}{\pi} \right)^{1/2}$$

$$(V_L)_{rms} = V_s \sqrt{\frac{2}{3}}$$

$$V_R = \left\{ \frac{1}{\pi} \left[\left(\frac{V_s}{3} \right)^2 \frac{\pi}{3} + \left(\frac{2V_s}{3} \right)^2 \frac{\pi}{3} + \left(\frac{V_s}{3} \right)^2 \frac{\pi}{3} \right] \right\}$$

$$V_{ph} = \frac{\sqrt{2}}{3} V_s$$

$$I_L = I_{ph} = \frac{V_{ph}}{\alpha} = \frac{\sqrt{2}}{3\alpha} V_s$$

$$(I_T)_{rms} = \frac{I_{ph}}{\sqrt{2}} \quad V_L = \sqrt{3} V_{ph}$$

$$(1) \quad V_{ph} = \frac{\sqrt{2} V_s}{3}$$

$$(2) \quad I_{ph} = \frac{V_{ph}}{r}$$

$$(3) \quad (I_T)_{rms} = \frac{I_{ph}}{\sqrt{2}}$$

(46)

$$(4) \quad P = 3 I_{ph}^2 r = \frac{3 V_{ph}^2}{r}$$

$$(5) \quad (V_L)_{rms} = \sqrt{3} V_{ph}$$

fourier series form & phase of waveform.

V_R

$$V_R = \sum_{n=6k \pm 1}^{\infty} \frac{a^n V_s}{n\pi} \sin n\omega t$$

NOTE: Even & triple harmonics are absent

$$V_{Rn} = \frac{a^n V_s}{n\pi} \sin n\omega t$$

$$(V_{Rn})_{rms} = \frac{\sqrt{2} V_s}{n\pi}$$

$$(V_{R1})_{rms} = \frac{\sqrt{2} V_s}{\pi}$$

$$g = \frac{V_{R1}}{V_R} = \frac{\frac{\sqrt{2} V_s}{\pi}}{\frac{\sqrt{2} V_s}{3}} = \frac{3}{\pi}$$

$$g = \frac{3}{\pi}$$

$$THD = 31\%$$

Let us consider, RLC load
in each phase.

$$V_{rn} = \frac{2V_s}{n\pi} \sin n\omega t$$

(147)

$$I_{rn} = \frac{V_{rn}}{Z_n} = \frac{V_{rn}}{|Z_n|/\phi_n}$$

$$I_{rn} = \frac{2V_s}{n\pi|Z_n|} \sin(n\omega t - \phi_n)$$

eg. I.M. $|Z_n|$ per phase = $\sqrt{R^2 + (n\omega L)^2}$

$$\phi_n = \tan^{-1} \frac{X_L}{R}$$

for $n=1$ (F)

Diode conducts for $\phi = \tan^{-1} \frac{X_L}{R}$ for RL load

if $\phi = \tan^{-1} \frac{X_C - X_L}{R}$ for RLC load

————— x —————

Line vlg.

$$V_{RY} = \sum_{\substack{n=1,3,5 \\ n=6k\pi}}^{\infty} \frac{4V_s}{n\pi} \sin \frac{n\pi}{3} \sin n\left(\omega t + \frac{\pi}{6}\right)$$


•

$$g = \frac{3}{\pi} \quad \text{THD} = 31\%$$




Disadvantage of 180° mode VSI

There is a possibility of S.C across the supply when incoming thyristor starts conducting before the outgoing thyristor belonging to the same phase stops conducting

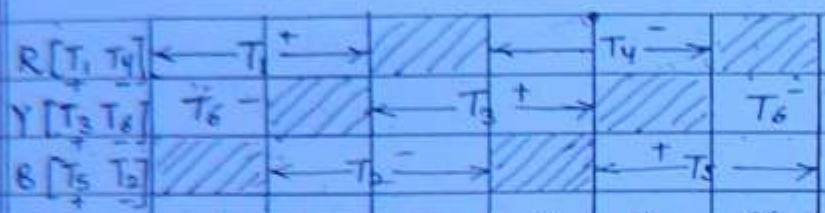
b) 120° mode → In 120° mode VSI we are allotting a conduction angle of 120° for each thyristor & the last 60° is allotted for commutation



(148)

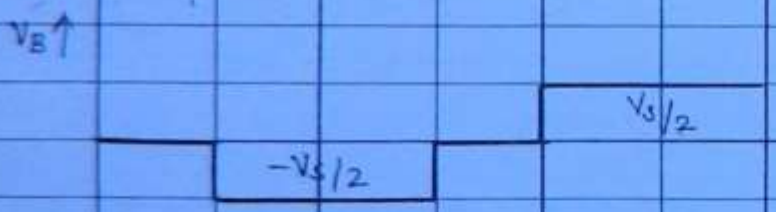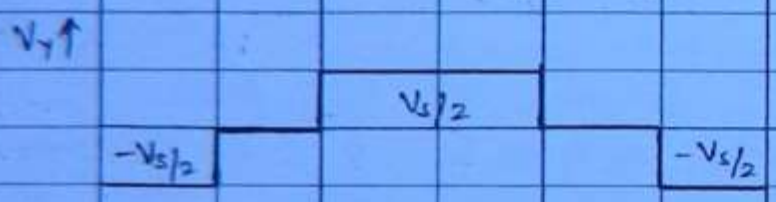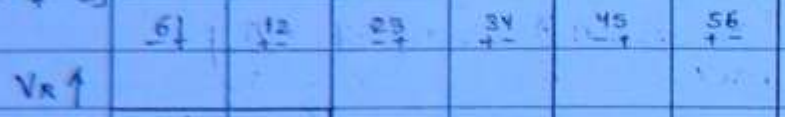

$V_{RY} \uparrow$
 $= V_R - V_Y$

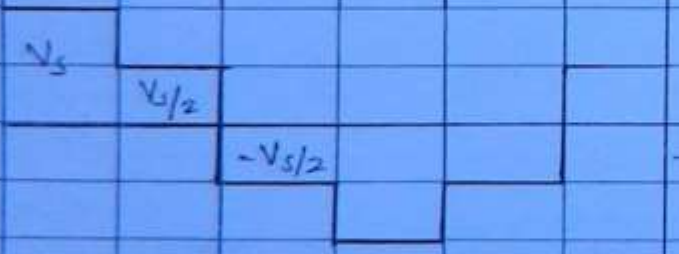

for Δ connection
 $V_{RY} \quad V_{YB} \quad V_{BR}$
→ displace this by 120° & 240° for V_{YB} & V_{BR}

$$(V_R)_{rms} = \frac{V_s}{2} \left(\frac{2\pi/3}{\pi} \right)^{1/2}$$

$$= \frac{V_s}{2\sqrt{3}}$$

$$(V_R)_{rms} = \frac{V_s}{\sqrt{6}} = V_{ph}$$

(149)

phase vlg

$$V_R = \sum_{\substack{n=6k+1 \\ n=1,3,5,\dots}}^{\infty} \frac{2V_s}{n\pi} \sin n\pi \sin n \left(\omega t + \frac{\pi}{6} \right)$$

NOTE: Even & triple harmonics are absent

$$g = \frac{3}{\pi} \quad THD = 31\%$$

line vlg

$$V_{RY} = \sum_{n=6k+1}^{\infty} \frac{3V_s}{n\pi} \sin n \left(\omega t + \frac{\pi}{3} \right)$$

NOTE: Even & triple harmonics are absent


$$g = \frac{3}{\pi} \quad THD = 31\%$$

For 120° & 180° mode


phase or line vlg

g & THD are same.

CSI

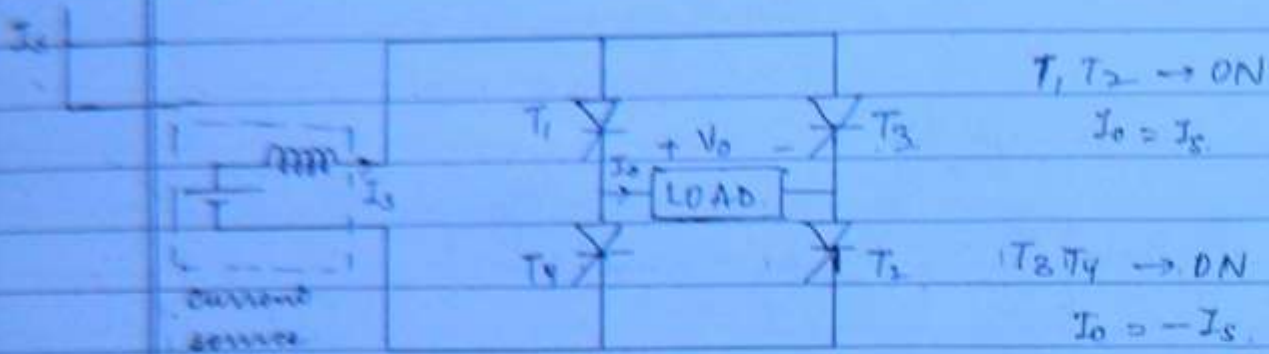

(150)

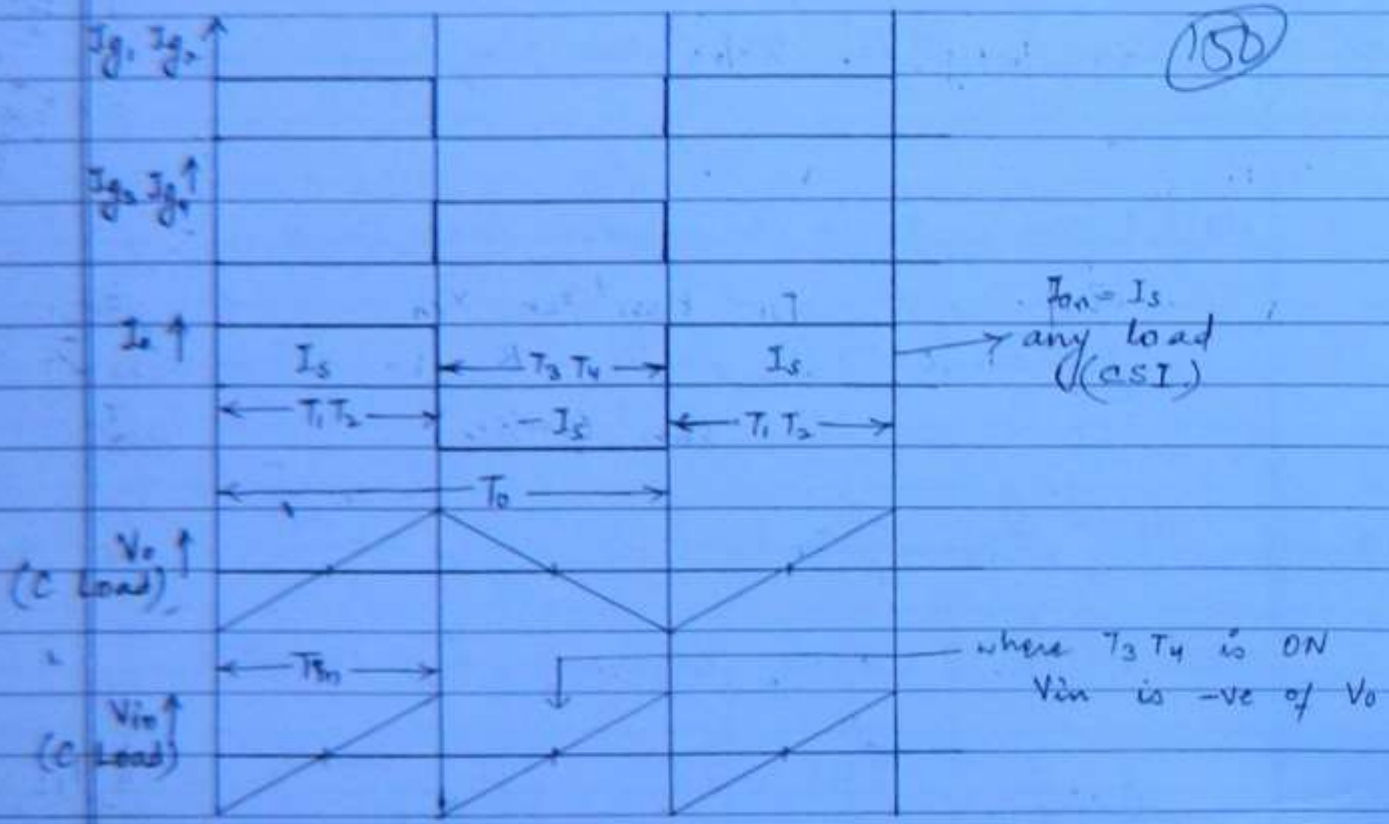

$$I_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4 I_s \sin n \omega t}{n \pi}$$

$$g = \frac{2\sqrt{2}}{\pi} \quad \text{THD} = 48.34\%$$

$$I_{o(n)} = \frac{4 I_s \sin n \omega t}{n \pi} \quad [\text{for any load}]$$

Let us consider an RLC load -

$$V_{on} = I_{on} \cdot Z_n \\ = I_{on} |Z_n| \angle \phi_n$$

(15)

$$V_{on} = \frac{4I_s}{n\pi} |Z_n| \sin(n\omega t + \phi_n)$$

$$Z_n = R + j(X_{Ln} - X_{Cn})$$

For 'C' load

$$|Z_n| = \frac{1}{n\omega C}$$


$$\phi_n = \tan^{-1} \frac{X_{Ln} - X_{Cn}}{R}$$

$$= \tan^{-1} \frac{0 - X_{Cn}}{0}$$

$$\phi_n = -90^\circ$$

$$V_{on} = \frac{4I_s}{n\pi} \left(\frac{1}{n\omega C} \right) \sin(n\omega t - 90^\circ)$$

$$V_{on} \propto \frac{1}{n^2}$$

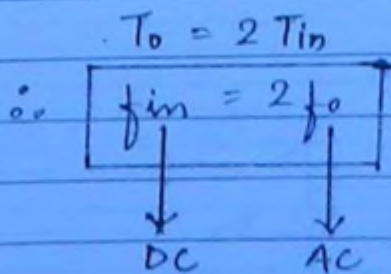


Advantages of CSI -

1. Feedback diodes are not required in CSI.
2. Commutation is simple.
3. For C loads there's a possibility of load commutation.
4. Inherently, there's a short-circuit protection for the source when the incoming thyristors are switched on before the outgoing thyristor becomes off due to the presence of high inductance.

Disadvantage of CSI -

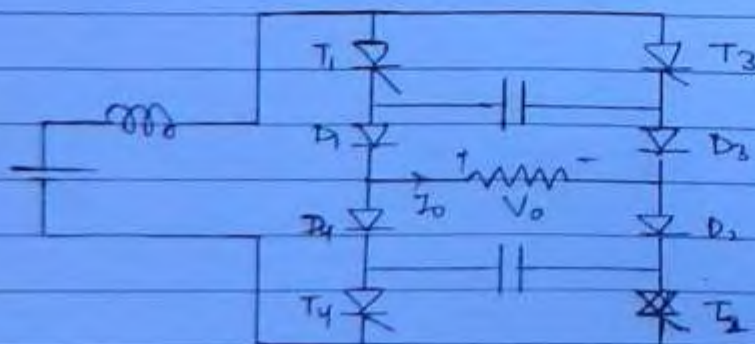1. The commutating element (along with the load) applies high reverse voltage across the power device used in CSI. ∴ the devices having low reverse voltage blocking capability such as GTO, IGBT & other transistors are not generally preferred in CSI. Here we prefer SCR because it has high reverse voltage blocking capability.
2. If commutating capacitor is directly connected across the load, then it will be continuously discharging through the load. To avoid it we must connect the diode as shown in figure.




CWB chapter 2.

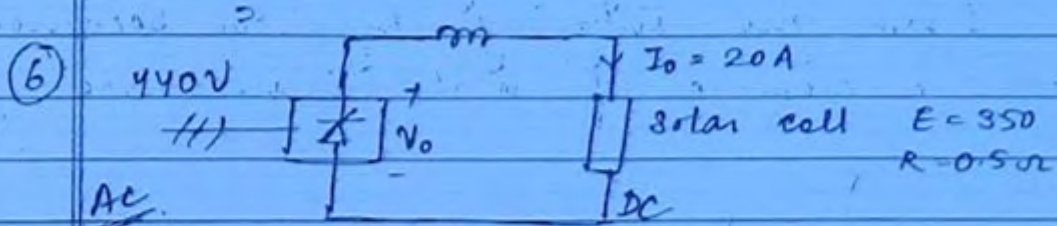(153)

⑤ $\alpha = 60$ FDF = $\cos \alpha = \cos 60 = 0.5$
(IDF)

PF = $\frac{P}{S} = \frac{P}{\sqrt{3} V_{ML} I_0}$
 $= \frac{3}{\pi} (\cos \alpha) = \frac{3}{\pi} \cdot \cos 60 = 0.476 (c)$



$P_{Ac} \leftarrow \frac{INV}{(\alpha > 90^\circ)} P_{Dc}$

$V_0 = -E + I_0 R$

$= -350 + 10 = -340$

$\frac{3 V_{ML} \cos \alpha}{\pi} = -E + I_0 R$

$\frac{3 \cdot 440 \sqrt{2} \cos \alpha}{\pi} = -340$

$\alpha = 125^\circ$

for $\alpha > 60^\circ$ $\omega t_c = \pi - \alpha = 180 - 125^\circ$
 $= 55^\circ (d)$

154

10


(155)

$$\alpha = 60^\circ, \text{ FDF} = \cos \alpha$$

$$= \cos 60 = 0.5$$

$$\text{PF} = g(\text{FDF}) = \frac{3 \times 0.5}{\pi}$$

$$= 0.478$$

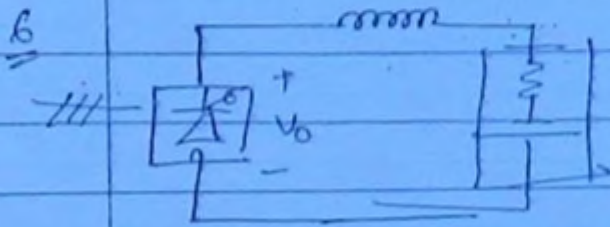

$P_{AC} \leftarrow P_{DC}$
inversion
 $\alpha > 90^\circ$

$$V_o = -E + I_o R$$

$$\cos \alpha \frac{3\sqrt{3} V_{mL}}{\pi \cos \alpha} = -350 + (20 \times 0.5)$$

$$\frac{3 \times 440 \sqrt{3}}{\cos \pi} \cos \alpha = -350 + 10$$

$$\cos \alpha \Rightarrow \alpha = 125^\circ$$

I $\alpha < 60^\circ, \omega t_c = \frac{4\pi}{3} - \alpha$

II $\alpha > 60^\circ, \omega t_c = \pi - \frac{\alpha}{3}$

$$= 180^\circ - \frac{125}{3}$$

$$= 55^\circ$$


VOLTAGE Control of Inverter

ISB


I - External control

It is like a change in v/g with change in frequency. i.e. change

a)

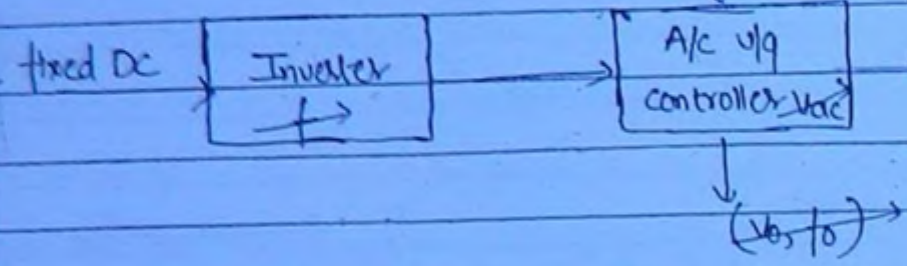

b)

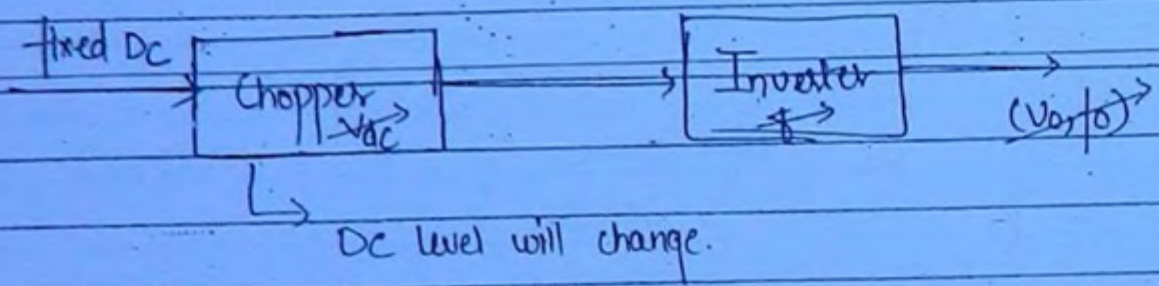

II

Internal v/q control using PWM technique:-

(157)


Advantages of PWM technique:-


1. We can get variable v/q within the inverter without increasing no. of stages.
2. We can eliminate some of the lower order harmonics (higher order harmonics can be easily filtered).

Types of PWM techniques:-

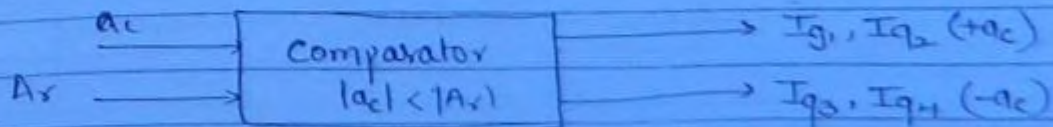1. Single PWM technique:-

Let us realise this modulation technique using full bridge inverter.



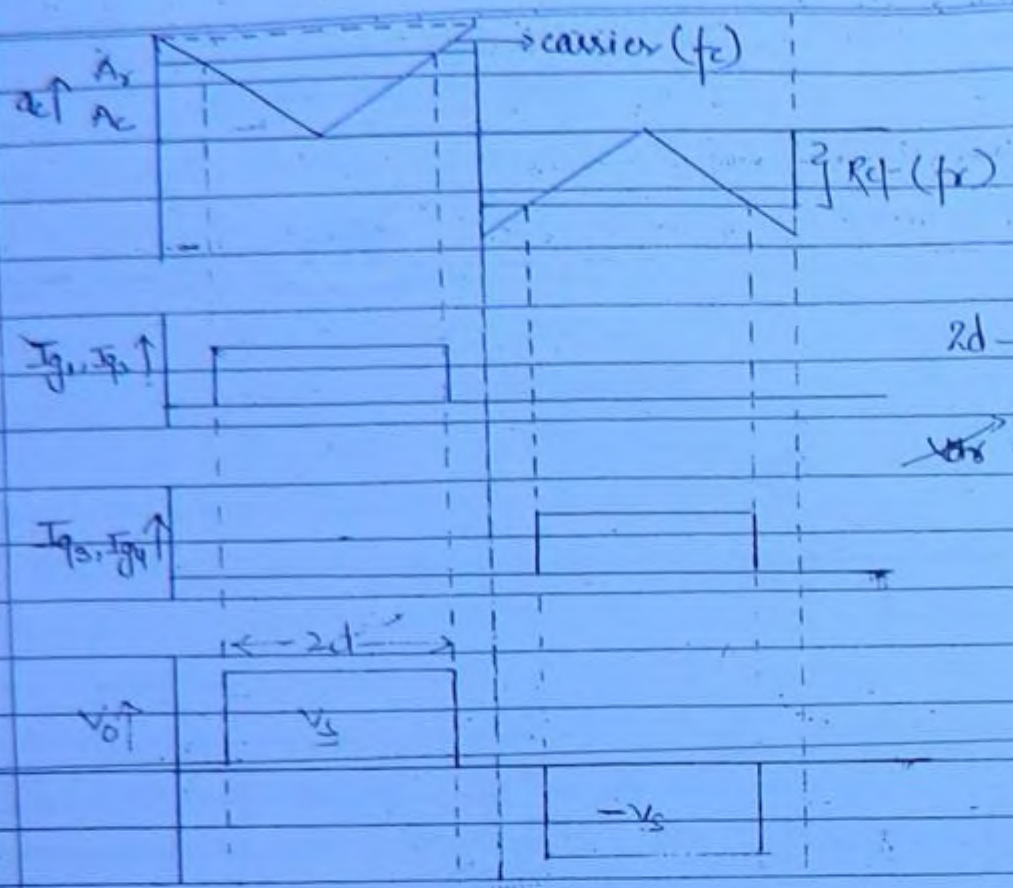

$2d \rightarrow$ Total pulse width

$$V_{rms} = V_s \left(\frac{2d}{\lambda} \right)^{1/2}$$

158

Power series for o/p vlg waveform:-

$$V_o = \sum_{n=1,3,5}^{\infty} \frac{4V_s}{n\pi} \sin n\omega t \cdot \frac{\sin n\pi}{2} \sin nd$$

$$V_{on} = \frac{4V_s}{n\pi} \frac{\sin n\pi}{2} \cdot \sin nd \cdot \sin n\omega t$$

$V_{on} = 0$ if $nd = \pi, 2\pi, 3\pi, \dots$

$$d = \frac{\pi}{n}, \frac{2\pi}{n}, \frac{3\pi}{n}, \dots$$

$2d \neq \frac{2\pi}{n}, \frac{4\pi}{n}, \frac{6\pi}{n} \rightarrow$ valid only if $2d \leq \pi$
 \rightarrow condition to eliminate nth harmonic

To eliminate 3rd harmonic

$$2d = \frac{2\pi}{3}, \frac{4\pi}{3}, \frac{6\pi}{3}, \dots$$

\therefore $\xrightarrow{\quad > \pi \quad}$ Since it is less than π

$$2d = \frac{2\pi}{3} = 120^\circ$$

(159)

To eliminate 5th harmonic

$$2d = \frac{2\pi}{5}, \frac{4\pi}{5}, \frac{6\pi}{5}, \dots$$

$\xrightarrow{\quad \text{both less than } \pi \quad}$

$$2d = 72^\circ, 144^\circ$$

$$V_{on} = \frac{4V_s}{n\pi} \left| \sin\left(\frac{n\pi}{2}\right) \right| \sin nd \cdot \sin n\omega t$$

\hookrightarrow for $n=1, 3, 5, \dots$ it is ± 1 , for rms value calculation it is always 1

$$(V_{on})_{\text{rms}} = \frac{4V_s}{n\pi} \frac{\sin nd}{\sqrt{2}} = \frac{2\sqrt{2}V_s \sin nd}{n\pi}$$

$$(V_{o1})_{\text{rms}} = \frac{2\sqrt{2}V_s \sin d}{\pi}$$

$$g = \frac{(V_{o1})_{\text{rms}}}{V_{or}} = \frac{2\sqrt{2}V_s \sin d}{\pi V_s \left(\frac{2d}{\pi}\right)^{1/2}}$$

$$g = \frac{2\sqrt{2} \cdot V_s \sin d}{\sqrt{2d} \cdot \pi}$$

$$\text{THD} = \left(\frac{1}{g^2} - 1 \right)^{1/2}$$

$$2d = \alpha = 120^\circ$$

$$V_s = 1V$$

$$(V_{o1})_{rms} = \frac{2\sqrt{2}V_s \sin d}{\pi}$$

$$= \frac{2\sqrt{2}}{\pi} \sin 60^\circ$$

$$= 0.78$$

166

2.

$$2d = 72^\circ \text{ or } 144^\circ$$

3.

$$2d = 144^\circ$$

$$(V_{o3})_{rms} = \frac{2\sqrt{2}V_s \sin 3d}{3\pi}$$

$$(V_{o1})_{max} = \frac{2\sqrt{2}V_s}{\pi}$$

$$\frac{(V_{o3})_{rms}}{(V_{o1})_{max}} = \frac{\sin 3d}{3}$$

$$= 19.6\%$$

5.

$$2d = 150^\circ$$

$$(V_{o1})_r = \frac{2\sqrt{2}V_s \sin d}{\pi}$$

$$g = \frac{2\sqrt{2} \cdot \sin d}{\sqrt{(2d) \cdot \pi}}$$


$$= 0.95$$

$$THD = 0.32$$

$$= 31.83\%$$

Multiple pulse PWM technique :-

(TGI)

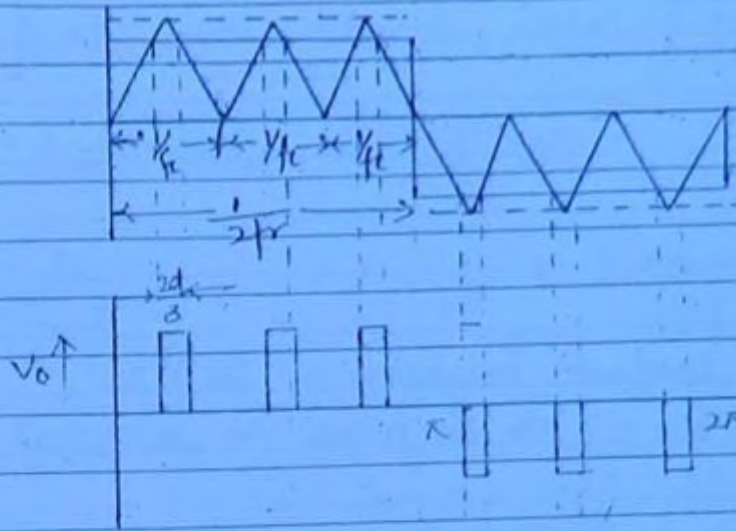

$$\frac{3}{t_c} = \frac{1}{2f_r}$$

$$3 = \frac{t_c}{2f_r}$$

$2d \rightarrow$ Total PW in each $\frac{1}{2}$ cycles

$$V_{or} = V_s \left(\frac{2d}{K} \right)^{1/2}$$


$$n = \frac{t_c}{2f_r}$$

$$\text{Pulse width (Pulse length)} = \frac{2d}{N} = \left(\frac{1 - V_r}{V_c} \right) \frac{\pi}{N}$$

\rightarrow Height of pulse is decided by supply, Only by changing supply, height of the pulse can be varied.

III

Sinusoidal PWM technique

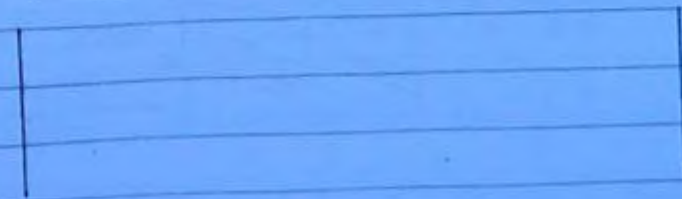

In sinusoidal PWM technique, the reference signal is taken as sine waveform.

Here we've two cases :-

I case:- Peak value of carrier coincident with zero of Ref. signal.

II case:- zero of carrier coincident with zero of reference.

Case-1 :- $N = \frac{f_c}{2f_r}$, Case-2 :- $N = \frac{f_c}{2f_r} - 1$

(162)

NOTE:-

Dominant harmonics = $2N \pm 1$.

$N \rightarrow$ No. of pulses in each half cycle


for $N=3$, Dominant harmonic = $6 \pm 1 = 5, 7$ -th.

for $N=9$, " " = $18 \pm 1 = 17, 19$ -th.

\rightarrow If domination is shown by lower order, it is difficult to filter them, we require big size filter to remove lower order harmonics.

\rightarrow If domination is shown by higher order, we can easily filter them.

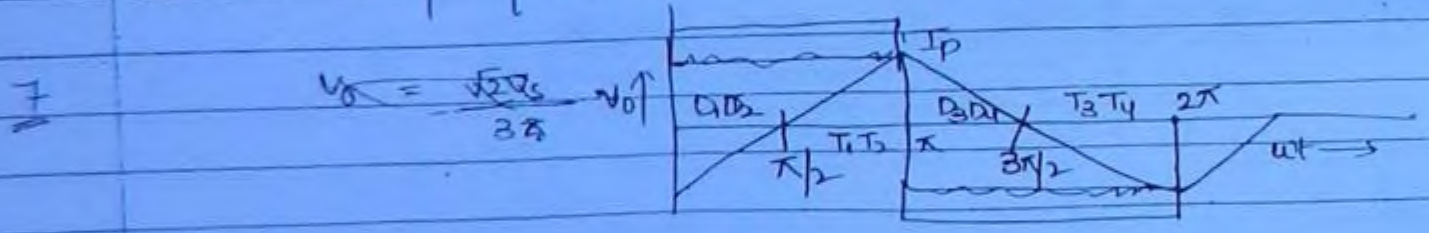In sinusoidal PWM tech, we \uparrow the no. of pulses in each half cycle & \uparrow the order of dominant harmonics so that they can be easily filtered.



$\frac{\pi}{2} \text{ to } \pi \rightarrow V_o = V_s = L \frac{di}{dt} = V_s$

$\omega di = \frac{\omega_s}{L} dt \quad \pi \Rightarrow \omega di = \frac{V_s}{L} d(\omega t)$
 $\int_0^{I_p} di = \frac{V_s}{\omega L} \int \frac{d(\omega t)}{\pi/2}$

$$I_p = \frac{200 \cancel{Z} \times \pi \cancel{Z}}{100 \cancel{Z} \times 0.1 \cancel{Z}}$$

$$= 10A$$

(163)

13

Since, Inductor $\rightarrow \phi = 90^\circ$

$$\omega t_c = \phi$$

$$t_c = \frac{\phi}{\omega} = \frac{90^\circ/180^\circ \times \pi}{2\pi f} = 5ms$$

12

3 ϕ VSI

\rightarrow pure inductive load, $|Z_n| = n\omega L$

$$V_{on} = \alpha V_{oi} \quad (\alpha_n < 1)$$

$$I_{on} = \frac{\alpha V_{oi}}{|Z_n|} = \frac{\alpha_n}{n} \frac{V_{oi}}{\omega L}$$

$$\frac{0.5 \times \pi}{2 \times f \times 50}$$

$$= \frac{\alpha_n}{n} I_{oi}$$

1.

$$R = 3\Omega, X_L = 12\Omega, X_C = ?$$

$$f = \frac{10^3}{0.02} = \frac{10^3 \times 10}{2} = 5000 \text{ Hz}$$

$$t_g = 12 \times 10^{-6} \text{ s}, SF = 2$$

$$t_c = 12 \times 2 \times 10^{-6}$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$12 \times 10^{-6} \times \frac{2 \times \pi \times 5000 \times 180^\circ}{\pi} = \tan^{-1} \left(\frac{12 - X_C}{3} \right)$$

$$X_L = X_C = 14.182$$

$$\frac{1}{2\pi f C} = X_C$$


$$C = 2.15 \mu\text{F}$$

CHOPPER


(164)

fixed DC \rightarrow variable DC

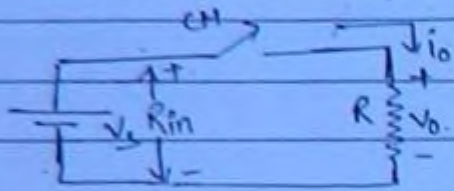1. Step-down Chopper :- ($V_o < V_s$) \rightarrow without filter



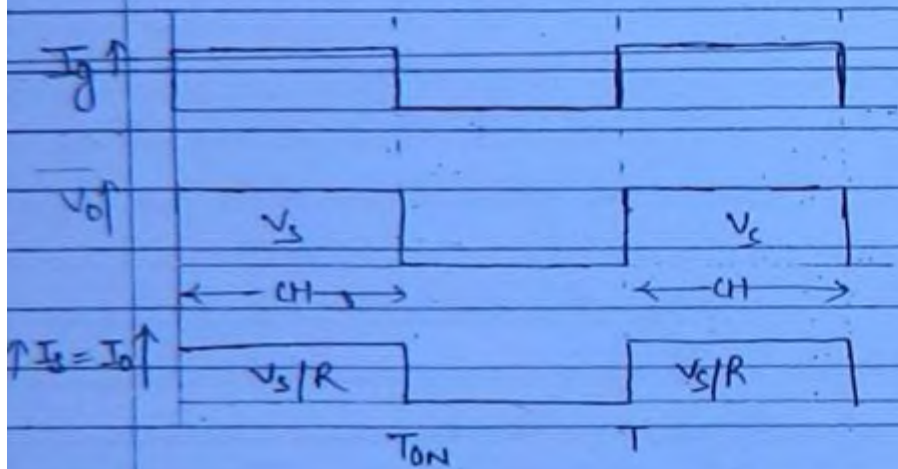Switch can be replaced by GTO or any power device for low power applⁿ but for high-power, it should be SCR with forced commutation.



$$\alpha = \frac{T_{ON}}{T}$$


= Duty cycle.

$$V_o = V_s \left(\frac{T_{ON}}{T} \right) = \alpha V_s$$

$$V_{rms} = \sqrt{\alpha} V_s$$

$$I_o = \frac{V_o}{R} = \frac{\alpha V_s}{R} = I_{s\alpha}$$
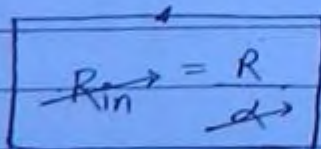
$$R_{in} = \frac{V_s}{I_s} = \frac{V_s}{\alpha \frac{V_s}{R}} = \frac{R}{\alpha}$$



$$V_o = \alpha V_s + \sum_{n=1}^{\infty} \frac{2V_s}{n\pi} \sin(n\omega t + \phi_n) \sin n\pi\alpha$$

where $\phi_n = \tan^{-1} \left[\frac{\cos n\alpha}{\sin n\alpha} \right]$

65

$$v_{on} = \frac{\alpha V_s + 2V_s \sin n\alpha}{n\pi} \cdot \sin(n\omega t + \phi_n)$$

$v_{on} = 0$ if $n\alpha = 1$


$\alpha = \frac{1}{n} \rightarrow$ condⁿ to eliminate n th harmonic

$$FF = \frac{V_{or}}{V_o} = \frac{\sqrt{\alpha} V_s}{\alpha V_s} = \frac{1}{\sqrt{\alpha}}$$

$$\downarrow VRF = \sqrt{FF^2 - 1} = \sqrt{\frac{1}{\alpha^2} - 1}$$

For High values of Duty cycle, harmonics are lesser.

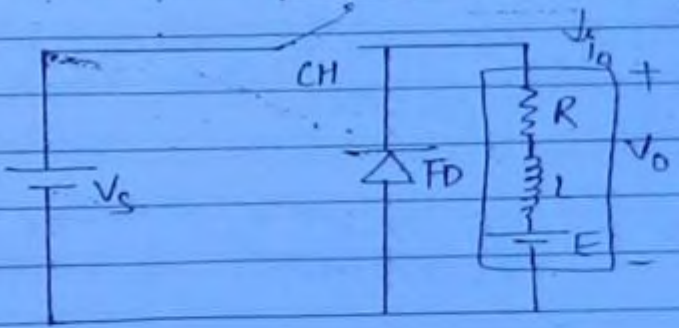
RLE load \rightarrow Cont. Conduction (waveform same for RL & RLE)



$$V_o = \alpha V_s$$

$$V_{or} = \sqrt{\alpha} V_s$$

$$I_o = \frac{\alpha V_s - E_b}{R}$$

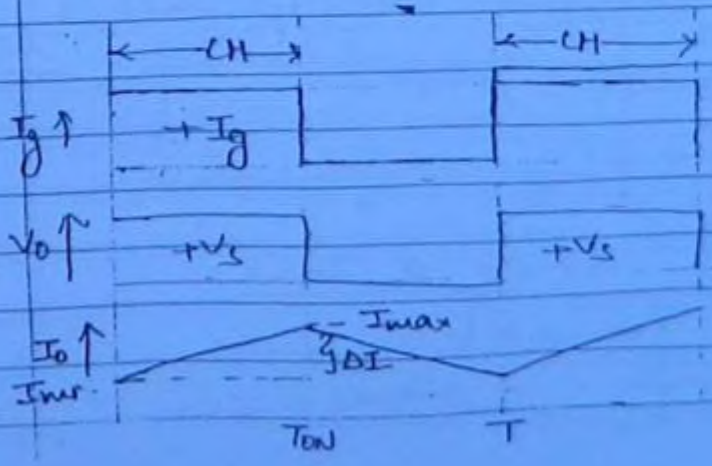

Avg. v/g will not depend on value of L but ripple will depend.

$$I_{\max} = \frac{V_s}{R_a} \left(\frac{1 - e^{-T_{on}/T_a}}{1 - e^{-T/T_a}} \right) - E_b / R_a \quad (1)$$

where $T_a = \frac{L_a}{R_a} \rightarrow$ w/c time const

(165) -

$$I_{\min} = \frac{V_s}{R_a} \left[\frac{e^{-T_{on}/T_a} - 1}{e^{T/T_a} - 1} \right] - E_b / R_a \quad (2)$$

$$\begin{aligned} \text{Ripple current} = \Delta I_o &= I_{\max} - I_{\min} \\ &= \frac{V_s}{R_a} \left\{ \frac{(e^{T_{on}/T_a} - 1)}{(e^{T/T_a} - 1)} \left(\frac{e^{T/T_a}}{e^{T_{on}/T_a}} \right) - \left(\frac{e^{-T_{on}/T_a} - 1}{e^{T/T_a} - 1} \right) \right\} \\ &= \frac{V_s}{R_a} \left\{ \left(\frac{e^{T/T_a} - 1}{e^{T_{on}/T_a} - 1} \right) \left(\frac{e^{-T_{on}/T_a} - 1}{e^{T/T_a} - 1} \right) \right\} \\ &= \frac{V_s}{R_a} \left[\frac{(1 - e^{-T_{on}/T_a})(1 - e^{-T_{off}/T_a})}{(1 - e^{-T/T_a})} \right] \end{aligned}$$

as α varies, ΔI_o varies.

$$T_{on} = \alpha T, \quad T_{off} = (1 - \alpha)T$$

$$\Delta I_o = \frac{V_s}{R_a} \left[\frac{(1 - e^{-\alpha T/T_a})(1 - e^{-(1-\alpha)T/T_a})}{(1 - e^{-T/T_a})} \right]$$

$$\frac{d \Delta I_o}{d \alpha} = 0 \Rightarrow \frac{V_s}{R_a} \left[\frac{(1 - e^{-\alpha T/T_a})^{-\alpha T/T_a} \times \frac{T}{T_a} + (1 - e^{-(1-\alpha)T/T_a})^{\alpha T/T_a} \times \frac{T}{T_a}}{(1 - e^{-T/T_a})^2} \right]$$

$$= \frac{(1 - e^{-\alpha T/T_a})^{-\alpha T/T_a} - (1 - e^{-(1-\alpha)T/T_a})^{\alpha T/T_a}}{(1 - e^{-T/T_a})^2} = 0$$

$$= e^{-(1-\alpha)T/T_a} - e^{-\alpha T/T_a}$$

$$\frac{(1-\alpha)T}{T_a} = \frac{\alpha T}{T_a}$$

$$\alpha = 1 - \alpha \Rightarrow 2\alpha = 1$$

$$\boxed{\alpha = 0.5} \quad \Delta I_{o \max}$$

$$\Delta I_o|_{\max} = \frac{V_s}{R_a} \frac{(1 - e^{-0.5T/T_a})^2}{(1 - e^{-T/T_a})}$$

$$= \frac{V_s}{R_a} \tanh\left(\frac{T}{4T_a}\right) \quad (167)$$

$$\Delta I_o|_{\max} \approx \frac{V_s \times T}{R_a \times 4T_a} = \frac{V_s}{R_a} \times \frac{1}{f \times 4 \times \frac{L_a}{R_a}}$$

$\Delta I_o|_{\max} \approx \frac{V_s}{4fL_a}$

→ at $\alpha = 0.5$

from this Eqⁿ ↓ Ripple current $\propto \frac{1}{\uparrow f L_a \uparrow}$

for $L_a = \infty \Rightarrow \Delta I_o|_{\max} = 0$

i.e. for Highly inductive load → Constt current.
 for High frequency → Ripple will ↓ ∴ Chopper is being operated at very high frequency i.e. in range of kHz.


⇒ At very high switching frequency we can reduce the ripple in the output without ↑ size of filter. SMPS operates on the same chopper principle.

Reasons for Discont. conduction



| Rectifier | Chopper |
|----------------------------|-------------------------|
| ↑ α → firing angle. | ↓ α → Duty cycle |
| ↓ L | ↓ L |
| ↓ I_o | ↓ I_o |

RLE load \rightarrow Discontinuous conduction

(168)

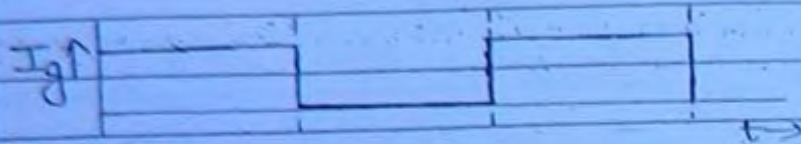

$T_{on} \rightarrow$ Extinction Time

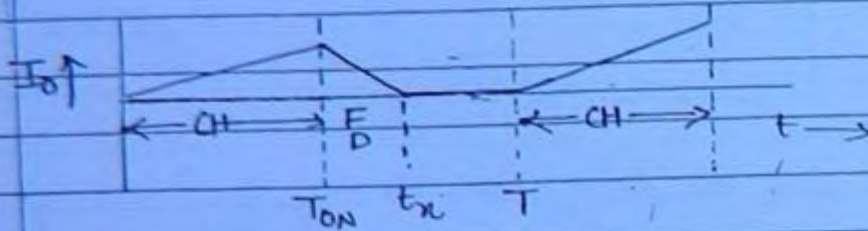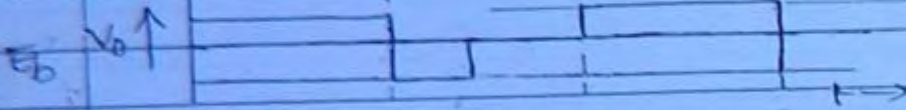


$$V_o = V_s \left(\frac{T_{on}}{T} \right) + E_b \left(\frac{T - t_x}{T} \right)$$

$$I_o = \alpha V_s + E_b \left(1 - \frac{t_x}{T} \right)$$

Duty cycle limit for continuous conduction :-

Let α' be the duty cycle at the boundary b/w continuous & discontinuous conduction.

at $t = T$, $I_{min} = 0$

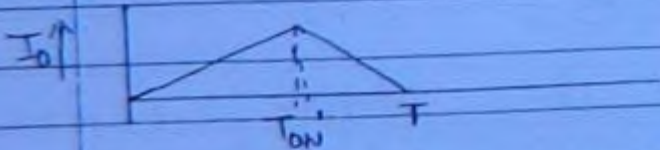

$$I_{min} = \frac{V_s}{R} \left(\frac{e^{T_{on}/\tau_a} - 1}{e^{T/\tau_a} - 1} \right) - \frac{E_b}{R_a} = 0$$

$$\frac{e^{T_{on}/\tau_a} - 1}{e^{T/\tau_a} - 1} = \frac{E_b}{V_s}$$

at boundary, $e^{T_{on}/\tau_a} - 1 = \frac{E_b}{V_s} (e^{T/\tau_a} - 1)$

$$e^{T_{ON}'/T_a} = \frac{E_b}{V_s} (e^{T/T_a} - 1) + 1 \quad (169)$$

$$T_{ON}' = T_a \ln \left[\frac{E_b}{V_s} (e^{T/T_a} - 1) + 1 \right]$$


$$\alpha' = \frac{T_{ON}'}{T} = \frac{T_a}{T} \ln \left[\frac{E_b}{V_s} (e^{T/T_a} - 1) + 1 \right]$$

$\alpha < \alpha' \longrightarrow$ Discontinuous conduction.

$\alpha > \alpha' \longrightarrow$ Continuous conduction.

Step-down chopper \longrightarrow with filter
Buck Regulator

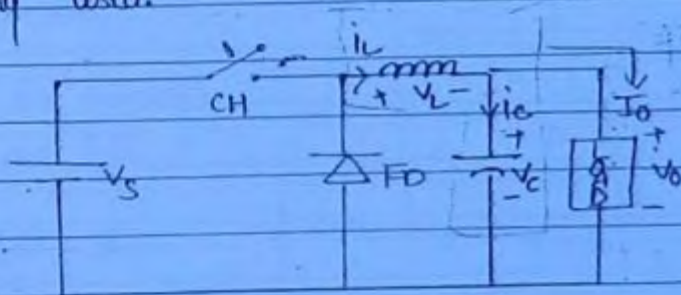In the step-down chopper, we could \downarrow the ripple in current by \uparrow L or f but ripple in v_L was unaffected \therefore to reduce ripple in v_L , step-down chopper with filter is being used.




$I_o \left\{ \begin{array}{l} (I_L)_{avg} \\ \Delta I_L \end{array} \right.$
Assume high value of capacitor across the load

which maintains almost const v_L across the load.

$$(I_L)_{avg} \rightarrow \text{DC component} = I_o$$

$$\Delta I_L = \Delta I_C$$

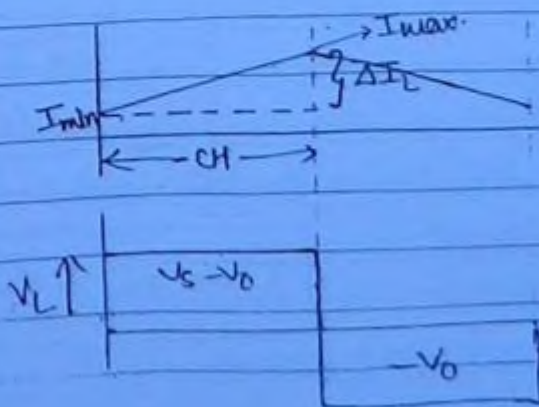

$$0 < t < T_{ON}$$

$$CH \rightarrow ON$$

$$-V_s + V_L + V_o = 0$$

$$V_L = V_s - V_o$$

$$L \frac{dI_L}{dt} = V_s - V_o$$

$$dI_L = \frac{V_s - V_o}{L} dt$$

$$\int_{I_{min}}^{I_{max}} dI_L = \frac{V_s - V_o}{L} \int_0^{T_{ON}} dt$$

$$(I_{max} - I_{min}) = \frac{(V_s - V_o) T_{ON}}{L}$$

$$\Delta I_L = \left(\frac{V_s - V_o}{L} \right) T_{ON}$$

$$= \frac{V_s (1 - \alpha) T_{ON}}{L}$$

$$\Delta I_L = \frac{V_s (1 - \alpha) \alpha}{fL}$$

$$\Delta I_L \propto \frac{1}{fL}$$

$$\frac{d\Delta I_L}{d\alpha} = \frac{T_s}{fL} (1 - 2\alpha) = 0$$

$$\alpha = 0.5 \text{ for } \Delta I_L \Big|_{max}$$

$$\Delta I_{L,max} \Big|_{\alpha=0.5} = \frac{V_s}{4fL}$$

$$I_s = I_{CH}$$

$$II \quad T_{ON} < t < T$$

$$CH \rightarrow \text{off}, \quad FD \rightarrow ON$$

$$+V_L + V_o = 0$$

$$\therefore V_L = -V_o$$

$$(V_L)_{avg} = 0$$

Ar. of (+ve) spike = Ar. of (-ve) spike

$$(V_s - V_o) T_{ON} = V_o T_{OFF}$$

$$V_o (T_{OFF} + T_{ON}) = V_s T_{ON}$$

$$V_o T = V_s T_{ON}$$

$$V_o = \frac{V_s T_{ON}}{T}$$

$$V_o = \alpha V_s$$

Assuming No loss in chopper
I/p power = o/p power

$$V_o I_o = V_s I_s$$

$$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \alpha$$

CHOPPER works as DC transformer.


$$I_s = \alpha I_o$$

$$I_o = \frac{I_s}{\alpha}$$

$$(I_{FD})_{avg} = (1 - \alpha) I_o$$

Ripple in capacitor voltage ($\Delta V_c = \Delta V_o$)

(17)

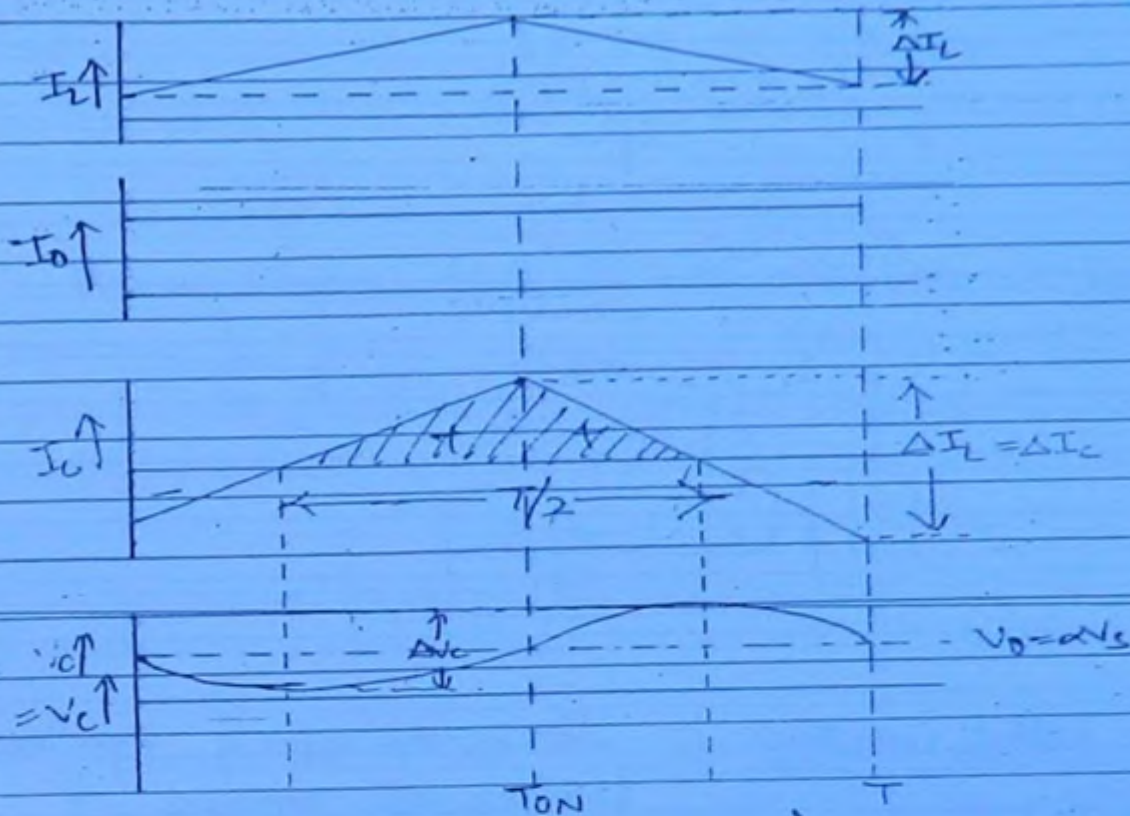

$$\Delta Q = C \Delta V_c \Rightarrow \Delta Q = \frac{\Delta I_L \times \frac{T}{2} \times \frac{T}{2}}{2} = \frac{\Delta I_L T^2}{8}$$

$$\Delta V_c = \frac{\Delta I_L}{8fC}$$

$$\Delta V_c \propto \frac{1}{fC}$$

$$\Delta V_c = \frac{\alpha(1-\alpha)V_s}{8f^2LC}$$

$$\Delta V_c|_{\max} \text{ at } \alpha=0.5 = \frac{V_s}{32f^2LC}$$

Critical Inductance :- It is the value of inductance at which the inductor current waveform is just continuous.

Symbol $\rightarrow L_c$

At the boundary b/w continuous & discontinuous conduction of I_c

$$I_0 = \frac{\Delta I_c}{2} = (I_c)_{\text{avg}}$$

(172)

$$I_0 = \frac{\alpha(1-\alpha)V_s}{2fL_c}$$

$$L_c = \frac{1}{2fI_0} \alpha(1-\alpha)V_s$$

$$L_c = \frac{1}{2f} \frac{\alpha V_s / R}{\alpha(1-\alpha)V_s} = \dots$$

$$L_c = \frac{(1-\alpha)R}{2f}$$

Critical Capacitance :- It is the value of capacitance at the boundary b/w continuous & discontinuous conduction for the capacitor v/q waveform.

At the boundary :- $V_0 = \frac{\Delta V_c}{2} = (V_c)_{\text{avg}}$

$$V_0 = \frac{\alpha(1-\alpha)V_s \times 1}{8f^2 L_c C_c} \times 2$$

$$\alpha V_s = \frac{\alpha(1-\alpha)V_s \times 1}{8f^2 L_c C_c} \times 2$$

$$C_c = \frac{(1-\alpha)}{16f^2 L_c}$$

$\alpha = 0.5, \Delta I_c = 1.6, I_0 = 5A$


$$(I_{L})_{max} = (I_{L})_{max}$$

(173)

$$(I_{L})_{max} = I_{0} + \frac{\Delta I_{L}}{2}$$

$$= \frac{1.6}{2} + 5 = 5.8 \text{ Amp}$$

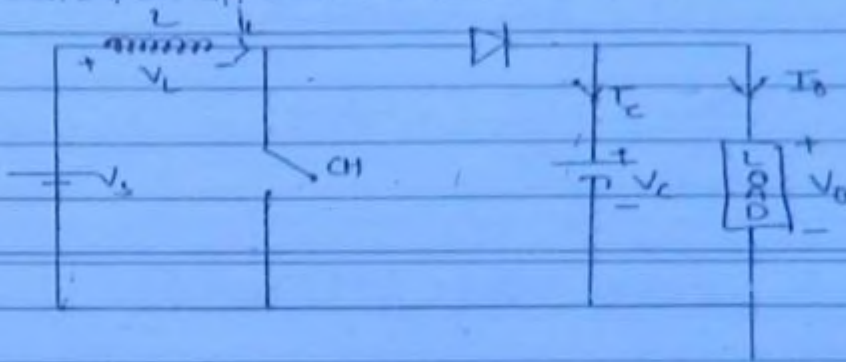3. Step-up chopper ($V_o > V_s$) (with filter) → Boost Regulator



(I) $0 \leq t \leq T_{ON} \rightarrow I_c = -I_0$

CH → ON, D → OFF


$$V_L = V_s$$

$$L \frac{dI_L}{dt} = V_s$$

$$\int_{I_{min}}^{I_{max}} dt = \frac{V_s}{L} \int_0^{T_{ON}} dt$$

$$\Delta I_L = \frac{V_s}{L} T_{ON}$$


$$\Delta I_L = \frac{\alpha V_s}{fL}$$

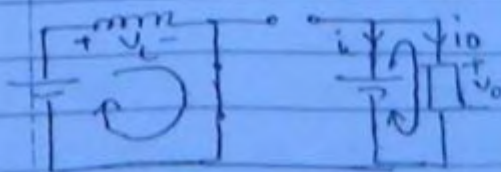

$$I_c = -I_0$$

II $T_{ON} \leq t \leq T$

CH → OFF, D → ON

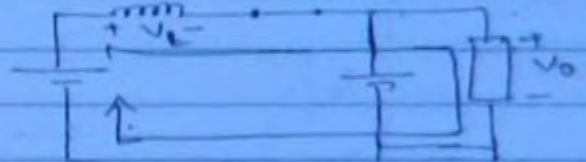


$$V_s = V_L + V_o$$

$$V_L = V_s - V_o = -(V_o - V_s)$$

Since it is step-up chopper,
 $V_o > V_s \Rightarrow V_L \Rightarrow$ +ve
 L is releasing energy.

$$I_L = I_c + I_0$$

$$I_c = I_L - I_0$$

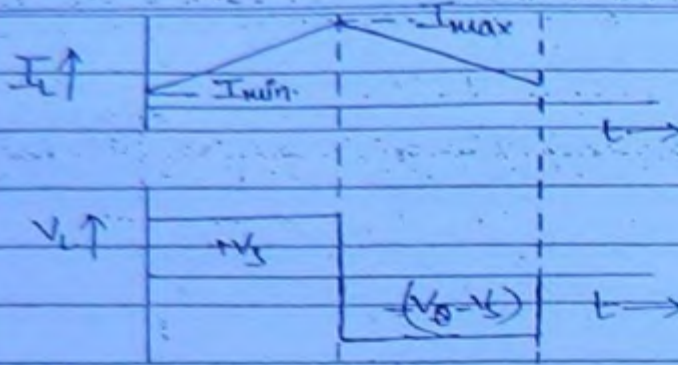

(174)

$$(V_L)_{avg} = 0$$

$$V_s T_{ON} - (V_o - V_s) T_{OFF} = 0$$

$$V_s (T_{ON} + T_{OFF}) = T_{OFF} V_o$$


$$V_s T = V_o T_{OFF}$$

$$V_s T = (1 - \alpha) V_o T_{OFF}$$


$$V_o = \frac{V_s}{1 - \alpha}$$

$$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \frac{1}{1 - \alpha}$$

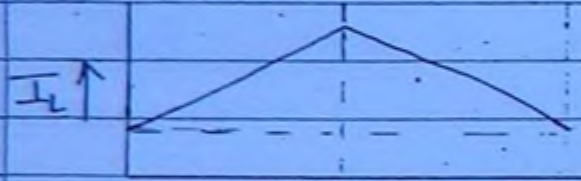
Ripple in capacitor voltage :- $(\Delta V_c = \Delta V_o)$




$$\Delta V_c = \frac{\Delta Q}{C}$$

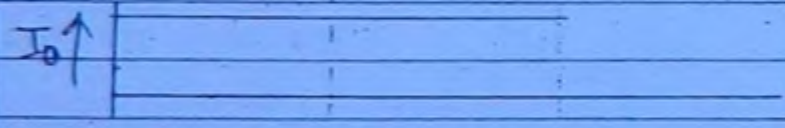

$$\Delta V_c = \frac{I_o T_{ON}}{C}$$

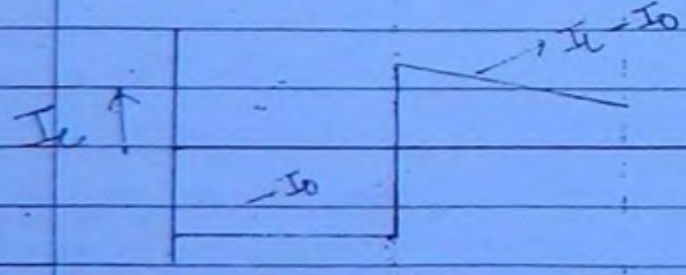

$$\Delta V_c = \frac{\alpha I_o}{f_c}$$

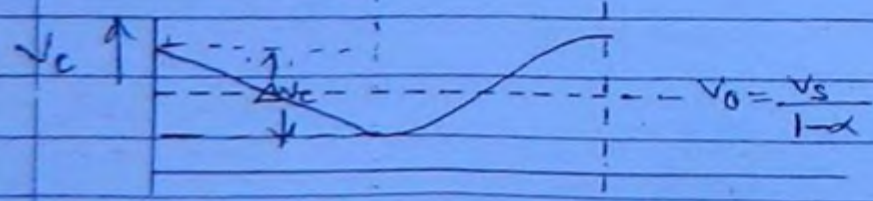

Critical Inductance (L_c):-

At the boundary condⁿ of I_2

$$I_0 = \frac{\Delta I_L}{2} = (I_L)_{av}$$

(125)

$$\frac{V_s}{R(1-\alpha)} = \frac{\alpha V_s}{2fL_c}$$

$$L_c = \frac{R(1-\alpha)\alpha}{2f}$$

Critical Capacitance (C_c):-


At the boundary condⁿ of V_c waveform:

$$V_0 = \frac{\Delta V_c}{2} = (V_c)_{av}$$

$$\frac{I_0 R}{2fC_c} = \alpha I_0$$

$$C_c = \frac{\alpha}{2fR}$$

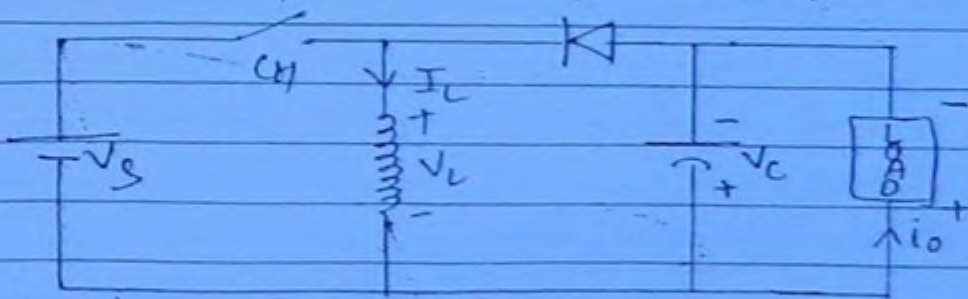Buck-Boost Regulator (Step up / Step down Chopper)




$\alpha > 0.5 \rightarrow$ step up
 $\alpha < 0.5 \rightarrow$ step down

Mode - I

$$0 \leq t < T_{ON}$$

Same as step-up chopper

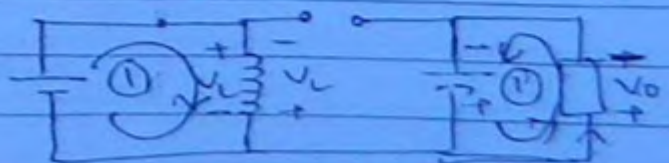

Mode-2 CH → OFF, D → ON $T_{ON} \ll T \ll T$

(196)

$$V_s = V_L$$


$$L \frac{di}{dt} = V_s$$

$$\int_{I_{min}}^{I_{max}} di = \frac{V_s}{L} \int_0^{T_{ON}} dt$$

$$\Delta I_L = \frac{V_s T_{ON}}{L}$$

$$\Delta I_L = \frac{\alpha V_s}{fL}$$

$$I_c = -I_o$$

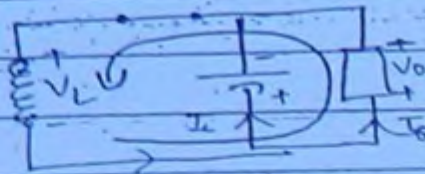


$$+V_L + V_o = 0$$

$$\therefore V_L = -V_o$$

$$I_L = I_c + I_o$$

$$I_c = I_L - I_o$$

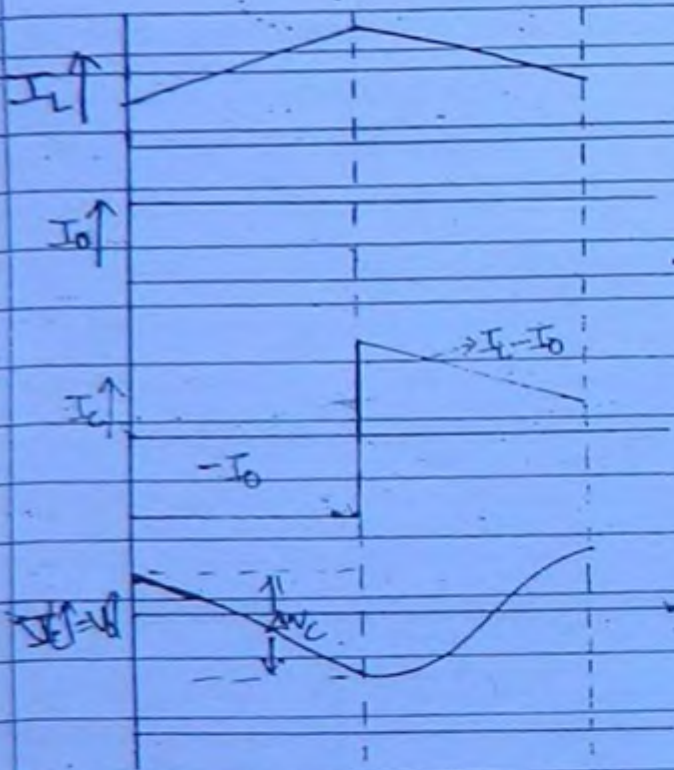

$$\int V_L dt = 0$$

$$V_s T_{ON} - V_o T_{OFF} = 0$$

$$V_s T_{ON} = V_o T_{OFF}$$

$$V_s \alpha T = V_o (1-\alpha) T$$

$$V_o = \frac{V_s \alpha}{1-\alpha}$$

$$\frac{V_o}{V_s} = \frac{I_c}{I_o} = \frac{\alpha}{1-\alpha}$$

$$\Delta V_c = \frac{\Delta Q}{C}$$

$$= \frac{I_o T_{ON}}{C} = \frac{\alpha I_o}{fC}$$

Critical Inductance (L_c):-

$$I_o = \frac{\Delta I_L}{2}$$

$$\frac{\alpha V_s}{(1-\alpha)R} = \frac{\alpha V_s}{2fL_c} \Rightarrow$$

$$L_c = \frac{(1-\alpha)R}{2f}$$

Critical Capacitance :-

$$V_o = \frac{\Delta V_c}{2}$$


(177)

$$\frac{\alpha V_s}{1-\alpha} = \frac{\alpha I_o}{2fC_c} = I_o R$$

$$C_c = \frac{\alpha}{2fR}$$

Classification of chopper based on quadrant operation

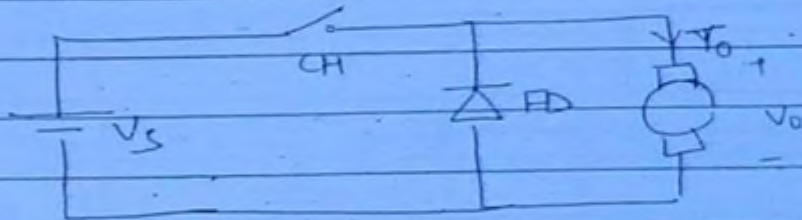I First quadrant chopper (Type A) (Stepdown chopper)




(I) CH → ON, $V_o = V_s$

$\therefore V_o (+ve), E_b (+ve)$

II CH → OFF


D → ON

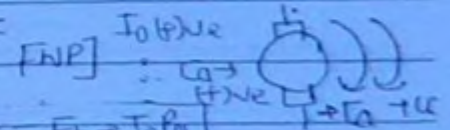

$V_o (+ve)$

$$V_s = E_b + I_o R$$

$P (+ve), \phi (+ve)$

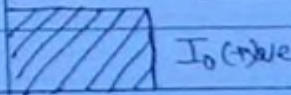


$I_o (+ve)$

Second quadrant operation (Type B Chopper)

178


Regenerating Braking of DC Motor :-

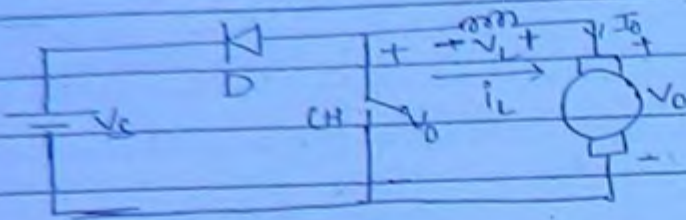

Assume that w/c is operating at rated speed b/t $T=0$ seconds.


Mech Energy = $\frac{1}{2} J \omega^2 \rightarrow$ Brake Energy

$$I_0 = \frac{V_0 - E_b}{R_a}$$

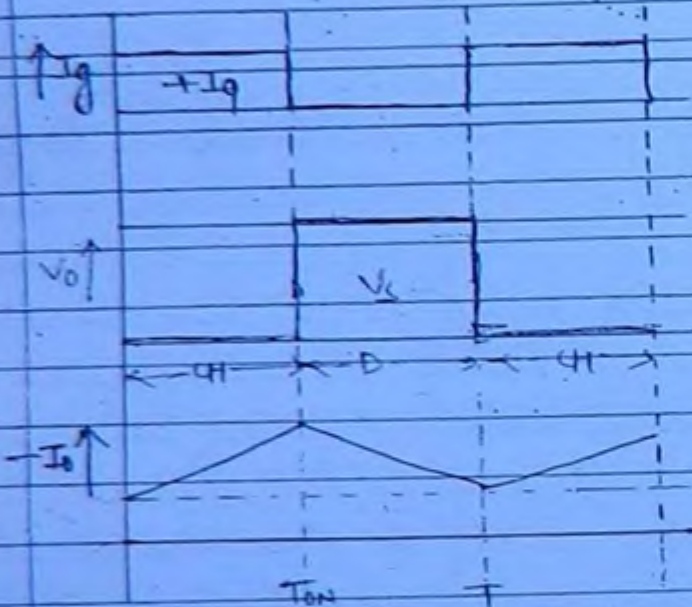


Mode-I
 $CH \rightarrow ON, D \rightarrow OFF$
 $0 < t < T_{on}$

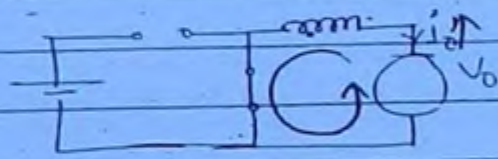$\therefore I_0 < 0, \therefore T_a \rightarrow \phi I_0 < 0$



$$\frac{1}{2} J \omega^2 \rightarrow \frac{1}{2} L i^2$$

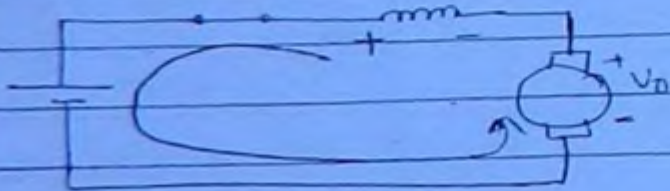Mode-II, $T_{on} < t \leq T, CH \rightarrow OFF, D \rightarrow ON$



$V_0 = V_c$
 $\frac{1}{2} L i^2 \rightarrow$ source
 Brake Energy to source
 Regenerative Braking


| | | |
|----|-------------|-------------|
| RB | $P_0 (-ve)$ | $V_0 = V_c$ |
| | $I_0 (-ve)$ | |

$$V_0 = V_c (T_{off}/T) = (1-\alpha) V_c$$

$$\text{Regenerated power} = V_0 I_0 = V_c (1-\alpha) \cdot I_0$$


III → Two quadrant operation (Type C Chopper)

1779

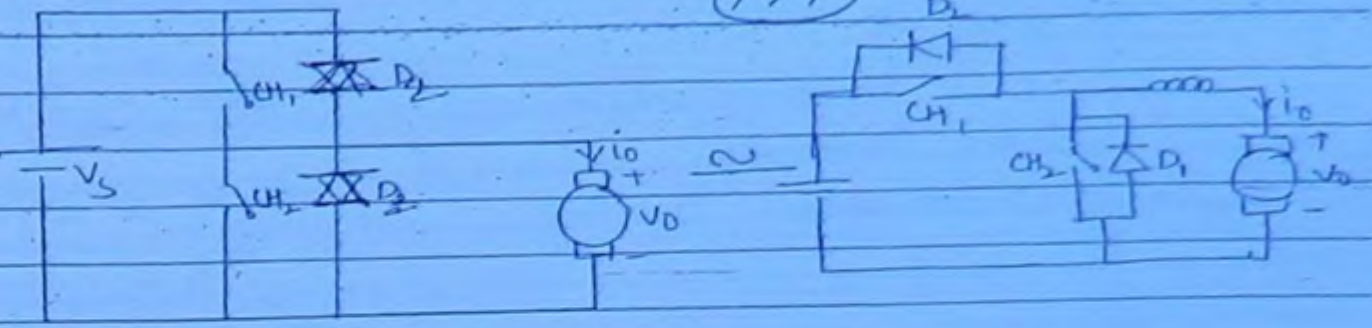

| | | |
|--|---------------------|--|
| <p>I $CH_2 \rightarrow ON$ $I_o \rightarrow (-ve), T_a (-ve)$ $\frac{1}{2} J \omega^2 \rightarrow \frac{1}{2} Li^2$</p> <p>II $CH_2 \rightarrow OFF$ $D_2 \rightarrow ON$ $\frac{1}{2} Li^2 \rightarrow \text{absorbed}$</p> <p>(RB)</p> | \uparrow V_o | <p>I $\rightarrow CH_1 \rightarrow ON, D_2 \rightarrow OFF$ $I_o (+ve), V_o (+ve), E_b (+ve), T_a (+ve), \text{active}$</p> <p>II $CH_1 \rightarrow OFF$ $D_1 \rightarrow ON (FWD)$ $\Delta V_c = E_b + I_o R_a$</p> <p>(FM)</p> |
| $(-ve) \leftarrow P_o$ | | $P_o \rightarrow (+)ve$ |
| | | $\rightarrow I_o$ |

IV → Four quadrant Chopper (Type-D)

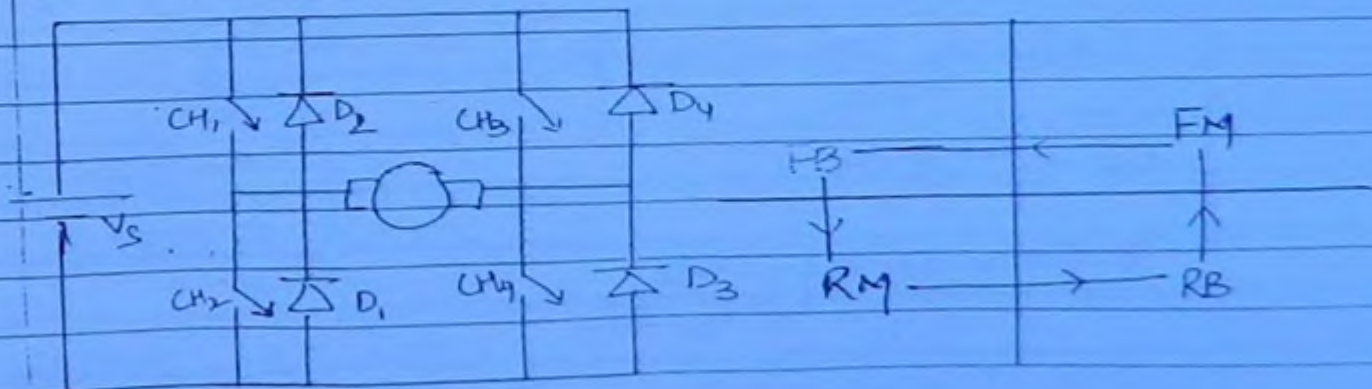

converter 11

3-φ semi-converter

$$I_a \neq 0 \rightarrow I_o \neq 0$$

$$I_o(\omega t) = 0$$

$$\text{at } \omega t = \beta, I_o(\omega t) = 0$$

ie. it is discontinuous conduction.

During discontinuity,

$$\text{load voltage} = \text{Back Emf}$$

18 $R_{max} = 100 \Omega, FSD \rightarrow 1mA$

Empirical \rightarrow measure Av. value \therefore

It will measure α up to only.

$$V_{do} = \frac{2V_m}{\pi} = I_f (100 + R_s)$$

$$\frac{2 \times 100\sqrt{2}}{\pi} = 10^3 (100 + R_s)$$

$$R_s = 89.9 K\Omega$$

19

$\alpha > 90^\circ \rightarrow$ Inversion mode

$$P_{ac} \leftarrow P_c$$

$$V_o = -E + I_o R_f \quad \text{--- (1)}$$

$$\Delta V_{do} = 4fL_c I_o$$

$$V_i = V_o \cos \alpha - 4fL_c I_o$$

$$\frac{2V_o}{\pi} = \frac{2V_m}{\pi}$$

$$= \frac{2 \times 120\sqrt{2}}{\pi}$$

$$V_o = \frac{240\sqrt{2}}{\pi} \cos 110^\circ - \frac{4 \times 50 \times 10^{-3} \times I_o}{200}$$

$$-80 + I_o \times \frac{240\sqrt{2}}{\pi} \cos 110^\circ$$

$$I_o (1.2) = \frac{240\sqrt{2}}{\pi} \cos 110^\circ + 80$$

$$I_o = 85.87 A$$

$$\Delta V_{do} = \frac{V_{do}}{2} [\cos \alpha - \cos(\alpha + \pi)] = 4fL_c I_o$$

$$\mu = 8.35^\circ$$

$$\text{Rectification Efficiency} = \frac{V_o I_o}{V_{or} I_{or}} = 55.05 \%$$

23

Pulse No \uparrow THD \downarrow

L filter, (Smoothness of waveform) \uparrow

THD \downarrow

C filter, VRF \downarrow

but THD \uparrow

1

$$V_o = 50\% (V_o)_{max}$$

$(V_o)_{max}$ when $\alpha = 0^\circ$

$$(V_o)_{max} = V_{do} = \frac{3V_{mL}}{2\pi}$$

$$V_o = \frac{1}{2} \left[\frac{3V_{mL}}{2\pi} \right] (1 + \cos \alpha) \text{ (AVG)}$$

$$V_o = \frac{V_{do}}{2} (1 + \cos \alpha)$$

$$\frac{1}{2} \left[\frac{3V_{mL}}{2\pi} \right] = \frac{3V_{mL}}{2\pi} (1 + \cos \alpha)$$

$$\frac{V_{mL} - \sqrt{3}V_{mL}}{\sqrt{3}} - 1 = \cos(\alpha + 30^\circ)$$

$$\alpha = 67.7^\circ$$

$$I_o = \frac{V_o}{R} = 7.17 \text{ Amp.}$$

$$I_{or} = \frac{V_{or}}{R} = 10.48 \text{ Amp.}$$

$$\alpha_{max} = 180 - (\omega t q + \mu_0)$$

$\mu_0 \rightarrow$ overlap \angle at $\alpha=0$

$$V_0 = E_b + I_0 R_a$$

$$V_0 = V_d \cos \alpha - 3fL_s I_0$$

$$E_b + I_0 R_a = V_d \cos \alpha - 3fL_s I_0$$

$$I_0 = \frac{V_d \cos \alpha - E_b}{R_a + 3fL_s}$$

$$V_d = \frac{3V_m}{2\pi} = 202.5V$$

$$I_0 = 14.71A$$

$$\frac{V_d (\cos \alpha - \cos(\alpha + \mu))}{2} = 3fL_s I_0$$

$$\mu |_{\alpha=0} = 17^\circ$$

$$\omega t q = 2\pi \cdot 250 \times 10^6 \cdot \frac{180}{\pi}$$

$$= 4.5^\circ$$

$$\alpha_{max} = 180 - 4.5 - 17$$

$$= 158.5^\circ$$

$$\text{at } \alpha=0 = \mu = 20^\circ$$

(781)

$$\frac{I_0}{I_{op}} = (\cos \alpha - \cos(\alpha + \mu))$$

$$I_{op} = 0.134$$

$$\text{at } \alpha=20^\circ$$

$$0.134 = \cos 20^\circ - \cos(20^\circ + \mu)$$

$$\mu = 12.94^\circ$$



$$\text{at } \alpha=60^\circ$$

$$0.134 = \cos 60^\circ - \cos(60^\circ + \mu)$$


$$\mu = 8.53^\circ$$

Choppers :-

1.

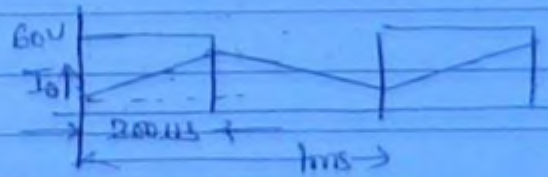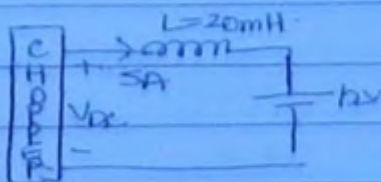

$$CH \rightarrow ON, V_{dc} = 60V$$

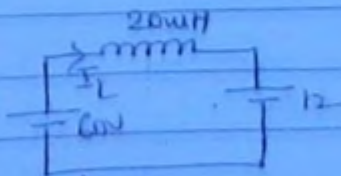

$$60 - 12 = L \frac{di}{dt}$$

$$\Delta I_L = \frac{48}{20 \times 10^{-3}} \times 200 \times 10^{-6}$$

$$= 480 \times 10^{-3} = 0.48A$$

$$\Delta I_L = \frac{48}{20 \times 10^{-3}} \times T_{ON}$$

$$V_s = 100V$$

$$\alpha = 0.8$$

182)

3

CASS-D commutation \rightarrow v/q commutation

$$(I_{FD}) = I_0 \frac{(T_{ON})}{T}$$

$$= I_0 (1-\alpha)$$

$$I_0 = \frac{\alpha V_s}{R}$$

$$= \frac{0.8 \times 100}{10} = 8$$

$$(I_{FD})_{av} = 8(1-0.8) = 1.6A$$

$$(T_{ON})_{min} \text{ of chopper} = \pi \sqrt{LC} = 40\mu s$$

$$V_0 = V_s \left[\frac{T_{ON} + 2t_{cm}}{T} \right]$$

$$(V_0)_{min} = 250 \left[\frac{40 \times 10^{-6} + 2t_{cm}}{10} \right] \times 10^3$$

$$t_{cm} = \frac{CV_s}{I_0} = \frac{10^{-6} \times 250}{10} = 25 \times 10^{-6}$$

$$(V_0)_{min} = 47.5V$$

$$(I_{TM})_{peak} = I_0 + V_s \sqrt{\frac{C}{L}} = 10 + 250 \sqrt{\frac{10^{-7}}{10^{-3}}} = 10 + 250 \times 10^{-2} = 12A$$

$$(I_{TA})_{peak} = I_0 = 10A$$

Step-down Chopper $\rightarrow \alpha = 0.5$

$$I_0 = \frac{\alpha V_s}{R} = \frac{0.5 \times 60}{3} = 10A$$

A_v value will not depend on Inductance.

$$T_{ON}' = T_A \ln \left[1 + \frac{E_b}{V_s} (e^{T/T_A} - 1) \right]$$

$$T_A = \frac{L}{R} = \frac{10^{-3}}{0.25} = 4 \times 10^{-3}$$

$$\frac{T}{T_A} = \frac{2.5 \times 10^{-3}}{4 \times 10^{-3}} = 0.625$$

$$T_{ON}' = 332.5 \mu \text{ sec}$$

9 $\alpha = \frac{1}{5} \Rightarrow VRF = \sqrt{\frac{1}{\alpha} - 1} = \sqrt{5 - 1} = 2$
183

10 $T_{min} = \pi \sqrt{LC}$
 $t_{max} = \pi \sqrt{LC} + \sqrt{LC} \sin^{-1} \left(\frac{I_0}{I_p} \right)$

$$I_p = \frac{V_s \sqrt{C}}{\sqrt{L}} = \frac{230 \times \sqrt{10 \times 10^{-6}}}{\sqrt{25.28 \times 10^{-6}}}$$

$$= 144.66$$

$t_{max} \approx 75 \mu s$
 $t_{min} = 50 \mu s$

11 $L = 64 \mu H$

$$(I_M)_{peak} = I_0 + V_s \sqrt{\frac{C}{L}} = 10.7 + 200 \sqrt{\frac{64 \times 10^{-6}}{16 \times 10^{-6}}}$$

$$= 110.7 A$$

12 c) $t_{cm} = \frac{CV_s}{I_0} = \frac{50 \times 10^{-6} \times 220}{80} = 137.5 \mu sec$


$$t_{ca} = \frac{\pi \sqrt{LC}}{2} = \frac{\pi \sqrt{20 \times 50} \times 10^{-6}}{2} = 49.67 \mu sec$$

a) $T_{on} / effective = T_{on} + 2t_{cm}$
 $= 800 + 2 \times 137.5 = 1075 \mu s$

$$(I_{TM})_p = I_0 + V_s \sqrt{\frac{C}{L}} = 427.85 \text{ Amp.}$$

$$(I_{TA})_p = I_0 = 8 \text{ Amp.}$$

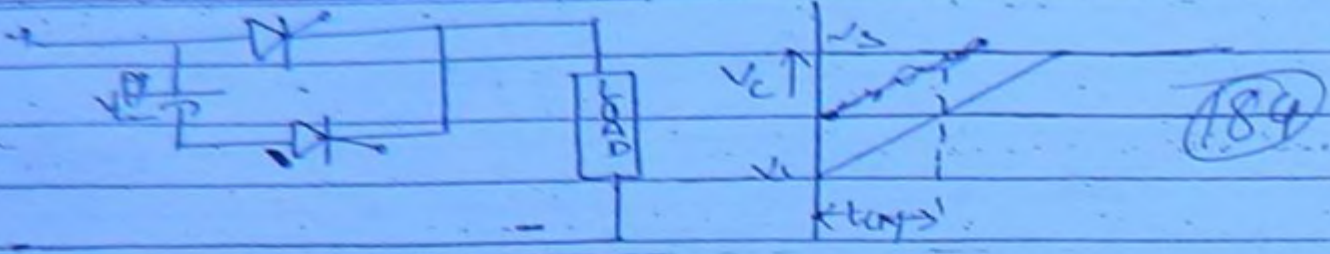Total Commutation Interval = $2t_{cm}$
 $= 2 \times 137.5 = 275 \mu s$





$$V_c = \frac{V_s \cdot t}{t_{avg}} \Rightarrow V_c = \frac{220 \cdot 150}{137.5} = 20V$$

AC VOLTAGE CONTROLLERS

fixed AC \rightarrow variable AC (V_o, f_o)

I Phase Control Technique -

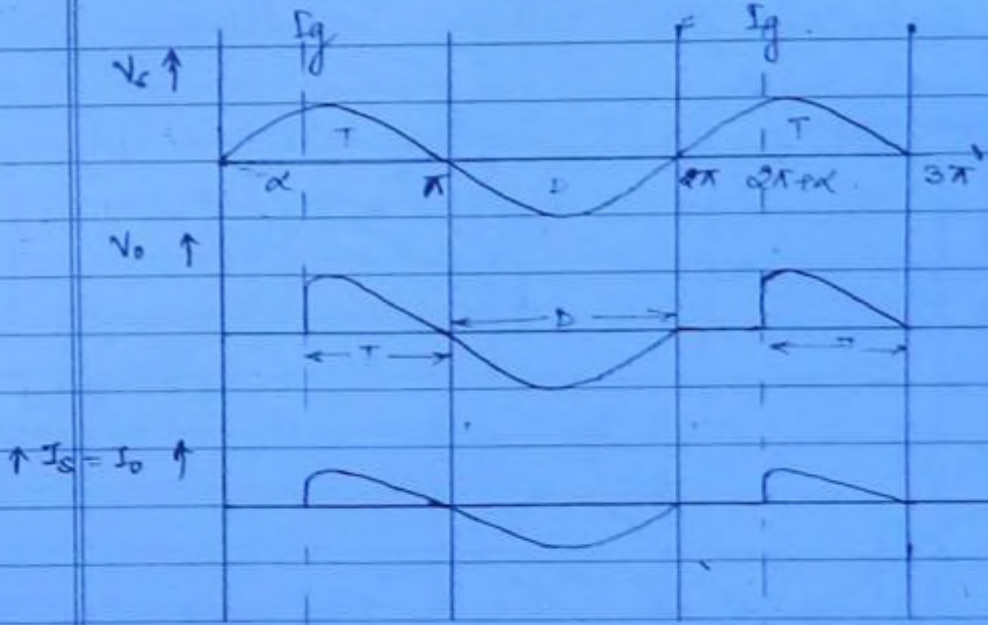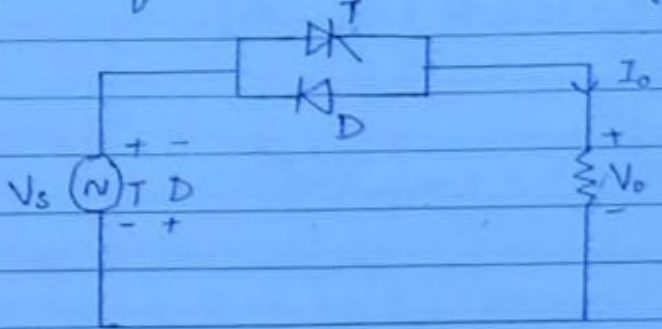a) 1- ϕ Half Controlled AC Voltage Controllers -



$$V_o = \frac{1}{2\pi} \int_{\alpha}^{2\pi} V_m \sin \omega t \, d(\omega t) = \frac{V_m}{2\pi} (\cos \alpha - 1)$$

$$(I_s)_{avg} = I_o = \frac{V_m}{2\pi R} (\cos \alpha - 1)$$

DC component

Drawback -

Source current contains DC component & saturates the supply transformer core.

(186)



$$V_{or} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\pi+\alpha} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$PF = \frac{V_{or}}{V_s} = \frac{1}{\sqrt{2}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

(b) 1- ϕ Full Controlled AG Voltage Controller -

1. R Load

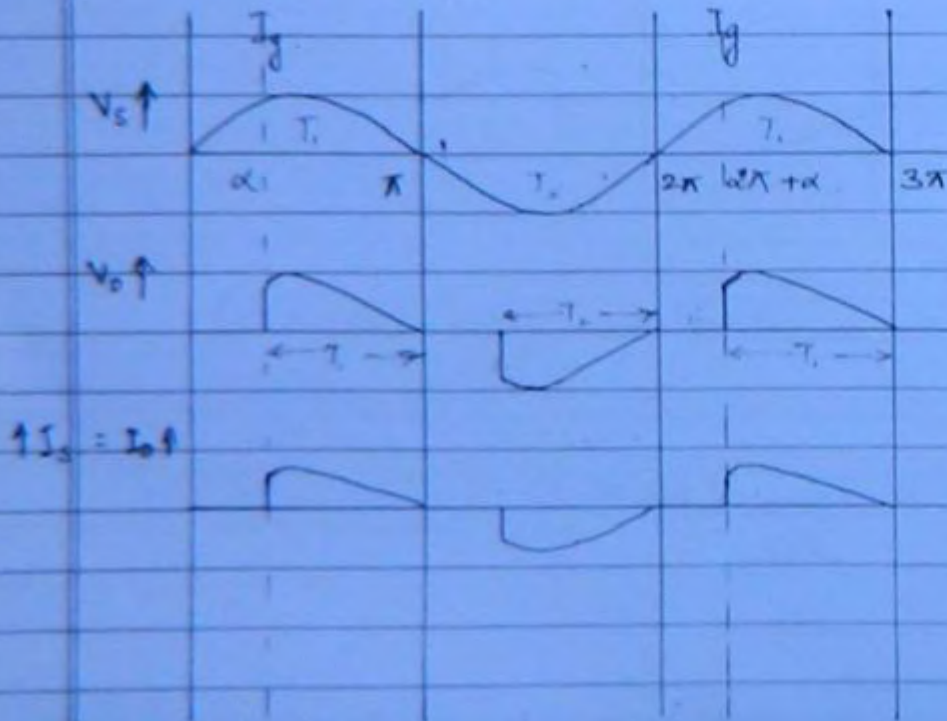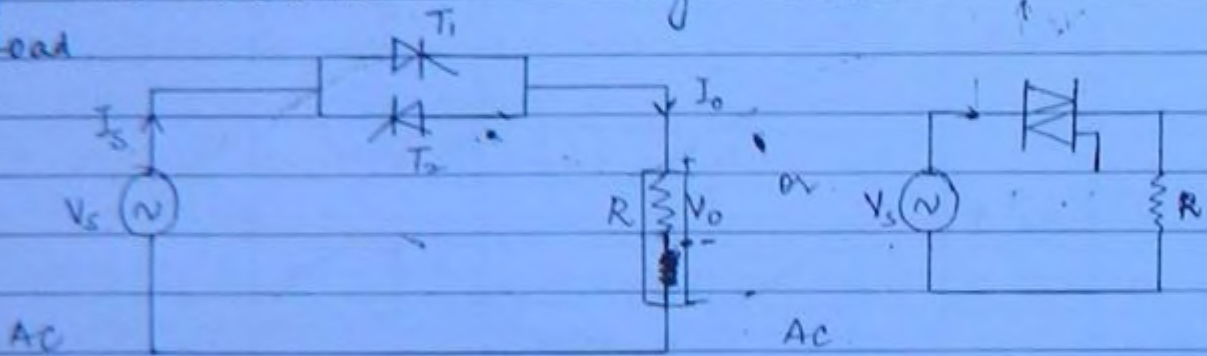



Q. RL load.

After reaching steady state I_o lags V_o by $\phi = \tan^{-1} \frac{\omega L}{R}$

(187)

(I) $\alpha > \phi$, V_o is controlled

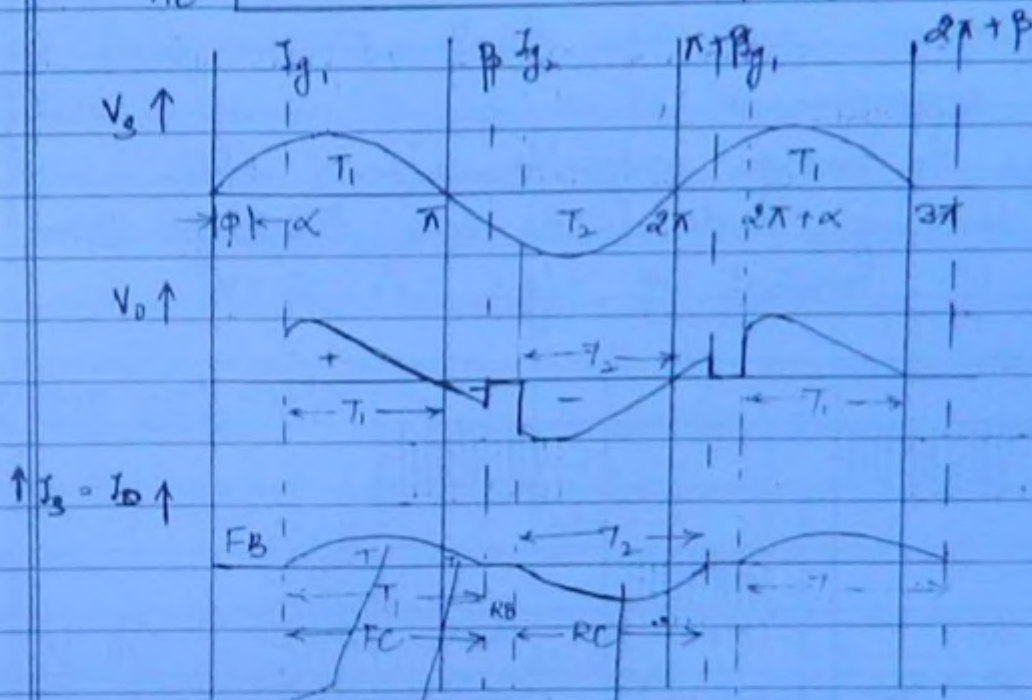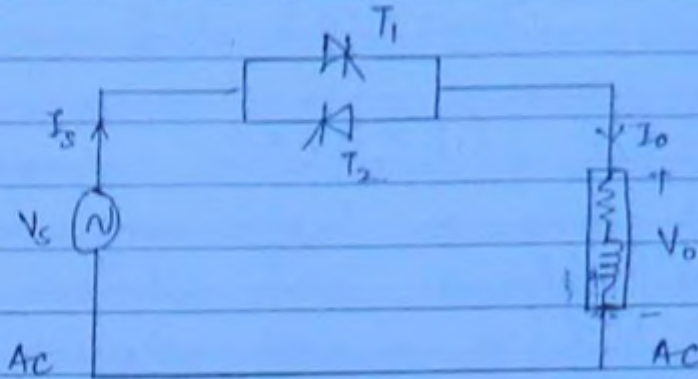(II) $\alpha \leq \phi$, V_o is uncontrolled.



$P(+)$
power flows
from source to
load

(I) $\alpha > \phi$ V_o is controlled \rightarrow (By α o/p vlg can be control)

$P(+)$
power again flows
from source to
load

$P(-)$
load \rightarrow source (Inductor changes polarity)

$$V_{oa} = \left\{ \frac{L}{\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

158

$$V_{oa} = \frac{V_m}{\sqrt{2}\pi} \left[(\beta - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right]^{1/2}$$

II $\phi > \alpha$

$L \uparrow \quad T \uparrow \quad \beta \uparrow \quad (\beta > \pi + \alpha)$


$$\uparrow \phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

→ continuous conduction of $-V_o$ occurs as β approaches $\pi + \alpha$

Only 2 modes available FC & RC

No blocking mode (SCRs are short ckted)

∴ No control of v_{gs} ∴ $V_o = V_a$

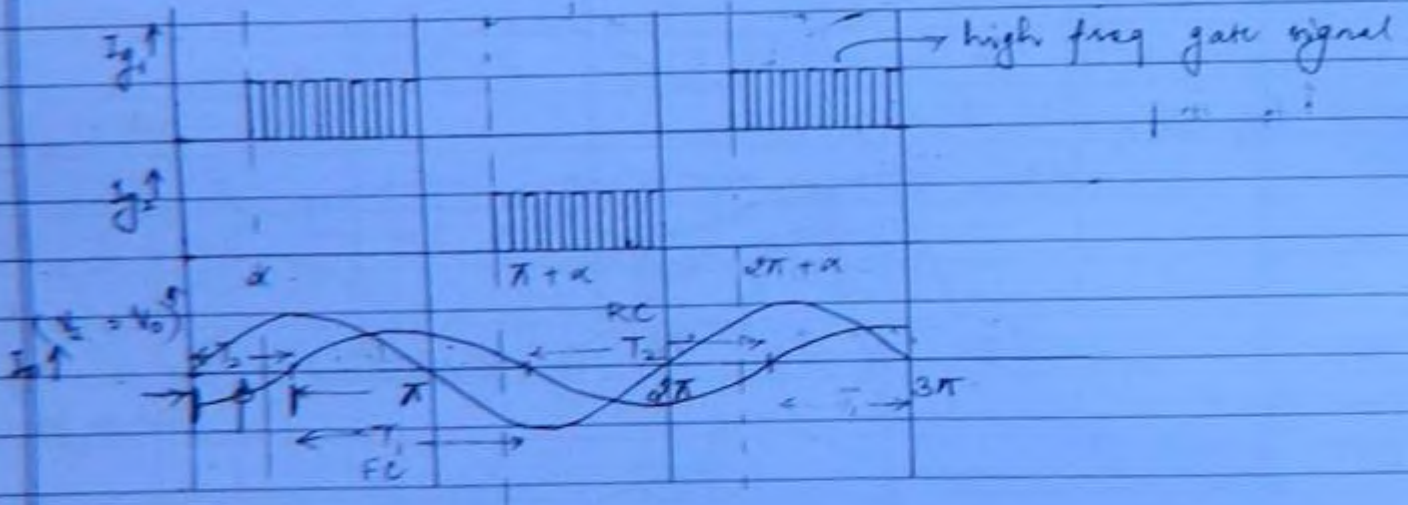

When T_1 stops conducting, but there is no gate signal for T_2 (I_{gr}), T_2 fails to turn-on & it behaves as a rectifier.

To avoid this continuous gate signal is given but that ↑ power loss & also may saturate pulse T_{max}

We get max^m output v_g when its uncontrolled

$$(V_o)_{max} = (V_s)_{max} = \frac{V_m}{\sqrt{2}}$$

(189)


$$(I_{or})_{max} = I_{oa} = \frac{(V_o)_{max}}{|Z|}$$

$$|Z| = \sqrt{R^2 + (\omega L)^2}$$


NOTE.

If pulse gate signal is given to AC v_g controller with inductive load, then it may behave as half wave rectifier. because of one of the SCRS fails to turn-on due to the absence of gate signal at that instant. ~~to~~ To avoid this problem we can give either continuous gate signal or high frequency gate signal.

c) Two stage AC v_g controller -

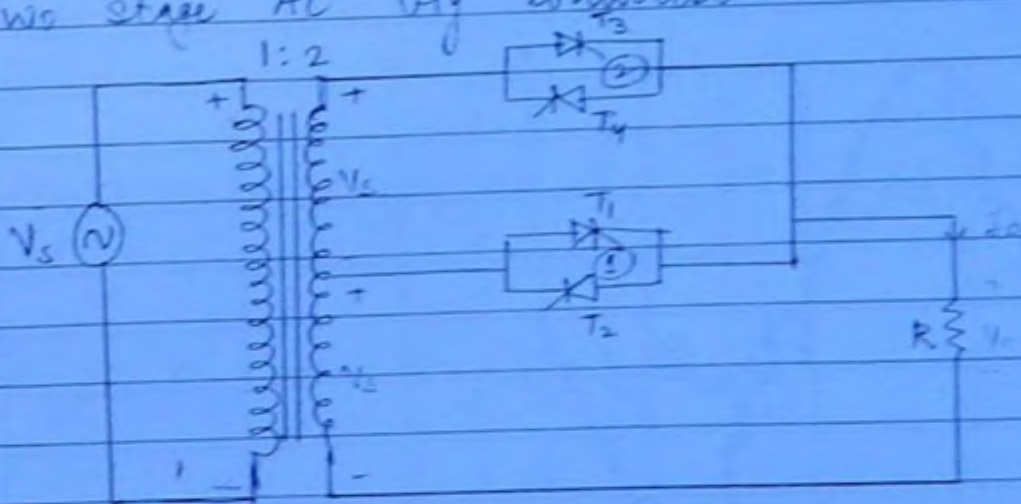

+ T₁ T₃ (FB)
 - T₂ T₄ (FB)
 fwd bias

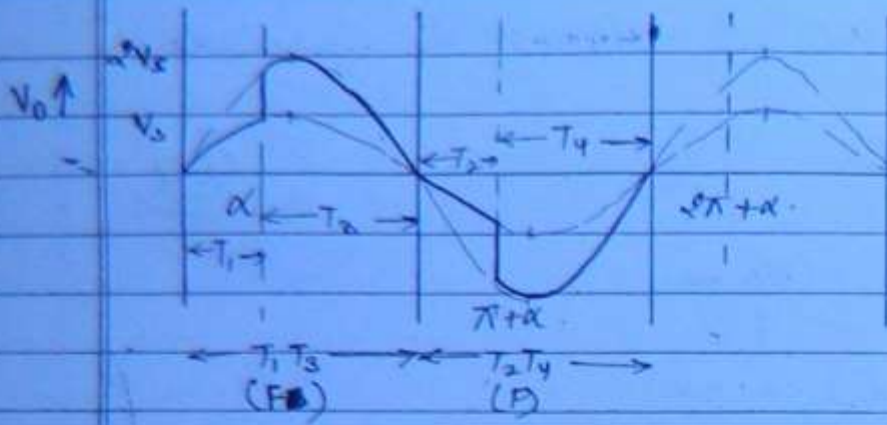


(*) Since waveform is approaching sine wave, the smoothness \uparrow with no. of stages
 Thus harmonic distortion \downarrow .

$$V_{avg} = \left\{ \frac{1}{\pi} \left[\int_0^{\alpha} V_m^2 \sin^2 \omega t \, d(\omega t) + \int_{\pi-\alpha}^{\pi} 4V_m^2 \sin^2 \omega t \, d(\omega t) \right] \right\}^{1/2}$$


$$= \frac{V_m}{\sqrt{2\pi}} \left\{ [\alpha - 1 \sin 2\alpha] + 4 \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right] \right\}$$

d) Multistage Regulators -

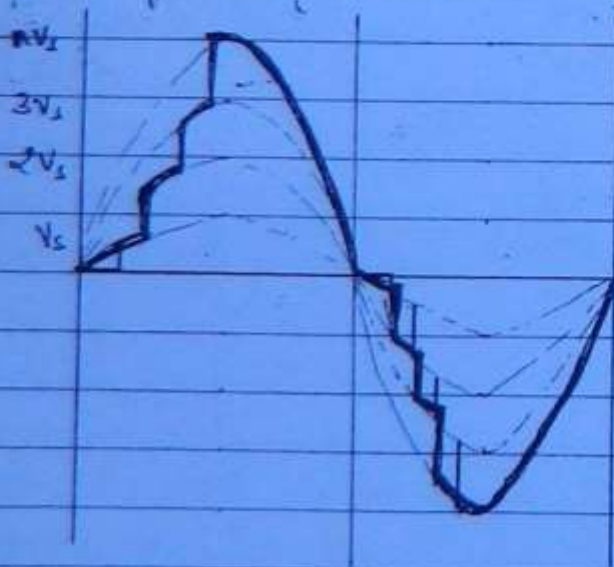

II Integral Cycle Control (ON/OFF)



(91)

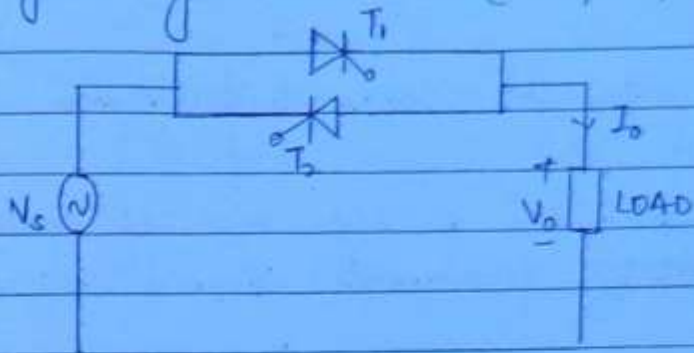

m cycles (ON) [$m=3$]
 n cycles (OFF) [$n=2$]

I_g ($0, 2\pi, 4\pi, \cancel{6\pi}, \cancel{8\pi}, 10\pi, 12\pi, 14\pi, \cancel{16\pi}, \cancel{18\pi}, \dots$)

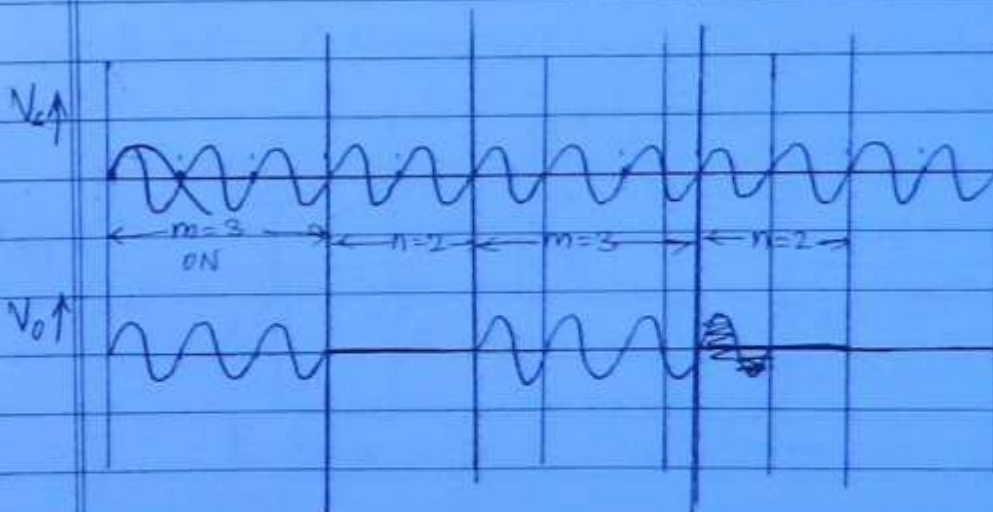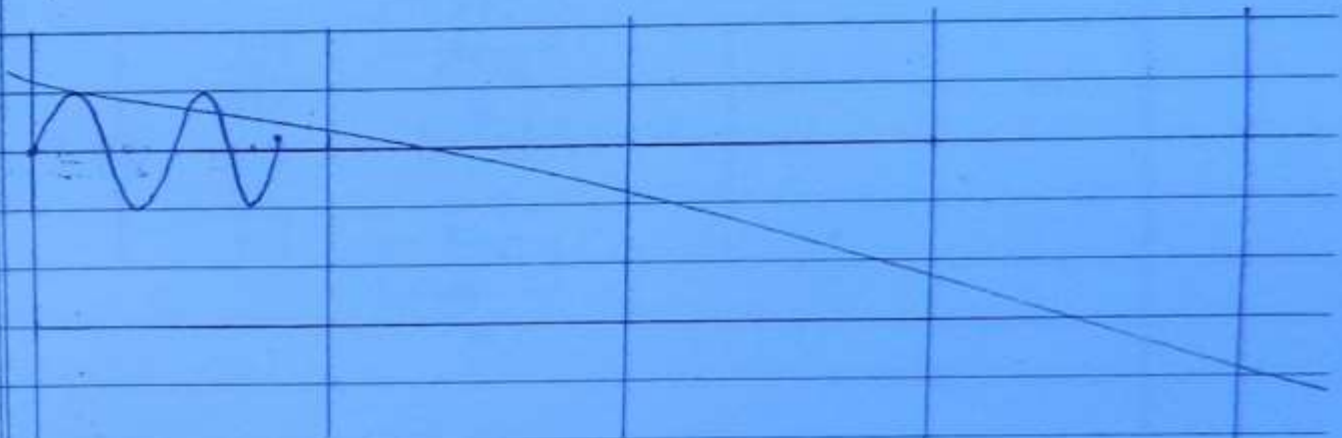I_g ($\pi, 3\pi, 5\pi, \cancel{7\pi}, \cancel{9\pi}, 11\pi, 13\pi, 15\pi, \cancel{17\pi}, \cancel{19\pi}, \dots$)



$$V_{or} = V_{sr} \left(\frac{m}{m+n} \right)^{1/2}$$

$$V_{or} = \sqrt{k} V_{sr} \quad \text{when } k = \frac{m}{m+n}$$

Applications --

(92)

It can be used for AC loads with ~~low~~ ^{high} time constant

eg It can be used for a big size of motor with high MOI & mech time constant.

Limitations --

We cannot get wide range of control i.e. control is limited.

CYCLOCONVERTER


(193)

Fixed AC \rightarrow Variable AC
 (V_s, f_s) , (V_o, f_o)


$f_o < f_s \Rightarrow$ step-down cycloconverter

$f_o > f_s \Rightarrow$ step up cycloconverter

Mid-Point Cycloconverter -

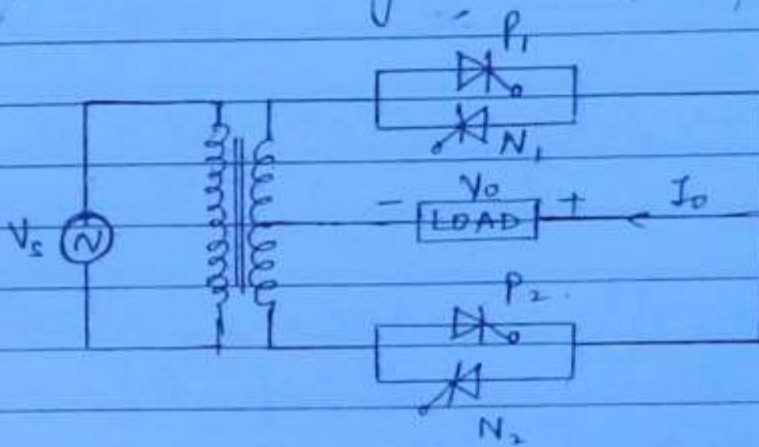


Bridge Cycloconverter

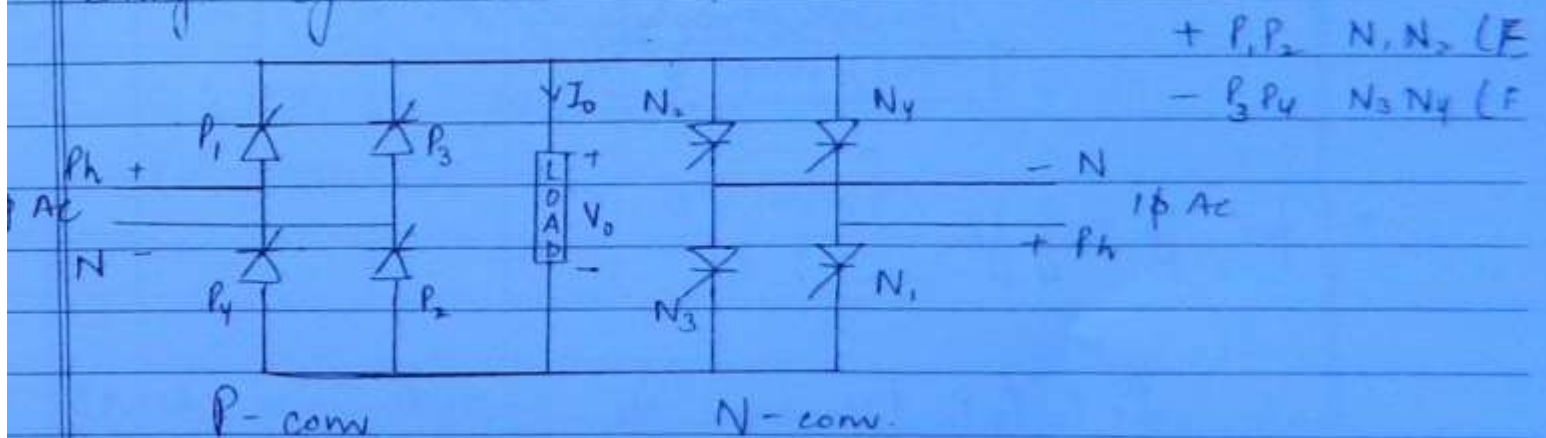

Stepdown cycloconverter ($f_0 < f_s$)
 let $f_0 = \frac{1}{3} f_s$ $\therefore T_0 = \frac{3}{8} T_s$


10/11

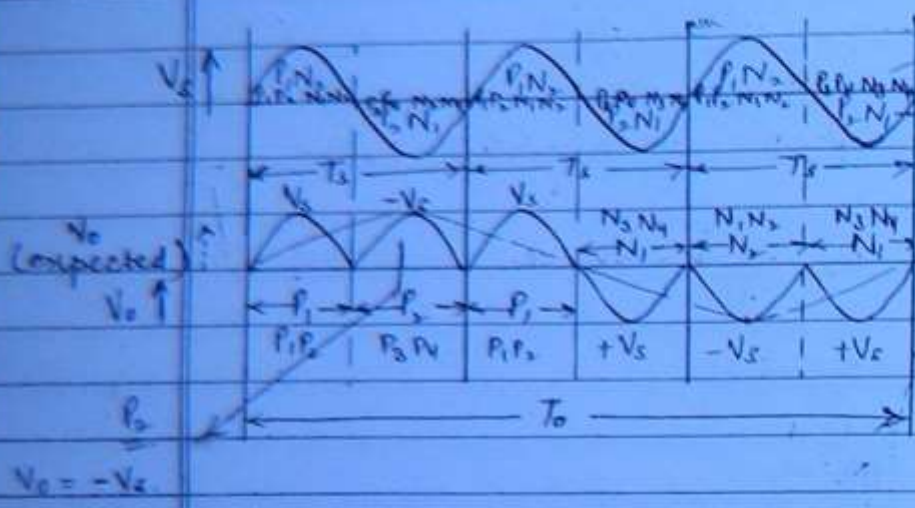


→ Bridge cycloconv.
 → Mid pt cycloconv.
 For +ve cycle of expected consider P thyristors of V_s .

Shortcut →

⇒ for $f_0 = \frac{1}{3} f_s$

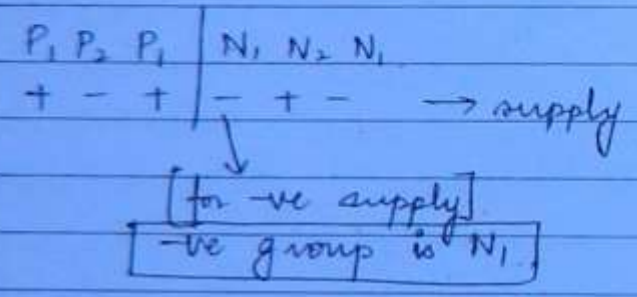

⇒ for $f_0 = \frac{1}{4} f_s$

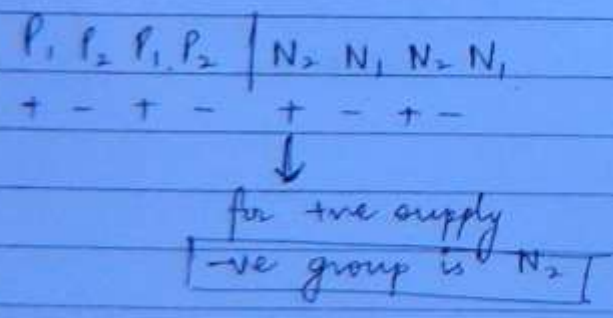

Here only frequency is varied α is kept 0 but if variation in both V_o & f_o is required, with this scheme vary α .

(195)

R-Load -


$$V_{oa} = \frac{V_m}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

RL-Load -

$$V_{or} = \frac{V_m}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right]$$

Step Up Cycloconverter - ($f_o > f_c$)

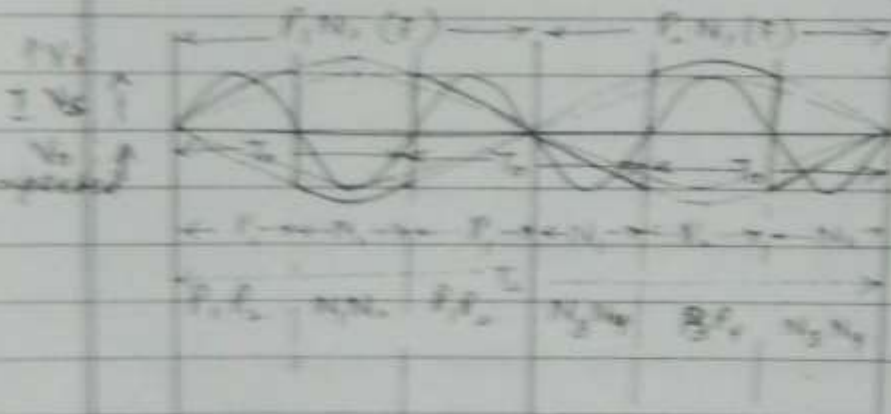Let $f_o = 3f_c \quad \therefore T_c = \frac{1}{3} T_o \quad \therefore T_o = 3 T_c$



- Freewheeling is required in step up cycloconverter
- Harmonic distortion is more in cycloconverters than half wave at low f_o .


Applications -

(196)

Its used for high speed power, low speed and reversible AC drives
 eg in S_f I.M for controlling speed.

AC DRIVES -


1. Stator voltage control of I.M -

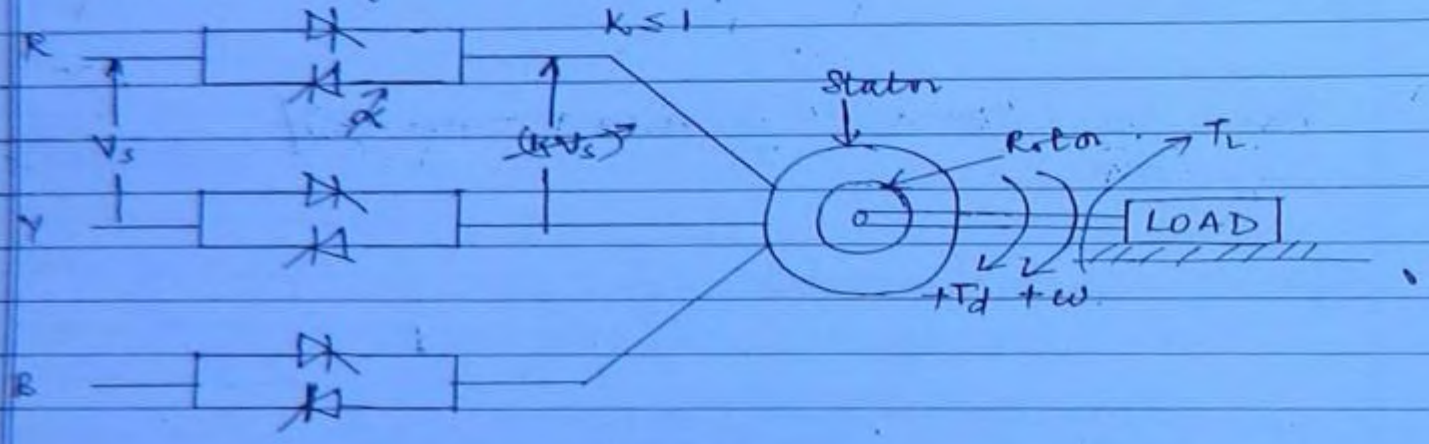

At starting $T_d > T_l$ $\omega \uparrow$

After reaching steady state speed $T_d = T_l$

$T_d < T_l$ $\omega \downarrow$

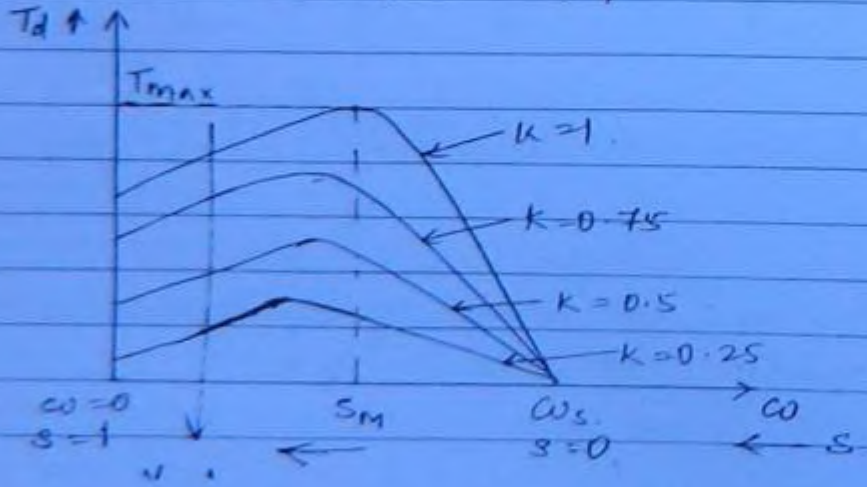

$$T_d = \frac{3}{\omega_s} \frac{(kV_s)^2 R_{N'} / s}{\left(R_s + \frac{R_{N'}}{s}\right)^2 + (X_s + X_{N'})^2} \quad (199)$$

$$s = \frac{N_s - N}{N_s} = \frac{\omega_s - \omega}{\omega_s}$$

Mech Load -

1. $T_L = \text{const.}$
2. $T_L \propto \omega$
3. $T_L \propto \omega^2$
4. $T_L \propto \frac{1}{\omega}$

! \Rightarrow Check whether constant load torque is suitable or not suitable for the given electrical drive

Let us consider the m/c is running at rated speed

$$\therefore T_d = T_L$$

$$(kV_s) \downarrow, T_d \downarrow \quad (T_d < T_L)$$

$$\therefore \omega \downarrow, s \uparrow, I \uparrow \therefore T_d \uparrow$$

Here m/c will slow down if \uparrow the T_d until it balances the constant T_L .

Here the m/c draws more current from the supply mains in order to \uparrow the T_d for balancing the T_L . \therefore m/c gets overheating

Hence this mech load is not suitable for the drive.

$$\Rightarrow T_e \propto \omega^2$$

$$(kV_e) \downarrow \quad T_d \downarrow \quad (T_d < T_e)$$

$$\omega \downarrow \quad T_e \downarrow$$

(198)

Here speed will slow down until the ϕ decreased T_e balances the T_d . Here the m/c will not draw more ^{current from} supply line.

\therefore This type of mech load is suitable for given electrical drive.

Applications -

Used where $T_e \propto \omega^2$.

eg. fan loads, reciprocating pumps, compressors etc.

2. Stator Frequency Control of I.M -

(a) V/f control ($\omega < \omega_n$)

To maintain const flux we go for V/f control.

If ϕ is not maintained const

overfluxing occurs

- $I_m \uparrow$
- harmonic distortion \uparrow
- losses \uparrow
- $f/f \downarrow$

→ We can ~~not~~ realize V/f control by using cycloconverters. but its used only for high power low speed. With cycloconverters the maximum speed is limited to 40% of rated speed.

→ We can also realise the V/f control by using PWM inverters. With PWM inverters -

↳ smooth rotation is possible and some lower order harmonics can be eliminated.

(199)

(b) Constant V (for $\omega > \omega_n$)

At rated speed $V_s = V_{rated}$

$$V_s \propto \phi f \uparrow$$


$$N \uparrow \quad f \uparrow \quad \phi \downarrow$$

Here as $f \uparrow \Rightarrow \phi \downarrow$ because we cannot ~~exceed~~ \uparrow the stator vlg beyond rated value. \therefore stator vlg is fixed at rated value in this method.

We can realise this method by:


→ Square Wave Inverter

→ PWM Inverter

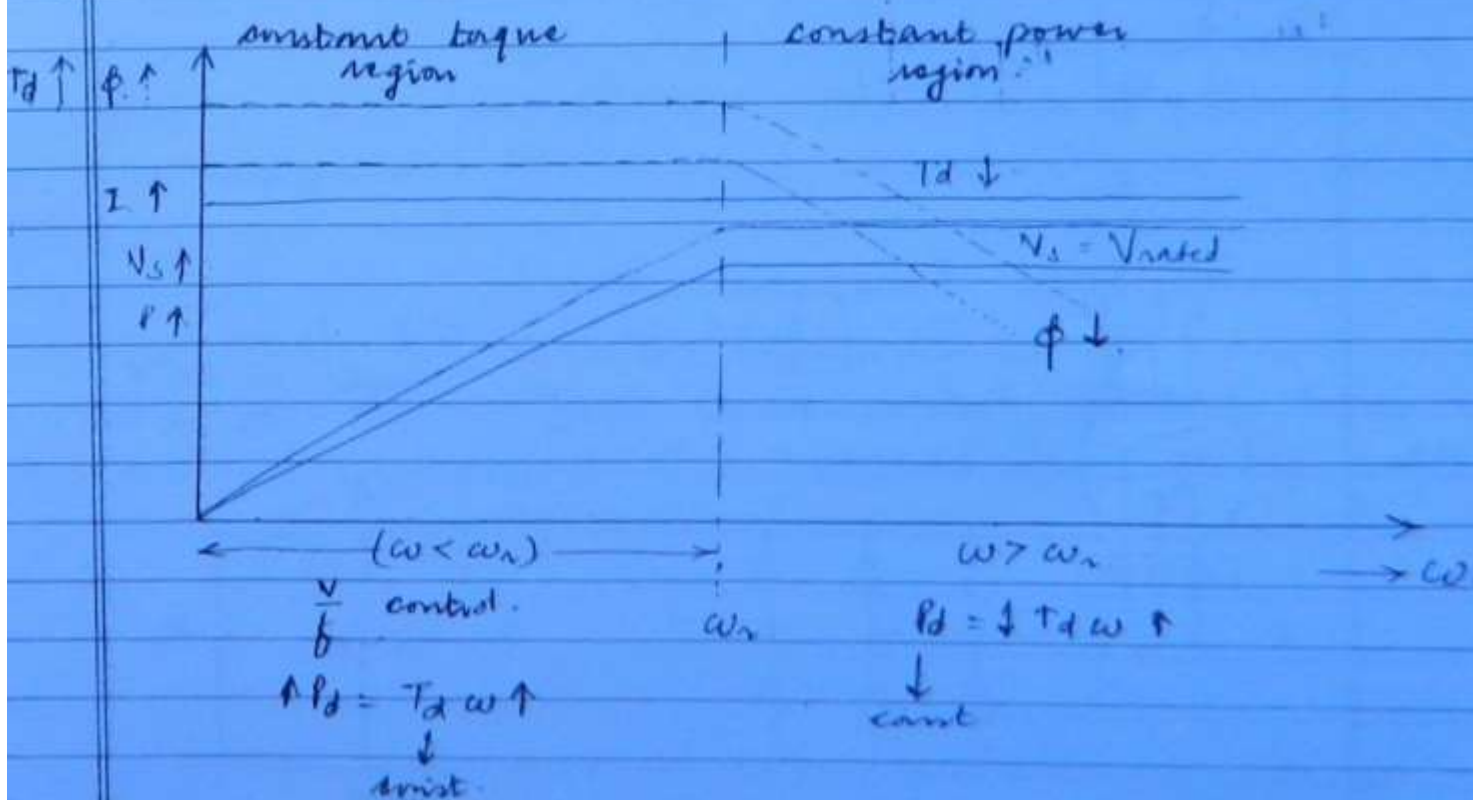

Rotor Resistance Control -

200

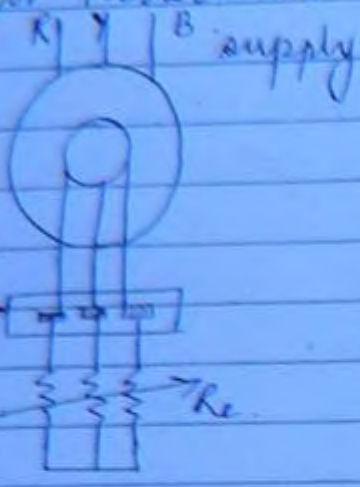


Total Cu loss = $s I_g^2$

$3 I_N^2 [R_r + \uparrow R_e] = \uparrow s I_g^2$


$s \uparrow \therefore \omega \downarrow$

Chopper Controlled Resistance -

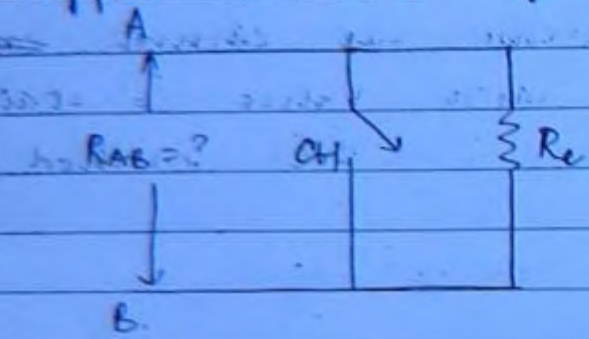

$R_{AB} = R_e \left(\frac{T_{OFF}}{T} \right)$


$R_{AB} = R_e (1 - \alpha)$

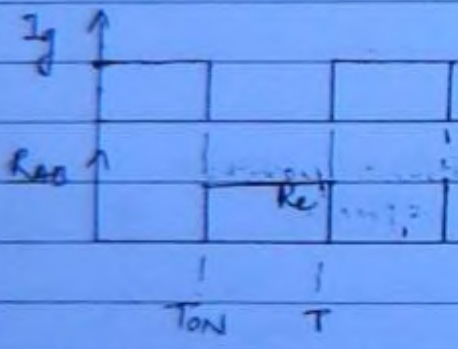

Stator Rotor Resistance Control

$f_0 = 6. s f_s$

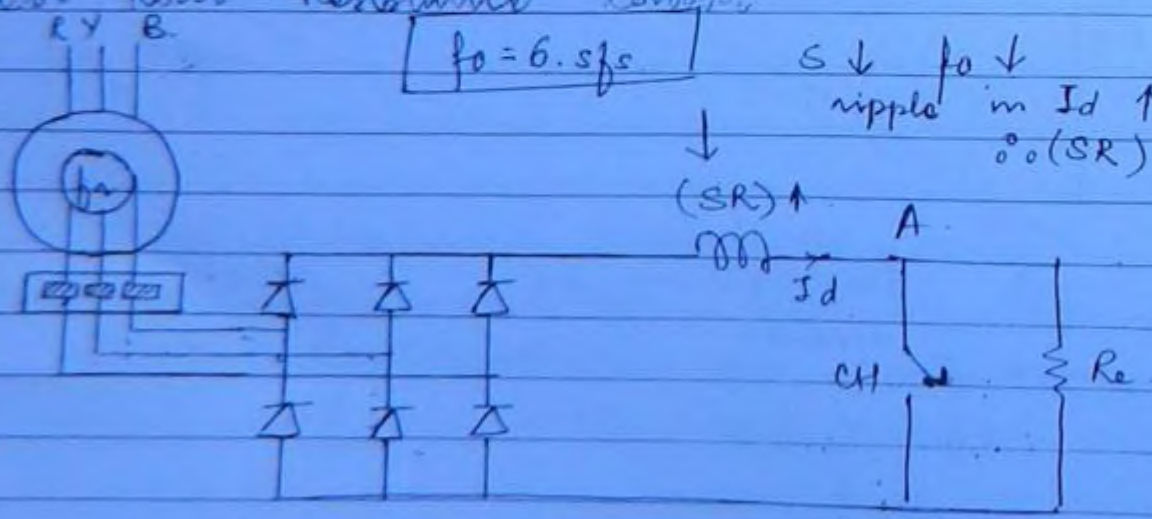$s \downarrow \therefore f_0 \downarrow$
 ripple in $I_d \uparrow$
 $\therefore (SR) \uparrow$



Q) What is the effective resistance connected in series per phase with the rotor wdg per phase for the above system? (201)

$$\text{Total Cu loss} = s P_g$$

$$3 I_r^2 R_r + I_d^2 R_e (1 - \alpha) = s P_g$$

$$I_{cr} = I_o \sqrt{\frac{2}{3}} \Rightarrow I_r = I_d \sqrt{\frac{2}{3}}$$

$$I_d = I_r \sqrt{\frac{3}{2}}$$

$$\Rightarrow 3 I_r^2 R_r + \frac{3}{2} I_r^2 R_e (1 - \alpha) = s P_g$$

$$\Rightarrow 3 I_r^2 [R_r + 0.5 R_e (1 - \alpha)] = s P_g$$

$$\propto 3 I_r^2 [R_r + (C)]$$


↓
eff resistance in series with rotor wdg per phase

This is not an efficient control cuz the slip power is dissipated in external resistance.

4. Slip Power Recovery

This is an efficient speed control method because the slip power can be utilised or given back to supply line.

a) Static Kramer Drive

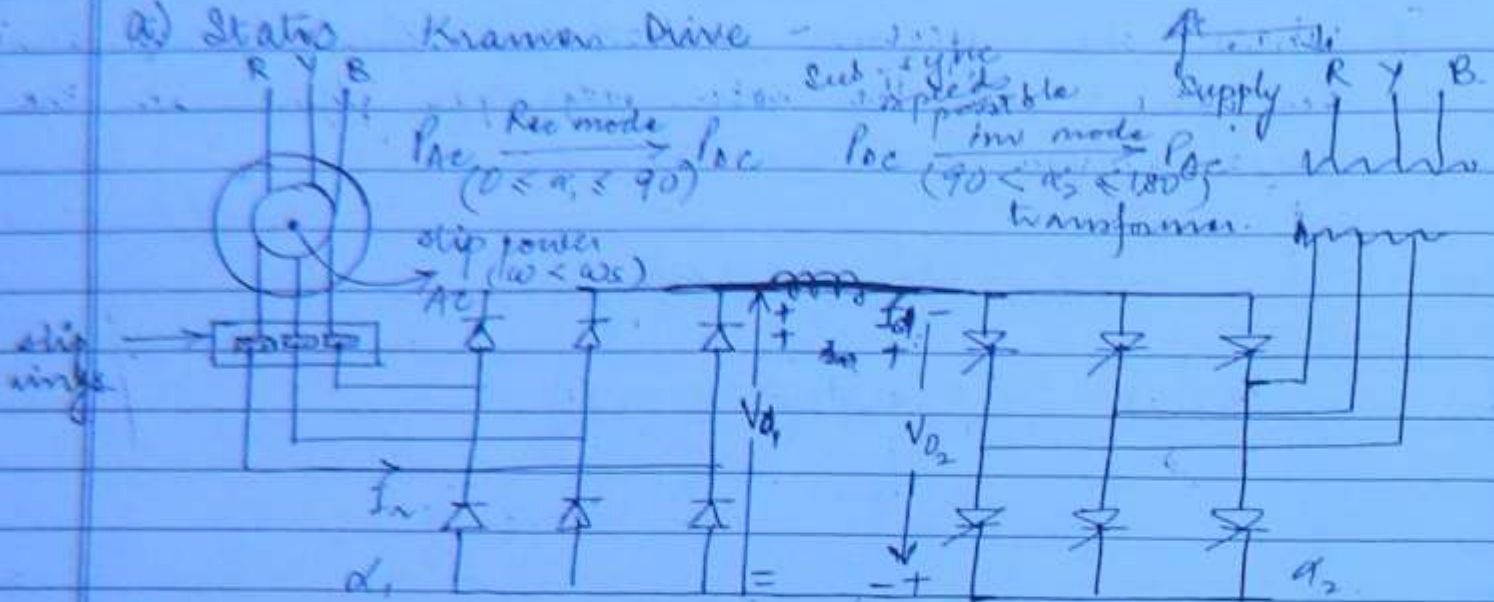

\pm } Ref polarities of converter

90°


\pm } Actual polarities of converter.

$$V_o = \frac{3V_{ML}}{\pi} \cos \alpha$$


$\alpha < 90^\circ$ $V_o +$ (Rec mode)

$\alpha > 90^\circ$ $V_o -$ (Inv mode)

b) Static Scherbius Drive

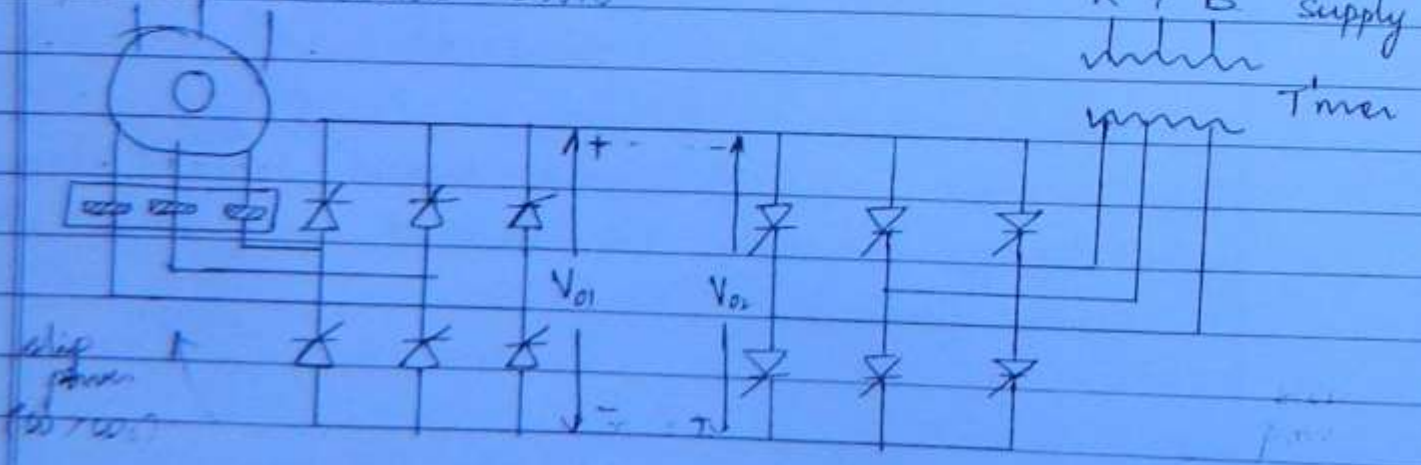

CWB chapter 5.

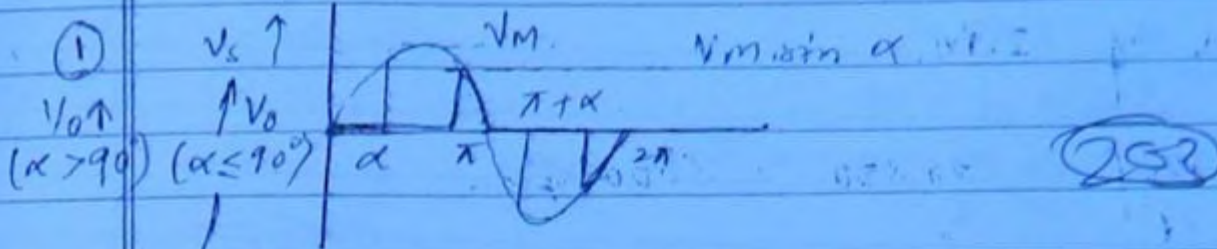

peak power = $\frac{V_m^2}{R} = \frac{(\alpha 30 \sqrt{2})^2}{R} = \frac{(\alpha 30 \sqrt{2})^2}{10}$
 $= 10580 \text{ W (d)}$

peak power $\Rightarrow \frac{(V_m \sin \alpha)^2}{R}$

② V_o is uncontrolled at $\alpha \leq \phi$
 $\phi = \tan^{-1} \frac{\omega L}{R} \Rightarrow \phi = \tan^{-1} \frac{50}{50}$
 $= 45^\circ$
 $0 \leq \alpha \leq 45^\circ$ (a)

③ ~~hand~~ Per unit power = $\frac{P_o}{P_{max}}$
 $= \frac{V_{or}^2 / R}{V_{sr}^2 / R}$
 $= \left(\frac{V_{or}}{V_{sr}} \right)^2 = PF^2$

$PF = \sqrt{\text{per unit power}}$ (b)

Control of I.M -

$$N_s = \frac{100f}{P} = \frac{100 \times 50}{2} = 2500 \text{ rpm}$$

204

$$s = \frac{N_s - N_r}{N_s} = \frac{2500 - 2350}{2500}$$

$$s = 0.05$$


$N = ?$ at $\frac{1}{2} s_c$ $f = 90 \text{ Hz}$

$$N_s = \frac{100 \times 90}{2} = 4500$$

$$0.05 = \frac{4500 - N_r}{4500}$$

$$N_r = 4395 \text{ rpm} \quad (c)$$

R_a - in series with rotor

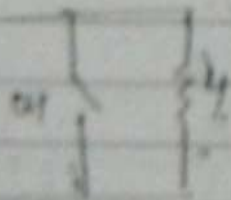

$$R_{eff} = R + 0.5 R_r (1 - \alpha)$$

$$= 2 + 0.5 \times 4 \left(1 - \frac{I_a}{I}\right)$$

$$= 2 + 0.5 \times 4 \left(1 - 4 \times 10^{-3} \times 200\right)$$

$$= 1.8 \quad (c)$$

(14) PF at $\frac{1}{2} N_s$?

$$N_s = N_s$$

$$PF = \frac{V_o}{V_{max}}$$

At $\frac{1}{2} N_s$

PF = $\frac{3}{\pi} \cos \alpha$ (28)

$$V_o = I_b + I_o \alpha$$

$$V_o = \frac{3 \sqrt{V_{ms}} \cos \alpha}{\pi} = I_b$$

$$\frac{3 \sqrt{V_{ms}} \cos \alpha}{\pi} = \frac{200 \times 440}{2}$$

$$\frac{3 \times 440 \sqrt{2} \cos \alpha}{\pi} = \frac{200 \times 440}{2}$$

$$\cos \alpha = \frac{\pi \times 1}{2 \sqrt{2} \times 3}$$

$$PF = \frac{3}{\pi} \cos \alpha = \frac{1}{\sqrt{2}} = 0.354 \text{ (A)}$$

(15) As $\alpha \uparrow$ ripple \uparrow smoothness \downarrow

At $\alpha \downarrow$ (smoothness of V_o waveform) \uparrow

$\alpha \downarrow$ $V_o \uparrow$: $\omega \uparrow$

high speed.


(16) Regenerated power = $V_o I_o$
 $= V_s (1 - \alpha) I_o$
 $= 600 (1 - 0.7) 100$
 $= 18 \text{ kW (c)}$

TRENDS IN TRANSMISSION OF POWER


1. EHVAC

206

Features -

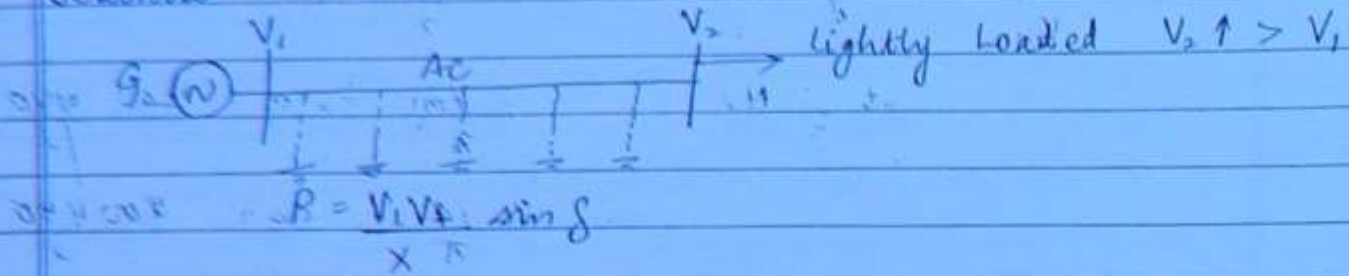

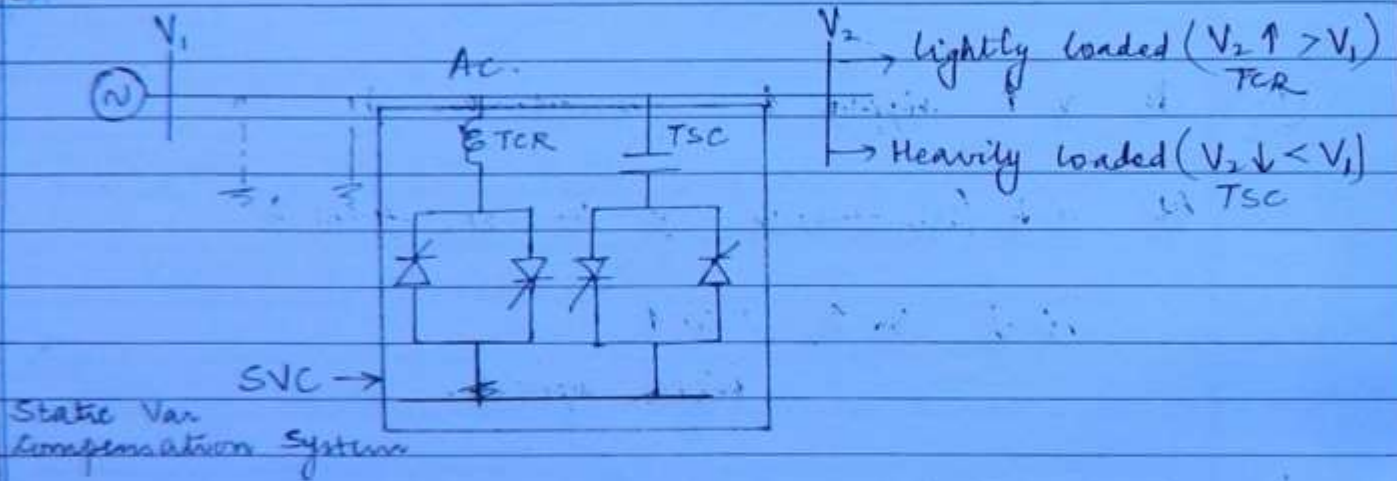* \rightarrow We cannot control the power flow magⁿ & dirⁿ quickly & easily



Thyristorised Controlled Reactor \rightarrow TCR

Thyristorised Switched Capacitance \rightarrow TSC



* \rightarrow There is continuous variation of reactive power flow in the line & hence responsible for voltage fluctuations & additional power loss

* \rightarrow Intermediate substations are installed in the AC line for every 200-300 kms to compensate the

reactive power as per the requirement of reactive power in the line.

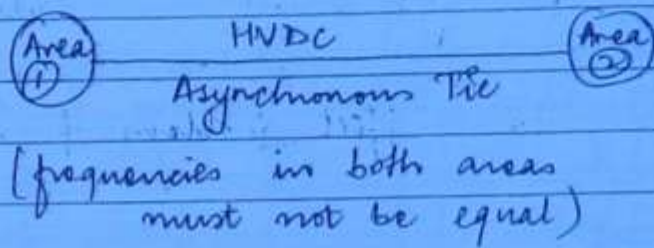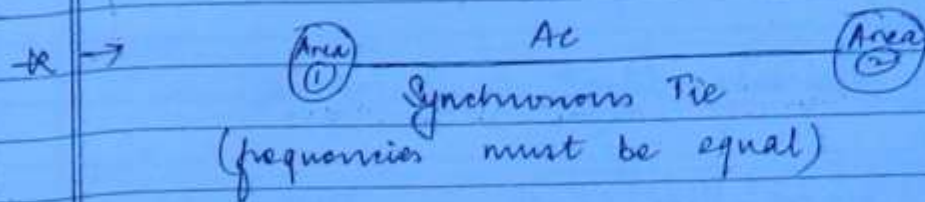(207)

- * → Other problems in the AC line is
 - Skin Effect
 - Corona loss.



- * → System disturbance in one of the area leads to power swings. If the power swings are unstable that may lead to cascaded tripping of alternators (if protection system fails)

- * → With AC interconnection frequency disturbance is carried forward to other areas.

- * → If multiple number of independent areas is interconnected by AC lines then the fault level of the system increases.

2. HVDC

* HVDC is economical to transmit large amount of power over long distance.

(2.08)

* Advantages -


1. The power flow magnitude & direction can be quickly and easily controlled.
2. The transient stability limit is improved.
3. We can fast clear the fault in HVDC line.
4. There is no Skin Effect problem & Corona loss is reduced.
5. HVDC can utilise Earth for its return path.
6. The phase to phase clearance, phase to ground clearance & tower height requirement is lesser in HVDC line.
7. Power handling capacity of a Bipolar HVDC line is almost twice that of 3 ϕ single circuit AC line.
8. We can interconnect independent areas at different frequencies because it is an asynchronous tie.
9. Frequency disturbance is not transferred to other independent areas, with HVDC interconnection.
10. If multiple no. of independent areas is

i interconnected by HVDC line the fault level of the system will not substantially increase. (209)

ii HVDC is used for underground or submarine cables even for short distance because there is no continuous charging of DC cables.

* Types of HVDC

BIPOLAR

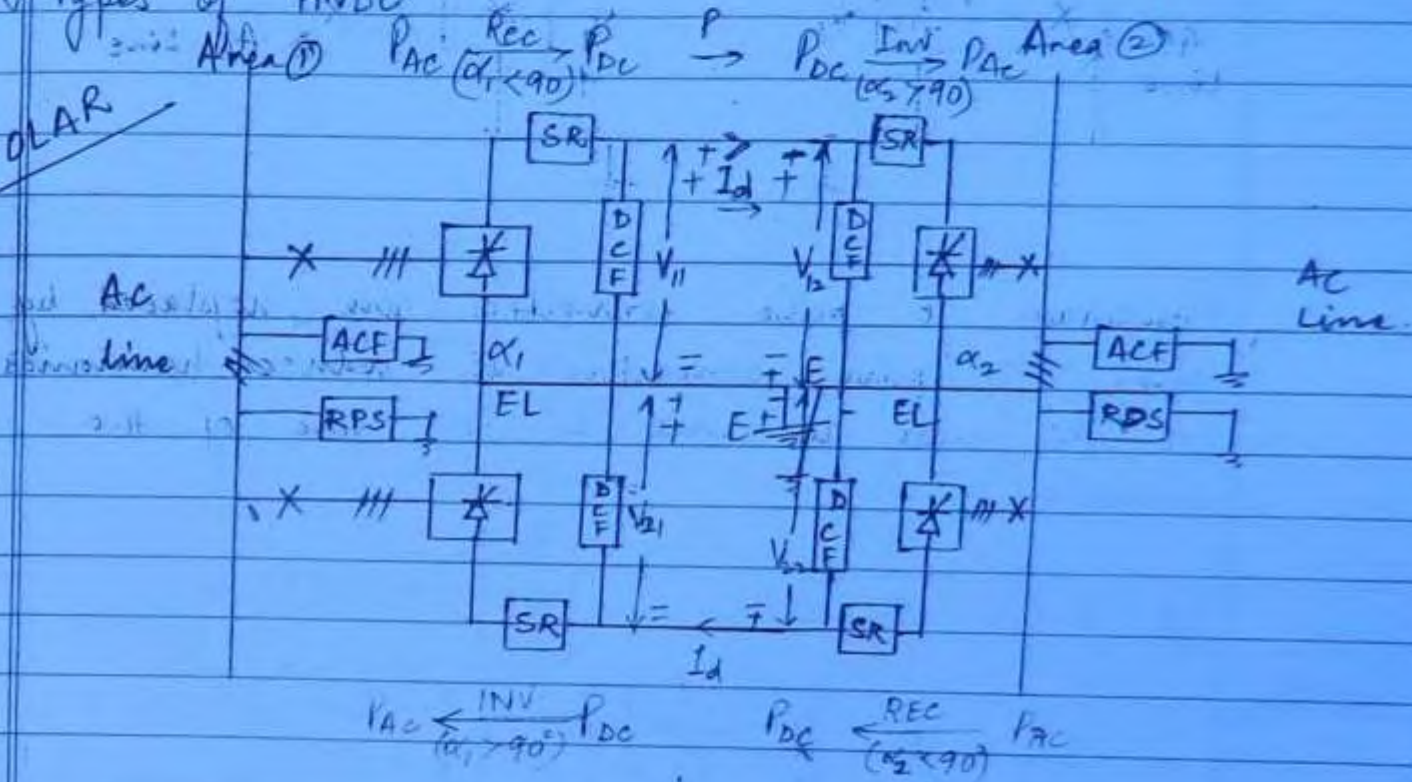

Smoothing Reactor (SR)

Used for smoothing

DC Filter (DCF)

Reduces harmonics on DC side of the converter (output side)

AC Filter (ACF)

Reduces harmonics on AC side of the converter


Reactive Power Source (RPS)

(216)

to compensate the reactive power required for converters

MONOPHASE Area ①


Area ②




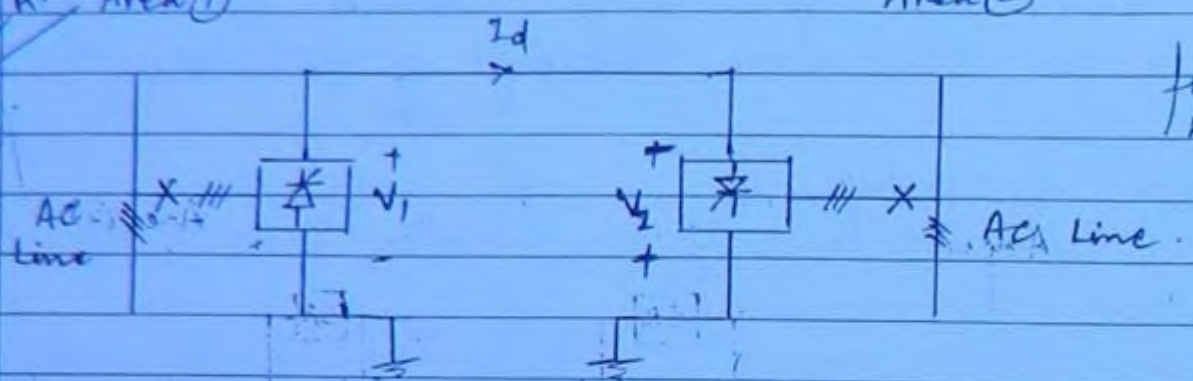


filters are understood

Nowadays 6 pulse converters are replaced by 12 pulse converters to reduce harmonics on AC side as well as DC side of the converter.

12 Pulse Converters -

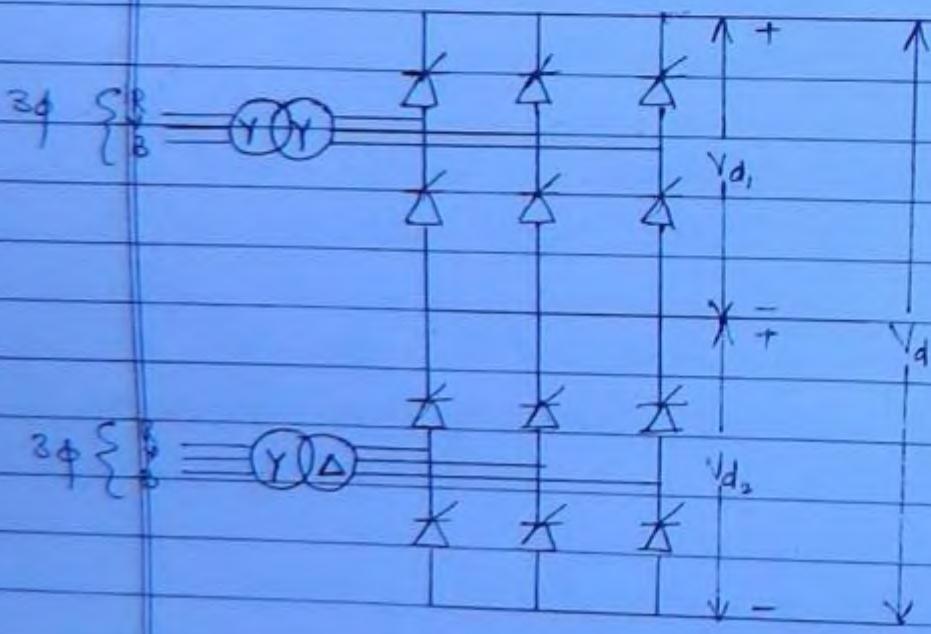

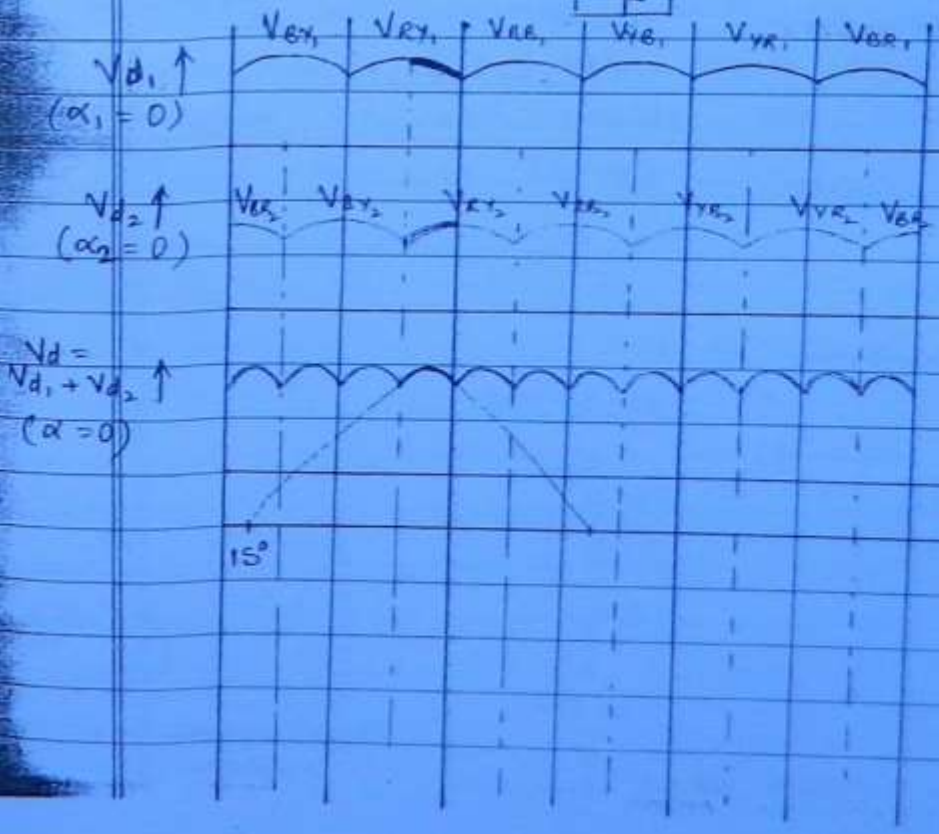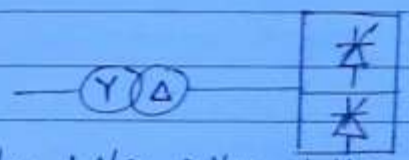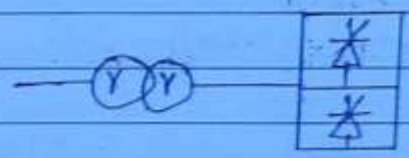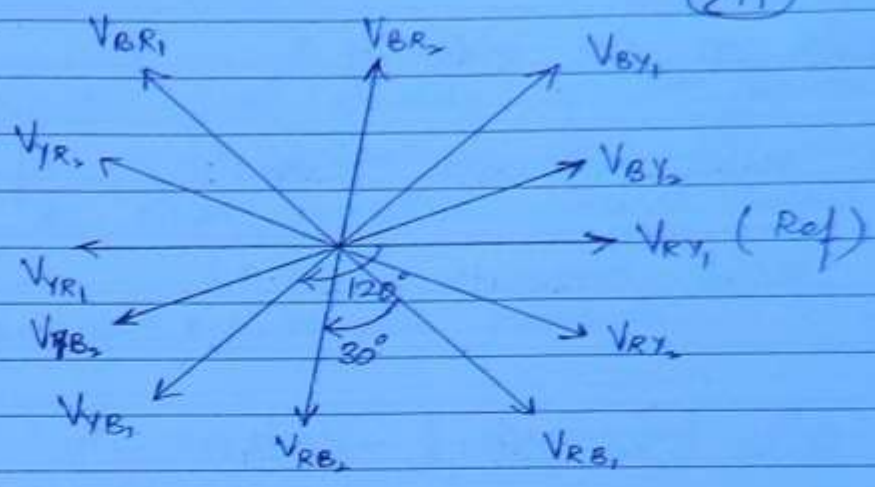

$$V_{RY1} = V_{ML} \sin \omega t$$

$$V_{RY2} = V_{ML} \sin(\omega t - 30^\circ)$$

$$V_{RY} = V_{RY1} + V_{RY2}$$

$$= V_{ML} [\sin \omega t + \sin(\omega t - 30^\circ)]$$

$$= V_{ML} [\sin(\omega t - 15^\circ)]$$

* Harmonics on AC side of δ

m pulse converter $\rightarrow mk \pm 1$

2 pulse converter $\rightarrow 2k \pm 1$
 $= 3, 5, 7, 9, 11, \dots$

6 pulse converter $\rightarrow 6k \pm 1$
 $= 5, 7, 11, 13, 17, 19, \dots$

12 pulse converter $\rightarrow 12k \pm 1$
 $= 11, 13, 23, 25, \dots$

* Harmonics on DC side of δ

m pulse converter $\rightarrow mk$

2 pulse converter $\rightarrow 2k$
 $= 2, 4, 6, 8, 10, 12, \dots$

6 pulse converter $\rightarrow 6k$
 $= 6, 12, 18, \dots$

12 pulse converter $\rightarrow 12k$
 $= 12, 24, 36, \dots$


SMPS


(213)

- * SMPS provides good quality of DC power supply required for some applications like ICs, digital circuits & other sensitive circuit boards.
- * SMPS operates on chopper principle.
- * At very high switching frequency, the ripple is almost reduced.
- * At such a high frequency we can reduce the size of the filter as well as transformer.
- * In SMPS the transistor operates in the switched mode (cut-off region is used for OFF state & saturation region for ON state)
- * SMPS is more efficient & compact in size compared to linear power supplies. In linear power supplies transistor operates in the active region & hence power loss is higher.

Types of SMPS -

1. Flyback converter

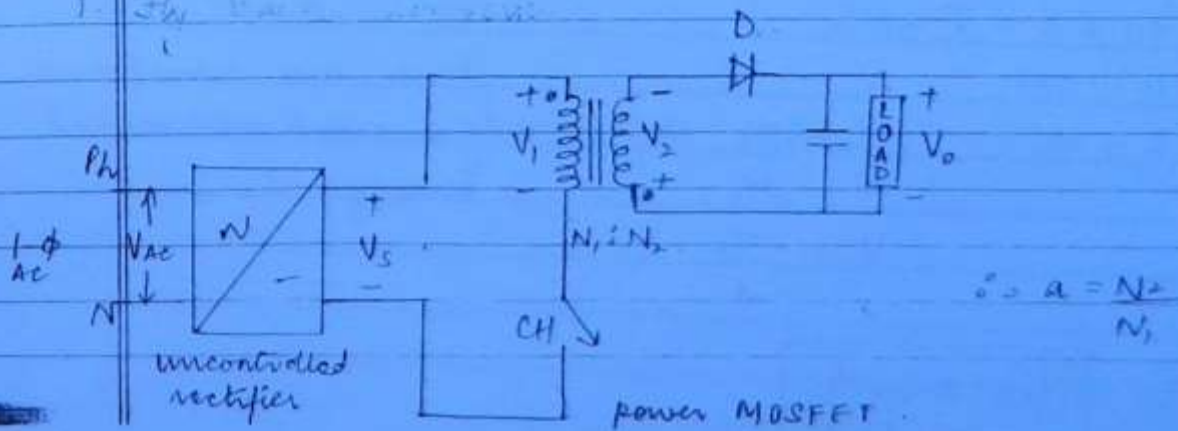

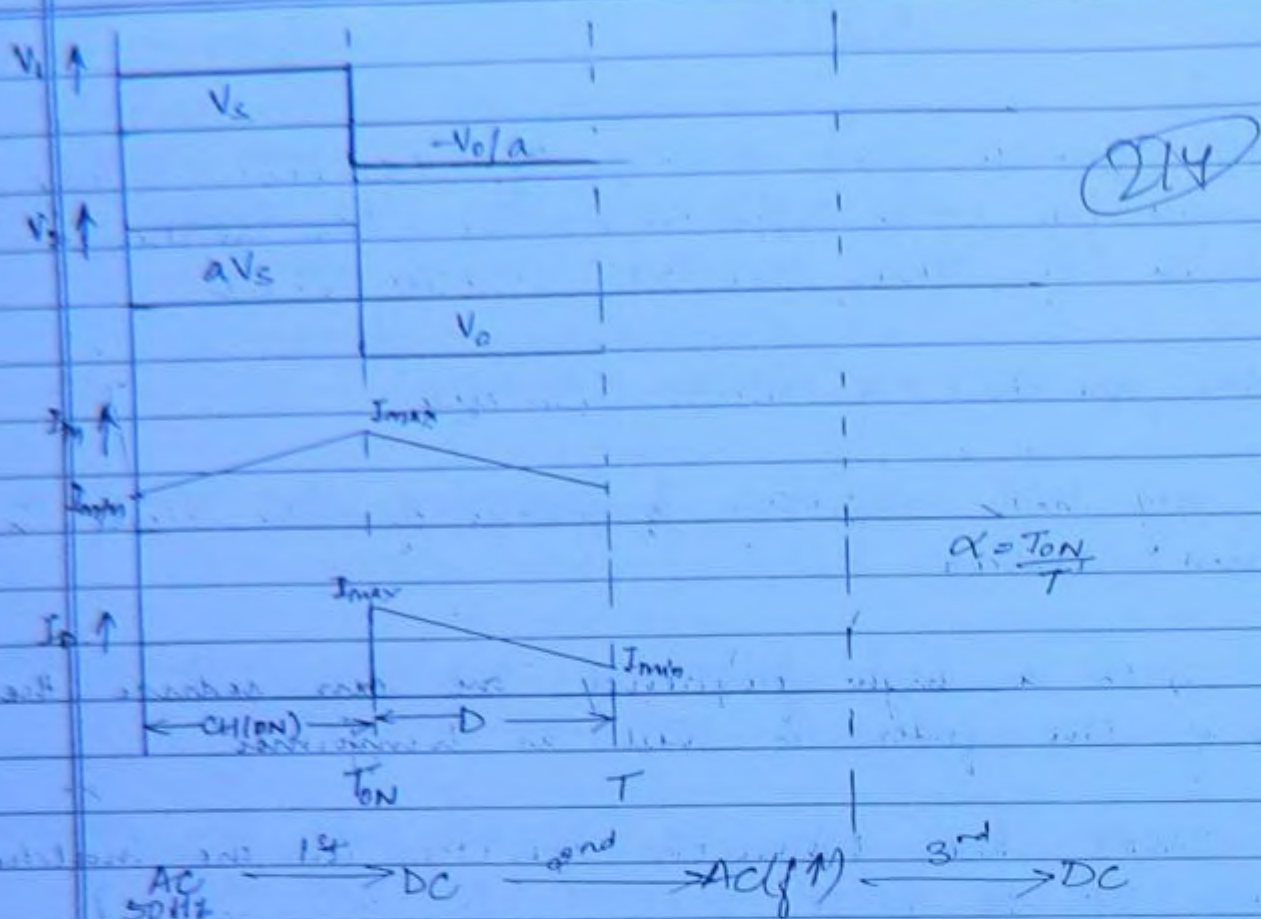

① $0 \leq t \leq T_{ON}$

CH \rightarrow ON $\quad V_1 = V_s$
 D \rightarrow OFF $\quad V_2 = \frac{N_2}{N_1} V_1$

$V_2 = a V_1$

Transformer stores energy $\therefore I_m \uparrow$

CH is in ON state

D is RD $\therefore I_D = 0$

② $T_{ON} \leq t \leq T$

CH \rightarrow OFF $\quad V_2 = -V_o$
 D \rightarrow ON $\quad V_1 = \frac{N_1}{N_2} V_2$
 $V_1 = -\frac{V_o}{a}$

Here the transformer releases the stored energy $\therefore I_m \downarrow$

Avg $\Rightarrow \boxed{V_o = a \frac{\alpha V_s}{1-\alpha}}$

CWB chapter 7.

$$(4) \quad V_o = \frac{\alpha a \cdot V_s}{1 - \alpha} \quad (215)$$

$$= \frac{\alpha \cdot N_2 \cdot T_{ON}}{N_1 \cdot T_{OFF}} \quad (c)$$

Peak Forward Blocking Voltage of chopper switch

$$= V_s + \frac{V_o}{a}$$

$$(3) \quad \text{PFB v/g} = \frac{V_s + V_o}{a}$$

$$= V_s + V_s \left(\frac{\alpha}{1 - \alpha} \right)$$

$$= V_s \left[1 + \frac{\alpha}{1 - \alpha} \right] = 115\sqrt{2} \left[1 + \frac{0.3}{1 - 0.3} \right]$$

$$= 232.34 \text{ V} \quad (a)$$

Output dc v/g of front end section

→ without v/g doubling = V_m → peak ac i/p v/g


→ with v/g doubling = αV_m

(1) mark the highest freq given

2. Push-pull converter

216

3 Full Bridge Type -

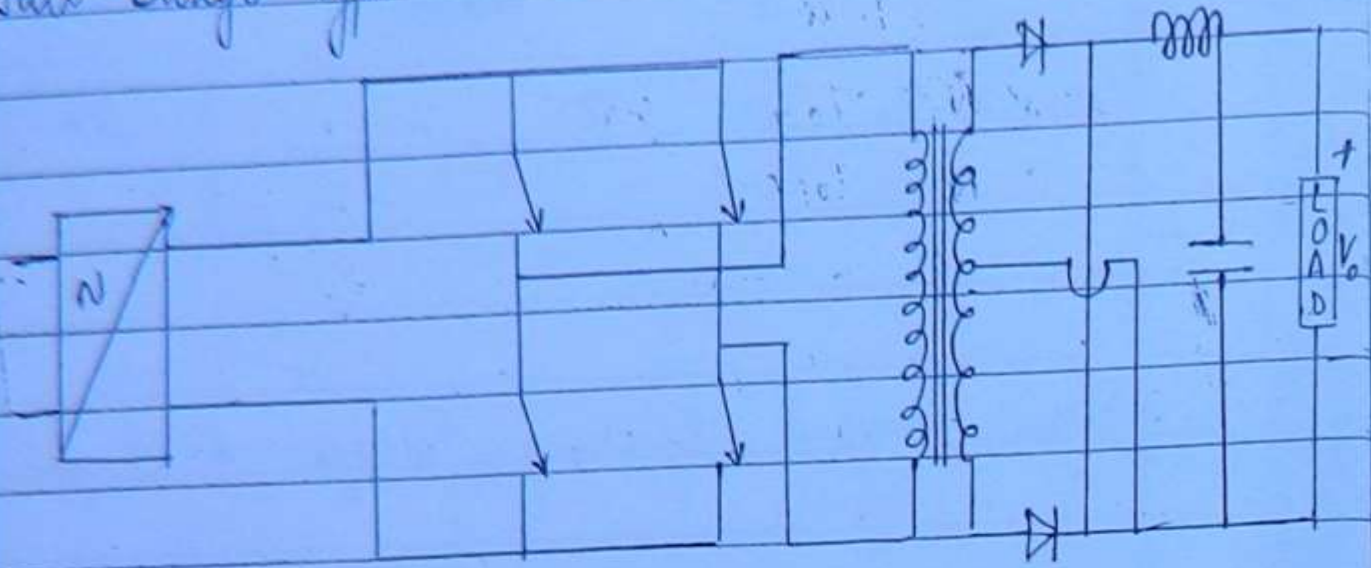

$V_o = \dots$

\dots

Remembering Formulas -

(217)

R-load -

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha) \rightarrow 1 \text{ pulse}$$

cont. $V_o \propto \cos \alpha$
discont $V_o \propto (1 + \cos \alpha)$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha) \rightarrow 2 \text{ pulse}$$

$$V_o = \frac{V_{mph}}{2\pi/3} [1 + \cos(\alpha + 30^\circ)] \rightarrow (\alpha > 30^\circ) \text{ 3 pulse.}$$

In 3 pulse
↳ $\alpha < 30^\circ$ cont.
↳ $\alpha > 30^\circ$ discont.

$$V_o = \frac{V_{mph}}{2\pi/6} [1 + \cos(\alpha + 60^\circ)] \rightarrow (\alpha > 60^\circ)$$

In 6 pulse.
↳ $\alpha < 60^\circ$ cont.
↳ $\alpha > 60^\circ$ discont.

$$V_o = \frac{V_{ML}}{\pi/6} [1 + \cos(\alpha + 60^\circ)] \rightarrow (\alpha > 60^\circ)$$