

POWER ELECTRONICS & PLC

(Diploma 5TH SEM)



Education for a World Stage

Prepared by
Mr. PRANJADIPTA SAHOO
Asst. Professor
Electrical Engineering
NM INSTITUTE OF ENGINEERING & TECHNOLOGY

214

219

3

-: HAND WRITTEN NOTES:-
OF
ELECTRICAL ENGINEERING

①

-: SUBJECT:-
POWER ELECTRONICS

3

TOPICS

1. Power semiconductor devices - 25%
2. Phase controlled rectifiers - 35%
Application → DC drives
→ Charging batteries
→ Solar batteries
3. Inverters - 12%
4. Choppers - 12-15%
5. AC Voltage controllers & cycloconverters - 3 to 4%
6. Other applications - 7-10%
→ AC Drives
→ HVDC
→ SMPS

③

Power Electronics - deals with control & conversion of high power applications.

Power Semiconductor devices - should be capable to handle large magnitudes of power

eg Power diode, SCR(PN), LASCR, GTO, ASCR, RCT, TRIAC, DIAC, Power transistors (BJT, MOSFET, IGBT, $f \uparrow$)

Signal Electronics - deals with control of low power applications.

Signal Devices - handle low power & very high switching frequencies

eg Signal diodes $\rightarrow$ Zener diode
 $\rightarrow$ LEDs
 $\rightarrow$ Varactor diode

Signal transistors $\rightarrow$ BJT
 $\rightarrow$ MOSFET
 $\rightarrow$ UJT etc.

* In the fabrication of semiconductor devices we must sacrifice one quality in order to improve the other quality


eg If the device operates at very high switching frequency the power rating is reduced.

* A switch can be utilized in 4 different modes but all the devices need not operate in all the 4 modes


* FOUR MODES OF A SWITCH (Ideal)

1. Forward Blocking Mode


(S)

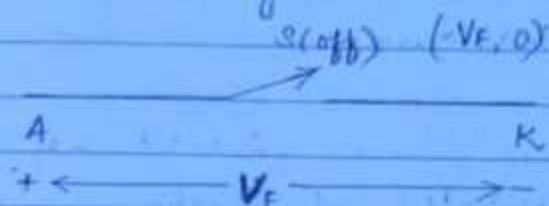



2. Forward Conduction Mode

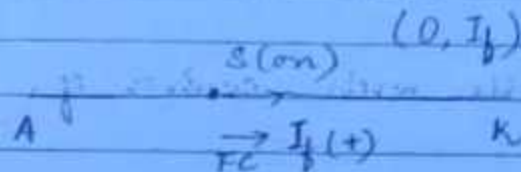

3. Reverse Blocking Mode

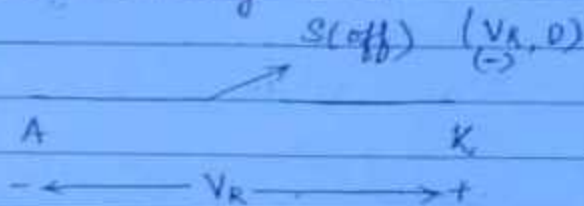


4. Reverse Conduction Mode

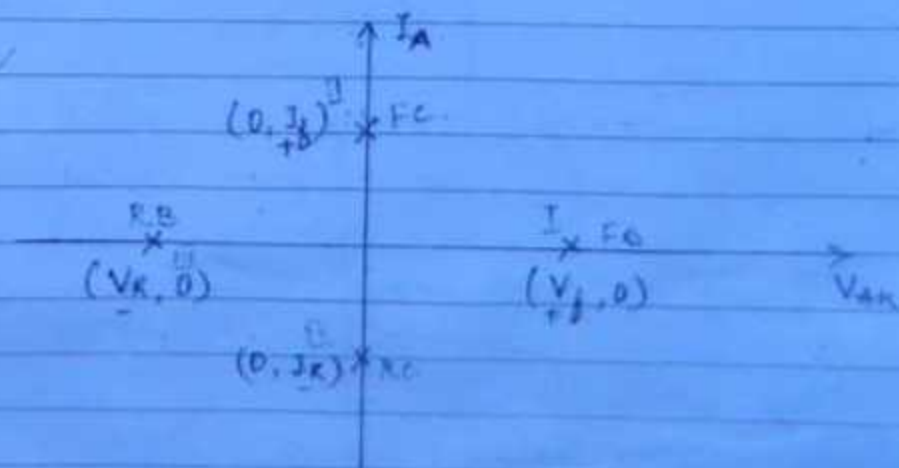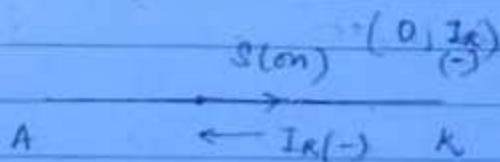

- * TRIAC will support all four modes of operation.
 $\therefore$ It is treated as an AC switch. (AC $\rightarrow$ AC)
 Applications $\rightarrow$ AC voltage controller (6)

- * SCR is a DC switch because it will not support reverse conduction.



POWER DIODE -

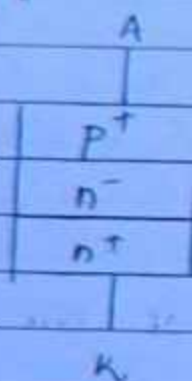


+ $\rightarrow$ heavily doped layer
 - $\rightarrow$ lightly doped layer

{ drift region

Signal Diode -

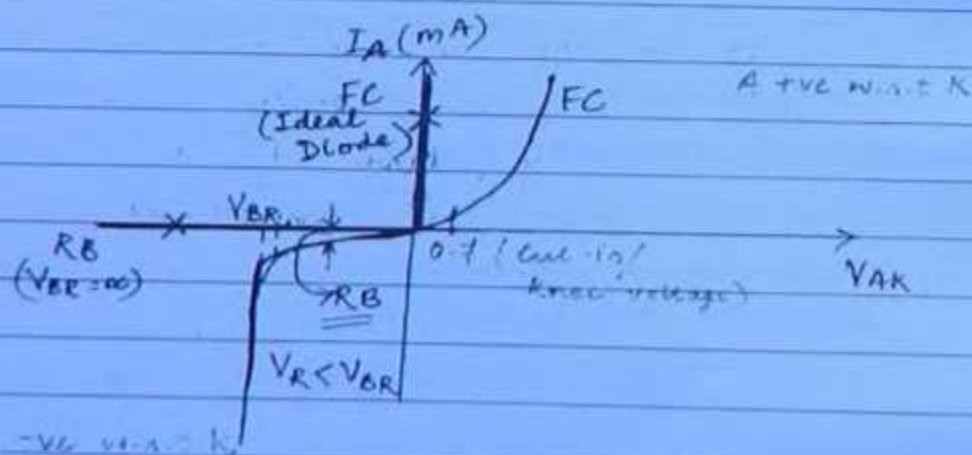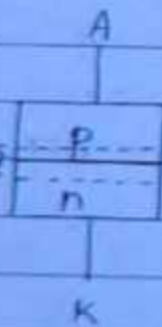

Power Diode -

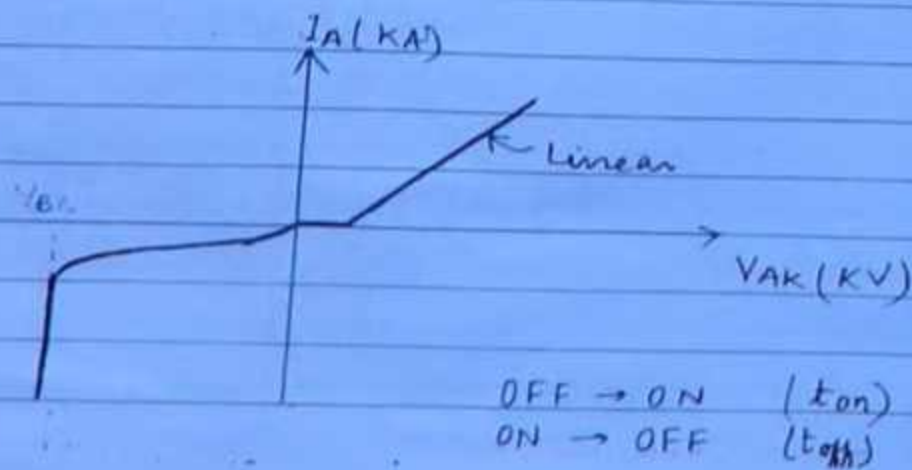

OFF $\rightarrow$ ON (t_{on})
 ON $\rightarrow$ OFF (t_{off})

Significance of drift region -

(7)


- * The thickness of the depletion layer decides the reverse blocking voltage capability.
- * The thickness of the depletion layer $\uparrow$ due to the n^- region (depletion layer penetrates more deeper into the lightly doped layer to equilibrate the charge) This $\uparrow$ the reverse blocking capability of the diode.

reverse current $\rightarrow$ $NR \uparrow$

REVERSE RECOVERY CHARACTERISTICS -

- * Explains the switching behaviour of the diode from ON time to OFF time.
- * When diode is conducting some excess is stored in the device. These excess charge carriers are mainly due to the minority carriers. When diode is switching from ON $\rightarrow$ OFF, the excess charge carriers are still present in the device after anode current becomes 0.
- * In order to remove these excess charge carriers and acquire equilibrium state, recombination process takes place & hence reverse current flows in the device until all the excess charge carriers are removed from the device.
- * This process is known as Reverse Recovery Process & the transition time during this process is known as Reverse Recovery Time (t_{rr}).

(8)

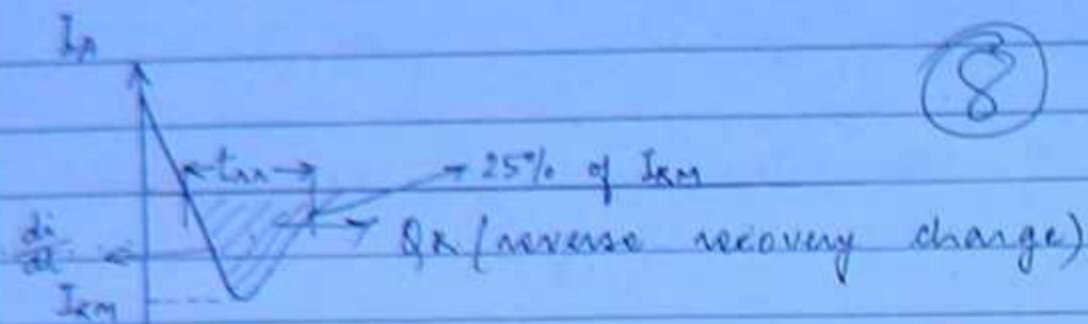

$t=0$

ON $\rightarrow$ OFF

$t_{on} \rightarrow (I_A = 0) \rightarrow t_{off} (\downarrow I_A = 25\% I_{RM})$

$$I_{RM} = \left[\frac{Q_R (di/dt)}{t_{on}} \right]^{1/2}$$

$$t_{on} = \left[\frac{Q_R}{di/dt} \right]^{1/2}$$

$\leftarrow Q_R$ depends on I_A .

$$I_A \uparrow \rightarrow Q_R \uparrow$$

$$\therefore I_{RM} \uparrow \text{ f thus } t_{on} \uparrow$$

$\leftarrow$ The t_{on} decides the switching frequency of the diode.
 $t_{on} \uparrow \Rightarrow f_s \downarrow$

Classification of Power Diodes based on Reverse Recovery Time (t_{rr}):

1. General Purpose Diode
2. Fast Recovery Diode
3. Schottky Diode

(Slow)

(High speed)

General Purpose Diodes

Fast Recovery Diode

Schottky Diode

(9)



- | | General Purpose Diodes | Fast Recovery Diode | Schottky Diode |
|----|---|---|---------------------------------------|
| 1. | $t_{rr} \rightarrow 25 \mu s$ | $t_{rr} \rightarrow 5 \mu s$ (Less) | $t_{rr} \rightarrow$ nano secs |
| 2. | Rating $\rightarrow$ 1A to several 1000s of A | Rating $\rightarrow$ 1A to several 100 of A | Rating $\rightarrow$ limited to 300 A |
| x | $V_{rating} \rightarrow 50V$ to 5kV | $V_{rating} \rightarrow 50V$ to 3kV | $V_{rating} = 100V$ |

- x In fast recovery diodes, the layers are doped with gold / platinum.
- x Gold / platinum doping reduces the lifetime of charge carriers & increases the speed of recombination. This reduces the reverse recovery time.
- x Used in choppers & inverters
- x Schottky diode is a metal to semiconductor junction diode. Here the conduction is only due to majority carriers.
- x Since there is no minority charge carriers the t_{rr} delay is very much reduced. $\therefore$ it operates at very high switching frequency.
- x Due to the absence of drift region, the thickness of depletion layer is reduced. $\therefore$ it can block a small reverse voltage limited to 100V.
- x Can be used in low power high switching frequency applications.
eg Switch Mode Power Supply (SMPS)
- x Used in uncontrolled rectifiers, free wheeling diode for rectifiers.


* Diode is an uncontrolled device because there is no control terminal to decide its on/off state.

(10)

SCR -

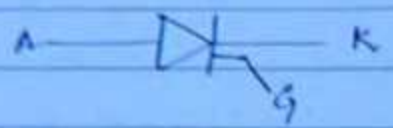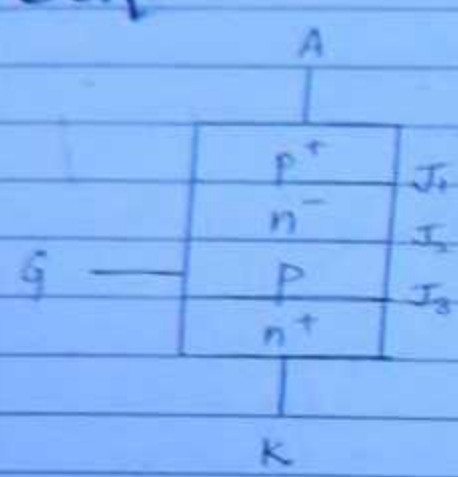

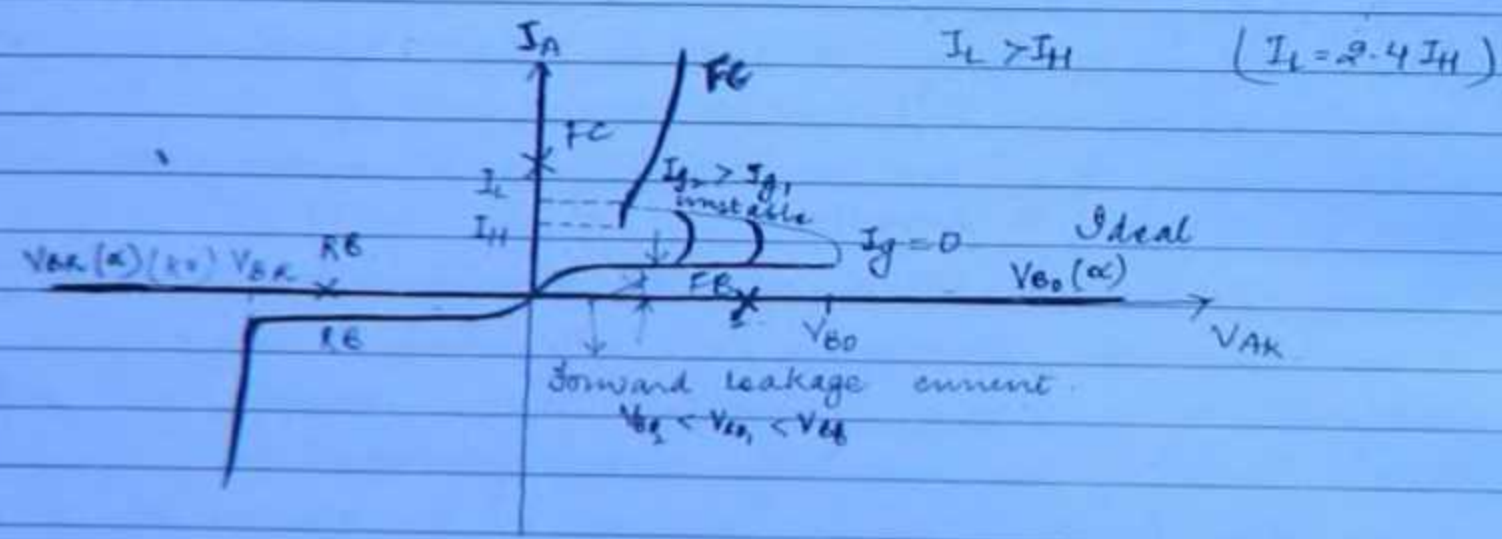A, K $\Rightarrow$ main terminals
 G $\Rightarrow$ control terminals
 (on) There is no control of gate when SCR is ON.
 Partially controlled device



Forward Blocking Mode - A +ve w.r.t K

$J_1, J_3 \Rightarrow FB$


$J_2 \Rightarrow RB$

$\therefore$ SCR $\rightarrow$ OFF

Forward Conduction Mode

(forward breakdown voltage)
 $V_{AK} \uparrow \Rightarrow V_{BO}$ then breakdown occurs at J_2 $\therefore$ SCR $\rightarrow$ ON

Significance of gate signal -

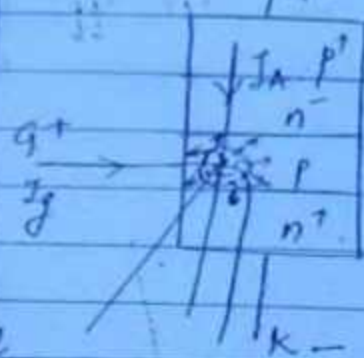

When gate signal is applied, charge gets accumulated in depletion region p. $I_A \uparrow$ and $\uparrow$ the charge accumulation as it gets a conduction path. This leads to $\uparrow$ of charge & thus breakdown of depletion region turning on the SCR.

If $I_g \uparrow \Rightarrow \frac{dI_g}{dt} \uparrow$ Initial conduction Area $\uparrow$

$\Rightarrow \frac{dI_A}{dt} \uparrow$ and lesser V_{tg} is used for breakdown i.e. less V_{co}

Reverse Blocking Mode -

A receives -ve w.r.t K

$J_2 \rightarrow FB$

$J_1, J_3 \rightarrow RB$

SCR $\rightarrow$ OFF

Significance of Latching Current -

Latching current is related to turn on process

When SCR is in the ON state, gate signal is removed to avoid the continuous gate power loss


If we remove the gate signal when $I_A < I_L$ then SCR fails to turn ON i.e. we must maintain the gate pulse width until I_A reaches I_L just above certain minimum value (Latching current)

When we remove gate signal, when $I_A > I_L$ then

Let continuous SCR continues to be the ON state.

Q What is the minimum gate pulse width required to turn on the SCR in the following circuit.

$$I_L = 100 \text{ mA}$$

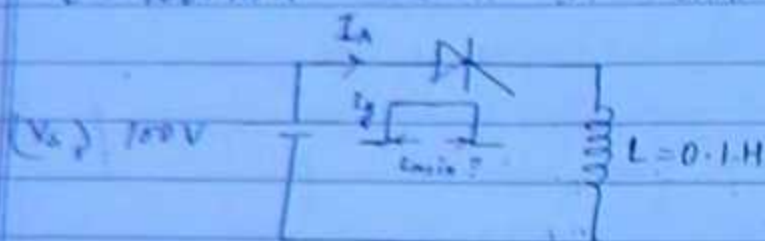

sol

$$V_s = L \frac{di_a}{dt}$$

$$\int di_a = \int \frac{V_s}{L} dt$$

$$I_A = \frac{V_s}{L} t \quad \Rightarrow \quad t_{\min} = \frac{I_A \times L}{V_s}$$

$$t_{\min} = \frac{I_L \times L}{V_s} = \frac{100 \times 10^{-3} \times 0.1}{100}$$

$$t_{\min} = 100 \mu\text{sec.}$$

* The minimum gate pulse width requirement to turn on the SCR depends on the load parameters.

eg. $L \uparrow \Rightarrow t_{\min} \uparrow$

Load is $R = 20 \Omega$ $L = 0.1 \text{ H}$ in prev ques.

$$V_s = L \frac{di_a}{dt} + R I_A$$

$$I_A = \frac{V_s}{R} (1 - e^{-t/\tau})$$

$$\tau = \frac{L}{R} = \frac{0.1}{20} = \frac{1}{200}$$

$$I_A = 5 (1 - e^{-200t})$$


$$I_L = 5 (1 - e^{-200 t_{\min}})$$

$$t_{\min} = 101 \mu\text{s}$$

Significance of Holding Current -

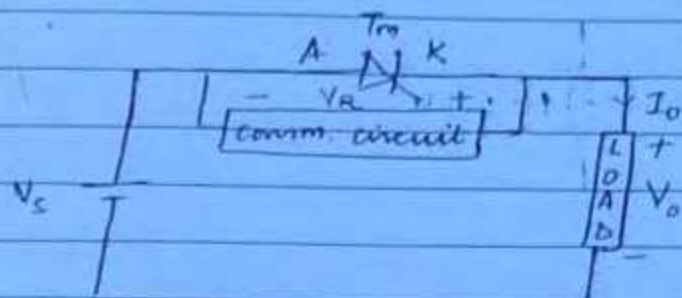(13)

Holding current is related to turn OFF process. Gate has no control to turn OFF SCR. In some cases we require commutation circuit to turn OFF SCR.



Comm ckt forces anode current to reduce below I_H . After that it applies reverse voltage to remove all charge carriers ~~from~~ ⁱⁿ the device.

* Procedure to turn OFF SCR using a commutation ckt -

Commutation circuit forces anode current to reduce below a certain minimum value I_H then it applies a reverse voltage across the SCR at least for a period of device turn off time or greater than that.

Circuit turn off time t_{co} -

It is the time for which the comm circuit applies a reverse voltage across after the anode current becomes 0. It

Device turn off time t_{rr} -

It is the time taken to remove charge carriers present in the device provides the t_{rr} .

will turn on before applying gate (behaves as diode)

Page

[For successful commutation $t_c > t_q$ always]

If $t_c < t_q$ commutation fails

(14)


Q What do you mean by commutation failure?

Ans If $t_c < t_q$ some excess charge carriers are still present in the device. For the next operation to turn on the SCR if A +ve w.r.t K, SCR will turn on before the gate signal is given. Here the SCR is losing forward blocking capability behaving as a diode. This is known as commutation failure.


To avoid this problem, the commutation circuit should apply reverse voltage across the SCR atleast for a period of t_q or greater than that.

Holding current is the minimum I_a below which the SCR becomes off and regains the forward blocking capability if a reverse voltage is applied across SCR atleast for a period of t_q or more than that.

Switching Characteristics of SCR -

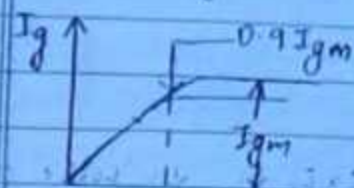

(15)

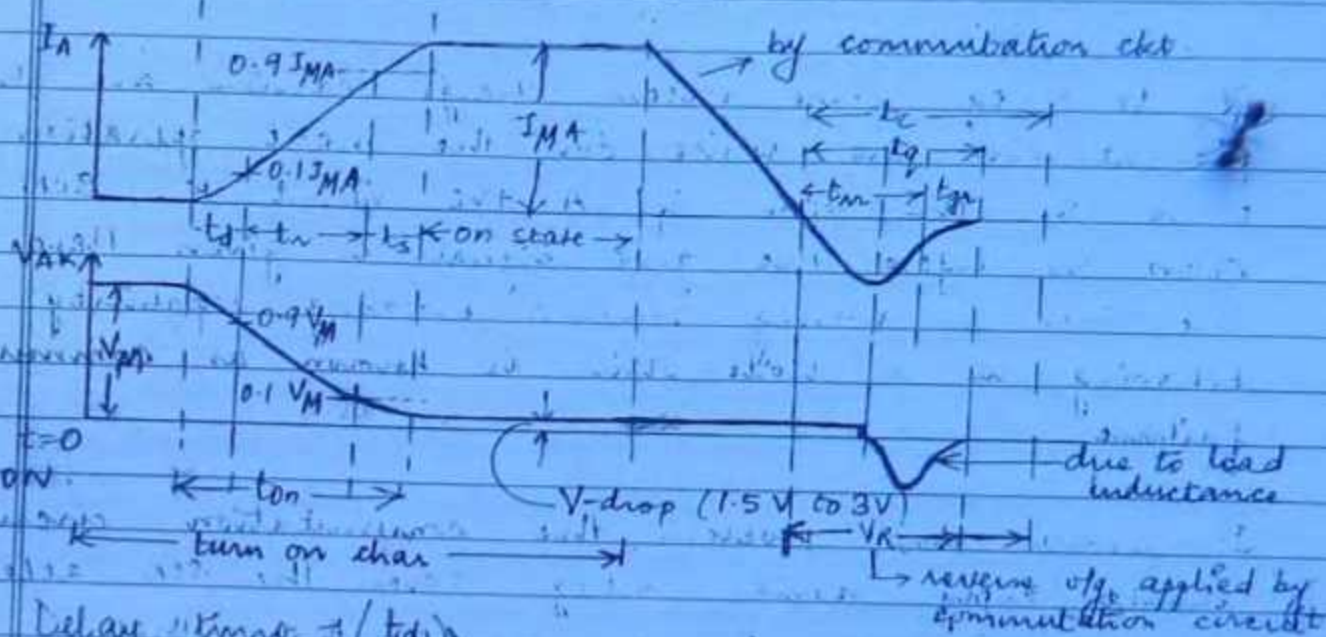

Delay time t_d

depends on gate signal magnitude & dI_g/dt of gate signal magnitude.

Delay time $\Rightarrow$ $0.9 I_{g_m}$ to $0.1 I_{MA}$
 $0.9 I_{g_m}$ to $0.9 V_M$

Delay time depends on $\Rightarrow I_g \uparrow$ & $\frac{dI_g}{dt} \uparrow \Rightarrow t_d \rightarrow 0N$
 $\therefore t_{on} \downarrow$

$\Rightarrow$ (initial conduction area) $\uparrow$
 $\frac{dI_a}{dt} \uparrow$ initial state
 $t_d \downarrow$


For successful commutation $t_c > t_q$

$$t_c = SF \cdot t_q$$

$SF > 1$ for successful comm.
(safety factor)


TURN-ON / TRIGGERING METHODS OF SCR -

1. Forward voltage triggering -

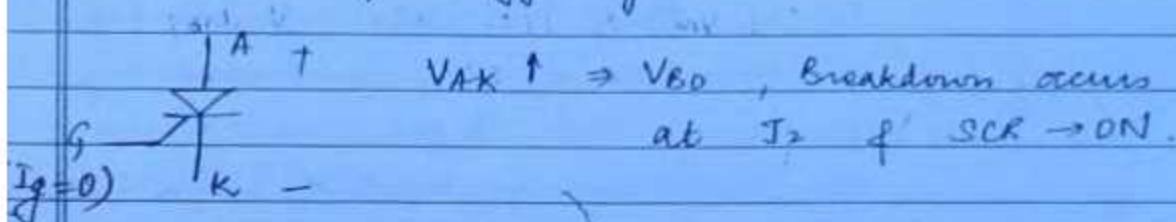

This method is generally not preferred because the SCR may get destroyed due to high power loss when triggered at high voltage.

2. $\frac{dv}{dt}$ triggering -

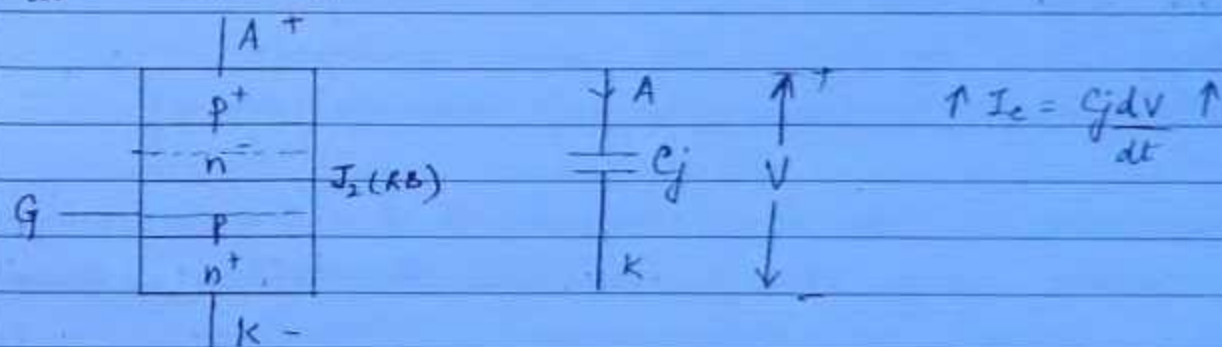


At high $\frac{dv}{dt}$ the charging current increases. If the increase in charging current is more than the latching current then SCR is turned on.

Critical $dv/dt \rightarrow$ Is the dv/dt at which SCR will turn on. At critical dv/dt charging current is equal to latching current $I_c = I_L$.

(18)

3. Light triggering -

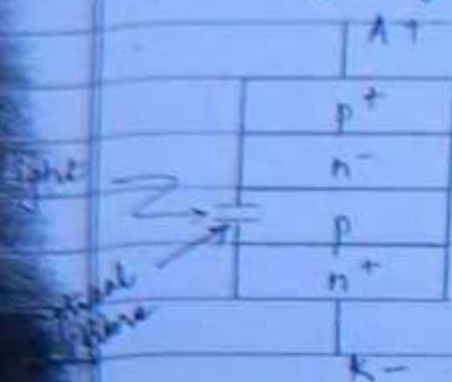

When light radiation is incident near the depletion layer then more number of e^- -hole pairs are produced by absorbing the light energy in the depletion layer, & this initiates the turn on process.

Application $\rightarrow$ Used in LASCRs for HVDC applications.

Thermal triggering -

When temperature is increased near the reverse biased gate junction, then the device is initiated to turn on by e^- -hole pairs produced in depletion layer absorbing the thermal energy.


Semiconductors are very sensitive & the character of the device may change as the temperature changes, so this method is not used.

Gate triggering -

(a) Continuous Gate Triggering -

Continuous gate signal is applied until the SCR is expected to be in the ON state. This is not efficient triggering due to continuous gate power loss.

(b) Pulse gate signal -

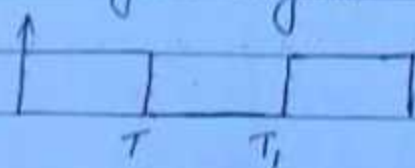

(79)


T = gate pulse width

$T > t_{min}$

T_1 → time period

$$\delta = \frac{T}{T_1} = \text{duty cycle}$$

(c) High frequency gate signal

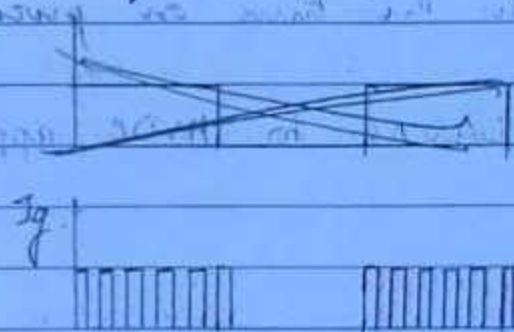



Adv

→ reduces the size of pulse transformer



provides electrical isolation b/w high power main circuit & low power gate firing circuit.

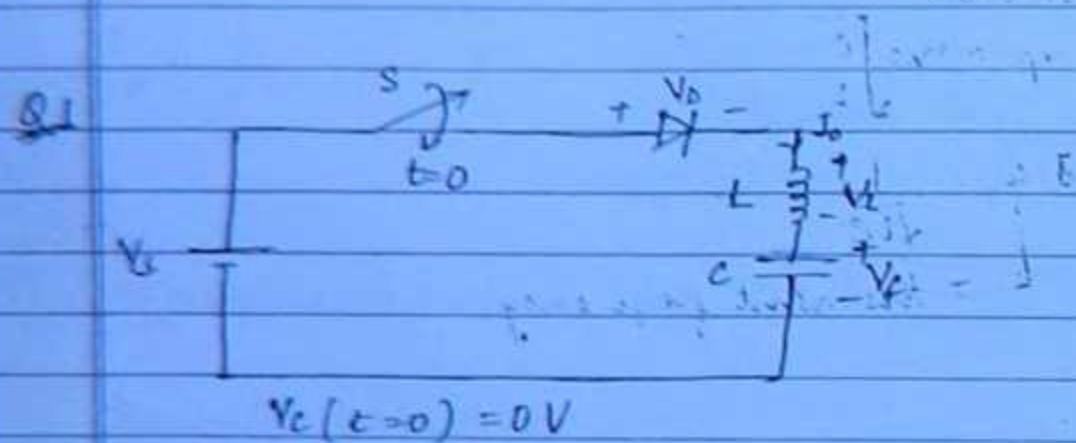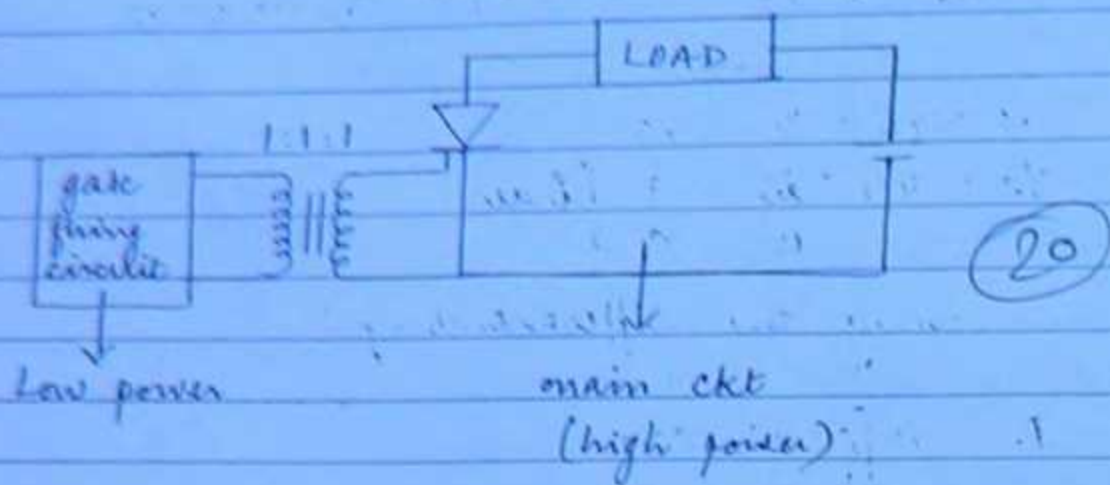→ we can trigger more than one SCR using a pulse transformer.



- i) When switch is closed at $t=0$ then diode conducts +
- $\frac{V_s}{\pi} \sqrt{LC}$
 - $\pi \sqrt{LC}$
 - $\frac{V_s}{\pi} \sqrt{LC}$
 - $2\pi \sqrt{LC}$
- ii) $V_C = ?$ when diode stops conducting
- V_s
 - $2V_s$
 - $-V_s$
 - $-2V_s$

3d i) $S \rightarrow ON$ ($t=0$) $P \rightarrow D=FB$ (on at $t=0$)

$$V_s = V_D + V_L + V_C$$

$$V_s = 0 + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

(21)

on solving the differential eq.


$$I_o = V_s \sqrt{\frac{C}{L}} \sin \omega_0 t$$

$$I_o = I_p \sin \omega_0 t$$

$$\text{where } I_p = V_s \sqrt{\frac{C}{L}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Resonant frequency

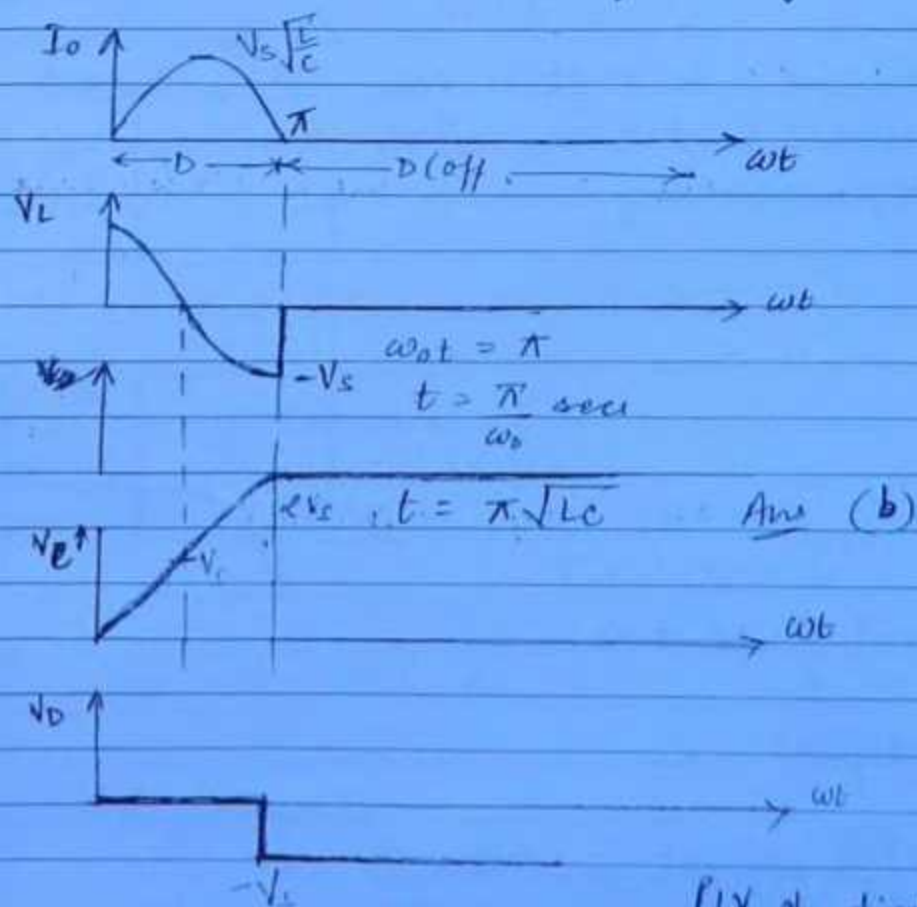

PIV of diode = V_s

$$V_L = L \frac{dI}{dt}$$

$$= L \frac{d(I_p \sin \omega t)}{dt}$$

$$V_L = V_s \cos \omega t$$

$$V_C = V_s - V_L$$

$$= V_s - V_s \cos \omega t$$

$$V_C = V_s (1 - \cos \omega t)$$

$$-V_s + V_D + 0 + 2V_s = 0$$

$$V_D = -V_s$$

(22)

From 0 to 90°

$$\text{Source} \rightarrow \frac{1}{2} LI^2 + \frac{1}{2} CV^2$$

From 90 to 180°

$$\frac{1}{2} LI^2 \rightarrow \frac{1}{2} CV^2$$

2. In prev ques assume $V_C(t=0) = V_0$ volts where $V_0 < V_s$.
 i) When switch is closed at $t=0$ sec what's the cap v/g (V_C) after the diode stops conducting.

- a) $\frac{1}{2}(V_s + V_0)$
- b) $\frac{1}{2}(V_s - V_0)$
- c) $\frac{1}{2}V_s + V_0$
- d) $\frac{1}{2}V_s - V_0$

$$S \rightarrow ON (t=0)$$

$$D = FB$$

$$V_s = 0 + L \frac{di}{dt} + \frac{1}{C} \int i dt + V_0$$

$$V_s - V_0 = L \frac{di}{dt} + \frac{1}{C} \int i dt$$

$$I_0 = (V_s - V_0) \sqrt{\frac{C}{L}} \sin \omega t$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$I_0 = I_p \sqrt{\frac{C}{L}} \sin \omega t$$

$$V_L = L \frac{d(I_p \sin \omega t)}{dt}$$


$$V_L = (V_s - V_o) \cos \omega t$$

$$V_c = V_s - V_L$$

$$= V_s - (V_s - V_o) \cos \omega t$$

$$V_c = V_s(1 - \cos \omega t) + V_o \cos \omega t$$


(23)

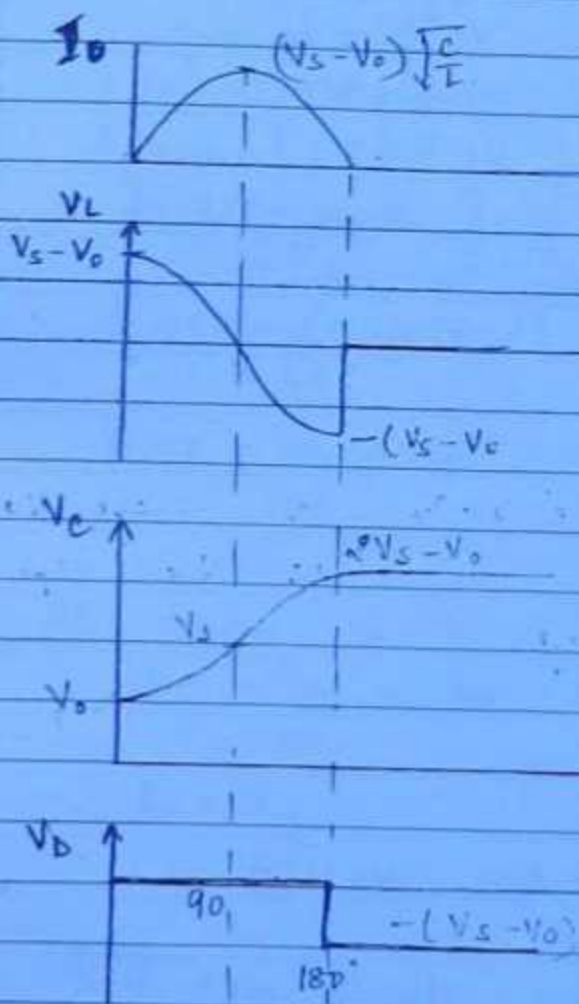

$$PIV = V_s - V_o$$

Ans $V_c = qV_s - V_o$

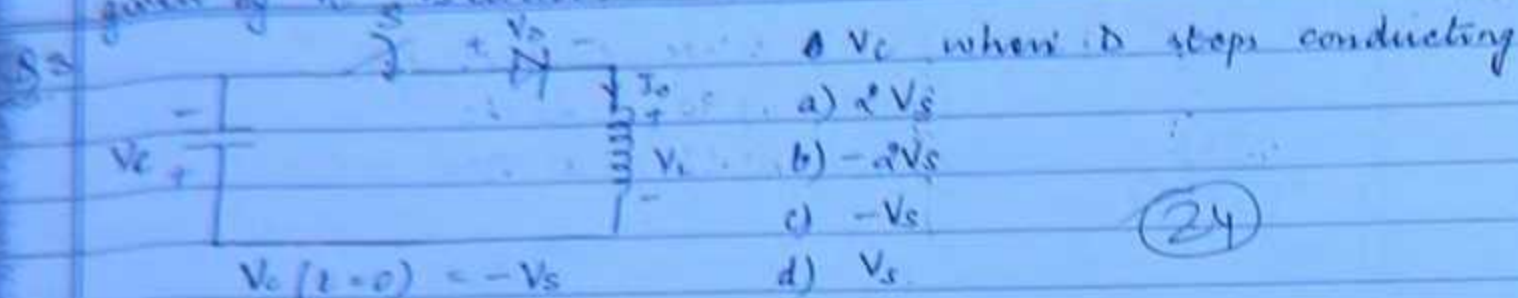then charging current of cap. behaves as $\sin$ wave given by $I_c = I_p \sin \omega t$ & charging vol of cap behaves as $\cos$ function given by $V_c = V_s \cos \omega t$.



$$V_c(t=0) = -V_s$$

$$V_c + V_L + V_R = 0$$

$$V_L + (V_c - V_s) = 0$$

$$V_s = V_L + V_c$$

$$V_s = L \frac{di}{dt} + \frac{1}{C} \int i dt$$

$$I_o = V_s \sqrt{\frac{C}{L}} \sin \omega t$$




$$V_L = L \frac{di}{dt} (I_p \sin \omega t)$$

$$V_L = V_s \cos \omega t$$

$$V_c = -V_L$$

$$V_c = -V_s \cos \omega t$$

Ans. $V_c = -V_s$ (a)

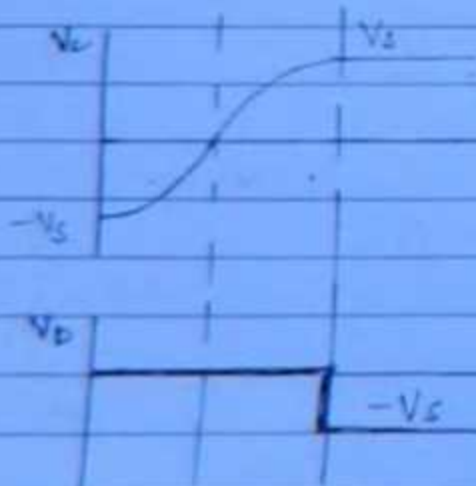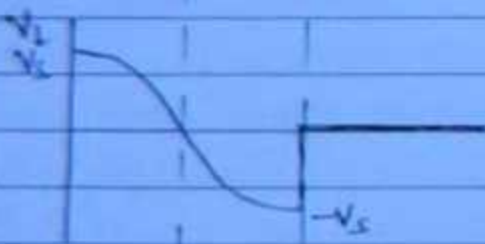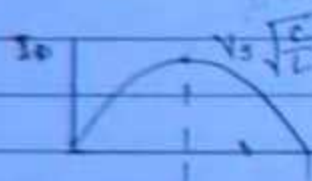


$$\text{Ans } V_c = V_s$$

$$PIV = V_s$$

Q3. If $V_c(t=0) = V_s$ then cap vol reverses & $V_c = -V_s$

ATE Q4

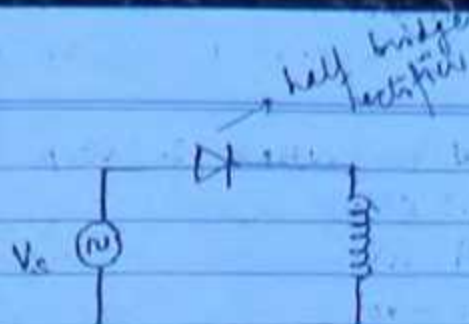

Diode conducts for
 a) 90° b) 180°
 c) 270° d) 360°

25

sol.

$$V_s = L \frac{di}{dt}$$

$$V_m \sin \omega t = L \frac{di}{dt}$$

$$\int di = \int \frac{V_m \sin \omega t}{L} dt$$

$$i = \frac{V_m}{\omega L} (\cos \omega t - 1)$$


$$i = -\frac{V_m}{\omega L} \cos \omega t + K$$

$$At \ \omega t = 0 \quad i = 0$$

$$0 = -\frac{V_m}{\omega L} \cos 0 + K$$

$$K = \frac{V_m}{\omega L}$$

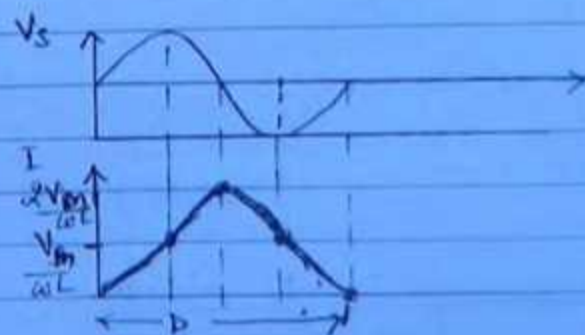
$$i = -\frac{V_m}{\omega L} \cos \omega t + \frac{V_m}{\omega L} = \frac{V_m}{\omega L} (1 - \cos \omega t)$$



Ans 360°

For 180° to 360° cycle the inductance energy forces the diode to maintain the conduction until it releases the complete energy.

Q5

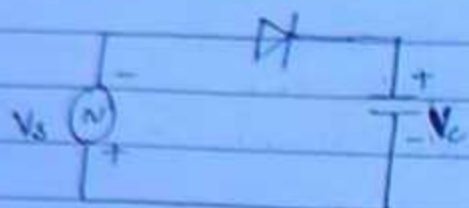

diode conducts for

- a) 90° b) 180°
c) 270° d) 360°

sol

$$V_c + V_s = 0$$

$$V_s = -V_c$$

$$V_m \sin \omega t = -\frac{1}{C} \int i \, dt$$

$$I = -V_m C \times \omega \times \cos \omega t$$

$$I = -V_m \omega C \cos \omega t$$

(26)

COMMUTATION TECHNIQUES


1. Natural / Line Commutation -

If nature of supply supports commutation process it's called natural commutation.

eg Rectifiers

AC vlg controllers


Step down cycloconverters

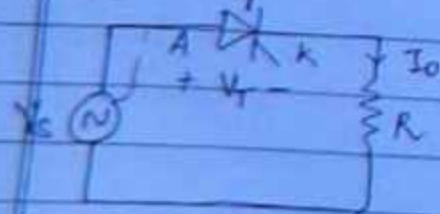

T → ON

$$I_o = \frac{V_s}{R}$$

$$I_o = \frac{V_m \sin \omega t}{R}$$

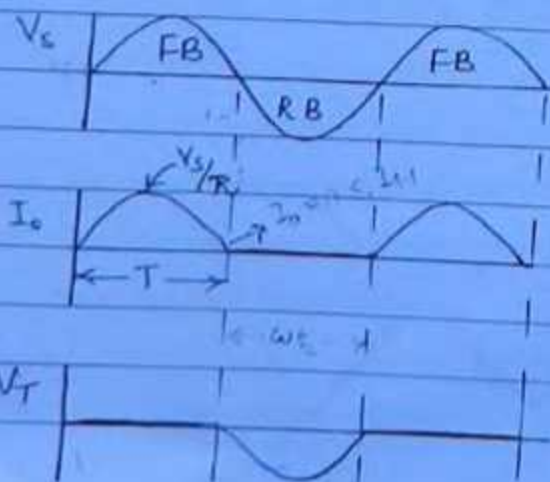

$$\omega t_c = \pi$$

$$t_c = \frac{\pi}{\omega} \text{ secs}$$

2 Forced commutation -

DC supply will not support the commutation process. We need a separate forced commutation circuit to turn off the SCR.

eg choppers

inverter



step up cycloconverter

(27)

a) Class A commutation circuits -

RLC should satisfy underdamped condition

$$\left(R^2 < \frac{4L}{C} \right)$$

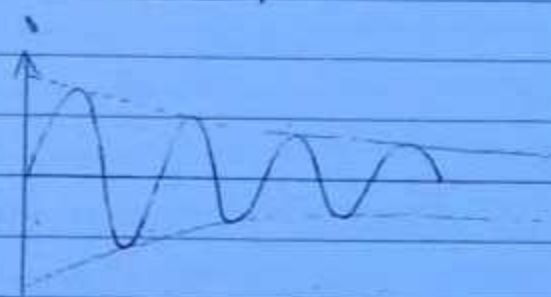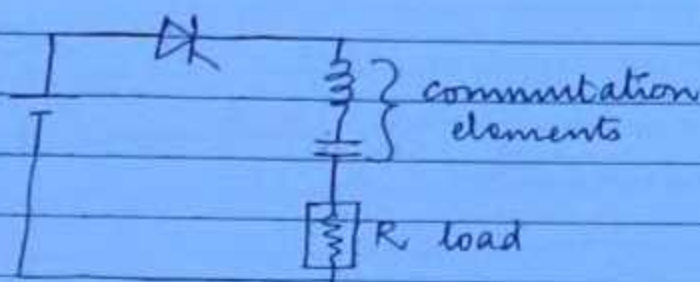


$$I = \frac{V_s}{\omega_n L} e^{-\delta t} \sin \omega_n t$$

$$\delta = \frac{R}{2L}$$

$$\omega_n = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

singing frequency

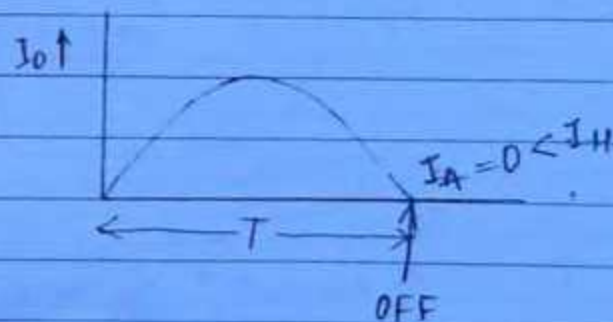

$$\omega_n t = \pi$$


$$t = \frac{\pi}{\omega_n}$$

conduction time of thyristor = $\frac{\pi}{\omega_n}$ sec.


Load commutation -

If the load elements support the commutation process then it is known as load commutation.

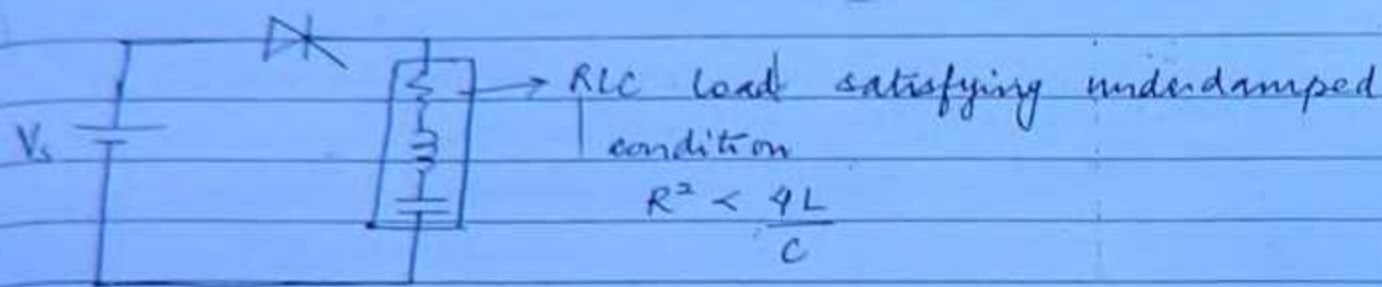If load is RLC load satisfying underdamped condition as shown in figure.



Class B - Current Commutation -

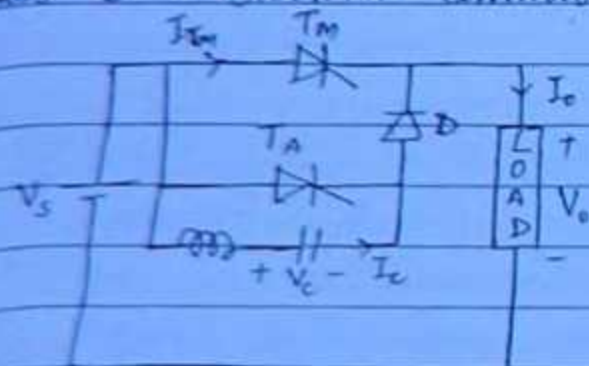

Assume $\rightarrow V_c(t=0) = V_s$

$\rightarrow I_o = \text{constant}$

(highly inductive load)


$\rightarrow T_m \rightarrow \text{ON } (t < 0)$

① Mode

$T_A \rightarrow \text{ON } (t=0)$

$$I_{Tm} = I_o$$
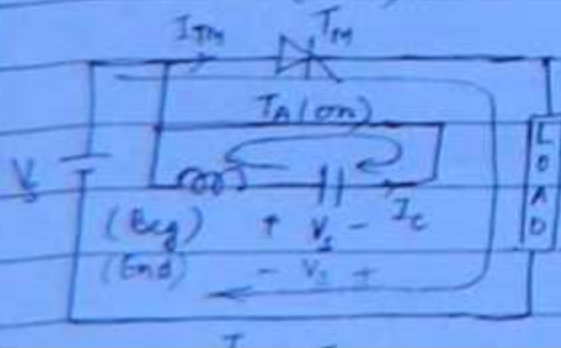
$$I_c = -I_p \sin \omega_o t \quad \left[\because \text{dir}^n \text{ is opp to reference } I_c \right]$$




$$V_c = V_s \cos \omega_o t$$


$$\text{End} \rightarrow V_c = -V_s$$

$$I_c = 0$$

(29)

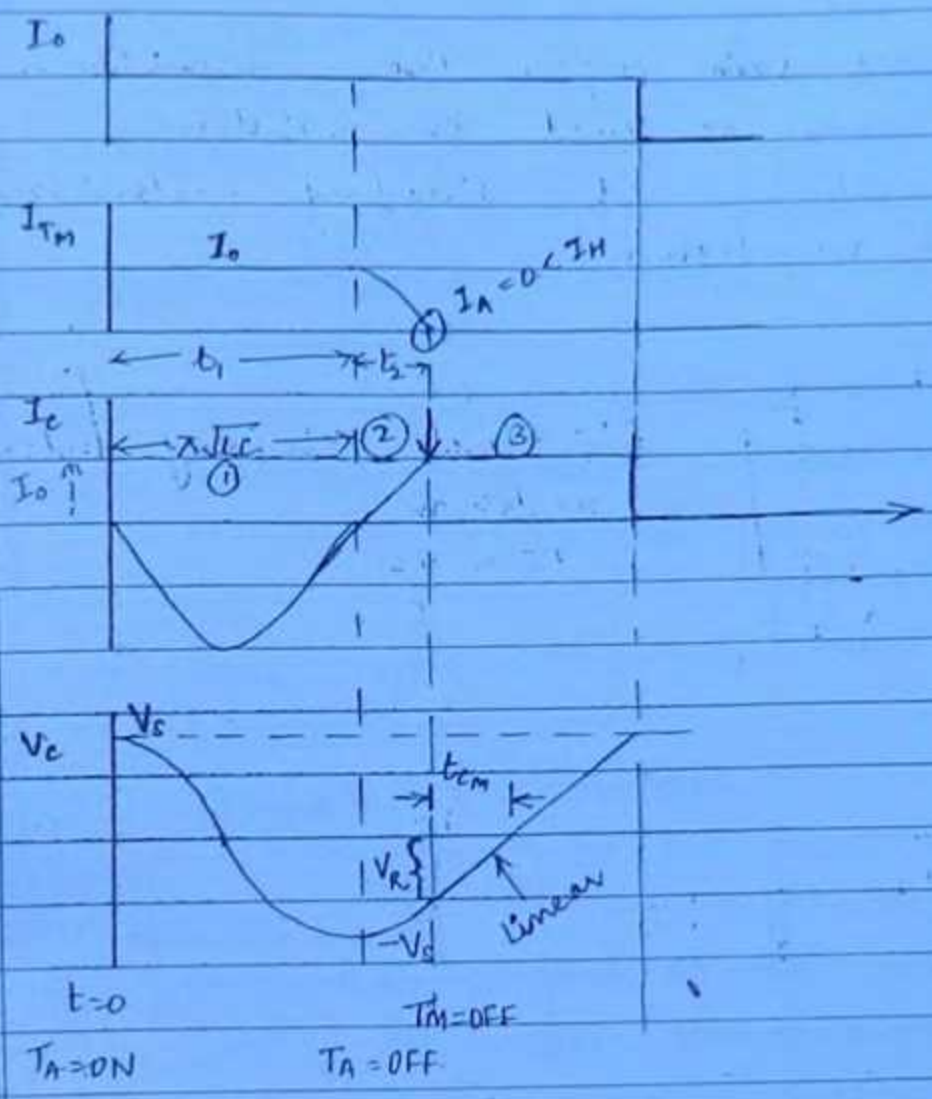

20

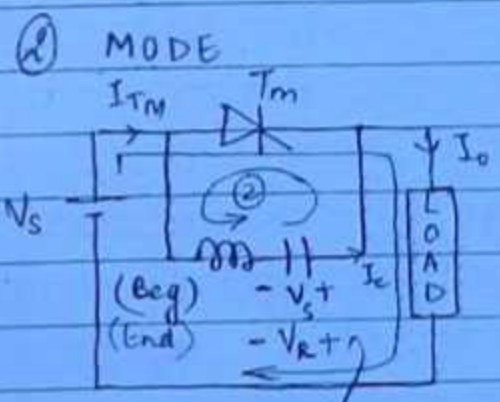

$$\downarrow I_{Tm} = I_o - I_c \uparrow$$

GRND $\rightarrow$ When $I_c = I_o$ $I_{Tm} = 0$
 $\therefore T_m \rightarrow OFF$

for this
also reference
is the initial
vlg V_c

$$I_p \sin(\omega_o t_2) = I_o$$

$$\omega_o t_2 = \sin^{-1} \frac{I_o}{I_p}$$

$$t_2 = \frac{\sqrt{LC} \sin^{-1} \frac{I_o}{I_p}}{I_p}$$

V_c at the end of mode ②

$$V_c = V_s \cos(\alpha + \omega t_2)$$

$$V_c = -V_s \cos(\omega t_2)$$

$$V_c = -V_s \cos \left[\sin^{-1} \frac{I_o}{I_p} \right]$$



(150)

At the end of mode ②

V_c is the reverse voltage of cap.

$$V_c = V_s \cos \left[\sin^{-1} \frac{I_o}{I_p} \right]$$

③ MODE

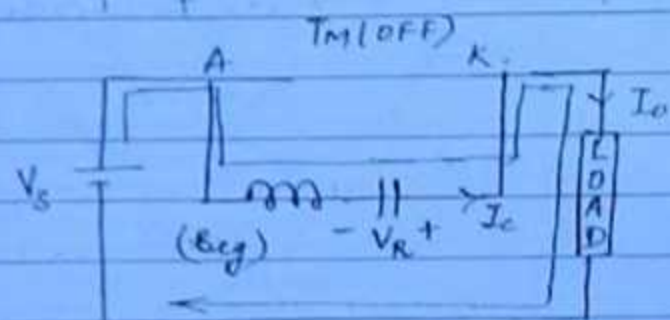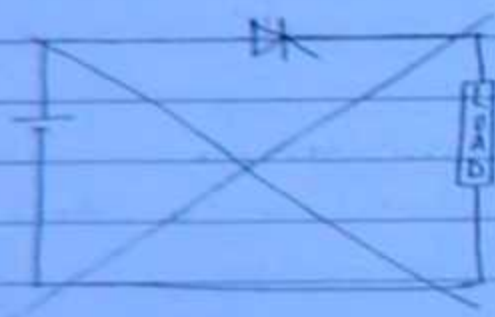

$$I_c = I_o$$

$$V_c = \frac{1}{C} \int i \, dt$$

$$V_c = \frac{I_o \, t}{C}$$

$$V_c = \frac{I_o \, t_{\text{com}}}{C}$$

$$t_{\text{com}} = \frac{V_c C}{I_o}$$

circuit turn off time
for main transistor

$$(I_{T_M})_{\text{peak}} = I_o$$

$$(I_{T_A})_{\text{peak}} = V_s \sqrt{\frac{C}{L}} \times I_p$$

(31)

$$\text{conduction time of } T_A = \lambda \sqrt{LC}$$

Min^m time required to turn OFF the main Thyristor after auxiliary Thyristor is switched ON.
 $t = \lambda \sqrt{LC}$ (for low values of load current I_o)

Max^m time required to turn OFF T_M

$$t = t_1 + t_2$$

$$= \lambda \sqrt{LC} + \sqrt{LC} \sin^{-1} \left(\frac{I_o}{I_p} \right)$$

3.38 ms

If $I_o > I_p$, commutation is not possible.
 ∴ $I_o \leq I_p$ to make commutation possible.

$$t_{CM} = \frac{CV_L}{I_o}$$


Max reverse v/g applied across the T_M when it is in off state is V_R .

$$V_R = V_s \cos \left[\sin^{-1} \frac{I_o}{I_p} \right]$$

If diode is not present, T_A has no control on commutation.

one of the
in chm
the

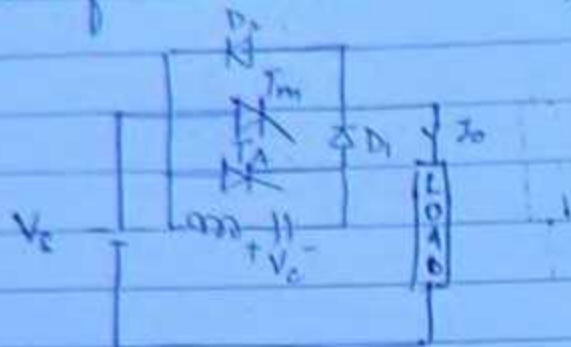Check if commutation is possible. If possible, calculate the circuit turn-off time of T_{A1} .




(32)

End of mode 1 reverses polarity of $+V_c$ to $-V_c$. In mode 2, T_{A1} is ON, T_{B1} reverses D_2 .

D_1 is FB and D_2 is RB. so commutation is possible. I_{A1} is RB, I_{B1} is FB. so it becomes same as class B.

1st two modes pair same as for case 1.

Mode (3)

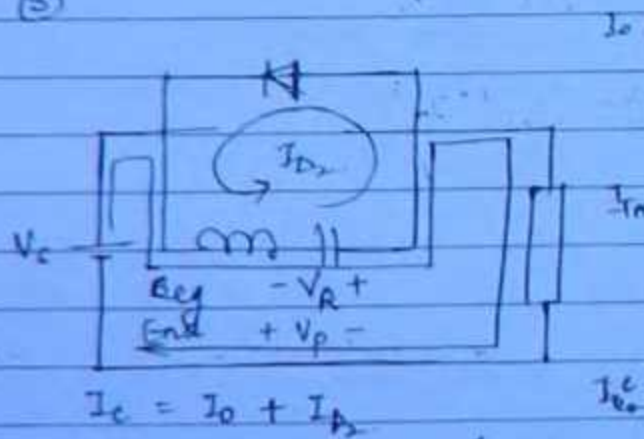


$$I_c = I_o + I_{D2}$$

$$I_{D2} = I_c - I_o$$


END → when $I_c = I_o$

$$I_{D2} = 0$$

$D_2 = \text{OFF}$

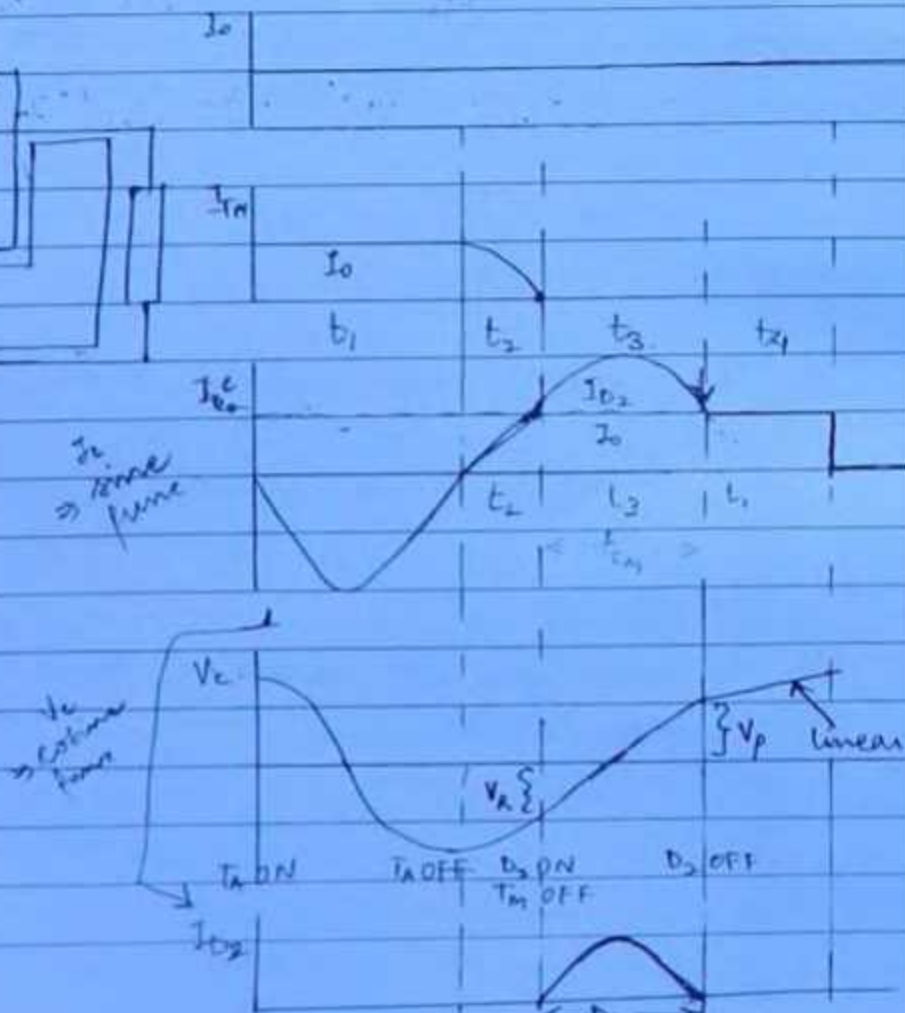

Mode (4)

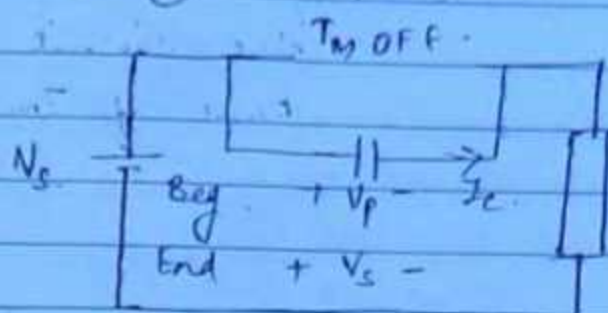

$$I_c = I_0$$

In mode (3): when D_2 is in the ON state, the drop of D_2 applies reverse vlg across the main thyristor. The conduction time of D_2 is equal to the turn off time of T_1 .

$$t_{cm} = t_3 = \lambda \sqrt{LC} - 2t_2$$


$$t_{cm} = \lambda \sqrt{LC} - 2\sqrt{LC} \sin^{-1} \left(\frac{I_0}{I_p} \right)$$

Applications -

This type of commutation technique is used in step down chopper. $\therefore$ it is also known as current commutation chopper.

(c) Class C - Complementary Commutation

34

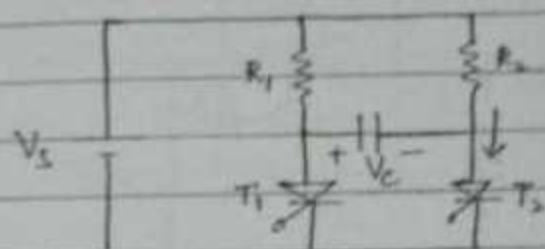


Assume

$$\begin{aligned} \rightarrow V_c(t=0) &= V_c \\ \rightarrow T_2 \rightarrow \text{ON} \\ T_1 \rightarrow \text{OFF} \end{aligned} \quad (t < 0)$$

Mode ①

At $t=0$, $T_1 \rightarrow \text{ON}$

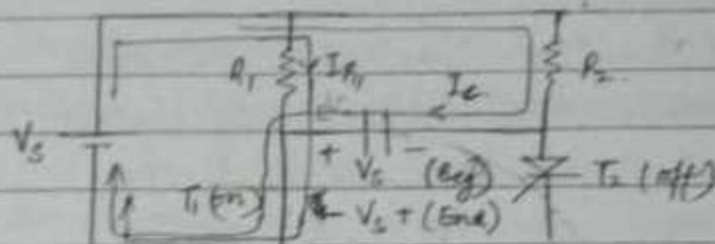

$$\begin{aligned} I_{T_1} &= I_{R_1} + I_c \\ &= \frac{V_s}{R_1} + \frac{V_c}{R_2} \end{aligned}$$

initial current

$$I_{T_1} = \frac{V_s}{R_1} + \frac{2V_s}{R_2} e^{-t/R_2 C}$$

steady state
current

transient
current

$$\begin{aligned} V_c &= \frac{1}{C} \int i_c dt = \frac{1}{C} \int \frac{V_c}{R_2} e^{-t/R_2 C} dt \\ &= \frac{1}{C} \left[-\frac{V_c}{R_2} e^{-t/R_2 C} \right] - V_c \end{aligned}$$

by trial f
error term

$$V_c = V_s (1 - e^{-t/R_2 C})$$



t_{cs} = cut time off time of T_2

$$V_s (1 - e^{-t_{cs}/R_2 C}) = 0 \quad V_c$$

At $t = t_{cs}$, $V_c = 0$

$$V_s (1 - e^{-t_{cs}/R_2 C}) = 0$$

$$t_{cs} = R_2 C \ln 2$$

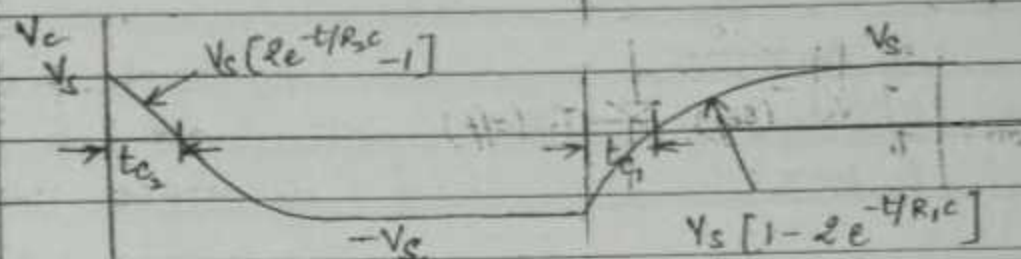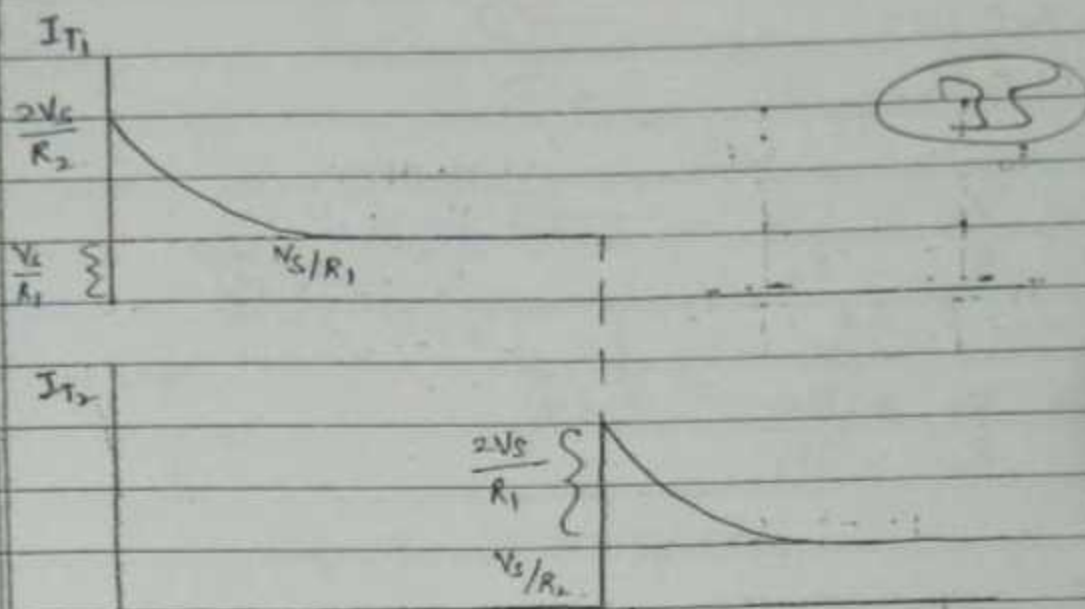

$t = 0$
 $T_1 \rightarrow \text{ON}$

(1)

$t = t_2$


(2)

$T_2 \rightarrow \text{OFF}$

$T_2 = \text{ON}$

Mode (2)

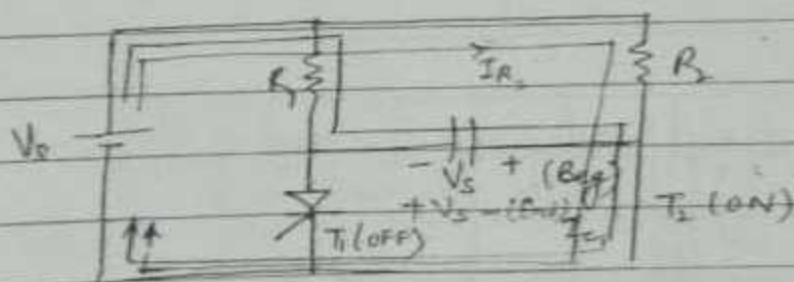At $t = t_2$, $T_2 \rightarrow \text{ON}$



$$I_{T2} = I_{R2} + I_C$$

$$I_{T2} = \frac{V_s}{R_2} + \frac{2V_s}{R_1} e^{-t/R_1 C}$$

Steady
state
current

Transient
current

$$t_{T1} = R_1 C \ln 2$$

$$* \quad t_{c2} = R_2 C \ln 2 \quad \text{--- (1)}$$

$$* \quad t_{c1} = R_1 C \ln 2 \quad \text{--- (2)}$$

$$* \quad (I_{T1})_{\text{peak}} = \frac{V_s}{R_1} + \frac{2V_s}{R_2} \quad \text{--- (3)}$$

(SF)

$$* \quad (I_{T2})_{\text{peak}} = \frac{V_s}{R_2} + \frac{2V_s}{R_1} \quad \text{--- (4)}$$

* Desired value of capacitance

from (1) $C = \frac{t_{c2}}{R_2 \ln 2}$

$$C = \frac{(SF) t_{c2}}{R_2 \ln 2} \quad \text{--- (5)}$$

from (2), $C = \frac{(SF) t_{c1}}{R_1 \ln 2} \quad \text{--- (6)}$

From eq (5) & (6) we get 2 different values for capacitance. We must consider the highest value of capacitance to make commutation possible.


Applications -

- Current source inverter (CSI)
- Parallel Inverter

(d) Class D - Voltage Commutation


It's used in step down choppers. i.e. it's also known as voltage commutation chopper.

(39)

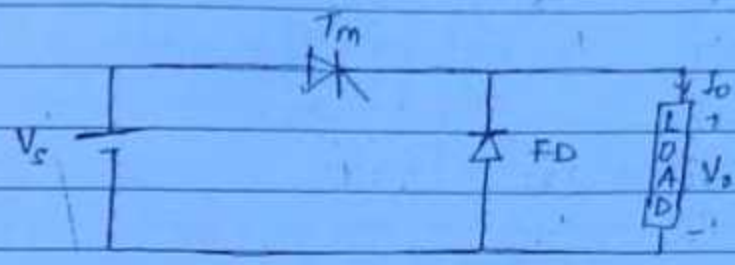

step down choppers


without commutation circuit:

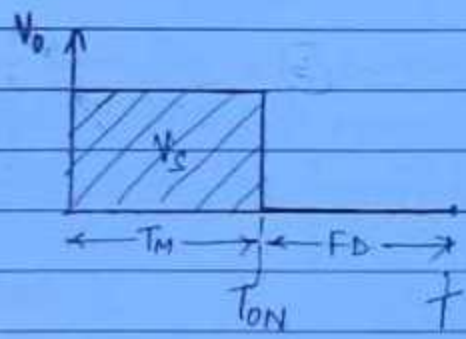

duty cycle $\alpha = \frac{T_{on}}{T}$

$V_o = \frac{\text{Area}}{\text{Time period}} = \frac{V_s T_{on}}{T}$

$V_o = \alpha V_s$



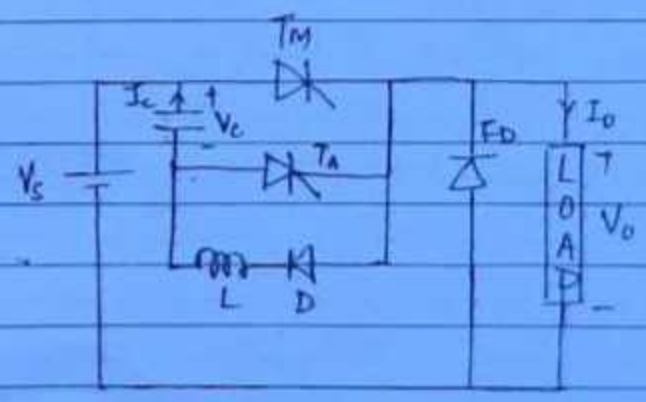


Assume

$\rightarrow V_c(t=0) = V_s$

$\rightarrow$ Consider highly inductive load so that load current

$I_o = \text{constant}$

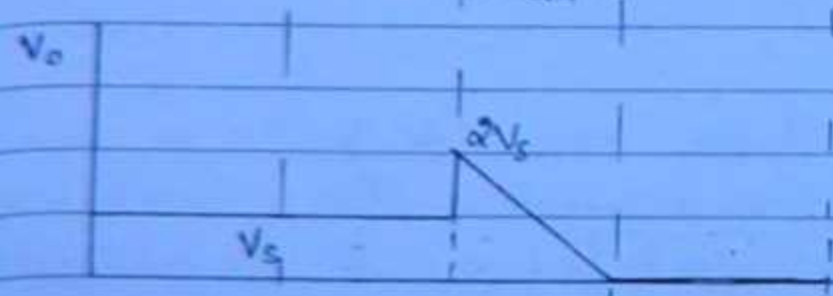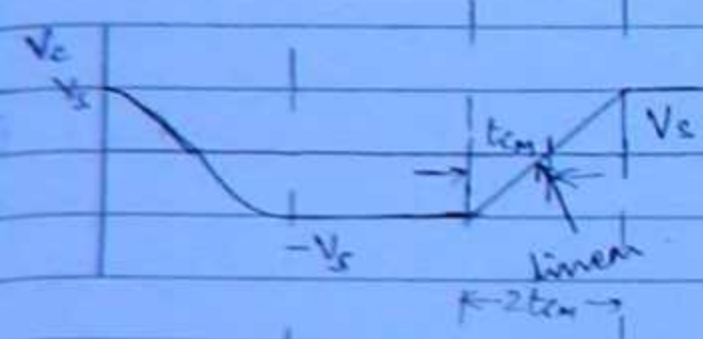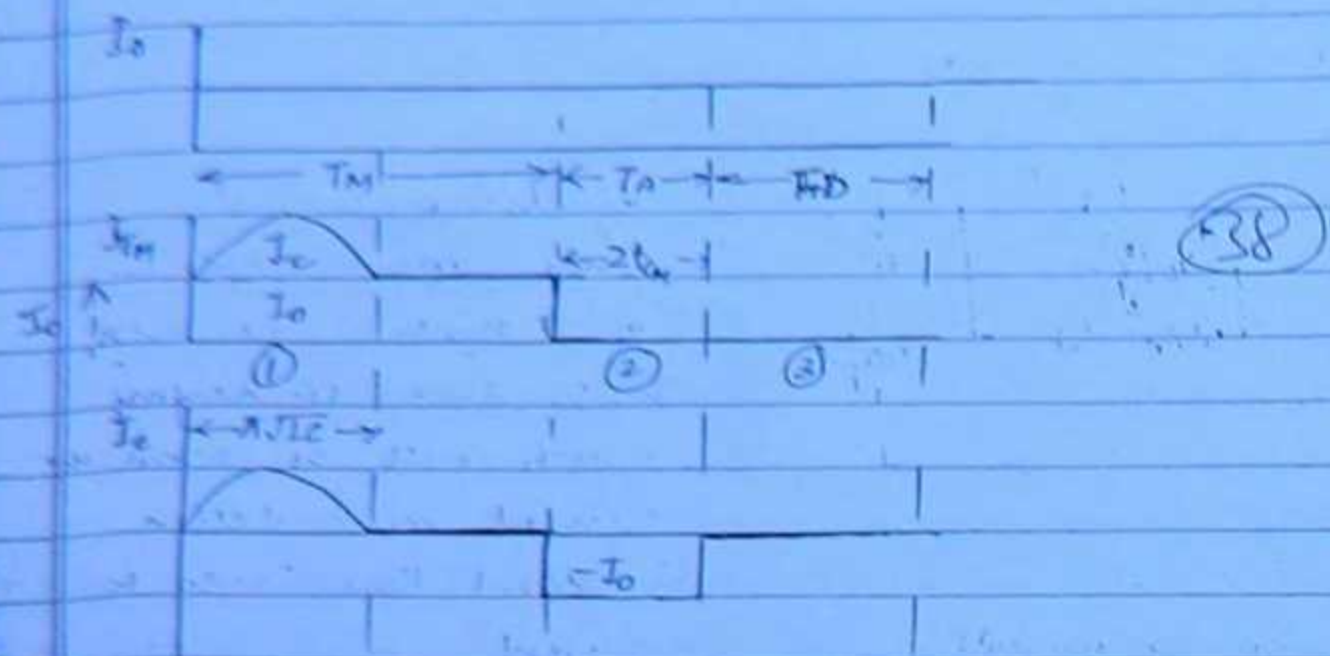


$t=0$ T_{on} T_{off} T $\alpha = \frac{T_{on}}{T}$
 $T_M \rightarrow ON$ $T_A \rightarrow ON$ $T_M \rightarrow OFF$

Mode (1)

At $t=0$ $T_M \rightarrow ON$

(39)

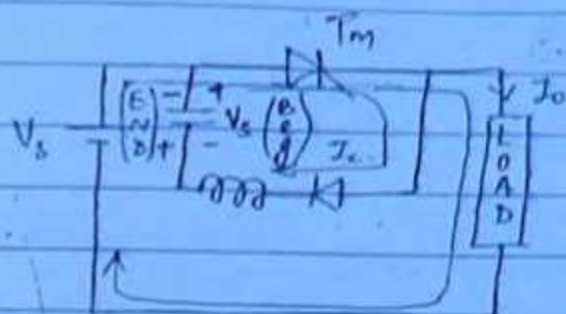

(*) If diode is not, there, after completion of mode 1 capacitor will start discharging which will be same as current commutation. To avoid this Diode is present.

$$I_{T_M} = I_o + I_c$$

$$I_c = I_p \sin \omega_0 t$$


$$V_c = V_s \cos \omega_0 t$$

End $\rightarrow V_c = -V_s$

$$I_c = 0$$

Mode (2)

At $t=T_{ON}$ $T_A \rightarrow ON$

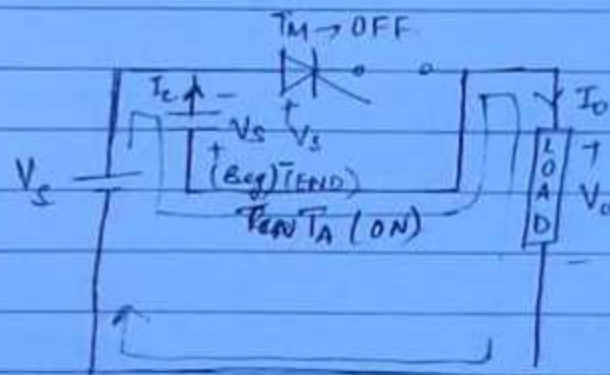

$$I_c = -I_o$$

$$V_c = -V_s$$

$$V_o = -2V_s$$


End $\rightarrow V_c = V_s$

$$V_o = 0$$

$$I_c = 0$$

$$T_A \rightarrow OFF$$

Mode ③

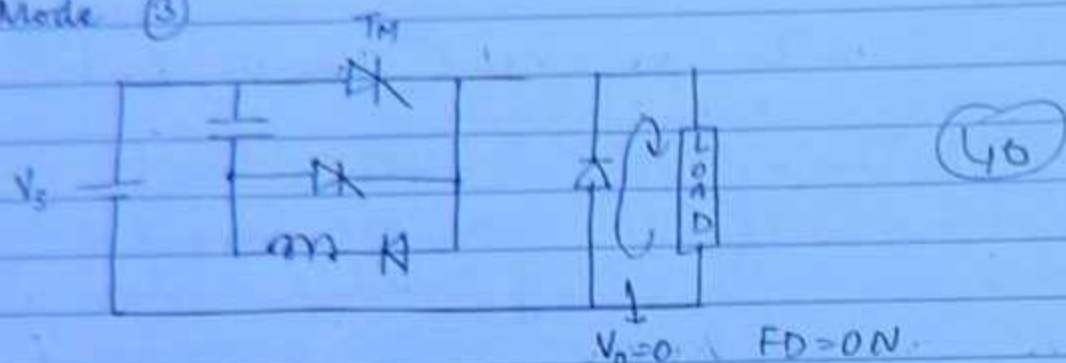

$$(I_{TA})_{peak} = I_o + V_s \sqrt{\frac{C}{L}}$$

$$(I_{TA})_{peak} = I_o$$

- Without completion of the 1st mode we cannot turn off the T_M i.e. the min turn ON time of the transistor is $\pi \sqrt{LC}$ sec.
(This is because the polarities will not change before the completion of 1st mode)

Min^{cycle} duty of the chopper

$$\alpha = \frac{(T_{on})_{min}}{T} = \pi \sqrt{LC} f$$

Circuit turn off time of T_M

$$V_c = \int i dt \Rightarrow V_c = I_o t \quad (\text{linear})$$

$$V_c = \frac{I_o t_{cm}}{C} \Rightarrow t_{cm} = \frac{C V_s}{I_o}$$

Conduction time of $T_A = \alpha t_{cm}$

Commutation interval = time taken to disconnect the load from the source once T_M is off.

$$= 2 t_{cm}$$

* PIV of FD is $2V_s$
 since its RB by the load, (when its off)
 so max vlg at load is $2V_s$

(41)

* PIV of $T_M = V_s$

* Average value of voltage

$$V_o = \frac{V_s T_{ON} + \frac{1}{2} \times 2t_{cm} \times 2V_s}{T}$$

$$V_o = V_s \left[\frac{T_{ON} + 2t_{cm}}{T} \right] = \frac{V_s (T_{ON})_{eff}}{T}$$


* Effective turn-on time of chopper
 i.e. $(T_{ON})_{effective}$

$$(T_{ON})_{effective} = T_{ON} + 2t_{cm}$$

* Minimum possible average voltage of chopper
 is

$$(V_o)_{min} = V_s \left[\frac{\pi \sqrt{LC} + 2t_{cm}}{T} \right]$$

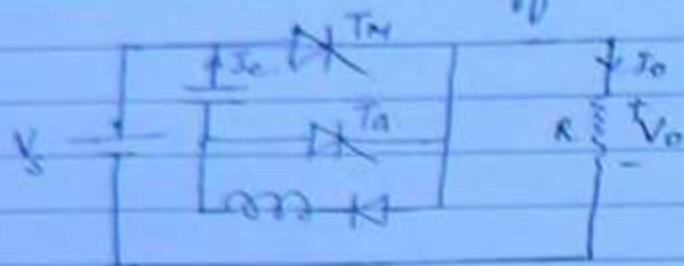Find the circuit turn off time of the main thyristor



(42)

Mode 1 is same as prev. case

Mode 2 $\rightarrow$ is not same as $I_o \neq 0$ due to R load.
(which forms RC ckt with cap C)

$$I_c = -I_o = -\frac{2V_s}{R} e^{-t'/RC}$$

$$I_o = \frac{2V_s}{R} e^{-t'/RC}$$

At $t' = 0$

$$I_o = \frac{2V_s}{R}$$

If load current is exponentially reducing.

$$I_c = -\frac{2V_s}{R} e^{-t'/RC}$$


current current $\downarrow$
exponentially

$\uparrow$
 V_c also.

$$V_c = V_s [1 - 2e^{-t/RC}]$$

At $t = t_{com}$ $V_c = 0$

$$t_{com} = RC \ln 2$$

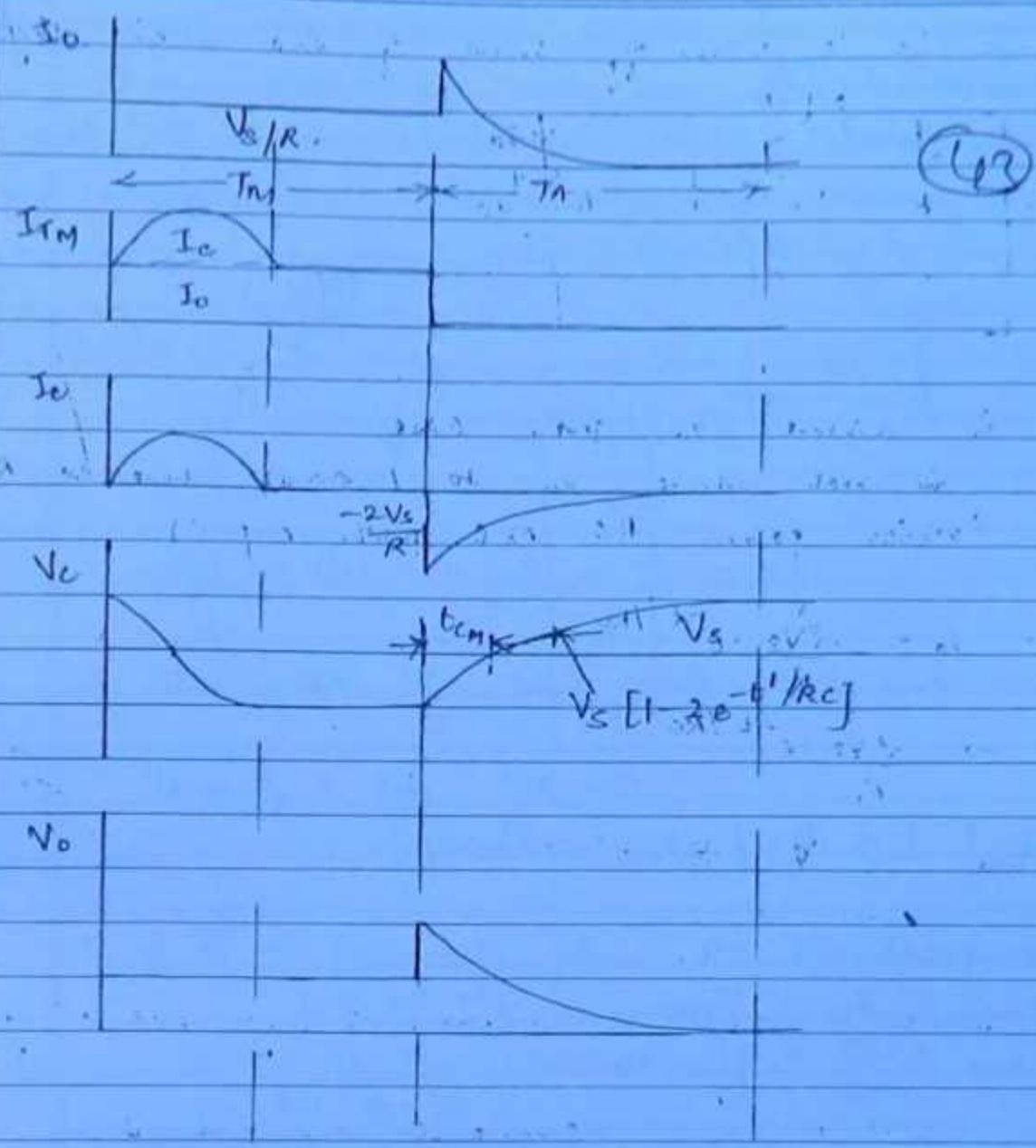


FIRING CIRCUITS

gives the required gate signal to turn ON the SCR.

1. Resistance Firing Circuit -

(44)

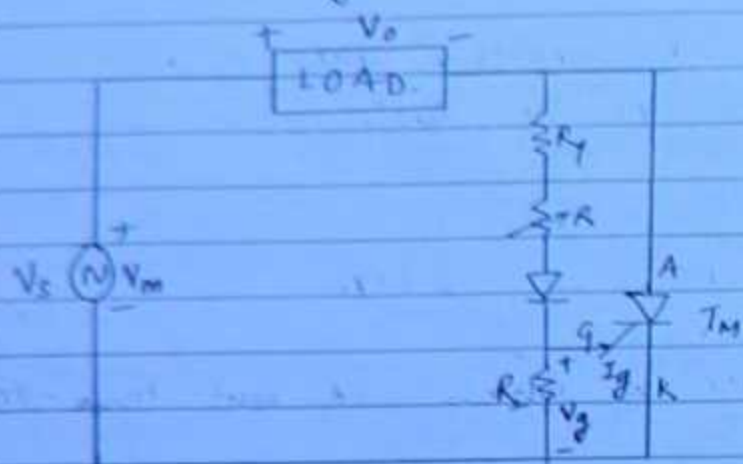

Main ckt : 1 ϕ Half Wave Rectifier

Gate specifications $\rightarrow$

$$I_{gmin} \leq I_g \leq I_{gmax}$$

$$V_{gmin} \leq V_g \leq V_{gmax}$$

R_1 $\rightarrow$ To limit gate current I_g within max^m value (I_{gmax})

For worst condition.

$$\text{Maximum gate current} = \frac{V_m}{R_1} \leq I_{gmax}$$

$$\therefore R_1 \geq \frac{V_m}{I_{gmax}}$$

R_2 $\rightarrow$ To limit gate vlg V_g within max^m value (V_{gmax})

For worst condition.

$$\text{Maximum gate vlg} = \left(\frac{V_m}{R_1 + R_2} \right) R_2 \leq V_{gmax}$$

From above eqⁿ we can design value of R_2 .

Variable R $\rightarrow$ To change the timing of gate signal is $\propto$

(43)

Diode $\rightarrow$ To avoid negative gate signal during negative cycle of source.

V_{gt} $\rightarrow$ Gate turn on voltage

is the gate V_g at which SCR will turn-ON

ie at $V_g = V_{gt}$ SCR $\rightarrow$ ON
($\omega t = \alpha$)

$$V_g = \left(\frac{V_m \sin \omega t}{R_1 + R + R_2} \right) R_2$$

$$V_g = \left(\frac{V_m R_2}{R_1 + R + R_2} \right) \sin \omega t$$

$$V_g = V_{gm} \sin \omega t \quad \text{where } V_{gm} = \frac{V_m R_2}{R_1 + R + R_2}$$

$$V_g = 0$$

$\rightarrow T_{on} = 0$

At $V_g = V_{gt}$ SCR $\rightarrow$ ON

$$V_{gm} \sin \alpha = V_{gt}$$

$$\alpha = \sin^{-1} \frac{V_{gt}}{V_{gm}}$$

$\uparrow R \quad V_{gm} \downarrow \quad \alpha \uparrow$

for example

(I) $R = R_a$

$\alpha = \alpha_a$

$$V_{gmx} = \frac{V_m R_a}{R_1 + R_a + R_2}$$

$$V_{g_a} = V_{gmx} \sin \omega t$$


II $\uparrow R = R_b$

$\alpha = \alpha_b$

$$V_{gmb} < V_{gmx}$$

$$V_{g_b} = V_{gmb} \sin \omega t$$

(4b)

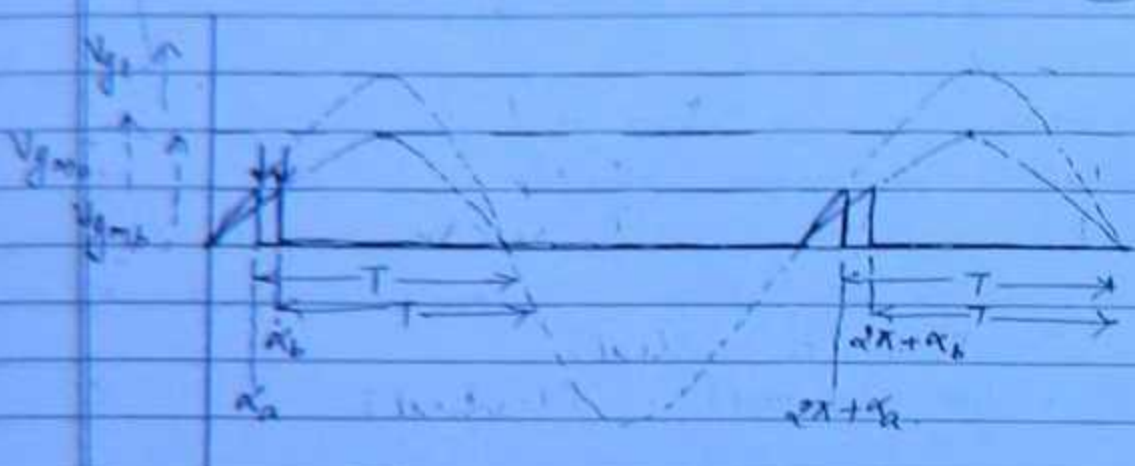


$\uparrow R \quad V_{gm} \downarrow \therefore \alpha \uparrow$


Limitation of R firing circuit.


The maximum firing angle is limited to 90°

3. RC firing circuit -

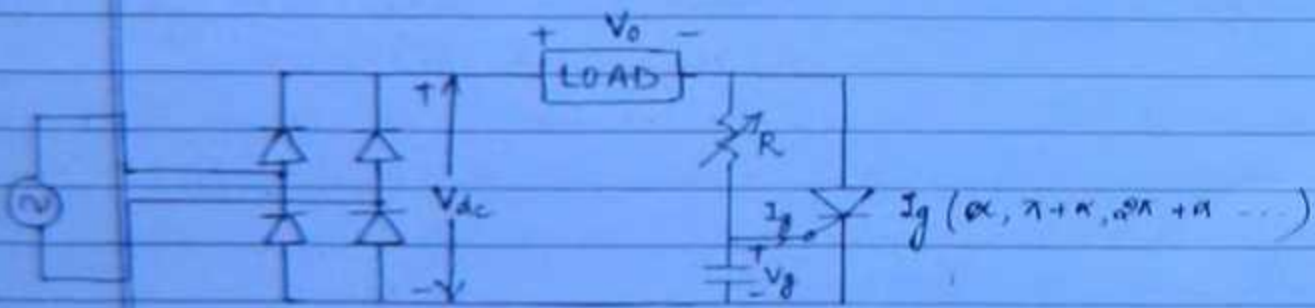

Main circuit: Full wave Rectifier

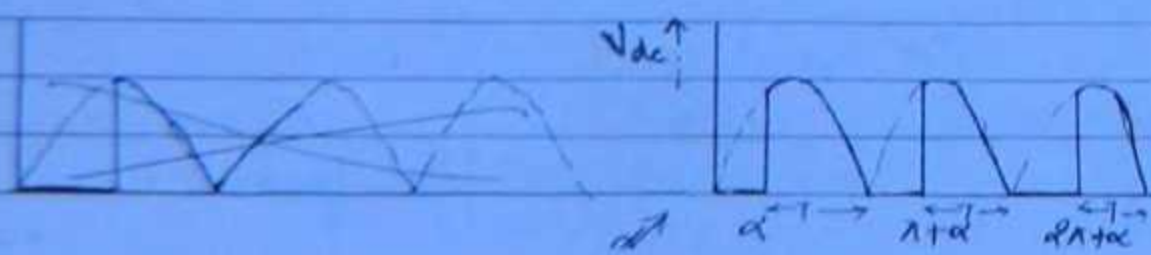

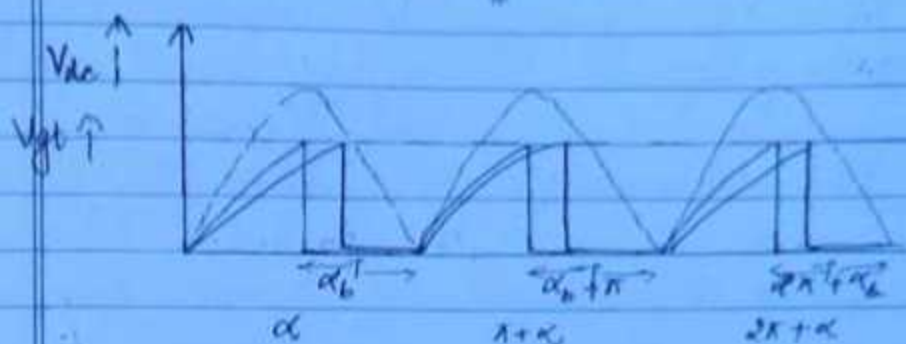

(97)

I $R = R_A$

$T = R_A C$

$V_{ga} \uparrow$

$\pi \cdot V_{gb} \uparrow$


$T = R_A C$

$R = R_B > R_A$

$0 < \alpha < 180^\circ$ (Ideal)
 $(5 \text{ to } 7^\circ) < \alpha < (165 \text{ to } 175^\circ)$ (Practical)

3 VJT firing circuit -

VJT

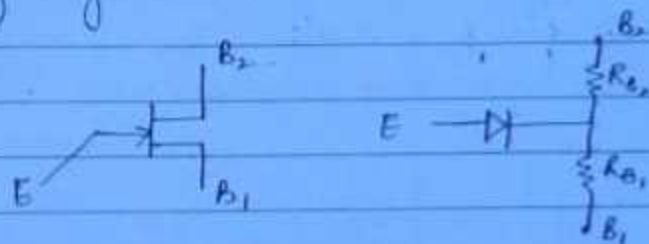


$B_1, B_2 \rightarrow$ Base terminals

$R_{B1}, R_{B2} \rightarrow$ Base resistances

$E \rightarrow$ Emitter terminal

When diode is ON
 VJT ON

When diode is OFF
 VJT OFF

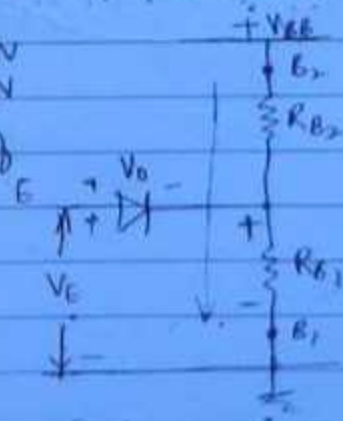

$$V_{R_{B1}} = \left(\frac{R_{B1}}{R_{B1} + R_{B2}} \right) V_{EE}$$

$$V_{R_{B1}} = \eta V_{EE}$$

$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$$

Intrinsic stand off ratio

$$V_E = V_{R_E} + V_D$$

$$= \eta V_{BB} + V_D$$

$$\boxed{\uparrow V_E \Rightarrow V_P}$$

then UJT $\rightarrow$ ON

UJT

(when $\uparrow V_E$ reaches V_P UJT $\rightarrow$ ON)

$$V_P = \eta V_{BB} + V_D$$

$\downarrow$

peak point voltage

OFF to ON state

When UJT is switching from the base resistance R_B starts decreasing i.e. UJT exhibits negative resistance behaviour. This reduces emitter vty.



$$\boxed{V_E \downarrow \Rightarrow V_V}$$

$\rightarrow$ UJT OFF

(when $\downarrow V_E$ reaches V_V UJT $\rightarrow$ OFF)

Valley voltage


UJT working as Relaxation Oscillator -

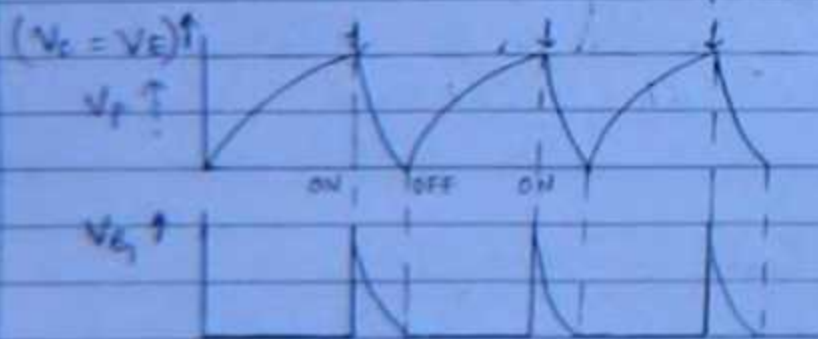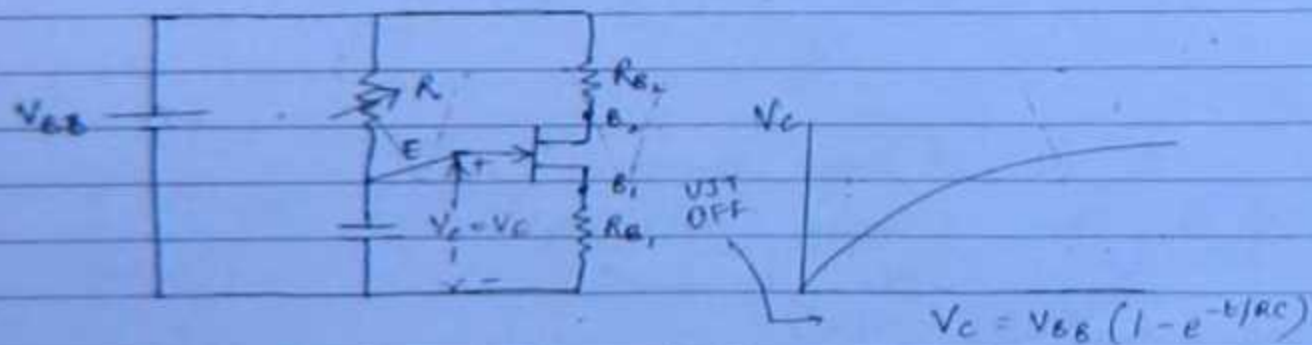


Synchronized UJT firing circuit -

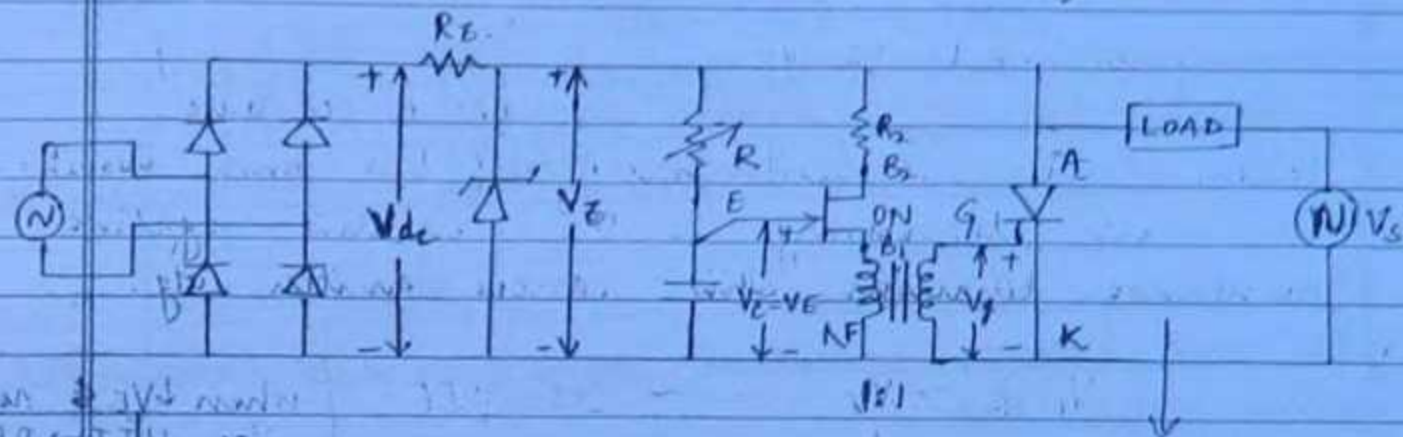(49)

We must synchronise the firing circuit with the main circuit in order to match the timing of 'gate pulse' in both the circuits. Here we must use same power supply in the main & firing circuits for the purpose of synchronisation.



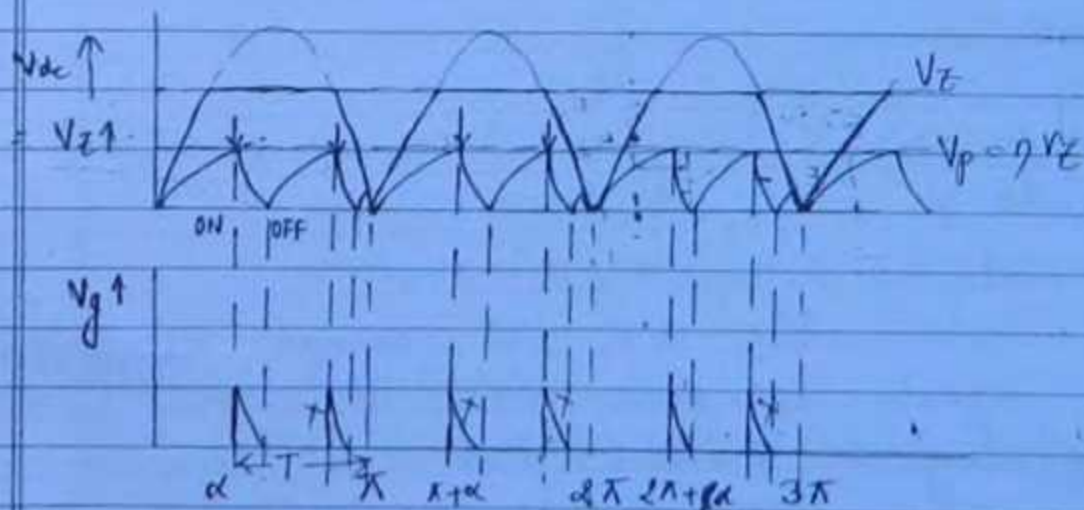main circuit
Half wave rectifier
 $I_g(\alpha, 2\pi + \alpha, \dots)$




PROTECTION OF THYRISTORS -

1 Over Current Protection -

50

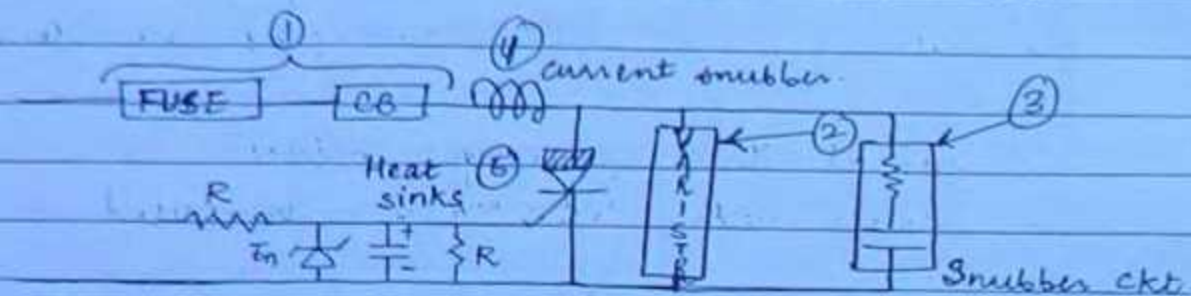For over current protection, we must connect fuse or circuit breaker in series with the SCR.



2 Over Voltage Protection -

For over voltage protection, varistors are connected across the SCR.


Varistors $\rightarrow$ Non-linear resistor



All metal oxide resistors behave as non-linear R.

3 dV/dt Protection -
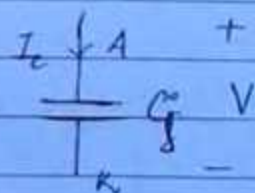
$$\uparrow I_c = C_g \frac{dV}{dt} \uparrow$$




At high dV/dt the SCR is turned ON before the gate signal is given. This is known as false triggering. To prevent this a capacitor is connected across SCR to limit dV/dt . A resistor is connected in series with the C, to reduce the discharge current magnitude. This is called Snubber circuit.

4 di/dt Protection

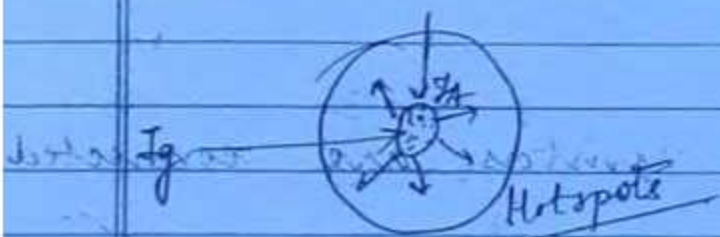(5)

When $di/dt >$ (spread velocity of charge carriers) the charge accumulation increases cumulatively in a small conduction area & leads to the formation of hot spots damaging the device.

To prevent this, a large inductor is connected in series with the SCR. This is called current snubber.



Initial conduction area $\uparrow$



(*) di/dt capability of thyristor can be improved by:-

i) $\rightarrow$ by increasing I_g or
 $\rightarrow$ by increasing $\frac{dI_g}{dt}$

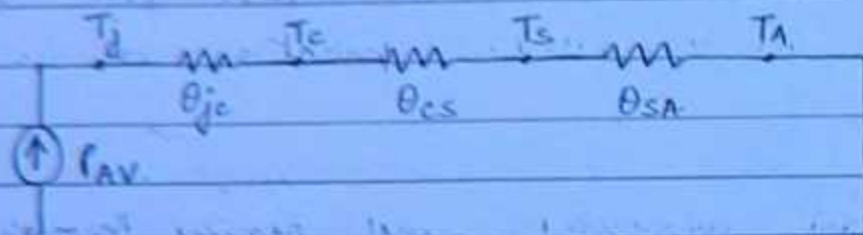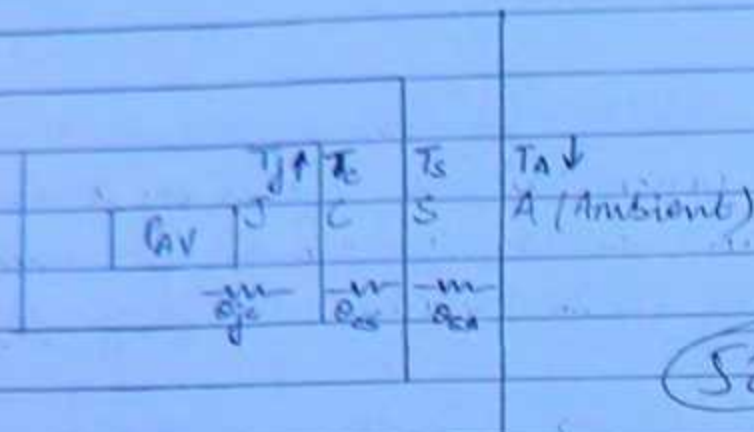ii) $\rightarrow$ by using Centre Gated Thyristor.
(initial conduction area is increased when centre gated SCR is preferred)

5 Thermal Protection -

Heat sinks are used for thermal protection.



$$P_{AV} = \frac{T_j - T_c}{\theta_{jc}} = \frac{T_c - T_s}{\theta_{cs}} = \frac{T_s - T_A}{\theta_{sa}} = \frac{T_j - T_s}{\theta_{jc} + \theta_{cs}} = \frac{T_c - T_A}{\theta_{cs} + \theta_{sa}} = \frac{T_j - T_A}{\theta_{jc} + \theta_{cs} + \theta_{sa}}$$

* Rating of SCR $\propto \sqrt{P_{AV}} \propto \sqrt{\frac{T_j - T_A}{\theta_{ja}}}$

* Rating of SCR is decided by cooling methods in the heat sink. Lesser the ambient temperature (T_A) higher the rating of the SCR.

6 Gate Protection. -

(53)

a) Over Current Protection

A resistance is connected in series with the gate to limit the gate current within the permissible value.

b) Over Voltage Protection

Zener diode is connected across gate cathode terminals for overvoltage protection in the gate.

c) Protection against noise signals -

Noise is an unwanted signal passing through the gate terminal. It will false turn ON the SCR.

To prevent it, we connect a parallel RC across gate cathode terminals, to protect the SCR against noise signals.

CWE chapter 1

Q1 (b)

$$\begin{aligned}T_j &= 125^\circ\text{C} \\T_s &= 70^\circ \\ \theta_{jc} &= 0.16 \\ \theta_{cs} &= 0.08\end{aligned}$$

$$P_{AV} = \frac{T_j - T_s}{\theta_{jc} + \theta_{cs}} = \frac{125 - 70}{0.16 + 0.08} = 229.167 \text{ W}$$


$$P_{AV} = \frac{125 - 60}{0.16 + 0.08} = 270.83 \text{ W}$$

$$\% \text{ Increase in Rating of SCR} = \frac{\sqrt{P_{AV2}} - \sqrt{P_{AV1}}}{\sqrt{P_{AV1}}} \times 100$$

$$= \frac{\sqrt{270.83} - \sqrt{249.16}}{\sqrt{249.16}} \times 100$$

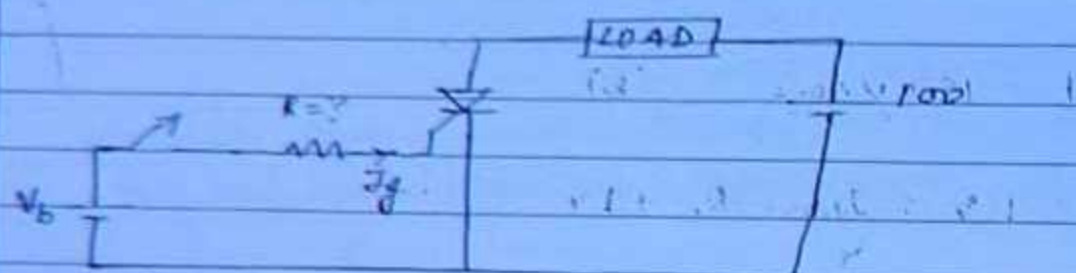(54)

$$\therefore \% \text{ Increase} = 8.7\%$$



$$V_b = 12 \text{ V}$$

$$I_{g \min} = 100 \text{ mA}$$

For worst condition


$$\text{Minimum possible } I_g = \frac{12 - V_f}{R}$$

$$\frac{12 - 4}{R} \geq 10 \text{ mA}$$

$$R \leq 800 \Omega \quad (d)$$

$$C = \frac{S F \times t_d}{R \ln 2} = \frac{2 \times 50 \times 10^{-6}}{50 \times \ln 2} = 2.88 \mu\text{F} \quad (a)$$
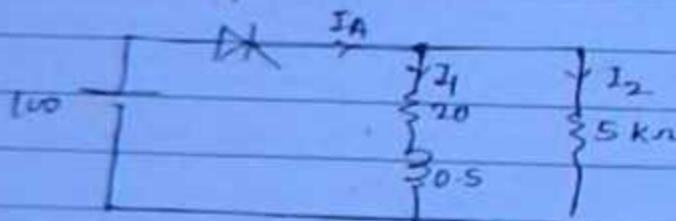
$$T_{on} = 5 \mu\text{sec} \quad I_L = 50 \text{ mA} \quad I_{H1} = 40 \text{ mA}$$



$$I_A = I_1 + I_2$$

$$= \frac{V_s (1 - e^{-t/T_1})}{R_1} + \frac{V_s}{R_2}$$

$$T_1 = \frac{L_1}{R_1} = \frac{0.5}{20} = \frac{1}{40}$$

$$I_A = \frac{100}{20} (1 - e^{-40t}) + \frac{100}{5 \times 10^3}$$

$$I_A = 5(1 - e^{-40t}) + (20 \times 10^{-3})$$

↓
kill I_L

(5)

$$50 \times 10^{-3} = 5(1 - e^{-40t}) + (20 \times 10^{-3})$$

$$\frac{30 \times 10^{-3}}{5} = 1 - e^{-40t}$$

$$t = 150 \mu\text{secs} \quad (b)$$

$$9V = 1V + I_{gmax} R + 1V$$

$$I_{gmax} = 150 \text{ mA}$$

$$R \geq 46.67 \Omega$$

$$9V = 1V + I_{gmin} R + 1V$$

$$I_{gmin} = 100 \text{ mA}$$

$$R \leq 70 \Omega$$

$$46.6 \leq R \leq 70$$

$$\text{Ans } 47 \Omega \quad (c)$$

Q8. Volt sec rating of pulse transformer
 $= 10V \times t_{g\text{pw}}$

(gate pulse width)

$$t_{g\text{pw}} > t_{min}$$

$$I_A = \frac{200}{1} (1 - e^{-t/\tau})$$

$$\frac{L}{R} = 150 \times 10^{-3} = 0.15$$

$$I_A = 200 (1 - e^{-t/0.15})$$


$$I_L \rightarrow 150 \text{ mA} = 200 (1 - e^{-t/0.15})$$

$$t_{min} = 187 \mu\text{s}$$

$$t_{g\text{pw}} > 187 \mu\text{s}$$

Ans (a)

12 GTO (Gate Turn OFF Thyristor)

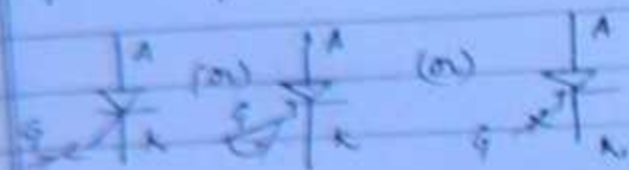


To turn ON $\rightarrow +I_g$ (When A +ve w.r.t. K)

To turn OFF $\rightarrow -I_g$ (When $I_{gN} \approx 20-25\% I_{TA}$ [I_{MA}])

The V-I characteristics of GTO for conventional thyristor (SCR) are similar.

Switching Characteristics of GTO

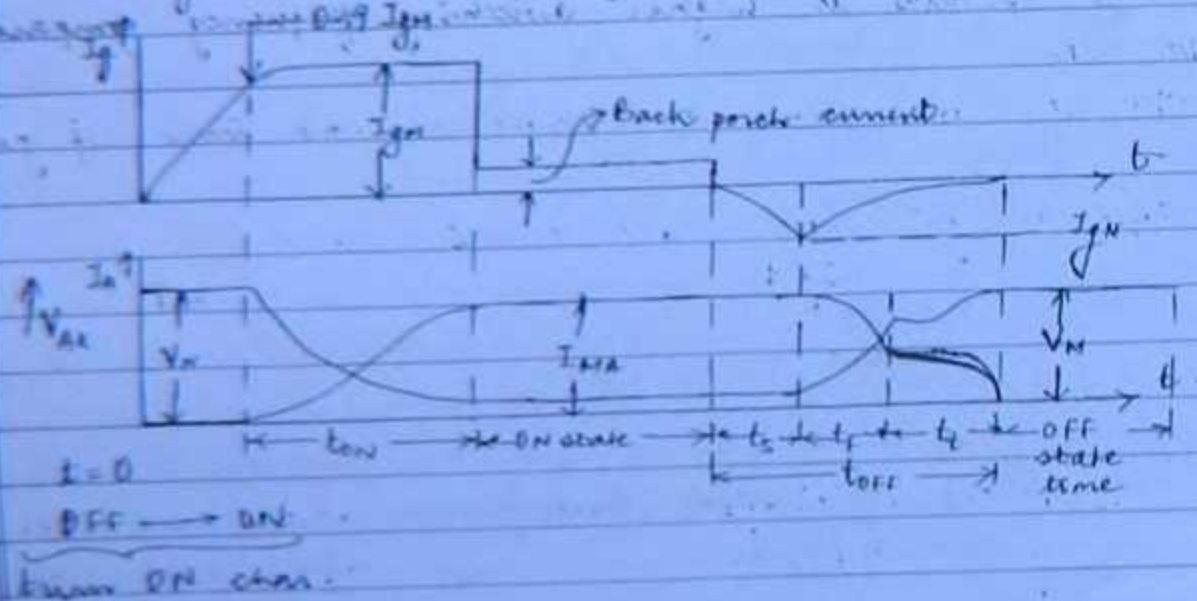

During storage time the stored charge carriers are removed from the device

t_s = storage time

During fall time rate of reduction of anode current is fast
 t_f = fall time

- * During tail time rate of reduction of anode current is slow.
- t_t = tail time

(57)

Compare GTO with conventional thyristor (SCR)

1. I_L & I_H are higher in GTO.
2. On state v_g drop is higher in GTO.
3. Gate signal requirement is higher in GTO.
4. Reverse v_g blocking capability is lesser than forward v_g blocking capability in GTO.
5. GTO is more efficient & compact compared to SCR unit.
6. GTO has fast turn-on & faster turn-off.
∴ it operates at higher switching frequency compared to SCR.
7. GTO has low turn-on gain & low turn-off gain.

$$\downarrow \text{turn-on gain} = \frac{I_{AS}}{(+I_g) \uparrow}$$

$$\downarrow \text{turn-off gain} = \frac{I_{AS}}{-I_{gAT}}$$


Applications —

- * In inverters & choppers we can replace the SCR by using a GTO to avoid commutation circuit.

ASCR (Asymmetrical SCR)

It's a special thyristor with reduced reverse vlg blocking capability. (58)

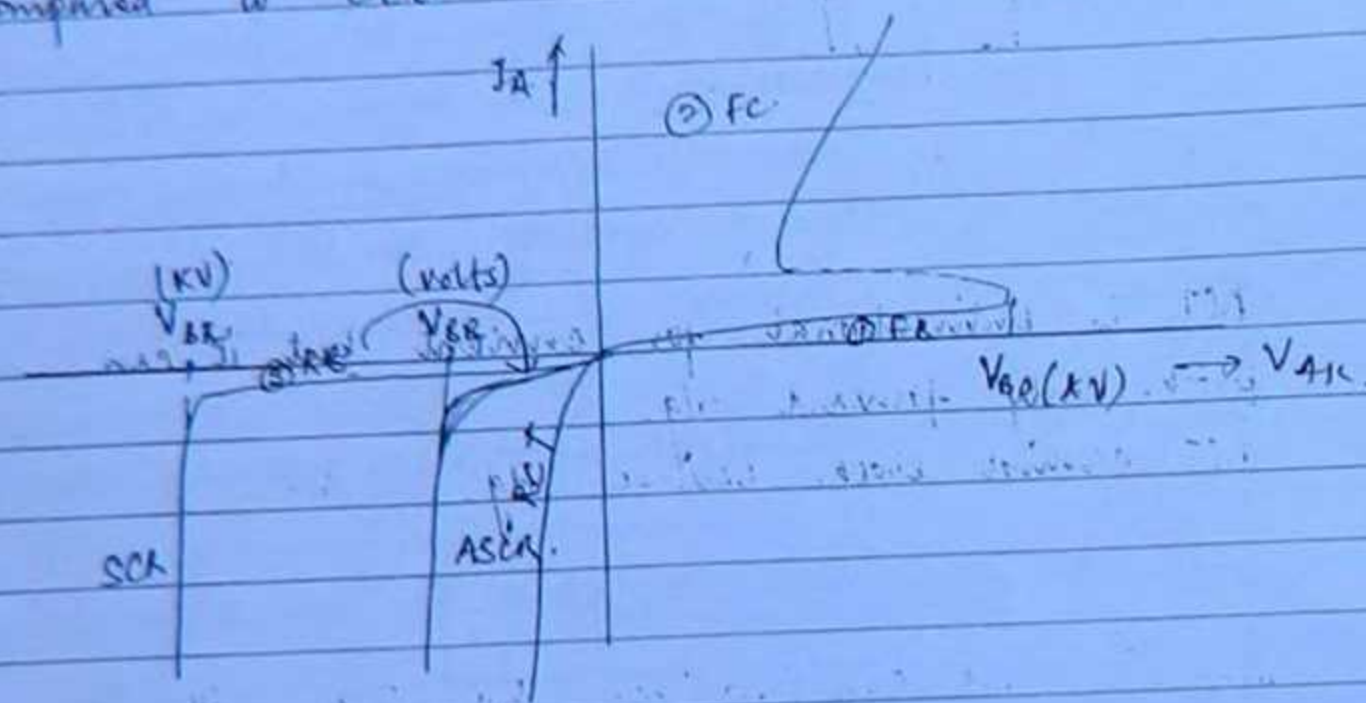ASCR has fast turn-on & turn off times
∴ it operates at higher switching frequency as compared to SCR.




Applications -

In vlg source inverters (VSI) we can replace the SCR by ASCR.

RCT (Reverse Conducting Thyristor)

An antiparallel diode is inbuilt across the SCR within the same structure.

(54)

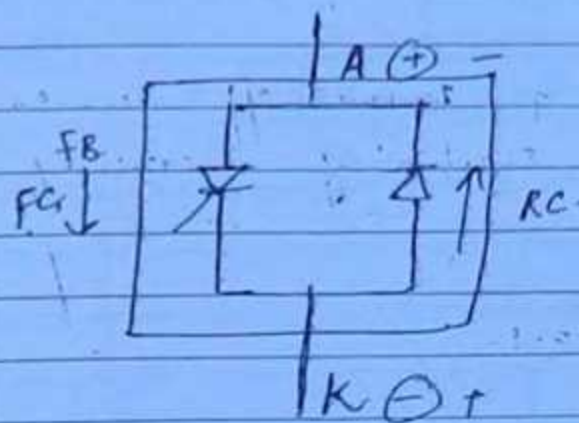



RCT is bidirectional for current but it can block only forward vlg.
RCT cannot block reverse vlg.

Applications -

In VSI, we can replace the SCR with an antiparallel diode by RCT.

TRIAC -

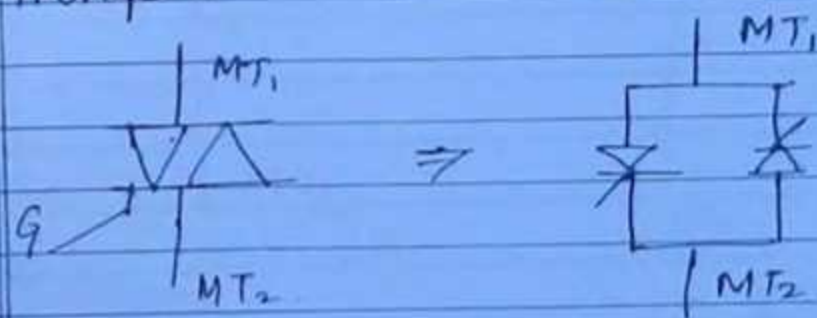

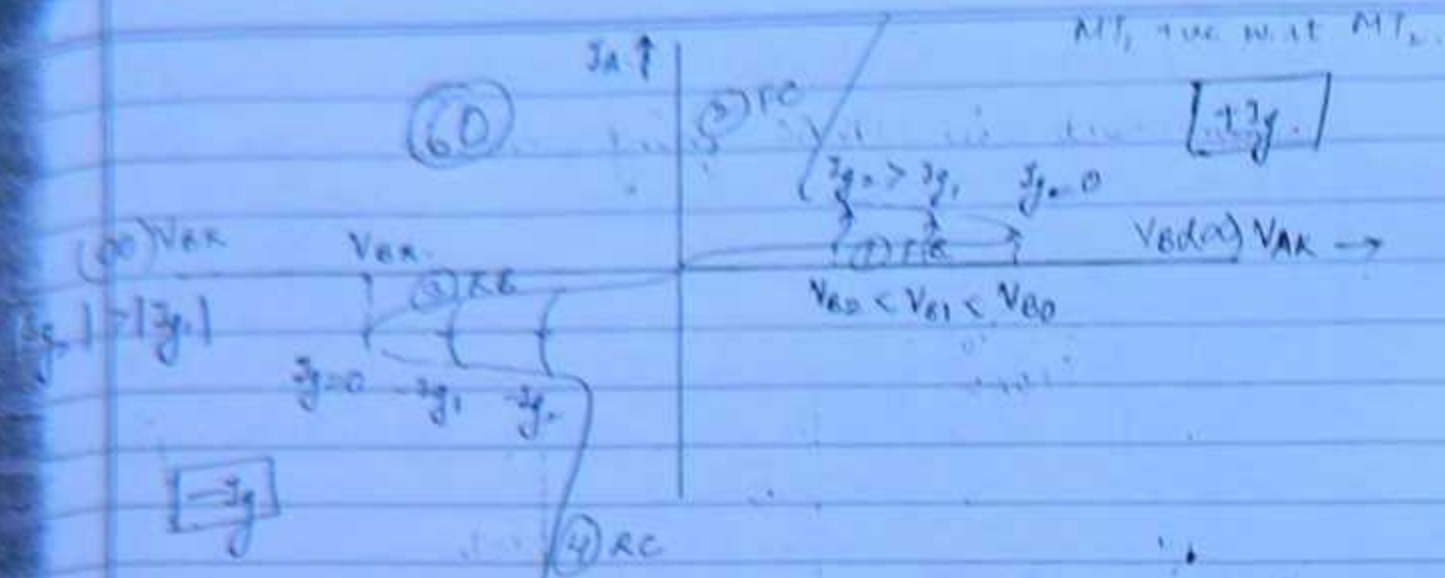

MT₁ -ve w.r.t MT₂


Applications -

used in AC v/f controllers as AC switch


Limitations of Triac -

In AC v/f controllers, it is used only for resistive loads and low inductive loads. It is not preferred for high inductive loads with high time constant.

DIAC

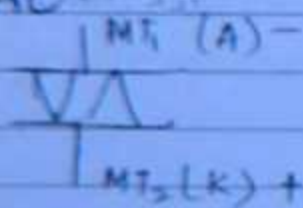

MT₁ +ve w.r.t MT₂

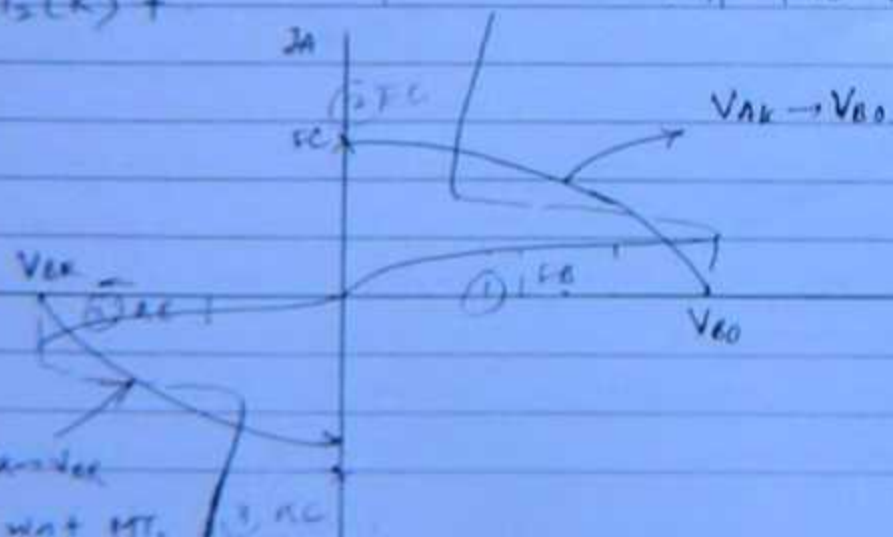


Applications -

Used in TRIAC firing circuit.


(6)

TRIAC firing circuit using DIAC

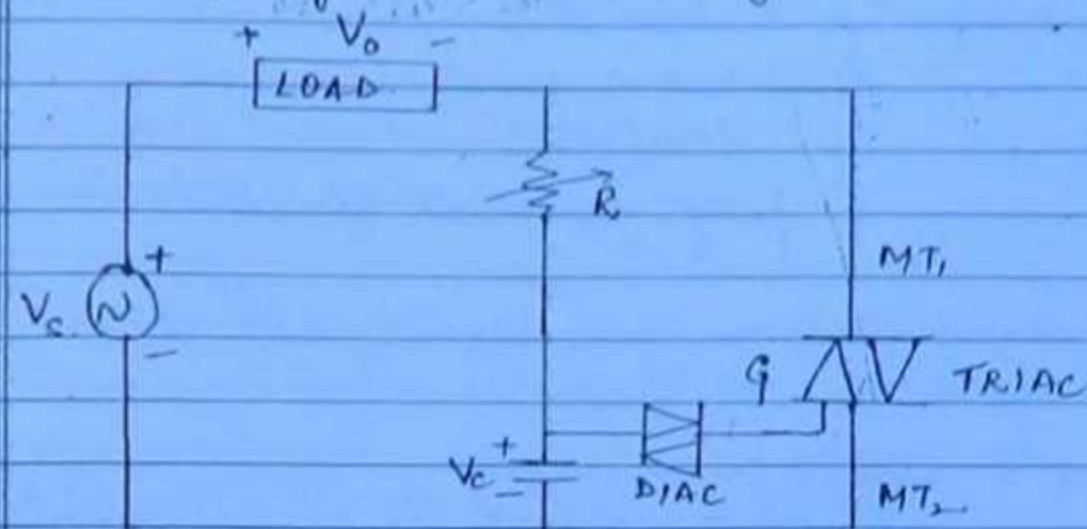


different DA and architectures also DA can have

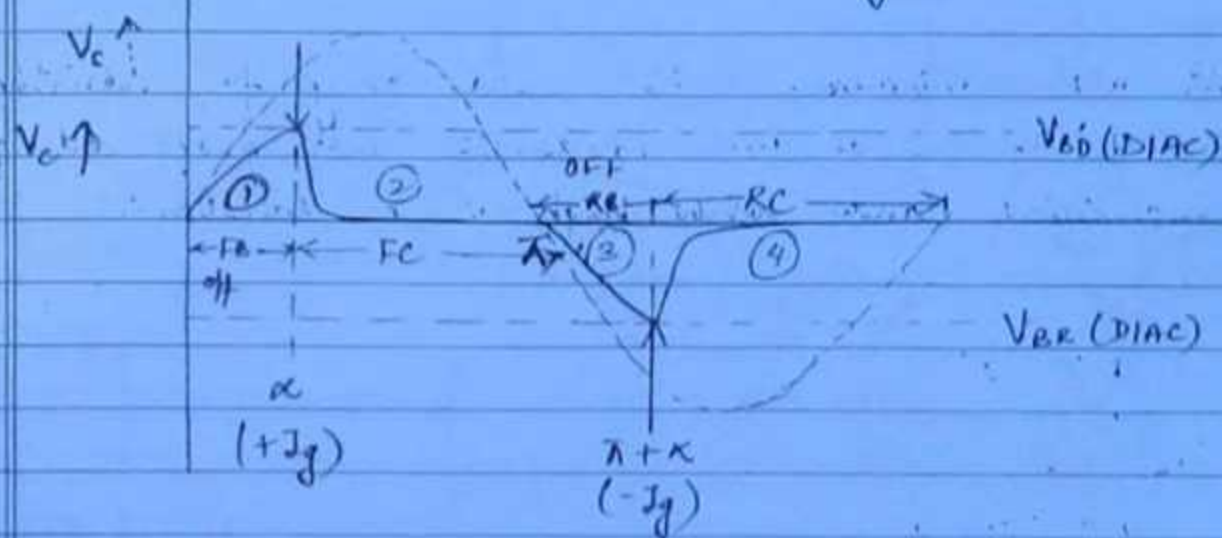main ck $\rightarrow$ AC vlg' controller.



POWER TRANSISTORS -

1. POWER BJT -

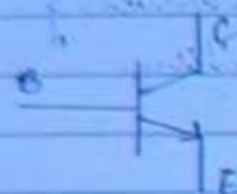



C, E $\Rightarrow$ Major terminals

B $\Rightarrow$ Control terminal

(ON/OFF)

$\therefore$ fully controlled device

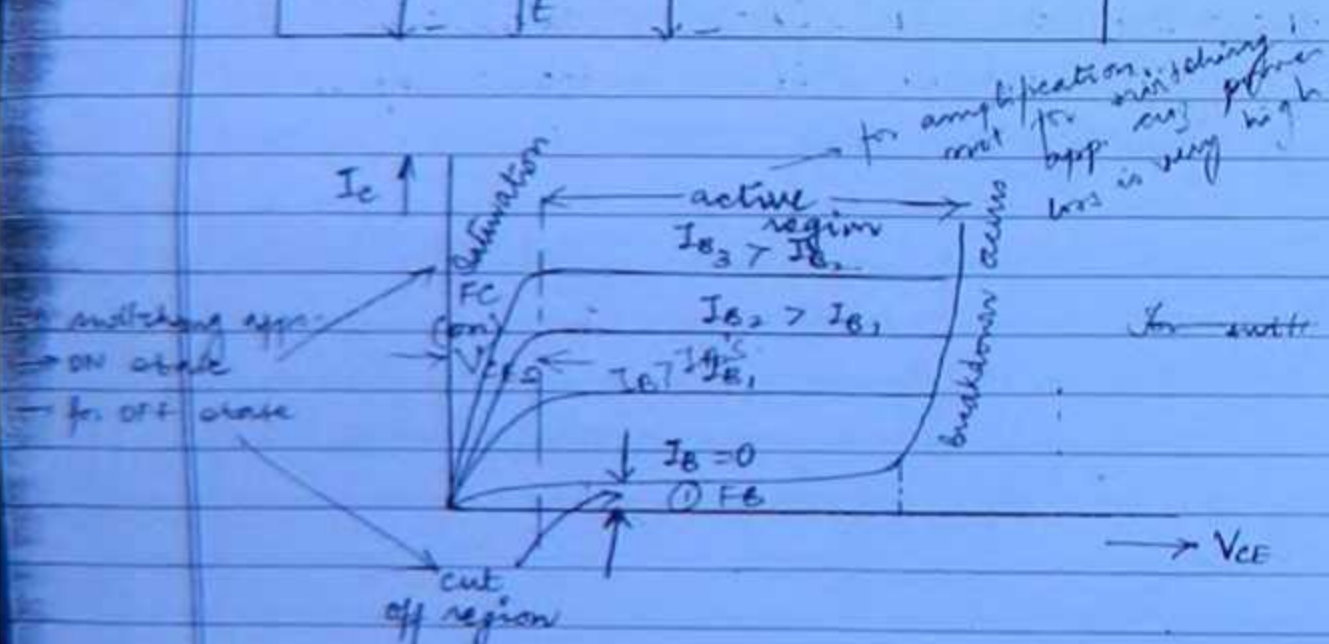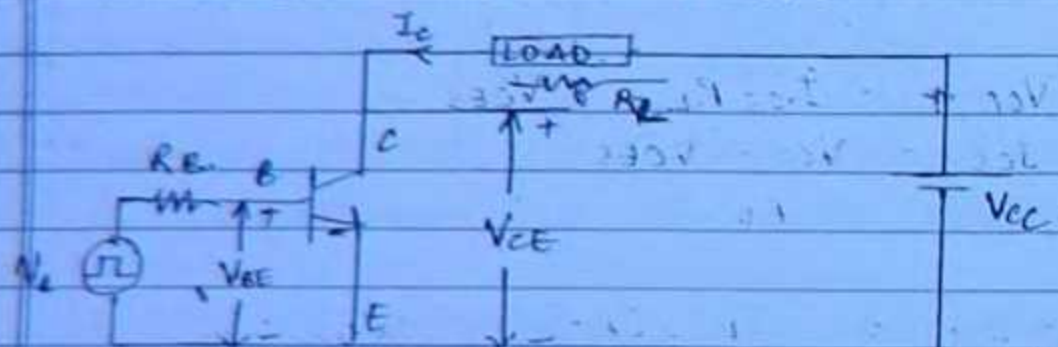* Here we require continuous gate signal (base) to maintain the device in ON state.



$I_{B2} \rightarrow$ min^m base current required to drive the transistor into saturation.

* For switching applications in PE, the transistor should be operated in the cut-off region for OFF state & saturation region for ON state. Active region is not preferred for switching applications. It's only preferred in amplifiers.

Consider transistor in

Saturation region

$$V_{CE} = V_{CES}$$

$$I_C = I_{CS}$$


KVL $\rightarrow V_{CC} = I_{CS} R_L + V_{CES}$

$$I_{CS} = \frac{V_{CC} - V_{CES}}{R_L}$$

$$I_{BS} = \frac{I_{CS}}{\beta} \quad \text{if } I_B > I_{BS} \rightarrow \text{saturation}$$

$$I_B < I_{BS} \rightarrow \text{active region}$$

Switching Characteristics of BJT -

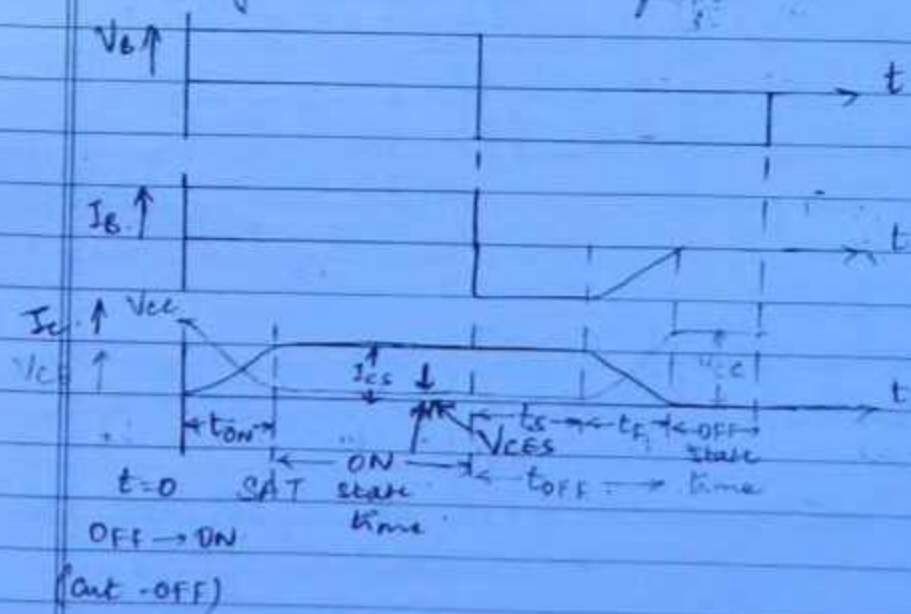


As during storage time, stored charges present in the base region is removed. (64)

Instantaneous power loss during t_{on} process $P(t) = V_{CE}(t) I_c(t)$

Energy lost during turn-on process $= \int_0^{t_{on}} P(t) dt$

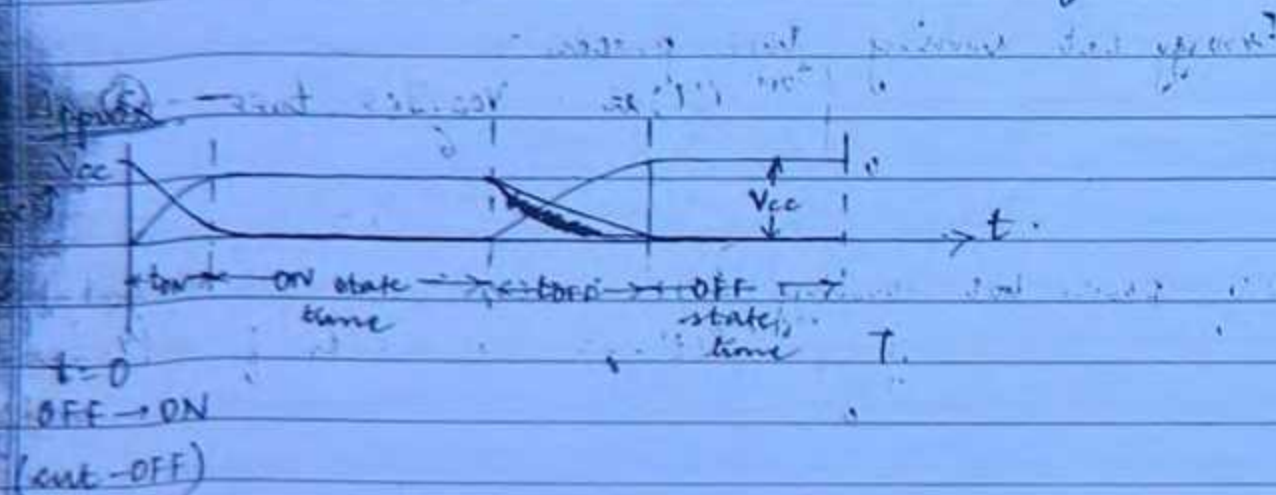Avg power lost during turn-on process $= \frac{1}{T} \int_0^{t_{on}} P(t) dt$



t_{on} process
 $I_c = \left(\frac{I_{CS}}{t_{on}} \right) t$

$V_{CE} = \left(\frac{-V_{CC}}{t_{on}} \right) t + V_{CC}$

t_{off} process
 $I_c = \left(\frac{-I_{CS}}{t_{off}} \right) t + I_{CS}$

$V_{CE} = \left(\frac{V_{CC}}{t_{off}} \right) t$

$$P(t) = V_{CE}(t) I_c(t)$$

$$= \left[\left(\frac{-V_{CC}}{t_{on}} t \right) + V_{CC} \right] \left[\left(\frac{I_{CS}}{t_{on}} \right) t \right]$$

Energy lost during t_{on} process $= \int_0^{t_{on}} P(t) dt = \frac{V_{CC} \cdot I_{CS} \cdot t_{on}}{6}$ (1)

Aug power lost during t_{on} process $= \frac{1}{T_0} \int_0^{t_{on}} P(t) dt$

$$= \frac{V_{CC} I_{CS} t_{on}}{6} f \quad (2)$$

Instantaneous power loss during t_{off} process

$$P(t) = V_{CE}(t) I_C(t)$$

$$= \left(\frac{V_{CC}}{t_{off}} t \right) \left(-\frac{I_{CS}}{t_{off}} t + I_{CS} \right)$$


Energy lost during t_{off} process =


$$\int_0^{t_{off}} P(t) dt = \frac{V_{CC} I_{CS} t_{off}}{6} \quad (3)$$

Avg power lost during t_{off} process =

$$\frac{1}{T_0} \int_0^{t_{off}} P(t) dt = \frac{V_{CC} I_{CS} t_{off}}{6} f \quad (4)$$

2 POWER MOSFET -

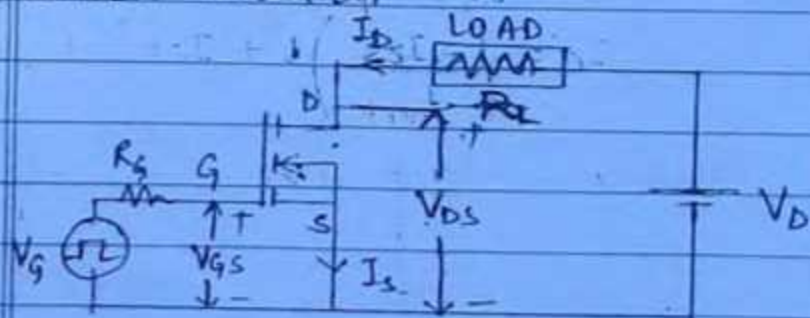

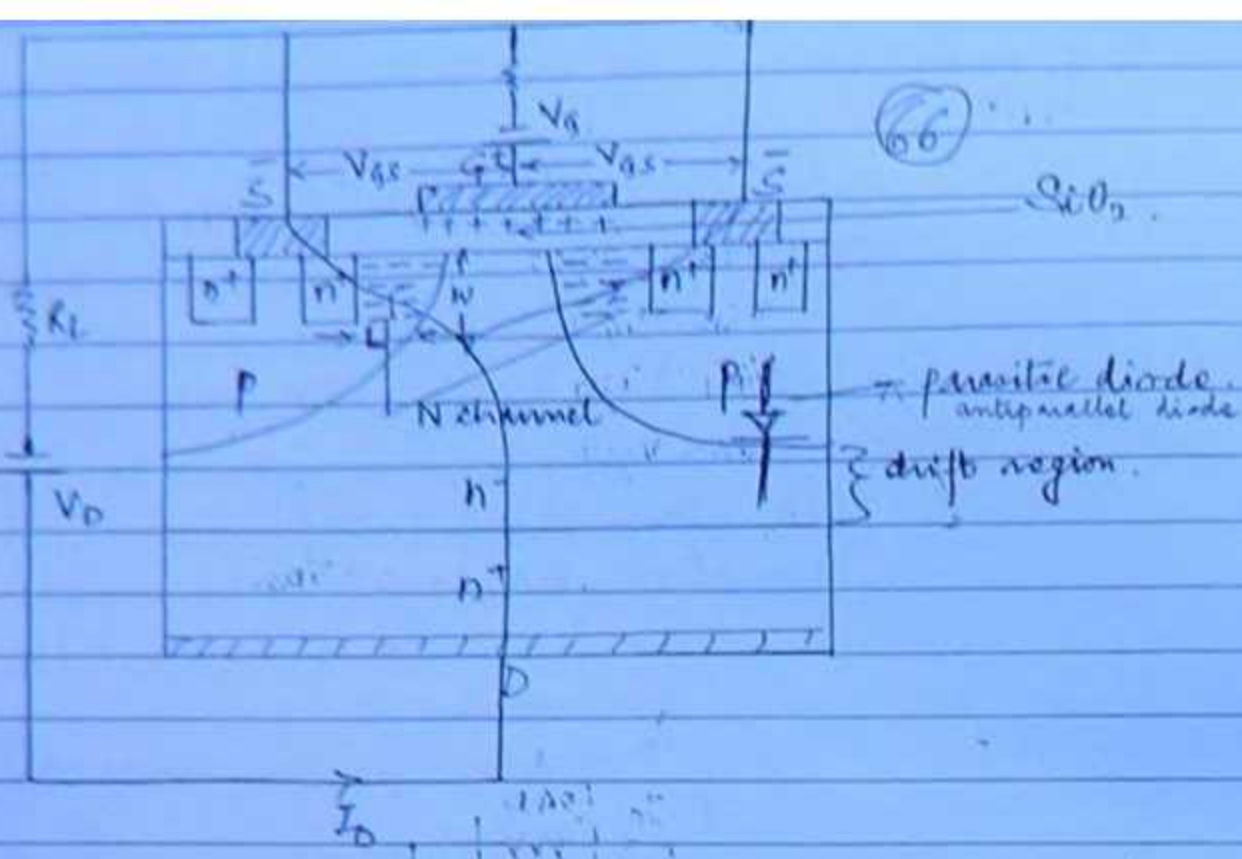

How MOSFET works:

The MOSFET starts conducting only after the formation of N-channel when positive gate signal is given. Here the conduction is only due to majority carriers, since there is no charge carrier f .

The reverse & recovery time delay is very much reduced. Hence MOSFET operates at high switching frequency.


$$V_{GS} \uparrow \therefore W \uparrow \therefore R_{ch} \downarrow \therefore I_D \uparrow$$

$$V_{GS} \uparrow, I_D \uparrow$$


$$I_D \uparrow, I_C \uparrow$$

$$\text{channel resistance} \downarrow R_{ch} \propto \frac{L}{W \uparrow}$$

$$V_{GS} \uparrow, W \uparrow$$

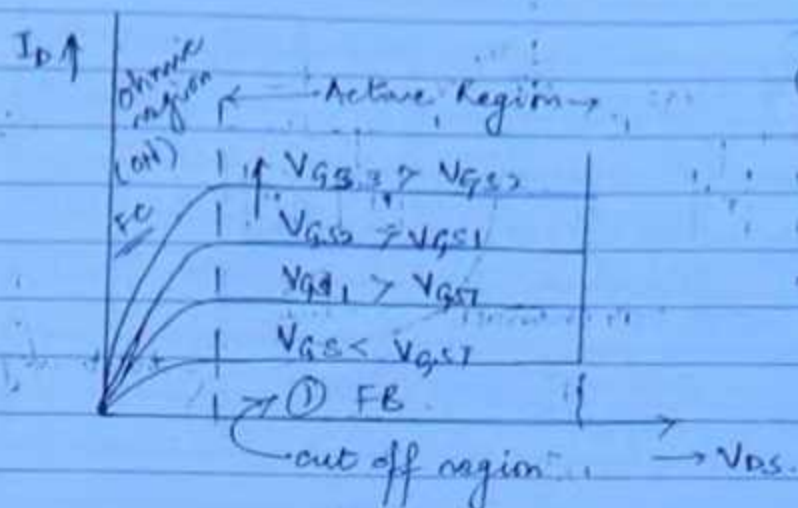


3 IGBT -

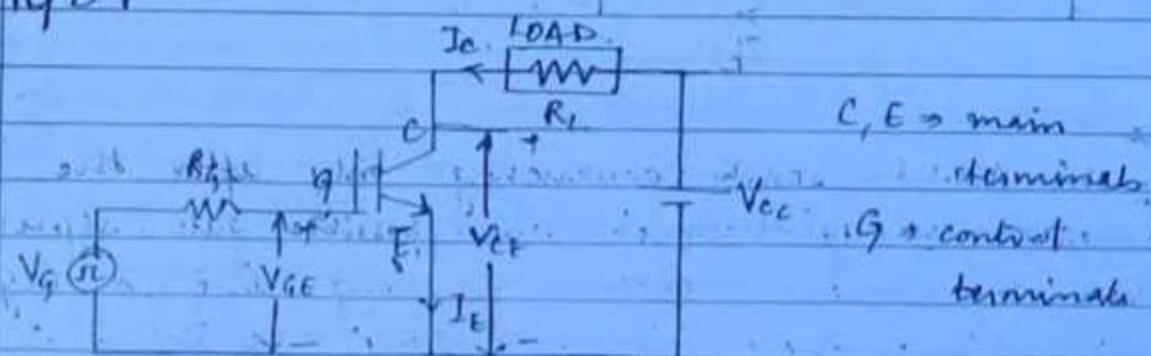


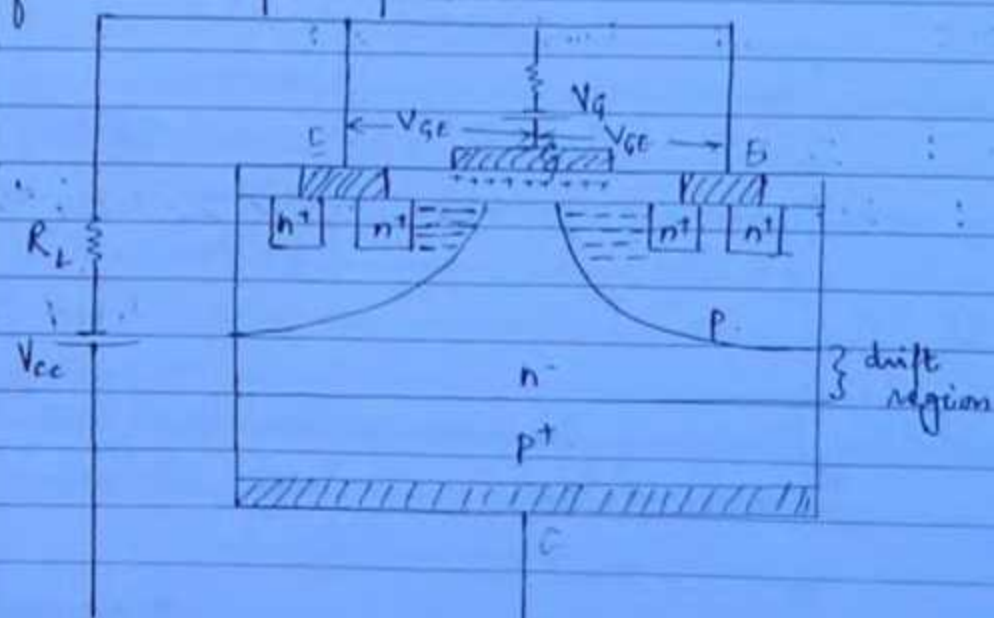9. control
termin

IGBT is a hybrid device that gives the advantages of both MOSFET & BJT.



drift
region

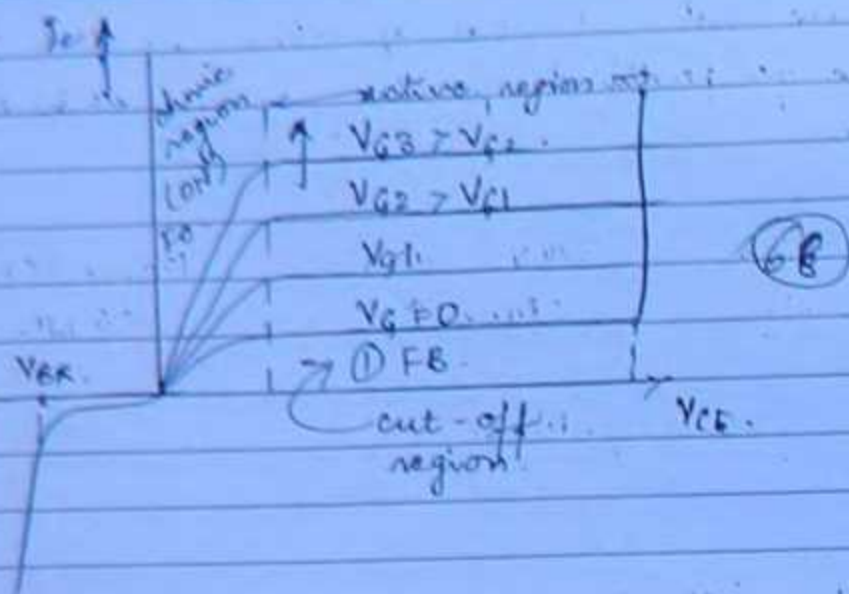

POWER BJT	POWER MOSFET	IGBT
1. Bipolar device	Unipolar	Bipolar
2. Current controlled device	Voltage controlled device	Voltage controlled device
3. Low i/p impedance	high i/p impedance	high i/p impedance
4. on state v/d drop & conduction loss is less	more	less
5. Switching loss higher	lower low	lower low
6. Negative Temp co-eff for $R_{DS(on)}$ Temp ↑ $R_{DS(on)}$ & I_T ↓	Positive Temp co-eff for $R_{DS(on)}$	Positive Temp co-eff for $R_{DS(on)}$
∴ Secondary Breakdown occurs	Secondary Breakdown will not occur	Secondary Breakdown will not occur

7. BJTs are not advisable for parallel operation. Parallel operation is possible. Parallel operation is possible.

(69)

8. Ratings

1200V, 800A
10-20 KHz



500V, 140A
1 MHz ↑

1200V, 500A
50 KHz

App

SMPS

chapter 1 CWB

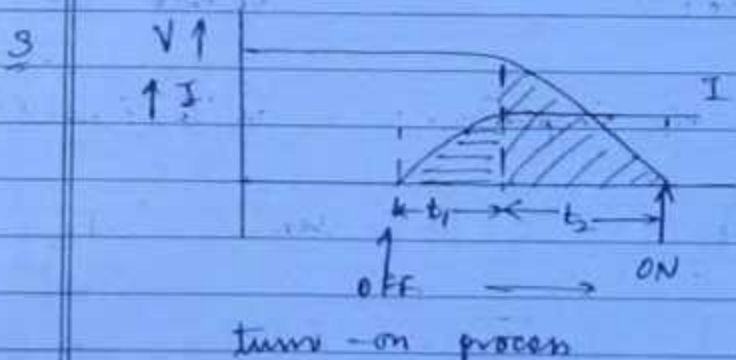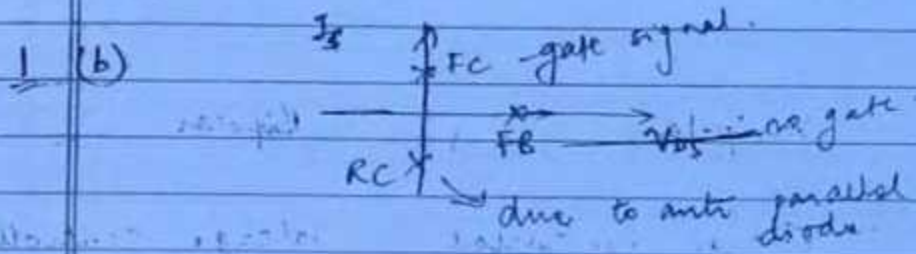


$$\text{Energy lost during } t_1 = V \int_0^{t_1} I dt$$


$$= V \cdot \frac{1}{2} I t_1 = \frac{1}{2} V I t_1$$

$$\text{Energy lost during } t_2 = I \left(\int_0^{t_2} V dt \right) = I \cdot \frac{1}{2} V t_2 = \frac{1}{2} V I t_2$$
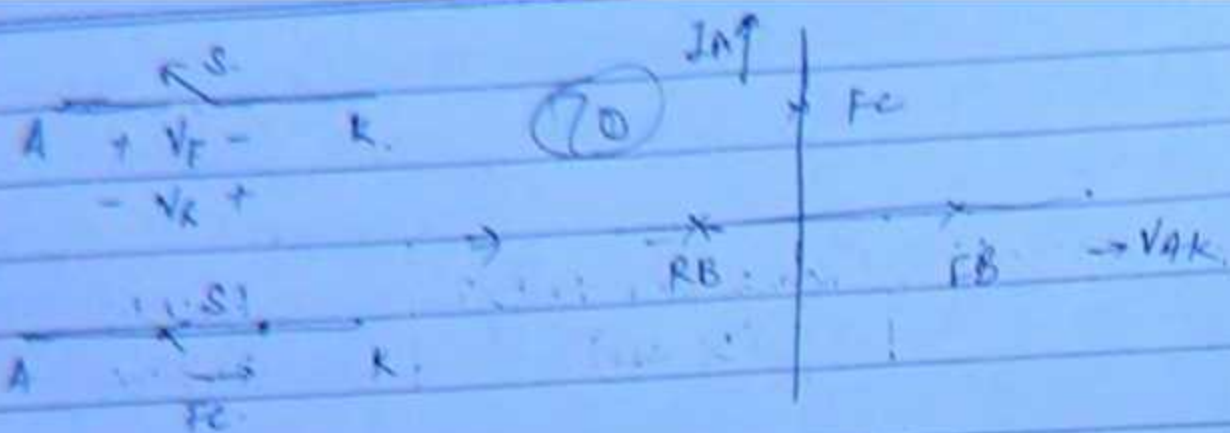
$$\text{Total} = \frac{1}{2} V I (t_1 + t_2) \quad (a)$$






Ans (c)

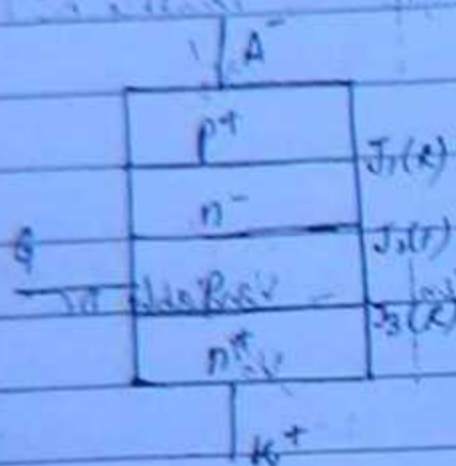

P + temp r Ic1


RECTIFIERS

(7)

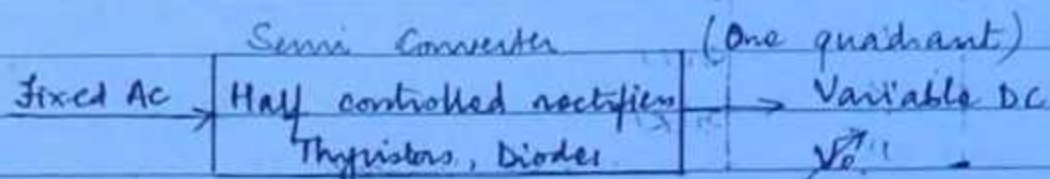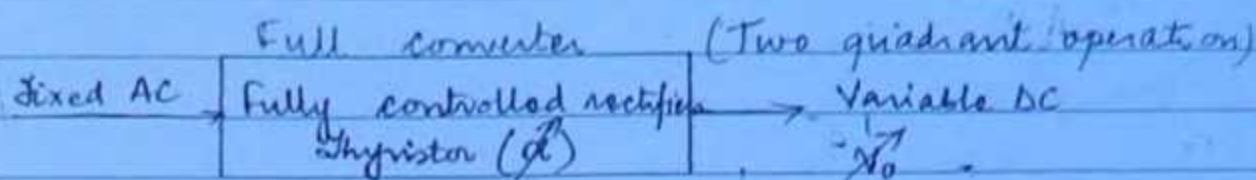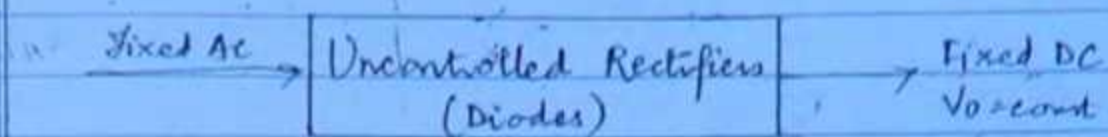


Classification of Converters based on Pulse number (m)


1. One pulse converter

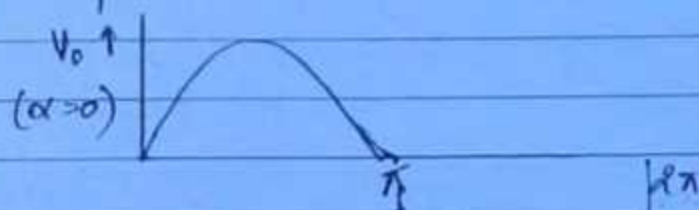

2. Two pulse converter

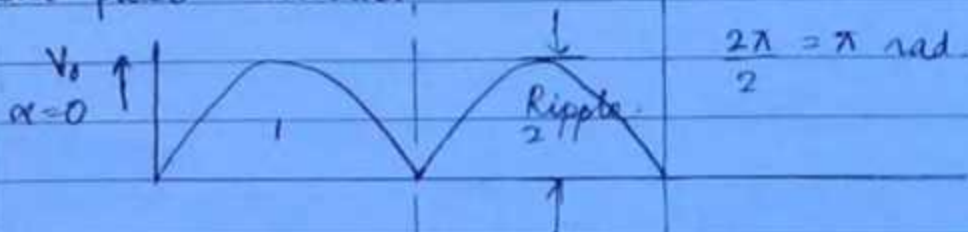


3. Three pulse converter

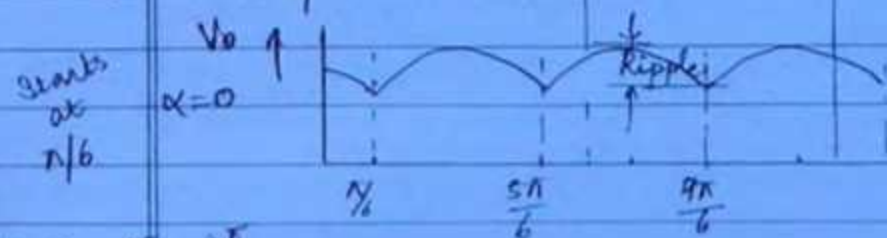

$$\text{So } \frac{\pi}{6} + \frac{\pi}{6} = \frac{\pi}{3}$$

Output ripple frequency = $f_0 = m f_s$
 peak to peak

4. 6 pulse converter.

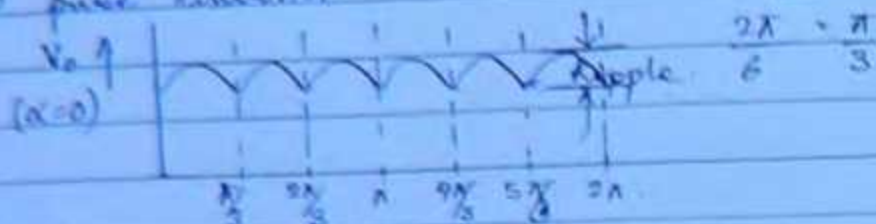

$$\frac{2\pi}{6} = \frac{\pi}{3}$$

$$f_0 = 6f_s$$

as $\uparrow$ ripple $\downarrow$ $\therefore$ harmonics $\downarrow$
 that's why we classify converters
 based on pulse number.


Applications

Performance of a DC motor fed with converters -
 for R loads (e.g. heater) harmonics are also useful so take V_{o1} not V_o

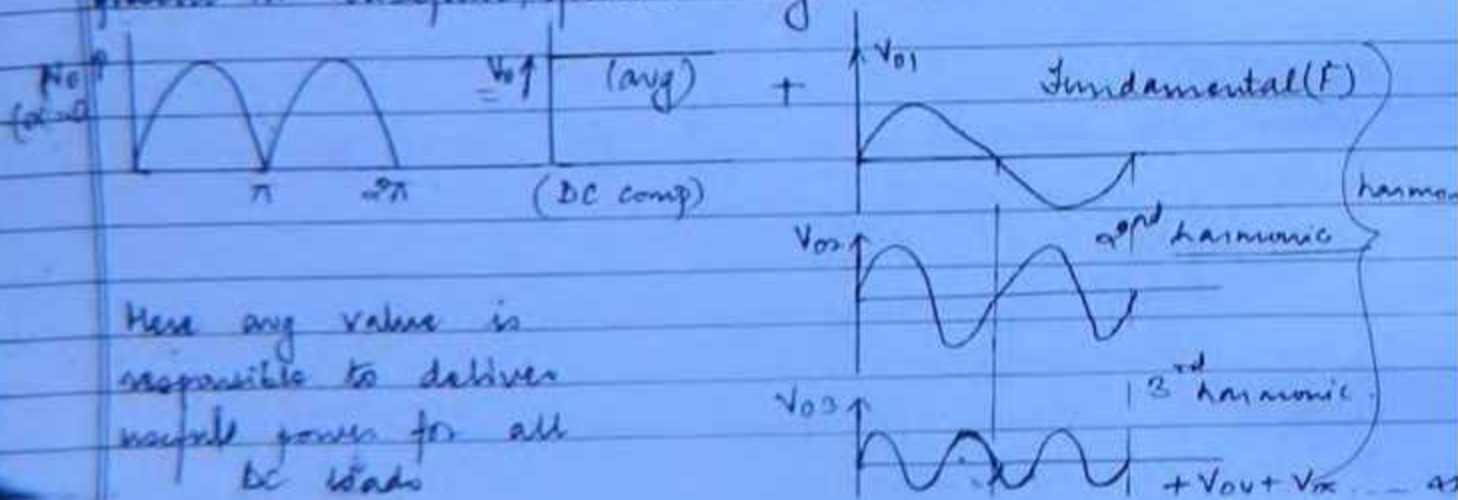1. Harmonics will overheat machine windings
 $\therefore$ we cannot utilise the m/c to its full capacity.
 $\therefore$ we must derate the m/c when fed with converters.
2. Harmonics produce pulsating torque in the motor
 $\therefore$ hence smooth rotation is not possible.

Harmonic Analysis on DC side of converter (V_o)

Output vlg waveform of a two pulse converter is distorted with harmonics. To find harmonic content present in waveform, Fourier analysis is done.



$$V_o = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

$$V_o = a_0 + \sum_{n=1}^{\infty} C_n \sin(n\omega t + \phi_n)$$

↑
avg (DC comp) where $C_n = \sqrt{a_n^2 + b_n^2}$

$$V_{or} = \sqrt{V_o^2 + (V_{o1})_{rms}^2 + (V_{o2})_{rms}^2 + (V_{o3})_{rms}^2 + \dots}$$

↑ ↑
RMS avg

Squaring both sides

$$V_{or}^2 = V_o^2 + (V_{o1})_{rms}^2 + (V_{o2})_{rms}^2 + (V_{o3})_{rms}^2 + \dots$$

$$\sqrt{V_{or}^2 - V_o^2} = \sqrt{(V_{o1})_{rms}^2 + (V_{o2})_{rms}^2 + (V_{o3})_{rms}^2 + \dots}$$

RMS value of harmonics

VRF = Voltage Ripple Factor

→ It is the measure of harmonics on DC side of converter.

$$VRF = \frac{\sqrt{V_{or}^2 - V_o^2}}{V_o} = \sqrt{\left(\frac{V_{or}}{V_o}\right)^2 - 1} = \sqrt{FF^2 - 1}$$

FF = form factor
= $\frac{(rms)}{(avg)}$

$$\boxed{VRF = \sqrt{FF^2 - 1}}$$

Quality of perfect DC -

1. $V_o = V_{av}$
avg rms

(74)

without harmonics $FF = 1$

with harmonics $FF > 1$

$FF \downarrow$ approaching unity
 $\Rightarrow$ smoothness of
waveform is improved
towards DC.

2. $FF = 1$

3. $V_{RF} = 0$

$\therefore$ no harmonics. no ripple.

• Form Factor $\rightarrow$ gives the information of shape of the waveform.

Harmonic analysis on AC side of converter -

* Consider an inverter. Output vlg waveform of inverter is not perfect AC. Its distorted with harmonics.

* For all AC loads, fundamental is responsible to deliver useful power.

$$V_{or} = \sqrt{V_o^2 + (V_{o1})_{rms}^2 + (V_{o2})_{rms}^2 + (V_{o3})_{rms}^2 + \dots}$$

$\uparrow \quad \uparrow$
RMS avg

$$\sqrt{V_{or}^2 - (V_{o1})_{rms}^2} = \sqrt{V_o^2 + (V_{o2})_{rms}^2 + \dots}$$

[THD]


~~Use~~ Total Harmonic Distortion = Method of harmonics on AC side of the converter.

$$THD = \frac{\sqrt{V_{or}^2 - V_{o1}^2}}{V_{o1}}$$

Distortion Factor (g) $\rightarrow g = \frac{(V_{o1})_{rms}}{V_{or}}$

(25)

w/o harmonics $g = 1$

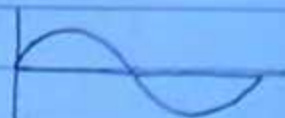

with harmonics $g < 1$ [$\because (V_{o1})_{rms} < V_{or}$]


As $g \uparrow$ & approaches unity, smoothness of waveform is improved towards AC.


Qualities of perfect AC

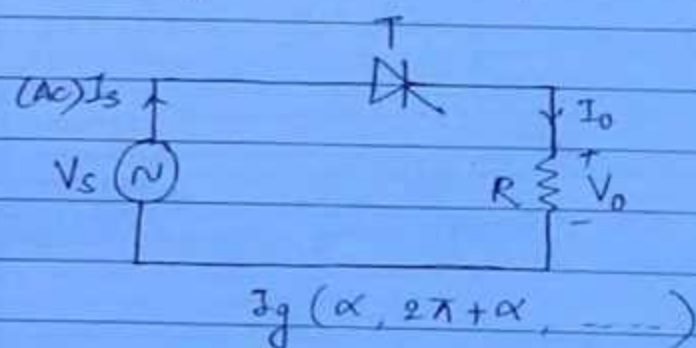1. $V_{or} = (V_{o1})_{rms}$
2. $g = 1$
3. $THD = \left(\frac{1}{g^2} - 1 \right)^{1/2}$

for perfect AC, $THD = 0$
 $\Rightarrow$ no harmonics

1 ϕ Half Wave Rectifier (one pulse converter)



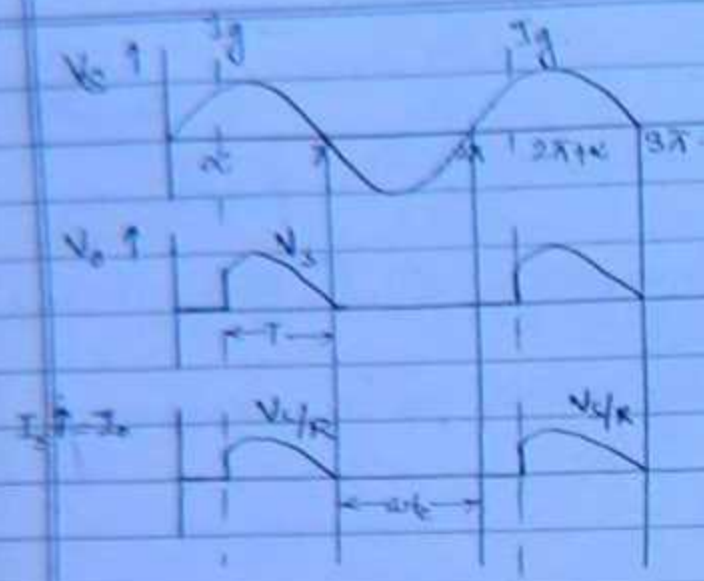

(96)

$$\omega t_c = \pi$$

$$t_c = \frac{\pi}{\omega}$$

$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$(I_o)_{avg} = I_o = \frac{V_o}{R} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

DC comp

Disadvantages -

- Source current contains DC component & saturates the supply transformer core.

$$\begin{aligned} V_{rms} = V_{or} &= \left\{ \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2} \\ &\Rightarrow V_{or} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \left(\frac{1 - \cos 2\omega t}{2} \right) d(\omega t) \right\}^{1/2} \\ &\Rightarrow V_{or} = \frac{V_m}{2\sqrt{\pi}} \left\{ (\omega t)_{\alpha}^{\pi} - \frac{1}{2} (\sin 2\omega t)_{\alpha}^{\pi} \right\}^{1/2} \end{aligned}$$

$$V_{or} = \frac{V_m}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}}$$

(27)

$$P_{in} = V_{or} I_{or} \cos \phi$$

$$P_o = V_{or} I_{or}$$

$$P_{in} = P_o$$

$$\cos \phi = \frac{V_{or} I_{or}}{V_{or} I_{or}}$$

$$\boxed{PF = \frac{V_{or}}{V_{sr}}}$$

$$PF = \frac{1}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}}$$


Power Factor depends on -

1. Firing angle - As $\alpha \uparrow$ $PF \downarrow$
2. PF also depends on the harmonics i.e. it depends on the shape of the source current waveform

$$\boxed{PF = g \times FDF}$$

$$\boxed{FDF} = \text{fundamental displacement factor}$$

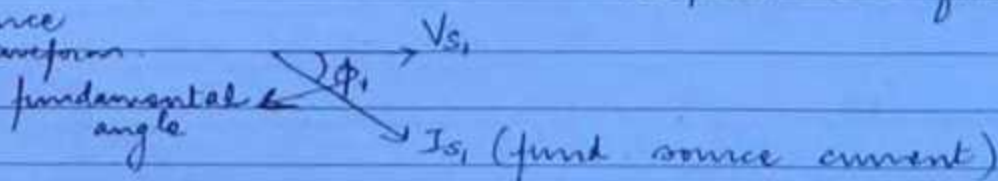distortion factor for source current waveform



$$FDF = \cos \phi_1$$

$$P_{in} = V_{s1} I_{s1} (PF) = V_{s1} I_{sh} (EDF)$$

$$PF = \frac{I_{s1}}{I_{s2}} (EDF)$$

(78)

$$PF = g(EDF)$$

$$g = \frac{I_{s1}}{I_{s2}}$$


3. PF also depends on load parameters.

Drawbacks of PE converters -

1. The converter inject harmonics into the supply system (or utility system) & reduce the quality of supply line. To rectify this problem, we must use AC filters on AC side of converter.
2. The converter draws reactive power from supply line for its operation. We must compensate the reactive power required for converter operation by using reactive power comp source on the AC side of the converter.

(II) 1 ϕ Half Wave Rectifier $\rightarrow$ RL load.

(1) α to π $T \rightarrow$ ON

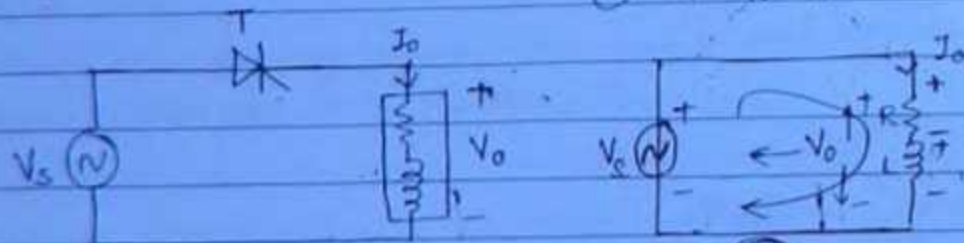

$$P_{source} \rightarrow P_{load} = \left(\frac{I^2 R + \frac{1}{2} L I^2}{2} \right)$$

L stores energy.

$$V_m \sin \omega t = R \dot{I} + L \frac{di}{dt}$$

$$I_o = I_{steady} + I_{transient}$$

(79)

$$I_{steady} = \frac{V_m \sin(\omega t - \phi)}{|Z|}$$

$$\text{where } |Z| = \sqrt{R^2 + (\omega L)^2}$$

$$\phi = \tan^{-1} \frac{\omega L}{R}$$

$$I_{transient} = K e^{-t/\tau}$$

$$I_o = I_{steady} + I_{trans}$$


$$I_o = \frac{V_m \sin(\omega t - \phi)}{|Z|} + K e^{-t/\tau}$$


$$\text{At } \omega t = \alpha \quad I_o = 0$$

$$t = \frac{\alpha}{\omega} \quad \tau = \frac{L}{R}$$

$$0 = \frac{V_m \sin(\omega t - \phi)}{|Z|} + K e^{-R\alpha/\omega L}$$

$$K = -\frac{V_m \sin(\alpha - \phi)}{|Z|} e^{R\alpha/\omega L}$$

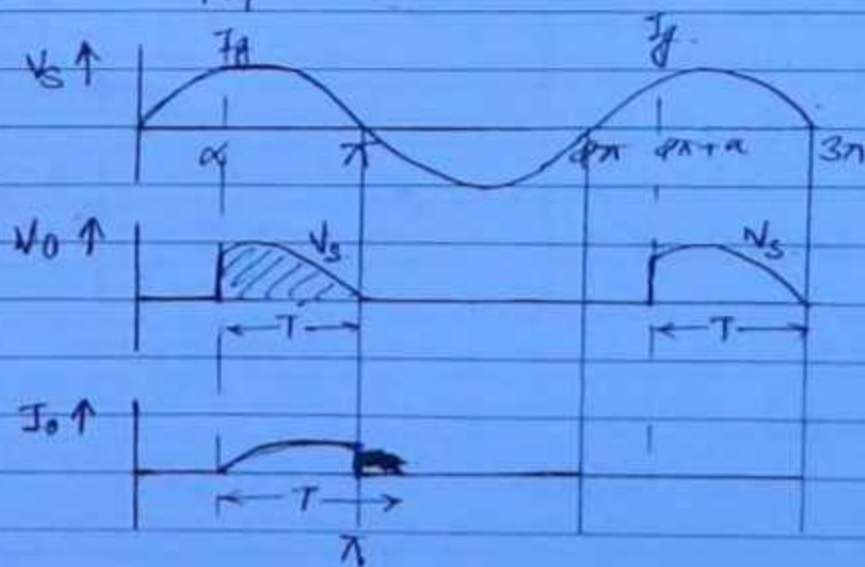


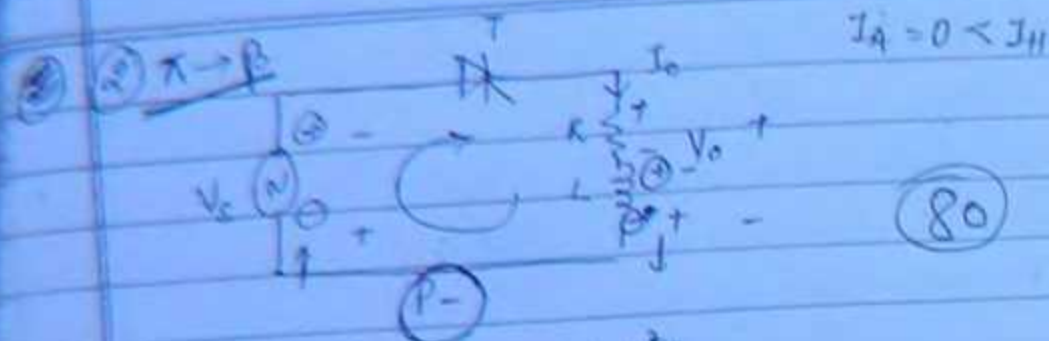

$$1. LI^2 \rightarrow \text{source} + I^2 R$$

⇒ The inductance energy maintains conduction of thyristor even in the -ve cycle until it releases the complete energy at $\omega t = \beta$.

$\beta = \text{extinction angle}$

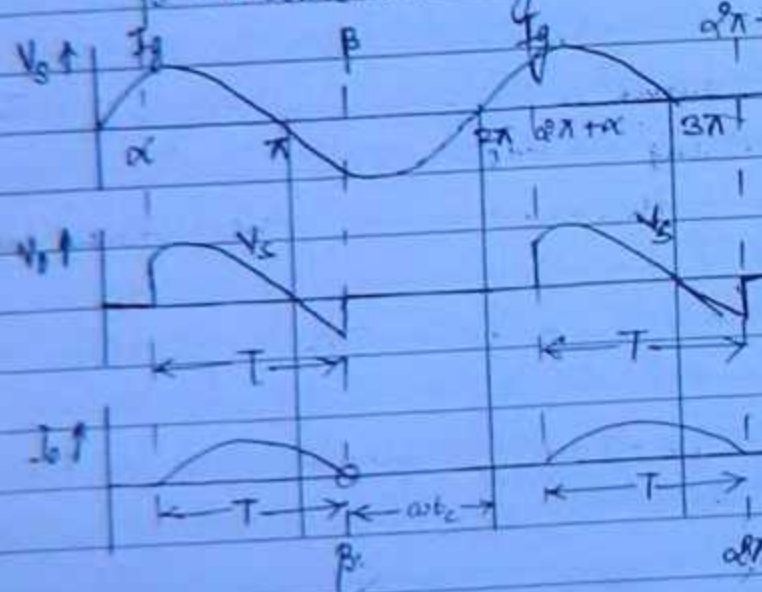

At $\omega t = \pi$ reverse v_g is applied across SCR but it's still conduct. SCR doesn't get turned OFF until $I_a = 0$.
 L : does not accept sudden change in i .
 I_a continues to flow till β → the point where L loses its energy completely.

$$\omega t_c = 2\pi - \beta$$

$$t_c = \frac{2\pi - \beta}{\omega}$$


$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t d(\omega t)$$

$$V_o = \frac{V_m}{2\pi} [\cos \alpha - \cos \beta]$$

$$V_{or} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{2\sqrt{\pi}} \left[(\beta - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right] \quad (81)$$

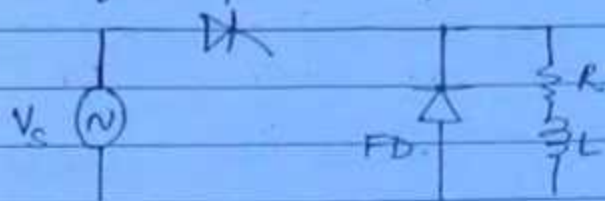(III) 1 ϕ Half Wave Rectifier $\rightarrow$ RL load with FD.




① mode is same.

② ~~free~~ freewheeling mode.

During free wheeling action, -ve spikes are removed.

L releases energy through $I^2 R \rightarrow$ takes more time $\beta \uparrow$

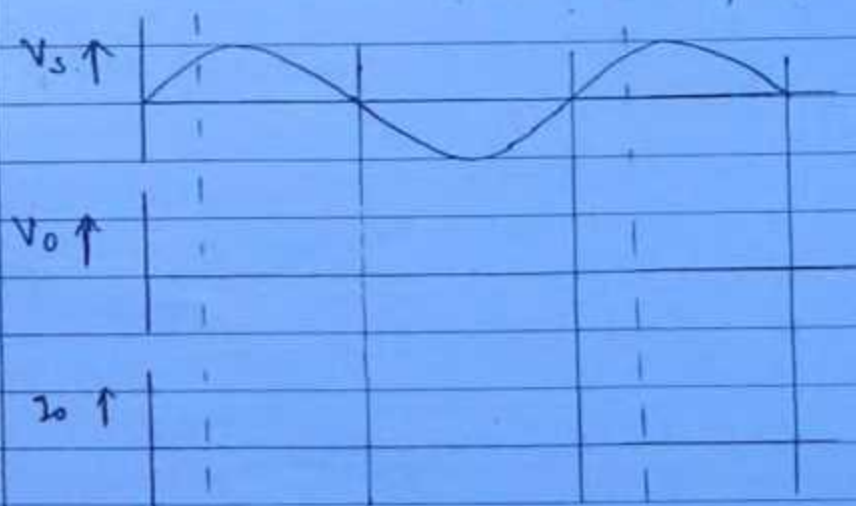smoothness improves $g \uparrow$ PF $\uparrow$




Advantages of FD -

(82)

1. PF is improved
2. no spikes in load vlg is improved. $\therefore$ this $\uparrow$ avg vlg.
3. Smoothness of output current waveform is improved as $\beta \uparrow$.
4. $\therefore$ the overall performance of the converter is improved with FD.
5. There will be freewheeling action in semiconverter $\therefore$ PF is better in semiconverter as compared to full converters.
6. Performance of semiconverter is superior to full converter.

2-12

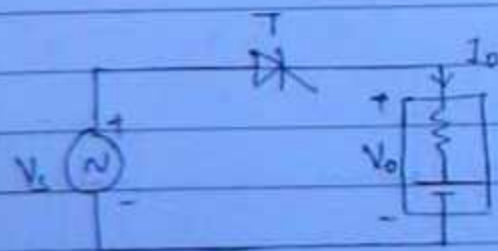Q 1- ϕ Half Wave Rectifier - charging a battery (R-E load)



At $\omega t = \theta_1$

$$V_s = E$$

$$V_m \sin \theta_1 = E$$

$$\alpha_{\min} = \theta_1 = \sin^{-1} \left(\frac{E}{V_m} \right)$$


$$\alpha_{\max} = \theta_2 = \pi - \theta_1$$

$$\theta_1 \leq \alpha \leq \theta_2$$

$$I_g(\alpha, 2\pi + \alpha, \dots)$$

$$T \rightarrow \text{ON} \Rightarrow V_o = V_s \Rightarrow V_s = I_o R + E$$
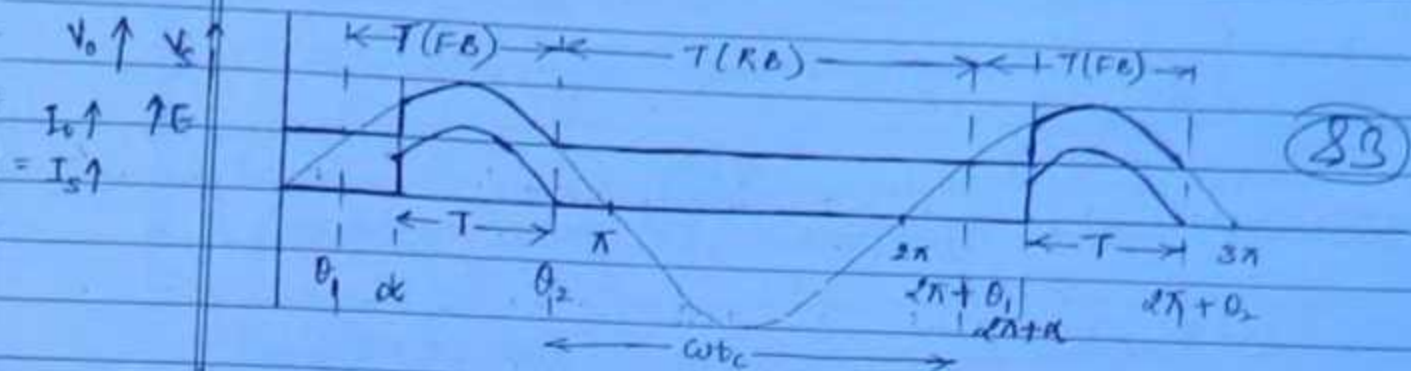
$$I_o = \frac{V_s - E}{R} = \frac{V_m \sin \omega t - E}{R}$$



$$t_c = \frac{\pi + 2\theta_2}{\omega}$$

$$PIV = V_m + E$$

$$V_o = \frac{1}{2\pi} \left[\int_{\alpha}^{\theta_2} V_m \sin \omega t d(\omega t) + \int_{\theta_2}^{2\pi + \alpha} E d(\omega t) \right]$$

$$V_o = \frac{1}{2\pi} \left[V_m (\cos \alpha - \cos \theta_2) + E (2\pi + \alpha - \theta_2) \right]$$

radians

* Avg charging current of the battery

$$I_o = \frac{1}{2\pi} \int_{\alpha}^{\theta_2} \frac{V_m \sin \omega t - E}{R} d(\omega t)$$

$$I_o = \frac{1}{2\pi R} \left[V_m (\cos \alpha - \cos \theta_2) - E (\theta_2 - \alpha) \right]$$

radians

$$P_{in} = V_{s_r} I_{s_r} (PF)$$

$$P_o = I_o^2 R + E I_o$$

$$PF = \frac{I_o^2 R + E I_o}{V_{s_r} I_{s_r}}$$


$$PF = \frac{I_o^2 R + E I_o}{V_{s_r} I_{s_r}}$$

$$I_{rms} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\beta} \left(\frac{V_m \sin \omega t - E}{R} \right)^2 d(\omega t) \right\}^{1/2}$$

(84)

1- ϕ Full Wave Rectifiers - (2 pulse converter)

Midpoint Rectifier -

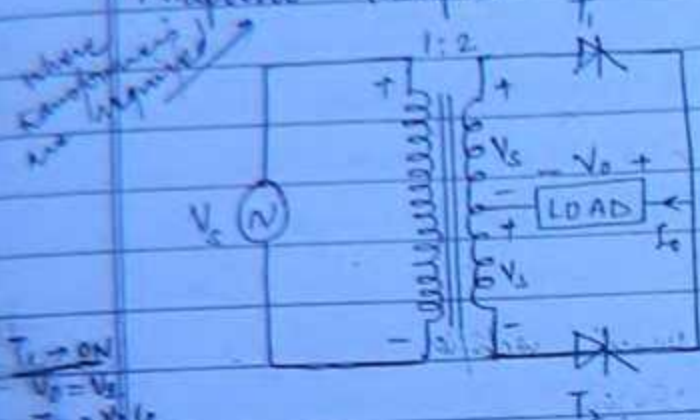


$T_1 \rightarrow ON$
 $V_o = V_s$
 $I_o = V_s/R$

$T_2 \rightarrow ON$
 $V_o = -V_s$
 $I_o = -V_s/R$

+ T_1 (FB) $I_g(\alpha, 2\pi + \alpha \dots)$
 - T_2 (FB) $I_g(\pi + \alpha, 3\pi + \alpha \dots)$

Bridge Rectifier -

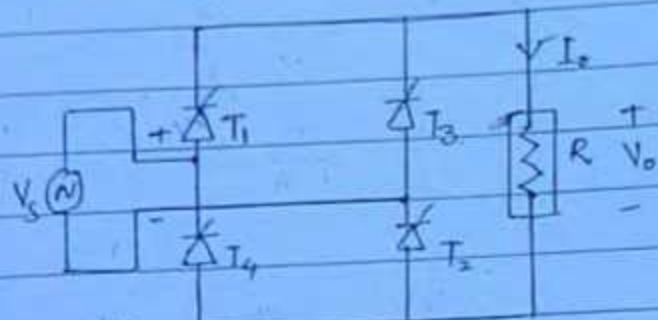


+ $T_1 T_2$ (FB) $I_g(\alpha, 2\pi + \alpha \dots)$
 - $T_3 T_4$ (FB) $I_g(\pi + \alpha, 3\pi + \alpha \dots)$

$T_1 T_2 \rightarrow ON$

$V_o = V_s$
 $I_o = V_s/R$

$T_3 T_4 \rightarrow ON$

$V_o = -V_s$
 $I_o = -V_s/R$

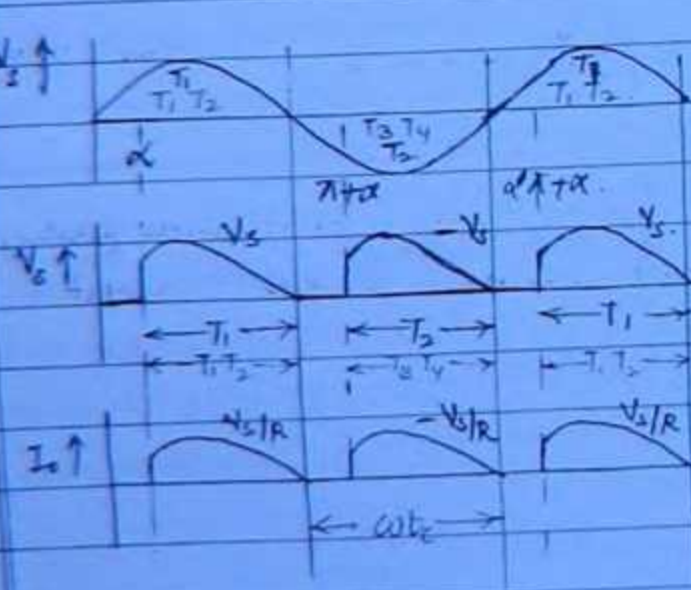

$\omega t_c = \pi$

$t_c = \frac{\pi}{\omega}$ sec

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

(85)

$$V_{or} = \left\{ \frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2}\pi} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$PIV = 2V_m$$

→ In mid-point rectifier

$$PIV = V_m$$



→ bridge rectifier

Advantages of Bridge Rectifier-

1. PIV of thyristor in bridge rectifier is half that of mid-point rectifier.
2. If same thyristors with same specifications (same v/f & current ratings) are same in both converters then power handled by bridge rectifier is double that of mid-point rectifier.

1- ϕ Full Wave Rectifiers (R-L Load) (Full converter)

Discontinuous Conduction

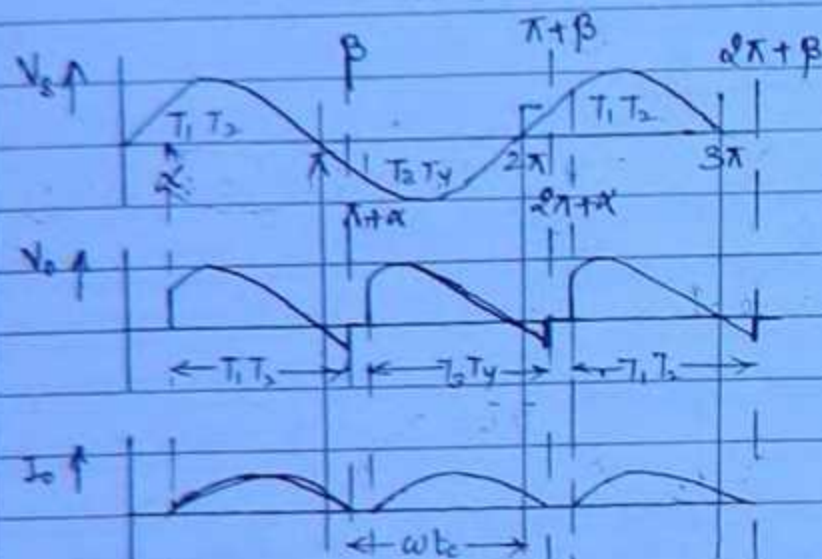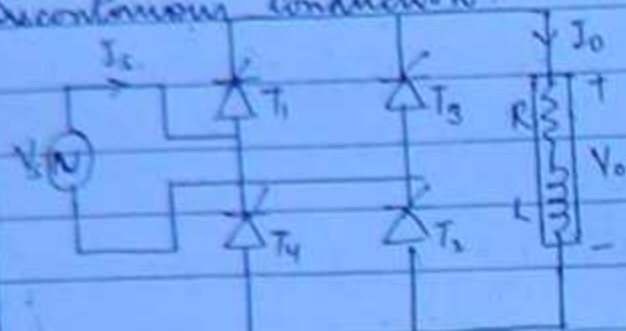

$$\omega t_c = 2\pi - \beta$$

$$t_c = \frac{2\pi - \beta}{\omega}$$

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\beta} V_m \sin \omega t d(\omega t)$$

$$V_o = \frac{V_m}{\pi} (\cos \alpha - \cos \beta)$$

$$V_{or} = \left\{ \frac{1}{\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2}\pi} \left[(\beta - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right]^{1/2}$$

Reasons for Discontinuous Conduction -


1. $L \downarrow$ [Time constant $T \downarrow = \downarrow \frac{L}{R}$] or $R \uparrow$
 $T \downarrow \therefore \beta \downarrow$ [$\beta < (\pi + \alpha)$]
2. $\alpha \uparrow$ (High value of firing angle) $\rightarrow$ less energy is stored in inductor.
3. $I_o \downarrow \rightarrow E = \frac{1}{2} I_o^2 \downarrow$ not sufficient energy.

RL Load Continuous Conduction


1. $L \uparrow$ [$\uparrow T = \uparrow \frac{L}{R}$] 2. $\uparrow T \Rightarrow \uparrow \beta$ [$\beta > (\pi + \alpha)$]

2. $\alpha \downarrow$

3. $I_o \uparrow$

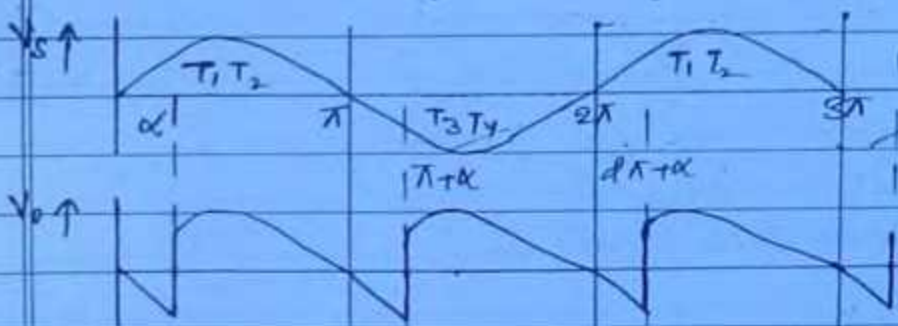


$T_1 = T_2$
 $T_3 = T_4$

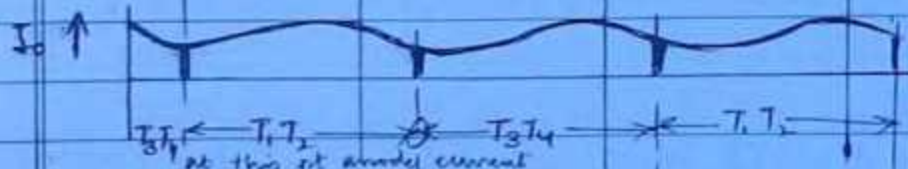

at this pt. another current of T_1, T_2 is charged. So, off time is taken from here.

For highly inductive load

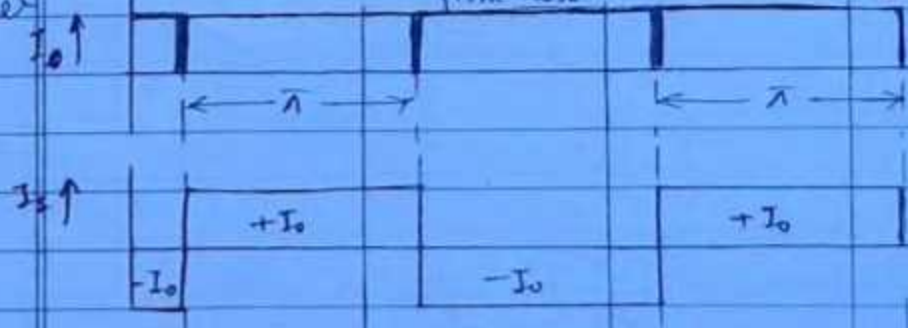

ripple free load current

$$V_o = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, d(\omega t)$$

$$V_o = \frac{2V_m \cos \alpha}{\pi}$$

(88)

$$V_o = \left\{ \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_o = \frac{V_m}{\sqrt{2}}$$

→ Squaring V_s or V_o waveform gives same waveform so their rms values are equal.

Hence Rms value of $V_s = \frac{V_m}{\sqrt{2}}$

$$\omega t_c = 2\pi - (\pi + \alpha)$$

$$t_c = \frac{\pi - \alpha}{\omega}$$

so is that of V_o

$$T_1, T_2 \rightarrow ON$$

$$I_s = I_o$$

$$T_2, T_4 \rightarrow ON$$

$$I_s = -I_o$$

Assume highly inductive load -

Conduction Angle of each thyristor = π rad [for every 2π rad]

$$(I_o)_{avg} = \frac{1}{2\pi} \int_{\alpha}^{\pi+\alpha} I_o \, d(\omega t) = \frac{I_o}{2}$$

$$= I_o \left(\frac{\pi}{2\pi} \right)$$

$$(I_T)_{avg} = \frac{I_o}{2}$$


$$(I_T)_{rms} = I_o \left(\frac{\pi}{2\pi} \right)^{1/2} = \frac{I_o}{\sqrt{2}}$$

Qo

$$I_{avg} = I_o$$


1- ϕ Half Controlled Rectifier - (Semi Converter)

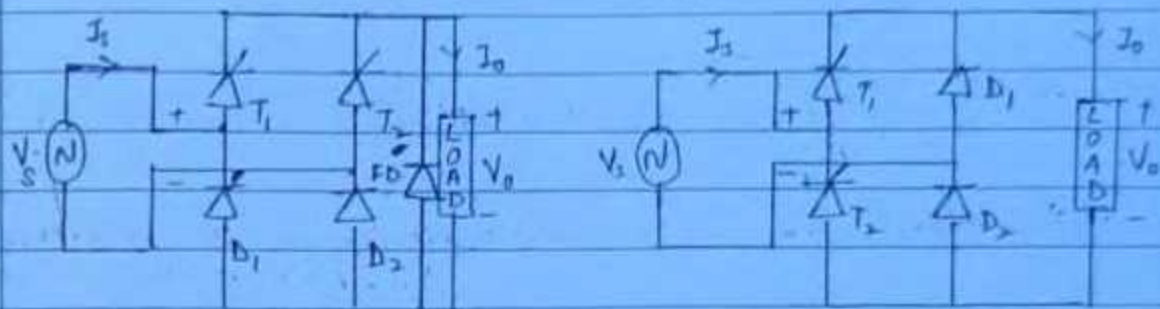Symmetrical Connection - Asymmetrical Connection -



+ $T_1 D_2$ (F)
- $T_2 D_1$ (F)


+ $T_1 D_2$ (F)
- $T_2 D_1$ (F)

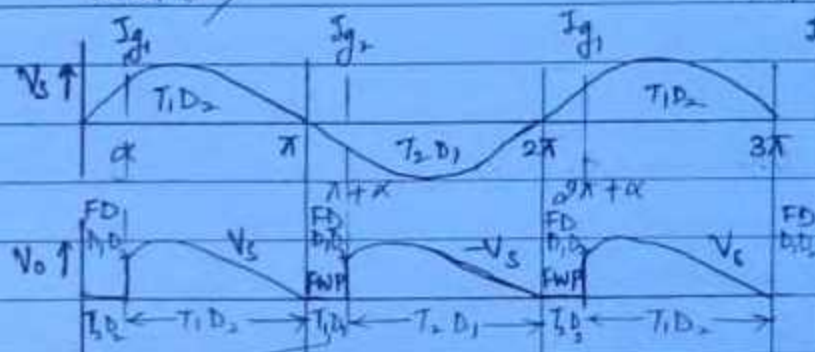

Due to freewheeling diode -ve spikes are removed. Thus the V_o becomes same as that of a load in full converter.

FWP
Free wheeling period
(that's why no need of separate FD)

Load current $I_o = 0$

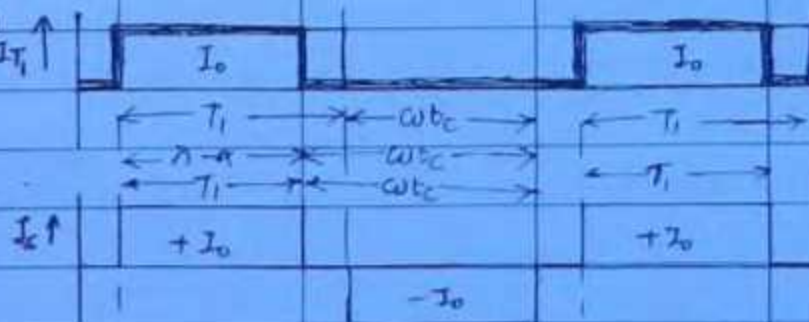

For resistive load waveform remains same for full converter & semi converter

Assume highly inductive load -

(90)

$$\pi \text{ to } \pi + \alpha \quad T_1, D_1 \rightarrow ON$$

$$\text{FWP} \quad V_o = 0$$

$$\text{FWP} \quad I_s = 0$$

$$T_1, D_2 \rightarrow ON \quad I_s = I_o$$

$$T_2, D_1 \rightarrow ON \quad I_s = -I_o$$

$$T_1 \text{ to } \pi \quad \omega t_c = \pi - (\pi + \alpha)$$

$$\boxed{t_c = \frac{\pi - \alpha}{\omega}}$$

$$\omega t_c = \alpha \pi - \pi$$

$$\bullet \boxed{t_c = \frac{\pi}{\omega}}$$

* In symmetrical connection there is a possibility of S.C across the supply when the incoming thyristor starts conducting before the outgoing thyristor stops conducting. Here the problem is severe, because before the incoming thyristor starts conducting, the free-wheeling action is through outgoing thyristor because of which S.C period is more.

* To rectify this problem we must use a separate FD.

Symmetrical connection with FD.

$$V_o = \frac{1}{\pi} \int_{\pi - \alpha}^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$V_o = \frac{V_m}{\pi} [1 + \cos \alpha]$$

$$V_{or} = \left\{ \frac{1}{\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2}\pi} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

(9)

Assume highly inductive load -

Conduction angle each thyristor = $(\pi - \alpha)$ rad [for every π rad]

$$= \pi - \alpha$$

$$2\pi$$

Conduction angle of FD = α rad [for every π rad]

$$= \frac{\alpha}{\pi}$$

$$\pi$$

$$(I_T)_{avg} = I_o \left(\frac{\pi - \alpha}{2\pi} \right)$$

$$(I_{FD})_{avg} = I_o \left(\frac{\alpha}{\pi} \right)$$



$$(I_T)_{rms} = I_o \left(\frac{\pi - \alpha}{2\pi} \right)^{1/2}$$

$$(I_{FD})_{rms} = I_o \left(\frac{\alpha}{\pi} \right)^{1/2}$$

$$I_{or} = I_o \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}$$

1 ϕ Full Converter - Charging a Battery

Q2

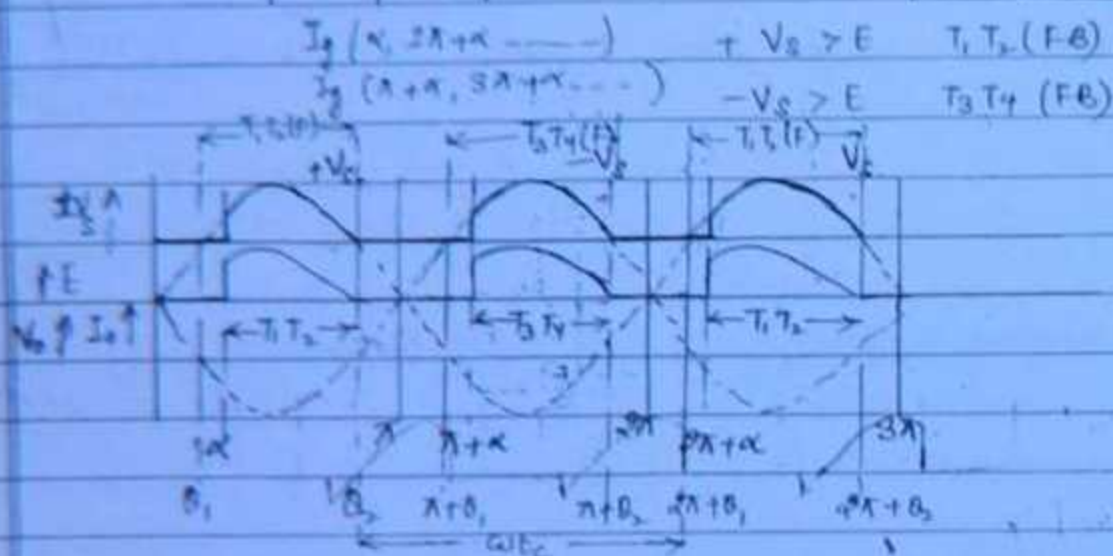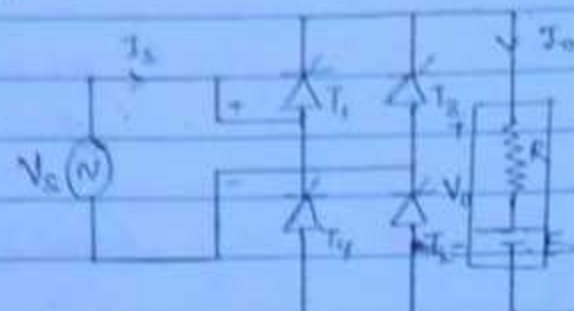

$$T_1 T_2 \rightarrow ON$$

$$V_o = V_s$$

$$I_o = \frac{V_s - E}{R}$$

$$\theta_1 = \sin^{-1} \frac{E}{V_m}$$

$$\theta_2 = \pi - \theta_1$$

$$I_o = \frac{V_m \sin \omega t - E}{R}$$

$$\omega t_c = (2\pi + \theta_1) - \theta_2$$

$$= (2\pi + \theta_1) - (\pi - \theta_1)$$

$$t_c = \frac{\pi + 2\theta_1}{\omega}$$




$$V_o = \frac{1}{\pi} \left[\int_{\theta_1}^{\pi + \alpha} V_m \sin \omega t d(\omega t) + \int_{\theta_2}^{\alpha + \pi} E d(\omega t) \right]$$

$$V_o = \frac{1}{\pi} \left[V_m (\sin \alpha - \cos \theta_2) + E (\pi + \alpha - \theta_2) \right]$$

$$I_0 = \frac{1}{\pi} \int_{\alpha}^{\beta} \left(\frac{V_m \sin \omega t - E}{R} \right) d(\omega t)$$

$$I_0 = \frac{1}{\pi R} \left[V_m (\cos \alpha - \cos \beta) - E(\beta - \alpha) \right]$$

1 ϕ Full Converter - DC Motor (RLE Load)

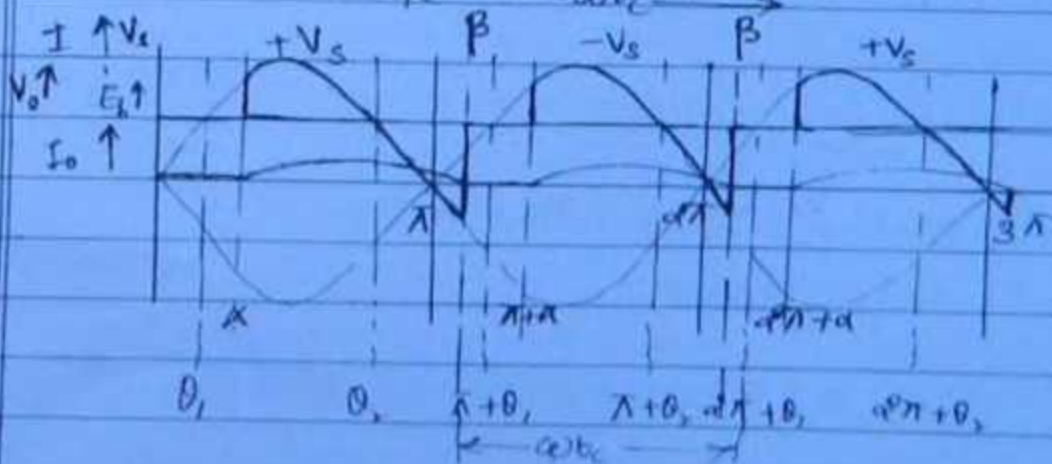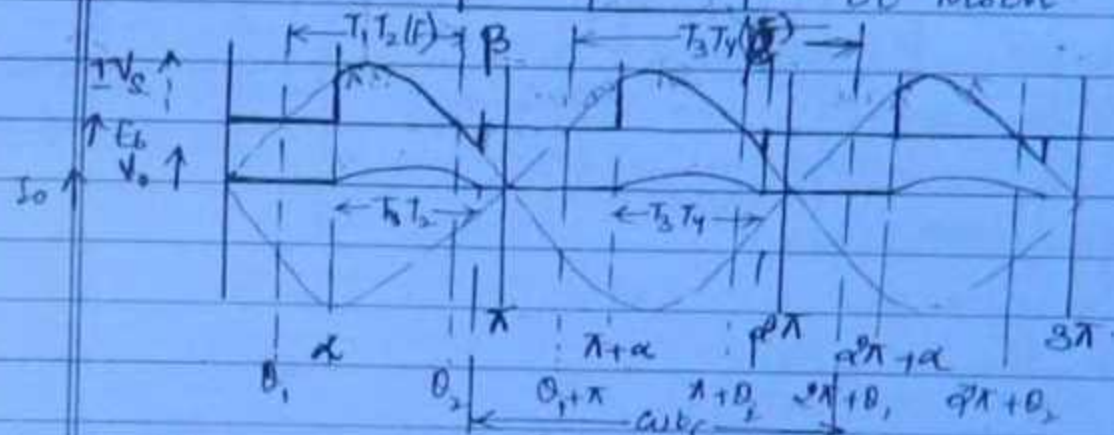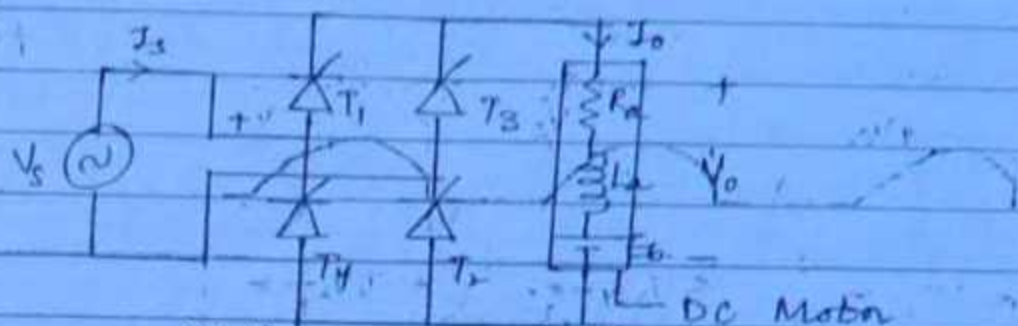

$$\omega t_c = (\alpha + \theta_i) - \beta$$

$$\downarrow t_c = \frac{\alpha + \theta_i - \beta}{\omega} \uparrow$$

(94)

For continuous conduction waveform remains same for RL & RLE load. $\therefore$

$$V_o = \frac{1}{\pi} \left[\int_{\alpha}^{\beta} V_m \sin \omega t \, d(\omega t) + \int_{\beta}^{\pi + \alpha} E_b \, d(\omega t) \right]$$

$$V_o = \frac{1}{\pi} \left[V_m (\cos \alpha - \cos \beta) + E_b (\pi + \alpha - \beta) \right]$$


For continuous conduction +

$$V_o = \frac{V_m}{\pi} \cos \alpha \quad \rightarrow \text{RL / RLE}$$

$$I_o = \frac{V_o}{R} \quad \rightarrow \text{RL}$$

$$I_o = \frac{V_o - E_b}{R_a} \quad \rightarrow \text{RLE}$$


1 ϕ Semiconverter - DC Motor (RLE load)

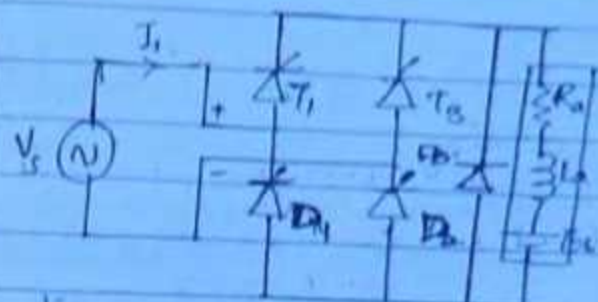

(95)


$\beta < \pi$

FD will not conduct

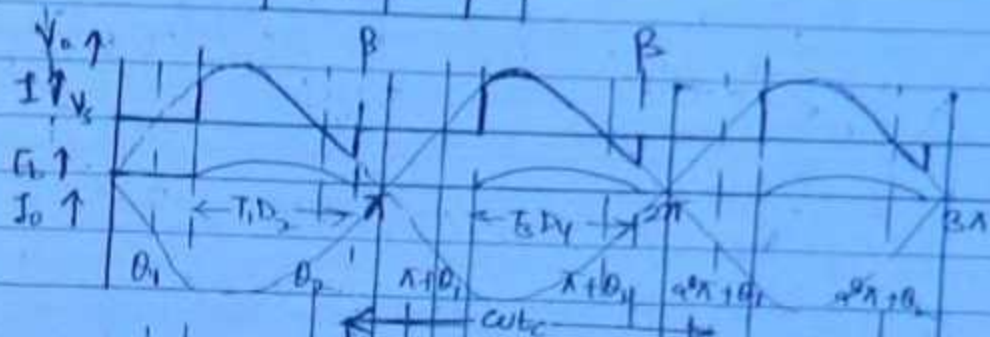

$\beta > \pi$

Conduction of FD = $(\beta - \pi)$ rad.

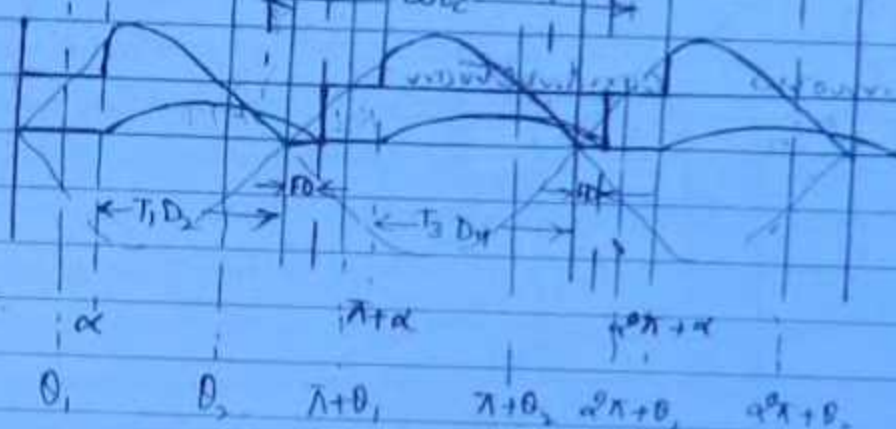

For $\beta > \pi$

$$V_o = \frac{1}{\pi} \left[\int_{\alpha}^{\pi} V_m \sin \omega t d(\omega t) + \int_{\pi}^{\beta} E_b d(\omega t) \right]$$

$$V_o = \frac{1}{\pi} \left[V_m (1 + \cos \alpha) + E_b (\pi + \alpha - \beta) \right]$$


For continuous conduction waveform remains same for RL & RLE load.

Back emf will not affect the avg value

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

Performance of 1 ϕ Full Converter -


96

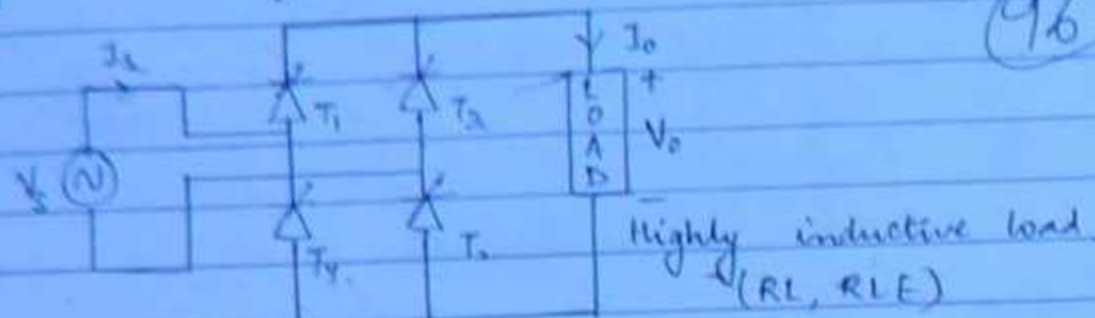

$$V_o = \frac{\alpha V_m \cos \alpha}{\pi}$$

$$V_{or} = \frac{V_m}{\sqrt{2}}$$

$$I_{sa} = I_o$$

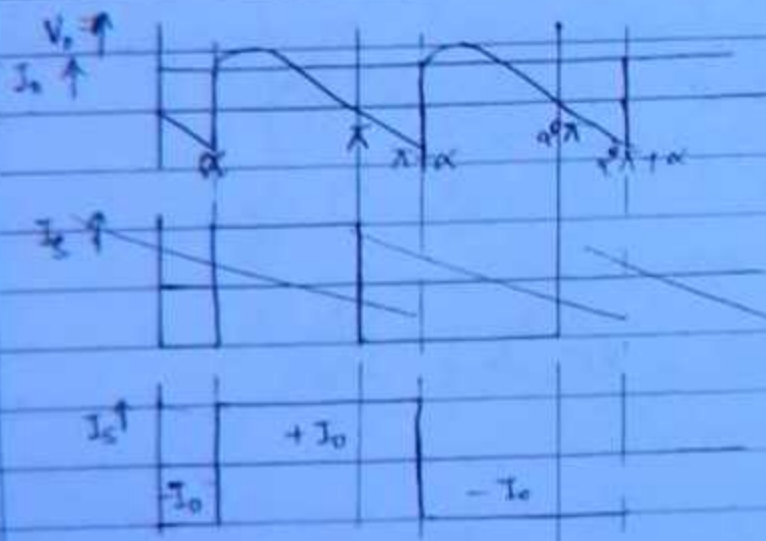

Harmonic Analysis on AC side of converter for source current (I_s)

$$I_s = \sum_{n=1,3,5,\dots}^{\infty} \frac{4I_o \sin(n\omega t + \phi_n)}{n\pi} = \frac{4I_o \sin(\omega t - \alpha)}{\pi} + \frac{4I_o \sin(3\omega t - 3\alpha)}{3\pi} + \frac{4I_o \sin(5\omega t - 5\alpha)}{5\pi} \dots$$

$$\phi_n = -n\alpha$$

$\hookrightarrow$ n^{th} harmonic displacement angle

$$I_{en} = \frac{4I_0}{n\pi} \sin(n\omega t + \phi_n)$$

$$(I_{en})_{rms} = \frac{2\sqrt{2}}{n\pi} I_0$$

$$(I_{e1})_{rms} = \frac{2\sqrt{2}}{\pi} I_0 \quad \text{--- (1)}$$

$$FDF = \cos \phi_1$$

$$FDF = \cos(-\alpha) = \cos \alpha \quad \text{--- (2)}$$

$$g = \frac{(I_{e1})_{rms}}{I_{sA}} \Rightarrow \frac{2\sqrt{2}}{\pi} \frac{I_0}{I_0}$$

$$g = \frac{2\sqrt{2}}{\pi} \quad \text{--- (3)}$$

$$PF = g(FDF)$$

$$PF = \frac{2\sqrt{2}}{\pi} \cos \alpha \quad \text{--- (4)}$$

$$THD = \left(\frac{1}{g^2} - 1 \right)^{\frac{1}{2}}$$

$$THD = \left(\frac{1}{\left(\frac{2\sqrt{2}}{\pi} \right)^2} - 1 \right)^{\frac{1}{2}} = 0.4834$$

$$THD = 48.34\% \quad \text{--- (5)}$$

avg delivered
useful power

avg delivered
useful power

Active power -

$$P = V_{as} I_{as} \cos \alpha = V_o I_o \quad \text{--- (6)}$$
$$= \left(\frac{V_m}{\sqrt{2}} \right) \left(\frac{2\sqrt{2} I_o}{\pi} \right) \cos \alpha$$

(98)

$$P = \frac{\pi V_m \cos \alpha}{\pi} \cdot I_o = V_o I_o$$

Reactive Power -

$$Q = V_{as} I_{as} \sin \alpha = V_o I_o \tan \alpha \quad \text{--- (7)}$$
$$= V_{as} I_{as} \cos \alpha \cdot \frac{\sin \alpha}{\cos \alpha}$$

$$Q = P \tan \alpha$$

Harmonics on DC side of converter - (V_o)

$$V_{RF} = \sqrt{FF^2 - 1}$$

$$FF = \frac{V_{o1}}{V_o} = \frac{V_m / \sqrt{2}}{\frac{\pi V_m \cos \alpha}{\pi}} = \frac{\pi \cos \alpha}{\pi \sqrt{2}}$$

$$V_{RF} = \sqrt{\frac{\pi^2}{8 \cos^2 \alpha} - 1}$$

When $0 \leq \alpha \leq 90^\circ$


$\alpha \uparrow$ ripple $\uparrow$ harmonics $\uparrow$

When $90 \leq \alpha \leq 180^\circ$

$\alpha \uparrow$ ripple $\downarrow$ harmonics $\downarrow$

Performance of 1 ϕ Semi Converter -


(99)

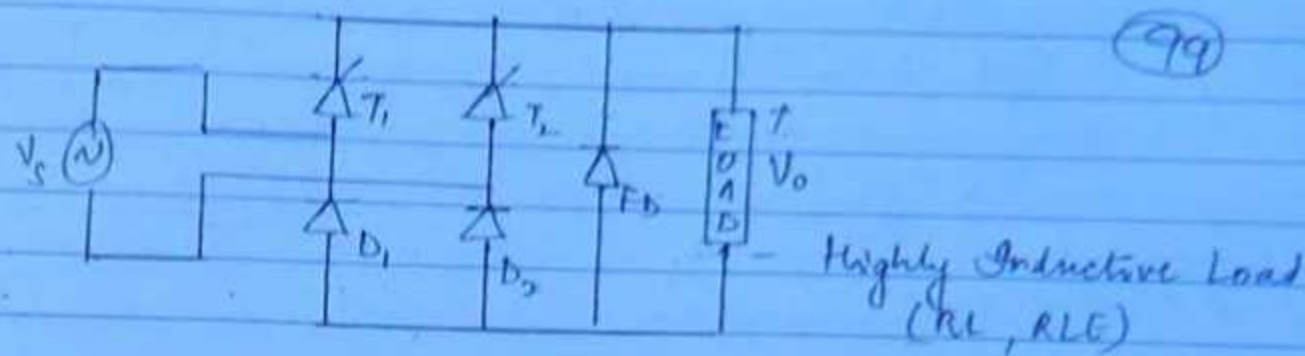

$$V_s = V_m \sin \omega t \quad V_{s1} = \frac{V_m}{\sqrt{2}}$$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$
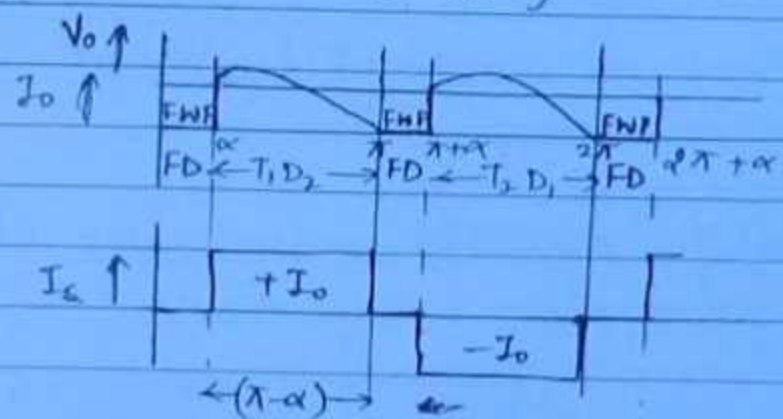
$$I_{s1} = I_o \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}$$



Harmonic Analysis of on Ac side of Converter (I_s)

$$I_s = \sum_{n=1,3,5}^{\infty} \frac{4 I_o \cos n \alpha}{n \pi} \sin(n \omega t + \phi_n)$$

$$\text{where } \phi_n = -\frac{n \alpha}{2}$$

$$(I_{s1})_{rms} = \frac{\sqrt{2} I_o \cos \alpha}{2}$$

$$(I_{s1})_{rms} = \frac{\sqrt{2} I_o \cos \alpha}{2} \quad \text{--- (1)}$$

$$FDF = \frac{\cos \alpha}{2} \quad (2)$$

$$g = \frac{I_{S1}}{I_{S2}} = \frac{\frac{\alpha \sqrt{2}}{\pi} I_0 \cos \alpha / 2}{I_0 \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}} \quad (100)$$

$$g = \frac{\alpha \sqrt{2} \cos \alpha}{2 \sqrt{\pi (\pi - \alpha)}} \quad (3)$$

$$PF = g (FDF)$$

$$PF = \frac{\frac{\alpha \sqrt{2} \cos \alpha}{2} \cdot \frac{\sqrt{2} (1 + \cos \alpha)}{2}}{\sqrt{\pi (\pi - \alpha)}} = \frac{\alpha \cos \alpha (1 + \cos \alpha)}{2 \sqrt{\pi (\pi - \alpha)}} \quad (4)$$

$$THD = \left(\frac{1}{g^2} - 1 \right)^{1/2}$$

$$THD = \left[\frac{\pi (\pi - \alpha)}{8 \cos^2 \alpha} - 1 \right]^{1/2} \quad (5)$$

Active Power -

$$P = \frac{V_{S1} I_{S1} \cos \alpha}{2} = V_0 I_0 \quad (6)$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{2 \sqrt{2}}{\pi} I_0 \cos \alpha \cdot \frac{\cos \alpha}{2}$$

$$= \frac{V_m}{\pi} (1 + \cos \alpha) I_0$$

$$P = V_0 I_0$$

Reactive Power -

$$Q = V_{sr} I_{sr} \sin \frac{\alpha}{2} = V_o I_o \tan \frac{\alpha}{2} \quad - (7)$$

$$Q = P \tan \frac{\alpha}{2}$$

(10)

Harmonics on DC side of converter (V_o)


$$V_{RF} = \sqrt{FF^2 - 1}$$

$$FF = \frac{V_{or}}{V_o}$$


$$V_{or} = \frac{V_m}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

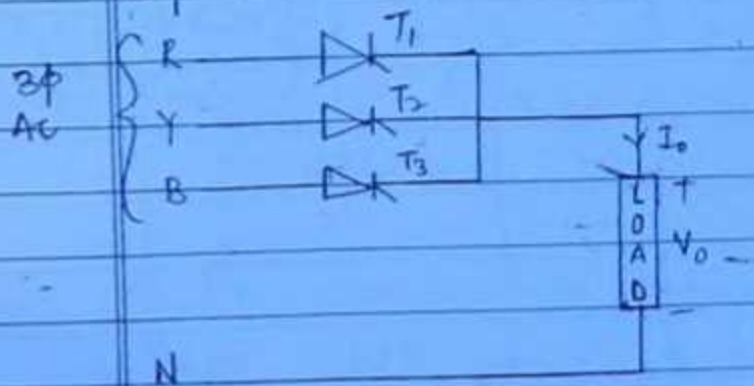3 ϕ HALF WAVE RECTIFIER (3 pulse converter)



RYB phase sequence

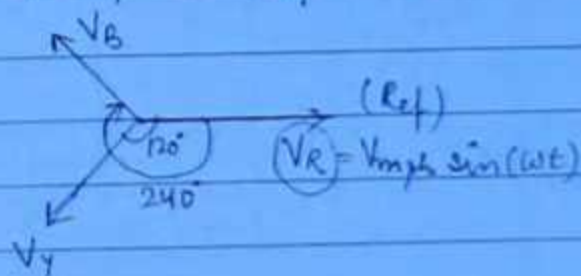


$$I_L = I_{ph} = I_T$$

$$V_{ML} = \sqrt{3} V_{mph}$$


(102)

on peak from lag to condition

from cross over point of thyristor

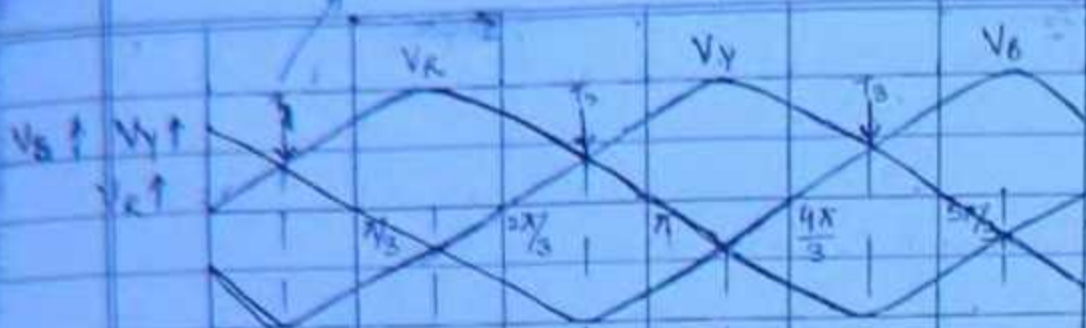


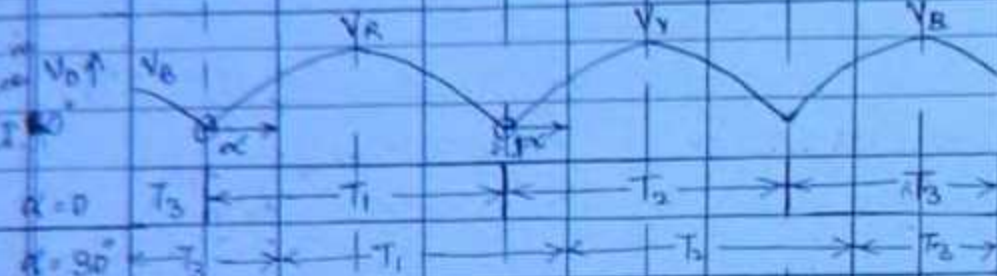max. v_g available in 120° conduction angle




Always output voltage is taken the max v_g (in which else phase it might be)

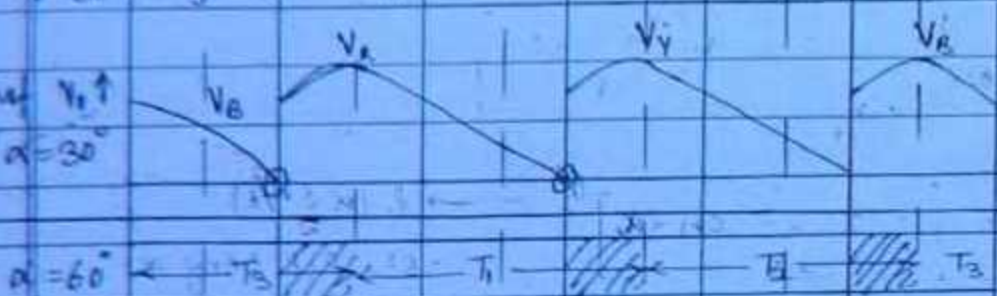max. v_g available in 120° conduction angle



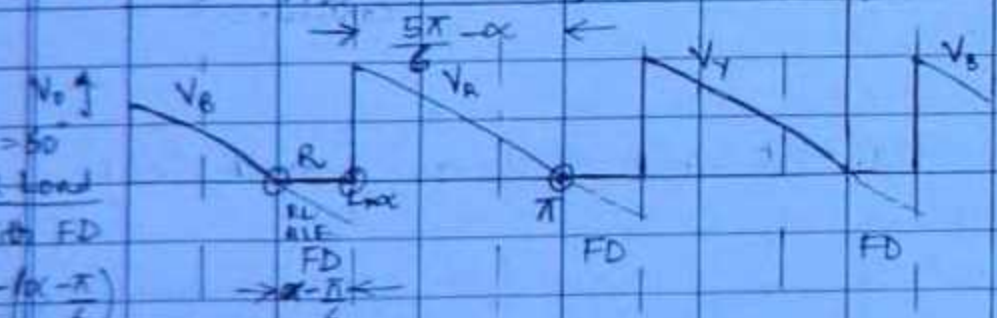max. v_g available in 120° conduction angle



FD → (α - π/6)


For R load, upper limit remains π only as it is independent of α. Even if α ↑ from 60° to 90° the thyristors are removed at π only.

RL load with FD

$$T \rightarrow \frac{2\pi - (\alpha - \pi)}{3} = \frac{\pi - \alpha}{3}$$

$$T = \frac{5\pi - \alpha}{6}$$

Highly inductive w/o FD

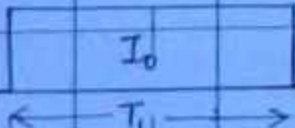

for 1 load -ve spikes occur.

I $\alpha \leq \frac{\pi}{6}$ $\Rightarrow$ continuous conduction for R_L load

$$V_o = \frac{1}{2\pi/3} \int_{\alpha+\pi/6}^{\alpha+5\pi/6} V_{mph} \sin \omega t d(\omega t)$$

103

$$V_o = \frac{3\sqrt{3} V_{mph}}{2\pi} \cos \alpha = \frac{3V_{mL}}{2\pi} \cos \alpha$$

$R_L (\alpha \leq \pi/6)$

RL, RLE
(any α)
Continuous

$$V_{or} = \left\{ \frac{1}{2\pi/3} \int_{\alpha+\pi/6}^{\alpha+5\pi/6} V_{mph}^2 \sin^2 \omega t d(\omega t) \right\}^{1/2}$$

$$V_{or} = V_{mL} \left[\frac{1}{6} + \frac{\sqrt{3}}{8\pi} \cos 2\alpha \right]^{1/2}$$

$R (\alpha \leq \pi/6)$

RL, RLE (Any α)
Continuous

II $\alpha > \frac{\pi}{6}$ $\Rightarrow$ discontinuous conduction for R load.

$$V_o = \frac{1}{2\pi/3} \int_{\alpha+\pi/6}^{\pi} V_{mph} \sin \omega t d(\omega t)$$

$$V_o = \frac{3V_{mph}}{2\pi} \left[1 + \frac{\cos(\alpha+\pi)}{6} \right]$$

$R_L (\alpha > \pi/6)$

RL, RLE with FD ($\alpha > \pi/6$)

$$V_{or} = \left\{ \frac{1}{2\pi/3} \int_{\alpha+\pi/6}^{\pi} V_{mph}^2 \sin^2 \omega t d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_{mL}}{2\sqrt{\pi}} \left[\left(\frac{5\pi}{6} - \alpha \right) + \frac{1}{2} \sin \left(2\alpha + \frac{\pi}{3} \right) \right]^{1/2}$$

$R (\alpha > \pi/6)$

RL, RLE with
FD ($\alpha > \pi/6$)

Assume highly Inductive Load with FD -

I $\boxed{\alpha \leq \pi/6}$ FD will not conduct

(104)

∴ Conduction angle of each thyristor = $\frac{2\pi}{3}$ i.e. 120°
[for every 2π rad.]

$$V_{0.4} (I_T)_{avg} = I_0 \left(\frac{2\pi/3}{2\pi} \right) = \frac{I_0}{3}$$

$$(I_L = I_{ph} = I_T)_{avg} = \frac{I_0}{3}$$

$$(I_L = I_{ph} = I_T)_{rms} = \frac{I_0}{\sqrt{3}}$$

II $\boxed{\alpha > \pi/6}$ Conduction angle of FD = $\left(\frac{\alpha - \pi/6}{6} \right)$ for every $2\pi/3$ radians

Conduction angle of each thyristor = $\left(\frac{5\pi/6 - \alpha}{6} \right)$ for every $2\pi/3$ radians

$$(I_L = I_{ph} = I_T)_{avg} = I_0 \left[\frac{(5\pi/6 - \alpha)}{2\pi} \right]$$

$$(I_L = I_{ph} = I_T)_{rms} = I_0 \left[\frac{(5\pi/6 - \alpha)}{2\pi} \right]^{1/2}$$

$$(I_{FD})_{avg} = I_0 \left[\frac{(\alpha - \pi/6)}{2\pi/3} \right]$$

$$(I_{FD})_{rms} = I_0 \left[\frac{(\alpha - \pi/6)}{2\pi/3} \right]^{1/2}$$

Assume highly Inductive Load without FB -

Any α

(105)

Conduction angle of each thyristor = $\frac{2\pi}{3}$ [for every 2π rad]

$$(I_t = I_{ph} = I_f)_{avg} = I_o \left(\frac{2\pi/3}{2\pi} \right) = \frac{I_o}{3}$$

$$(I_t = I_{ph} = I_T)_{rms} = \frac{I_o}{\sqrt{3}}$$

$$\rightarrow (I_s)_{avg} = \frac{I_o}{3} \text{ (DC comp)}$$

Drawback

The source current contains DC component & saturates the ~~trans~~ supply transformer core

RATINGS OF SCR -

1. $(I_T)_{RMS}$ Rating (RMS Rating of ON state current) provided by manufacturer

$(I_T)_{RMS}$ Rating $\geq (I_T)_{rms}$ value of in a converter

eg

$$1-\phi \text{ full conv } (I_T)_{rms} = \frac{I_o}{\sqrt{2}}$$

$$1-\phi \text{ semi conv } (I_T)_{rms} = I_o \left(\frac{\pi - \alpha}{2\pi} \right)^{1/2}$$

$$3 \text{ phase } (I_T)_{rms} = \frac{I_o}{\sqrt{3}}$$

2. (I_{TAV}) Rating [Average ON state current rating]


$$(I_{TAV})_{Rating} = \frac{(I_T)_{RMS} \text{ Rating}}{FF}$$

(106)

FF = form factor of ^{thyristor} current waveform in a converter
 ↓
 depends on shape of waveform.

CWB chapter 1

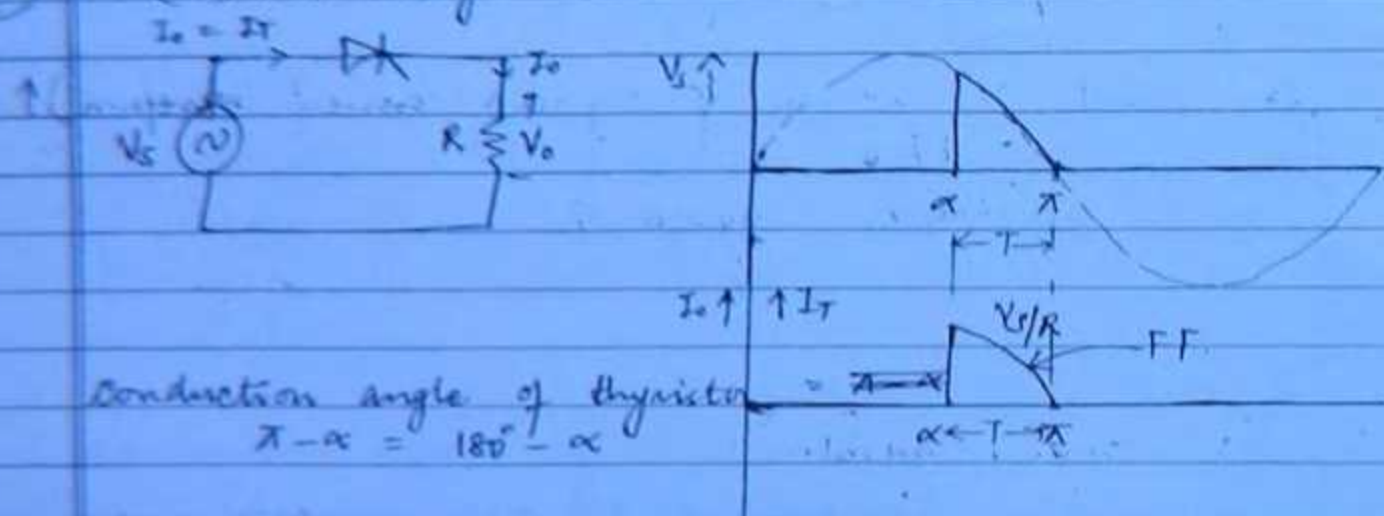(20) $(I_T)_{RMS} \text{ Rating} = 35 \text{ A}$



Given $180^\circ - \alpha = 30^\circ$

$\alpha = 150^\circ$

$$FF = \frac{(I_T)_{RMS}}{(I_T)_{avg}} = \frac{I_{O_{RMS}}}{I_o} = \frac{V_{O_{RMS}}/R}{V_o/R} = \frac{V_{O_{RMS}}}{V_o}$$

^{1/6 given}
 $FF = \frac{V_m}{\sqrt{2}\pi} \left[\left(\frac{\pi - \alpha}{2} \right) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$

$$\frac{V_m}{\sqrt{2}\pi} [1 + \cos \alpha]$$

$$= \frac{\sqrt{2}}{\pi} \left[\left(\frac{\pi}{6} \right) + \frac{1}{2} \sin \frac{300^\circ}{3} \right]^{1/2} = 1.94 \times 3.98$$

$[1 + \cos 150^\circ]$

$$I_{TAV} = \frac{(I_T)_{avg} \text{ Rating}}{FF} = \frac{85}{0.98} = 8.79 \text{ A} \quad (d)$$

(107)

Avg rating depends on -

Conduction angle of thyristor

As conduction angle $\uparrow \Rightarrow$ (smoothness of I_T waveform) $\uparrow$
 $\Rightarrow FF \downarrow$

Thus avg rating of thyristor $\uparrow$

Load parameters

eg $L \uparrow \Rightarrow$ (smoothness of thyristor current waveform) $\uparrow$
 $\Rightarrow FF \downarrow$
 $(I_{TAV}) \text{ Rating of thyristor} \uparrow$

(I^2t rating of thyristor)

provided by manufacturer - to select a proper fuse for the thyristor

I^2t rating of thyristor $\geq I^2t$ rating of fuse

Surge current Rating of thyristor

i) n cycle surge current rating - (I_{sn})

It's the surge current that the SCR can withstand for n cycles at the most

$$\therefore (I_{sn})^2 \cdot n \cdot \frac{T}{2} = I^2t \text{ rating}$$

ii) one cycle surge current rating (I_{sr}):
It is the surge current that the SCR can withstand for one cycle.

$$(I_{sr})^2 \cdot \frac{T}{2} = (I_{sn})^2 \cdot n \cdot \frac{T}{2}$$

$$I_{sr} = \sqrt{n} I_{sn}$$

iii) Sub-cycle surge current rating ($I_{s/n}$):
It is the surge current that the SCR can withstand for $1/n$ th period of a cycle.

$$(I_{s/n})^2 \cdot \frac{T}{2} \cdot \frac{1}{n} = (I_{sr})^2 \cdot \frac{T}{2}$$

$$I_{s/n} = \sqrt{n} I_{sr}$$

iv) Half cycle surge current.
 $I_{s/2} = \sqrt{2} I_{sr}$

CWB chapter 1

(19) $I_{s/n} = 3000$

$$I_{sr} = \frac{3000}{\sqrt{2}} = 2121.32 \text{ A} \quad (b)$$

(21) (c)

CWB chapter 2

- (2) (b) -ve spikes are removed.


- (3) Half wave rectifier.

(109)

PIV depends on secondary not on primary.

$$V_s = 50 \text{ V (rms)} \therefore V_m = 50\sqrt{2}$$
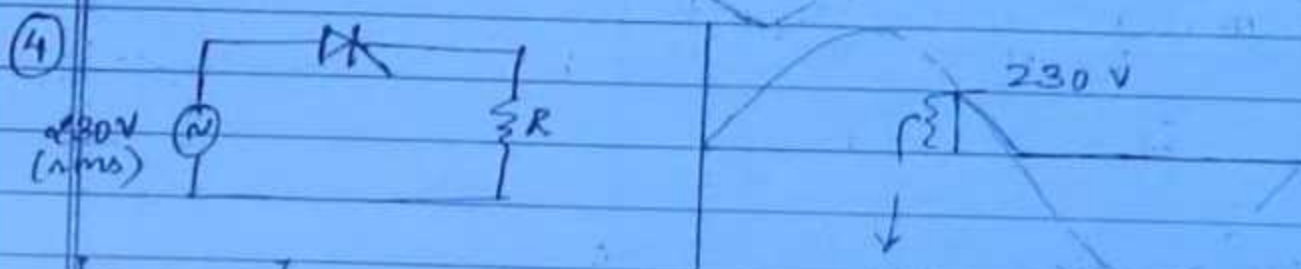
$$\begin{aligned} \text{PIV} &= 2V_m = 50\sqrt{2} (2) \\ &= 100\sqrt{2} \text{ (a)} \end{aligned}$$



$$V_o (wt) \Big|_{\text{peak}} = 230 \text{ V}$$

$$\begin{aligned} V_m \sin \alpha &= 230 \\ 230\sqrt{2} \sin \alpha &= 230 \end{aligned}$$

$$\sin \alpha = \frac{1}{\sqrt{2}}$$



$$\begin{aligned} V_o \text{ for } \alpha \leq 90^\circ \\ V_m &= 230\sqrt{2} \quad \times \end{aligned}$$

$$\text{So } \alpha > 90^\circ$$


$$\alpha = 45^\circ, 135^\circ$$

Any (b)

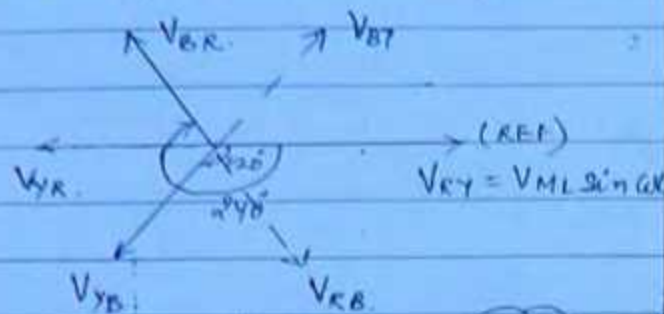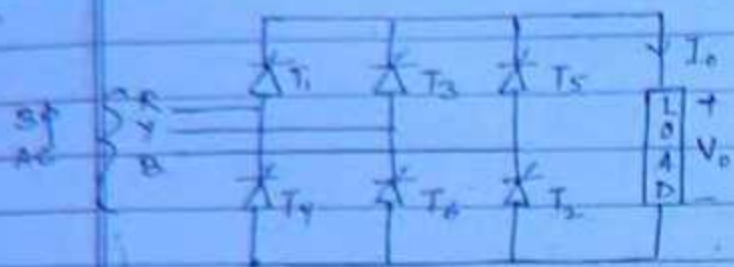3 ϕ Fully Controlled Rectifier (6 pulse converter)




110

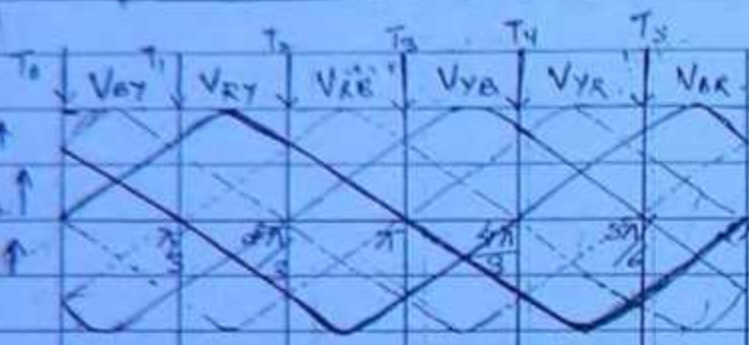

$\alpha = 0^\circ$	+	T_5	T_1	T_2	T_3	T_4	T_5
	-	T_6	T_2	T_3	T_4	T_5	T_6
$\alpha = 60^\circ$	+	T_5	T_1	T_2	T_3	T_4	T_5
	-	T_6	T_2	T_3	T_4	T_5	T_6

count α from crossover pt.
 + T_1, T_2, T_3 } seq. remains same
 - T_4, T_5, T_6 }

$\alpha = 90^\circ$	+	T_5	T_1	T_2	T_3	T_4	T_5
	-	T_6	T_2	T_3	T_4	T_5	T_6

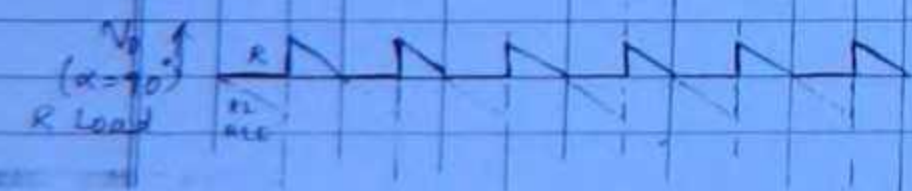

$$T_2 \rightarrow ON \quad V_{TH} = \frac{V_{RY}}{2}$$

$$T_5 \rightarrow ON \quad V_{TH} \rightarrow \frac{V_{RE}}{2}$$

RL, RLE
Highly
Inductive

(11)

$I_a \uparrow$

I_0

I_0

I_0

V_{RY}

T_2

V_{RE}

T_5

ωt_c

$V_{TH} \uparrow$
 $(\alpha = 0)$

T_1

T_1

T_2

T_3

$I(\alpha < 60^\circ) \uparrow$
 $\alpha = 30^\circ$

T_1

α

T_1

T_2

T_3

$I(\alpha > 60^\circ)$
 $\alpha = 90^\circ$

T_1

α

α

ωt_c

$\alpha \leq \pi/3 \rightarrow$ continuous conduction for R load

$$V_o = \frac{1}{\pi/3} \int_{\alpha+\pi/3}^{\alpha+\pi/3} V_{ML} \sin \omega t d(\omega t)$$

$$V_o = \frac{3V_{ML} \cos \alpha}{\pi} \rightarrow R (\alpha \leq \pi/3)$$

$$\rightarrow RL, RLE \text{ (Any } \alpha) \text{ continuous}$$

(112)

$$V_{or} = \left\{ \frac{1}{\pi/3} \int_{\alpha+\pi/3}^{\alpha+\pi/3} V_{ML}^2 \sin^2 \omega t d(\omega t) \right\}^{1/2}$$

$$= \left[\frac{3}{2\pi} V_{ML} \left\{ \frac{\pi}{3} + \frac{1}{2} \left[\sin \left(\frac{2\alpha + 2\pi}{3} \right) - \sin \left(\frac{2\alpha + 4\pi}{3} \right) \right] \right\} \right]^{1/2}$$

$\alpha > \pi/3 \rightarrow$ discontinuous conduction for R load -

$$V_o = \frac{1}{\pi/3} \int_{\alpha+\pi/3}^{\pi} V_{ML} \sin \omega t d\omega t$$

$$V_o = \frac{3V_{ML}}{\pi} \left[1 + \cos \left(\alpha + \frac{\pi}{3} \right) \right] \rightarrow R (\alpha > \pi/3)$$

$$V_{or} = \left\{ \frac{1}{\pi/3} \int_{\alpha+\pi/3}^{\pi} V_{ML}^2 \sin^2 \omega t d\omega t \right\}^{1/2}$$

$$= \left[\frac{3}{2\pi} V_{ML} \left\{ \left(\frac{2\pi}{3} - \alpha \right) + \frac{1}{2} \sin \left(\frac{2\alpha + 2\pi}{3} \right) \right\} \right]^{1/2} \rightarrow R (\alpha > \pi/3)$$

Assume highly inductive load - (R_L, R_{LE})

Conduction angle of each thyristor = $\frac{2\pi}{3}$ (for every $\frac{2\pi}{3}$ rad)

$$(I_T)_{avg} = I_o \left(\frac{2\pi/3}{2\pi} \right) = \frac{I_o}{3}$$

$$(I_T)_{rms} = \frac{I_o}{\sqrt{3}}$$

(13)

$$(I_R)_{rms} = I_o \left(\frac{2\pi/3}{\pi} \right)^{1/2}$$

$$I_{RR} = (I_R)_{rms} = I_o \sqrt{\frac{2}{3}}$$

Harmonic Analysis on AC side of converter for source current (I_s) waveform.

$$I_s = \sum_{n=1,3,5}^{\infty} \frac{4I_o}{n\pi} \frac{\sin n\pi}{3} \sin(n\omega t + \phi_n)$$

$\downarrow$
 $n = 6K \pm 1$

Since $\sin \frac{3\pi}{3} = 0$ so 3rd harmonic & multiples of 3 harmonics (triple harmonics) are absent. So are even harmonics.

NOTE: Even if triple harmonics are absent

$$\phi_n = -n\alpha \quad \phi_1 = -\alpha$$

$$(I_{s1})_{rms} = \frac{2\sqrt{2}}{n\pi} I_o \frac{\sin n\pi}{3}$$

$$(I_{s1})_{rms} = \frac{2\sqrt{2}}{\pi} I_o \frac{\sin \pi}{3}$$

$$(I_{s1})_{rms} = \frac{\sqrt{6}}{\pi} I_0 \quad \text{--- (1)}$$

$$FDF = \cos \phi_1$$

$$FDF = \cos \alpha \quad \text{--- (2)}$$

$$g = \frac{(I_{s1})_{rms}}{I_{s0}} = \frac{\frac{\sqrt{6}}{\pi} I_0}{I_0 \sqrt{\frac{2}{3}}}$$

174

$$g = \frac{3}{\pi} \quad \text{--- (3)}$$

$$THD = \left(\frac{1}{g^2} - 1 \right)^{1/2} = \left(\frac{\pi^2}{9} - 1 \right)^{1/2}$$

$$THD = 31\% \quad \text{--- (4)}$$

$m \uparrow$ $THD \downarrow$ $\therefore$ harmonics $\downarrow$

$$PF = g(FDF)$$

$$PF = \frac{3}{\pi} \cos \alpha \quad \text{--- (5)}$$

Active power $P = \sqrt{3} V_{s0} I_{s1} \cos \alpha \quad \text{--- (6)}$

$$= \sqrt{3} V_{ML} \frac{\sqrt{6}}{\pi} I_0 \cos \alpha$$

$$= \frac{3 V_{ML}}{\pi} \cos \alpha I_0 = V_0 I_0$$

Reactive power $\Rightarrow Q = \sqrt{3} V_{s0} I_{s1} \sin \alpha = V_0 I_0 \tan \alpha \quad \text{--- (7)}$

$$= P \tan \alpha$$

To find t_c & PIV across thyristor we need to plot V_T .

(115)

$$T_1 \rightarrow ON \quad V_T = 0$$

$$T_3 \rightarrow ON \quad V_T = V_{RT}$$

$$T_5 \rightarrow ON \quad V_T = V_{R2}$$

$$\omega t_c = \frac{4\pi}{3} \quad t_c = \frac{4\pi}{3\omega} \text{ sec.}$$

I) $\alpha < 60^\circ$

$$\alpha + \omega t_c = \frac{4\pi}{3}$$

$$\omega t_c = \frac{4\pi}{3} - \alpha$$

$$t_c = \frac{\frac{4\pi}{3} - \alpha}{\omega}$$

ω


II) $\alpha \geq 60^\circ$

$$\alpha + \omega t_c = \pi$$

$$\omega t_c = \pi - \alpha$$

$$t_c = \frac{\pi - \alpha}{\omega} \text{ sec.}$$

3 pulse converter -

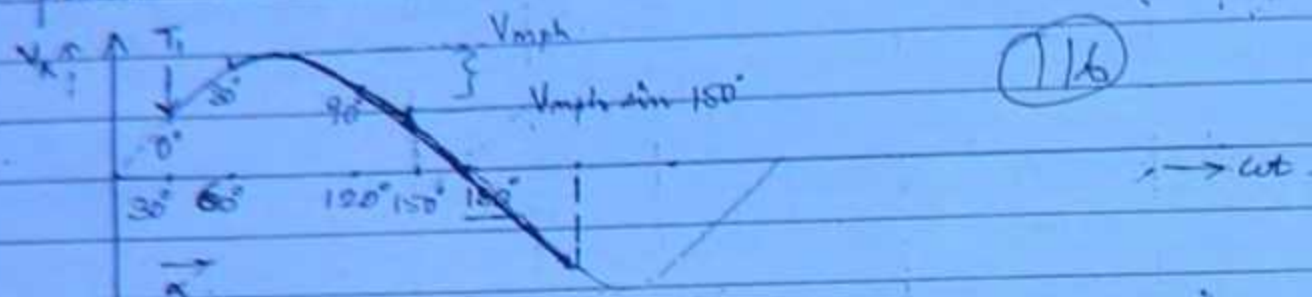

$$\alpha = \omega t - 30^\circ$$

$$\text{Length of pulse} = \frac{\pi}{3} = 120^\circ$$


$$0 \leq \alpha \leq 150^\circ$$

→ R load

$$0 \leq \alpha \leq 150^\circ$$

→ Inductive Load

3 pulse converter

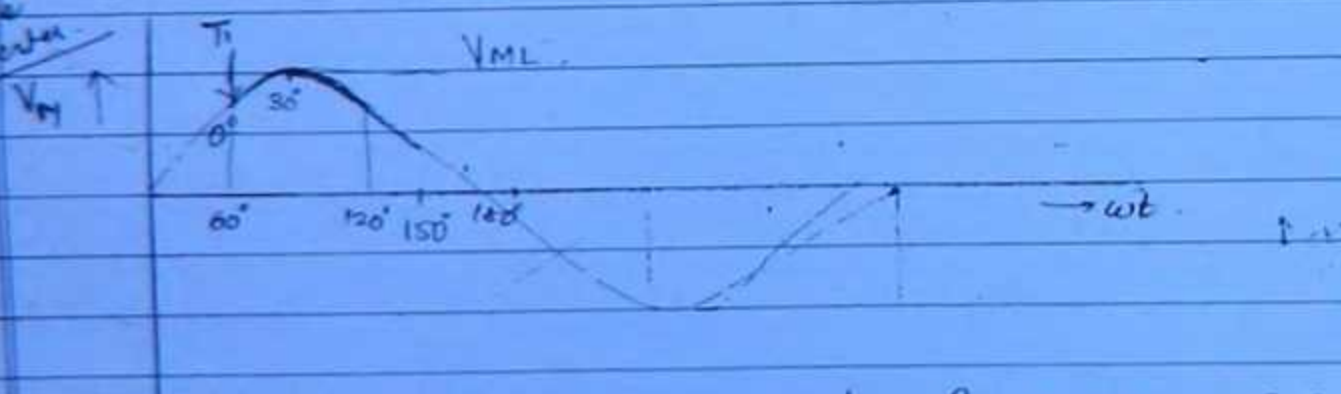

$$\alpha = \omega t - 60^\circ$$

$$\text{Length of pulse} = \frac{\pi}{3} = 60^\circ$$

for R load $\rightarrow 0 \leq \alpha \leq 150^\circ$




RL, RLE load $\rightarrow 0 \leq \alpha \leq 150^\circ$


CWB chapter 2

$$\begin{aligned} \text{① Peak to peak vlg ripple} &= \frac{V_{ML} - V_{ML} \sin 150^\circ}{V_{ML}} \\ \text{peak of dc voltage} &= 1 - \sin 150^\circ \\ &= 0.5 \quad (a) \end{aligned}$$

3 ϕ Half Controlled Rectifier

177

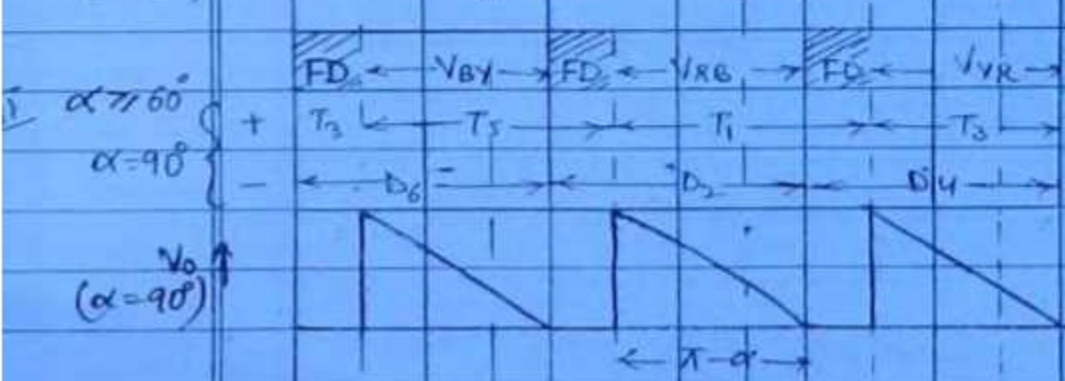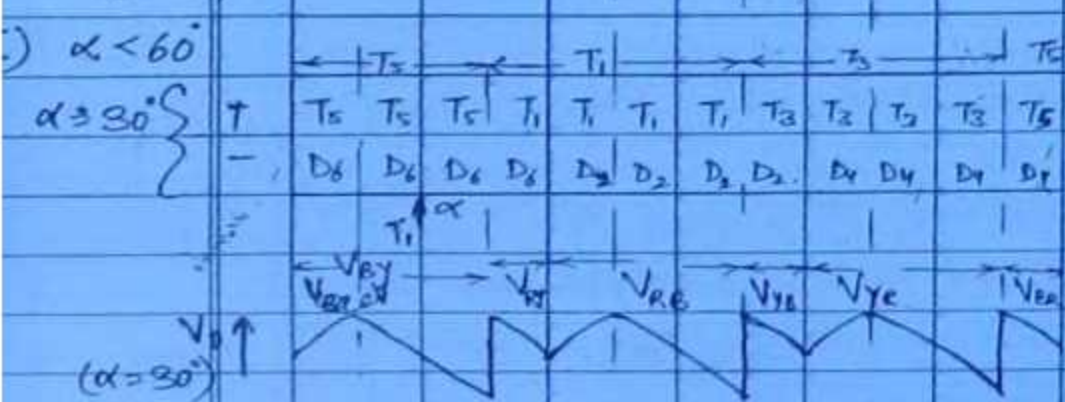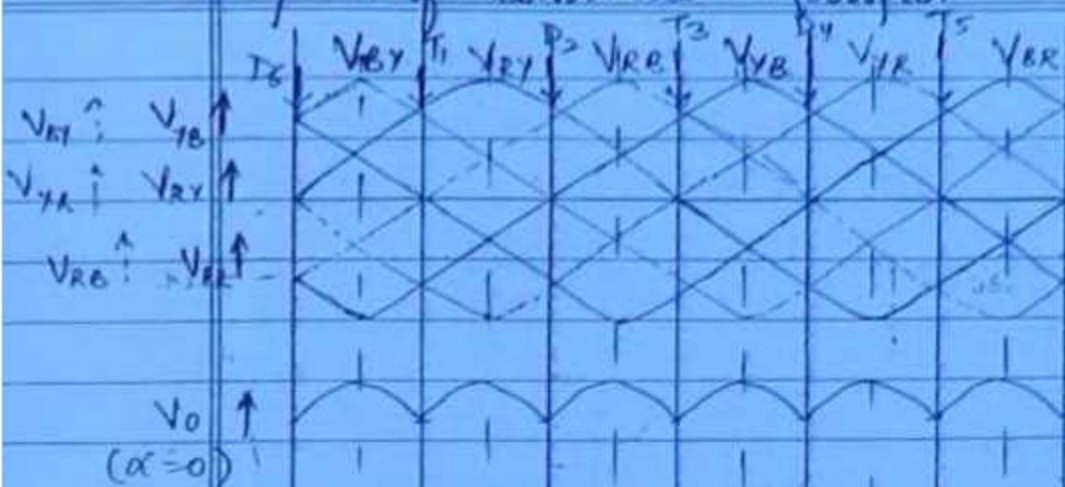
 $I_R \uparrow$

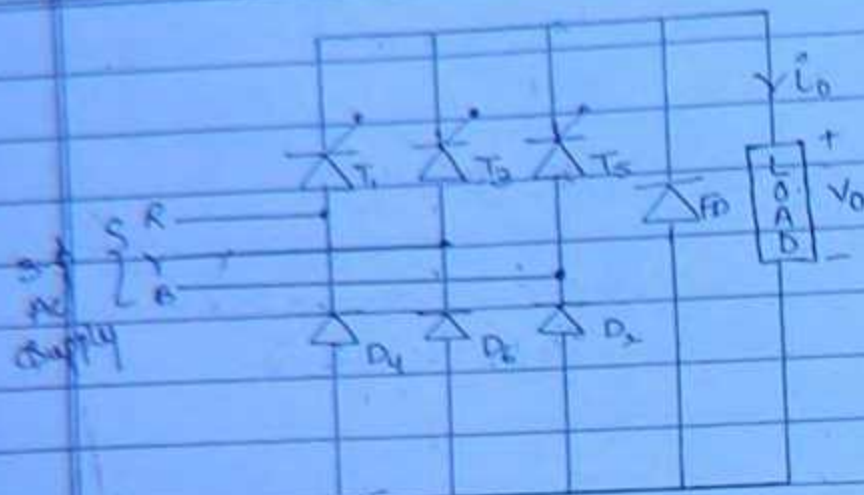



+ T_1, T_2, T_3
- D_4, D_5, D_6

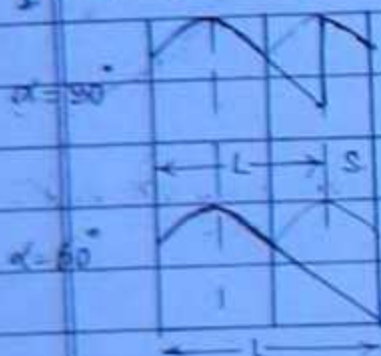(115)

Short method - 1 mark

I $\alpha < 60^\circ$ FD will not conduct.



$$\rightarrow S = 60 - \alpha$$

$$= 60 - 60$$

$$= 0$$

Take $V_o (\alpha = 0)$ as ref

Long pulse $= 60 + \alpha$

Short pulse length $= 60 - \alpha$

$\alpha < 60^\circ \Rightarrow 6$ pulse IES
 $\alpha \geq 60^\circ \Rightarrow 3$ pulse.

for $\alpha < 60^\circ$ FD will not conduct.


for $\alpha \geq 60^\circ$

conduction period of FD $= \left(\alpha - \frac{\pi}{3} \right)$ radians

conduction period of thyristor $= \frac{2\pi}{3} - \left(\alpha - \frac{\pi}{3} \right)$

$$= \pi - \alpha$$

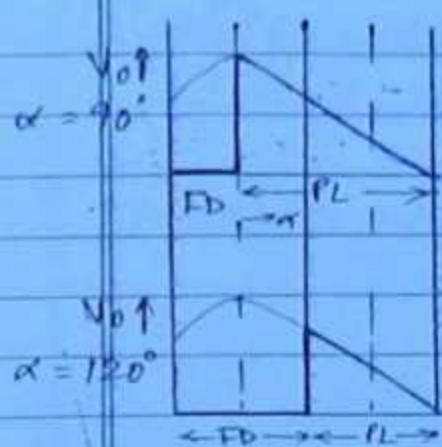$\therefore$ Length of pulse $= \pi - \alpha$



(7/19)

Take $V_o(\alpha = 60^\circ)$ as ref

$$FD \rightarrow \alpha - \pi/3$$

$$\text{Pulse length} = \pi - \alpha$$

As $\alpha \uparrow$ Free wheeling $\uparrow$

Pulse length $\downarrow$

Assume Highly Inductive Load =

$\alpha \leq 60^\circ$ FD will not conduct

Conduction angle of FD $= \alpha - \pi/3$

Conduction angle of thyristor $= \frac{2\pi}{3}$ rad (for every 2π radians)

$$(I_T)_{avg} = I_o \left(\frac{2\pi/3}{2\pi} \right) = \frac{I_o}{3}$$

$$(I_T)_{rms} = \frac{I_o}{\sqrt{3}}$$

$$I_{sa} = I_o \sqrt{\frac{2}{3}}$$

$\alpha > 60^\circ$ FD will conduct

Conduction angle of FD $= \alpha - \frac{\pi}{3}$ (for every $\frac{2\pi}{3}$ rad)

Conduction angle of thyristor $= \pi - \alpha$ (for every 2π rad)

$$(I_T)_{avg} = I_o \left(\frac{\pi - \alpha}{2\pi} \right)$$


$$(I_T)_{rms} = I_o \left(\frac{\pi - \alpha}{2\pi} \right)^{1/2}$$

$$I_{sa} = I_o \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}$$

$$V_o = \frac{3V_{mL}}{\pi} (1 + \cos \alpha)$$

(120)

Representation of semi-converter.

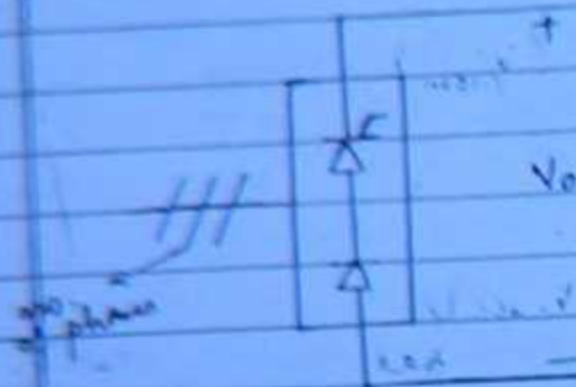


V_o

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha) \rightarrow 1\phi$$

$$V_o = \frac{3V_{mL}}{\pi} (1 + \cos \alpha) \rightarrow 3\phi$$

Representation of full converter.

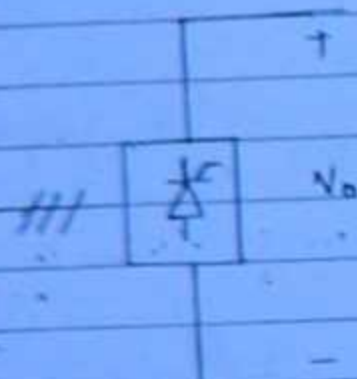


V_o

APPLICATIONS -

DC Drives -

1. Armature Voltage Control ($\omega < \omega_n$)

$\phi = \text{const}$

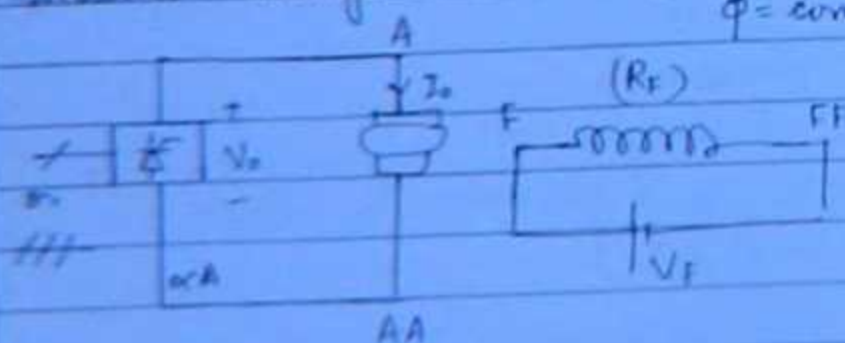

$$1\phi \quad V_o = \frac{1}{\pi} V_m \cos \alpha$$

$$E_b \propto \phi N$$

$$E \propto N \quad (\because \phi = \text{const})$$

$$E = KN$$

→ EMF const (V/rpm)
or Motor const

$$E = K\omega$$

→ EMF const (V.sec)/rad
or Motor const

$$T_a \propto \phi I_a$$

$$T_a \propto I_a \quad (\phi = \text{const})$$

$$T_a = K_t I_a$$

$$\rightarrow I_a = T_a / K_t$$

→ Motor const

or Torque const

$$\text{NM/A} = (\text{V.sec})/\text{rad}$$

$$\omega = \frac{2\pi N}{60}$$

$$N \rightarrow \text{rpm}$$

$$\omega \rightarrow \text{rad/sec}$$

For Motoring Mode

$$V_o = E_b + I_a R_a$$

$$V_o = K\omega + I_a R_a$$


$$\omega = \frac{V_o}{K} - \frac{I_a R_a}{K}$$

$$\omega = \frac{V_o}{K} - \frac{R_a}{K^2} T_a$$

$$\alpha_A \uparrow \quad V_o \downarrow \quad \therefore \omega \downarrow \quad (\omega < \omega_s)$$

(I) Field Control Method ($\omega > \omega_n$)

(122)

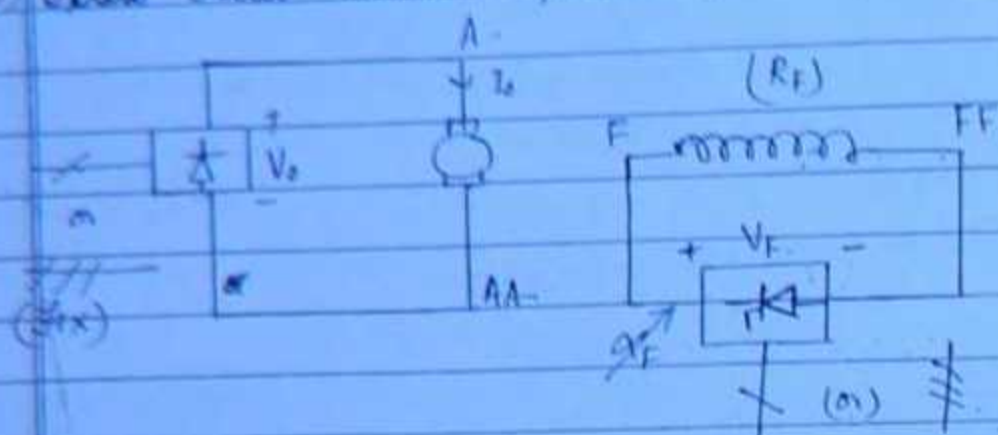

$$1\phi \quad V_F = \frac{\alpha V_m \cos \alpha_F}{\pi}$$

$$I_F = \frac{V_F}{R_F}$$

$$3\phi \quad V_F = \frac{3 V_{ML} \cos \alpha_F}{\pi}$$

$$\phi \propto I_F$$

$$\phi = K_F I_F$$

$$E_b \propto \phi N \propto (K_F I_F) N$$

$$E_b = K_1 (K_F I_F) N$$

$$E = \underbrace{K_1 I_F N}_{\text{EMF const or Motor const}}$$

$$\text{V/srpm} \cdot A$$

$$E = \underbrace{K I_F \omega}_{\text{EMF const or Motor const}}$$

$$\text{V/sec} \cdot \text{V.sec/rad} \cdot A$$

$$T_a \propto \phi I_a$$

$$T_a = K I_F I_a$$

$$T_a = \underbrace{K I_F}_{\text{Motor const or Torque const}} I_a \rightarrow I_a = \frac{T_a}{K I_F}$$

$$\text{V.sec/rad} \cdot A$$

$$\omega = \frac{a' \pi N}{60}$$

(123)

For Motoring Mode

$$V_o = E_b + I_o R_a$$

$$V_o = K I_f \omega + I_o R_a$$

$$\omega = \frac{V_o - I_o R_a}{K I_f}$$


$$\omega = \frac{V_o - R_a}{K I_f} \quad T_a$$

$$\alpha_f \uparrow \quad V_f \downarrow \Rightarrow I_f \downarrow \Rightarrow \omega_o > \omega_n$$

for Motoring Mode $\Rightarrow$ Torque developed is in same dir as speed

Current enters at +ve terminal of back emf, so that electrical effect absorbed is transformed in mech. energy.

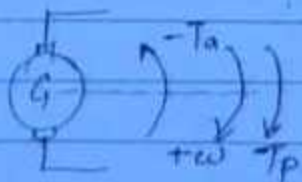
for Generating Mode $\Rightarrow$ Torque developed if speed in opp dir



Four Modes of DC M/c -

124


We can utilise DC m/c in 4 modes

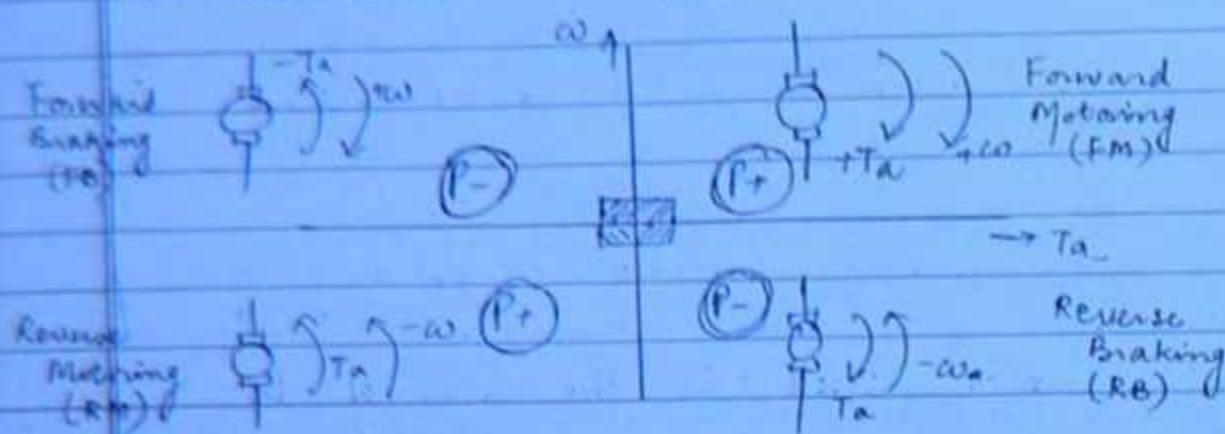


Quadrant Operation of Full Converter - (Two Quadrant Operation)

1 ϕ $V_o = \frac{\sqrt{2} V_m}{\pi} \cos \alpha$ $\alpha < 90^\circ$ $V_o +$
 $\alpha > 90^\circ$ $V_o -$

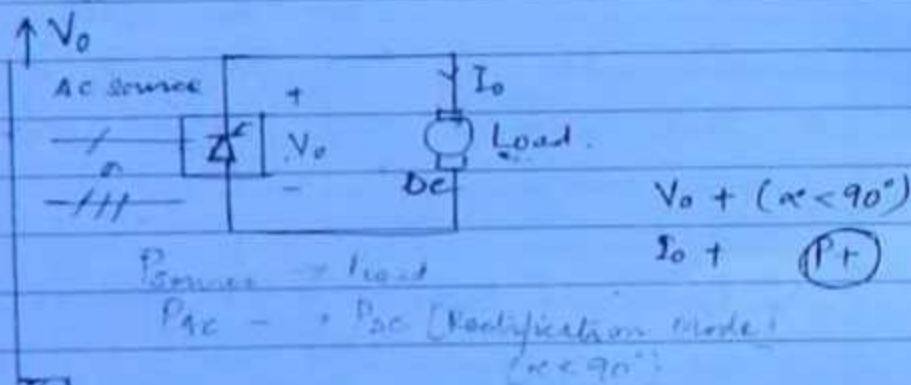3 ϕ $V_o = \frac{3 V_{mL}}{\pi} \cos \alpha$



I_o (always) $+$

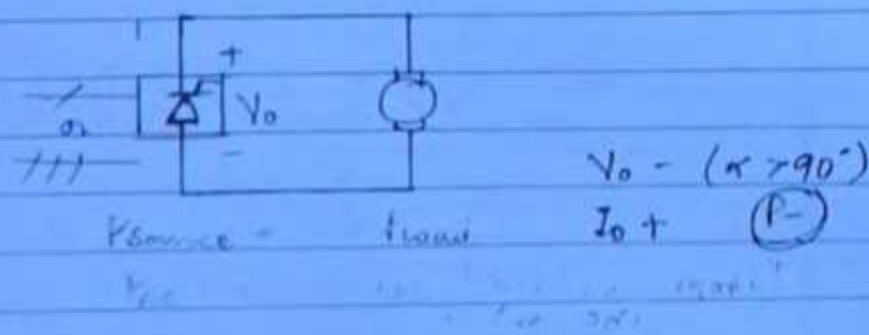

(125)


Rectification Mode -

- can be used for motoring mode of a DC m/c.
- can also be used to charge a battery.


Inversion Mode

- can be used for regenerative braking of DC m/c.
- solar energy stored in the form of DC can be given to the AC side of utility system where the converter is operating in ~~inversion~~ mode.

Full converter feeding DC m/c -

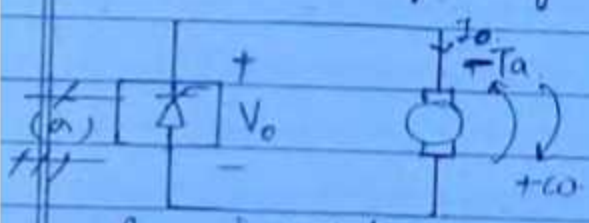

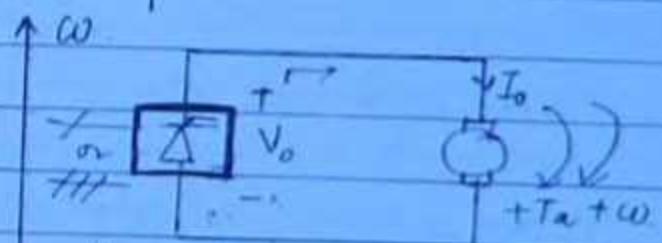$P_{AC} \xleftarrow{\text{Inv Mode}} P_{DC}$
($\alpha > 90^\circ$)



$P_{AC} \xrightarrow{\text{Rec Mode}} P_{DC}$
($\alpha < 90^\circ$)

Since ← Braking Energy
(regenerative braking)

$$\alpha < 90^\circ \quad V_o + E_b + \therefore \omega + I_a + \therefore T_a +$$

$$T_a \rightarrow \phi I_a$$

Converter will support the inversion if $\alpha > 90^\circ$
Load supports inversion if emf is having ability to deliver power.

Converter will support the rectification if $\alpha < 90^\circ$
Load supports rectification if emf is having ability to absorb the power.

$$V_o = -E_b + I_o R_a$$

126

$$V_o = E_b + I_o R_a$$

$$\omega = \frac{\alpha^2 V_m}{\pi K} \cos \alpha - \frac{R_a T_a}{K^2} \rightarrow 1\phi$$

$$\omega = \frac{3 V_m}{\pi K} \cos \alpha - \frac{R_a T_a}{K^2} \rightarrow 3\phi$$

$$T_a + \omega r \therefore (P+) (\phi +)$$

Quadrant Operation of Semi Converter
Supports

DUAL CONVERTER (Four Quadrant Operation)


T27

i) Non-Circulating Current Type -

In non-circulating current type dual converter, if one converter is in the ON state then other converter is in the OFF state.

Advantage -

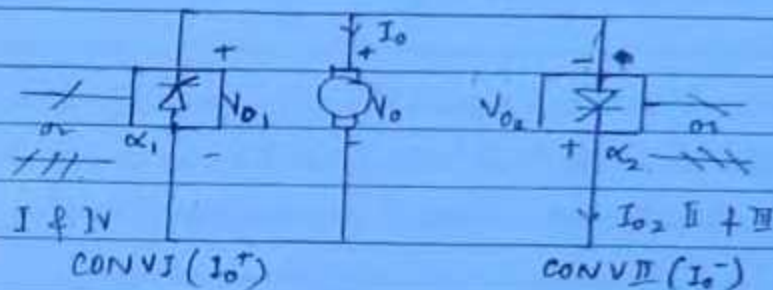There is no circulating current b/w the converters.




$$1\phi, V_{o1} = \frac{2V_m \cos \alpha_1}{\pi}$$

$$1\phi, V_{o2} = \frac{2V_m \cos \alpha_2}{\pi}$$

$$3\phi, V_{o1} = \frac{3V_{mL} \cos \alpha_1}{\pi}$$
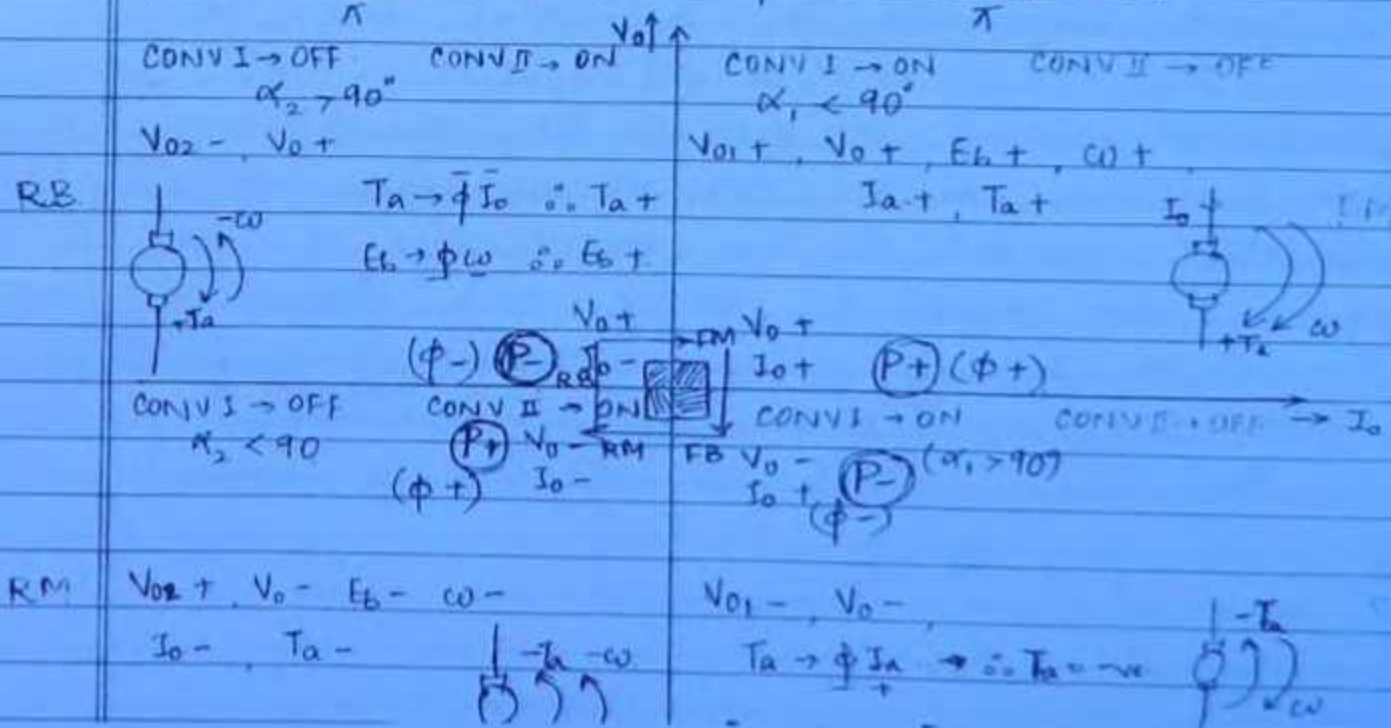
$$3\phi, V_{o2} = \frac{3V_{mL} \cos \alpha_2}{\pi}$$



Disadvantage -

- It gives slow speed response if the reversal of armature current is not smooth during switching transition of the converter.



We must provide commutation delay time (Δt_d) to the outgoing converter before the incoming converter is switched ON to avoid high circulating current during switching transitions of converter. This commutation delay time is responsible for slow speed response.


(ii) Circulating Current Type -

Here, both the converters are simultaneously in the ON state.

Disadvantage -

There will be circulating current b/w the converters & hence responsible for additional power loss.

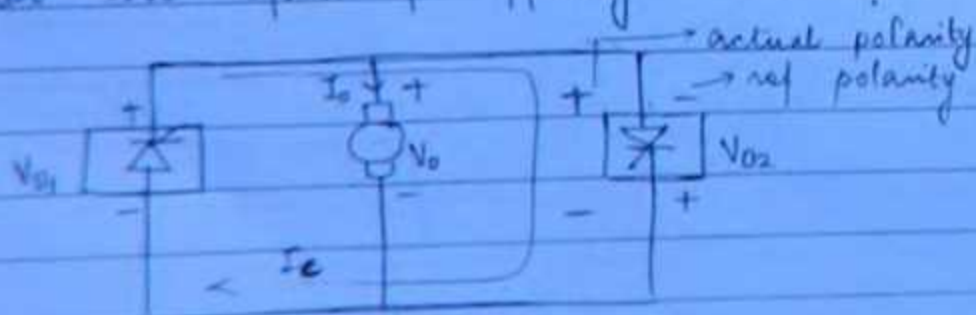Circulating current is due to the v_{lg} difference b/w the two converters. We can reduce the circulating current if the output v_{lg} of the converters are equal & opposing each other.



$$I_c \downarrow \rightarrow V_{o1} = -V_{o2}$$

$$\alpha_1 + \alpha_2 = 180^\circ$$

$$\frac{2V_m}{\pi} \cos \alpha_1 = -\frac{2V_m}{\pi} \cos \alpha_2$$

(129)


$$\cos \alpha_1 + \cos \alpha_2 = 0$$

$$\alpha_2 = 180 - \alpha_1$$

$$\alpha_1 + \alpha_2 = 180^\circ$$

Even after maintaining $\alpha_1 + \alpha_2 = 180^\circ$, still there is some circulating current due to the instantaneous vlt difference b/w the converters

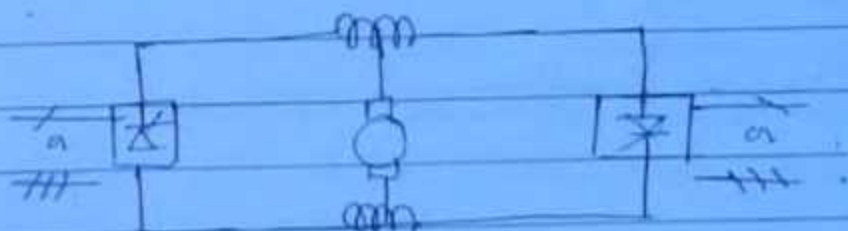- * To reduce this circulating current, we must connect a ~~reactive power~~ ^{reactor core} b/w the converters as shown.




- * In order to satisfy the relation $\alpha_1 + \alpha_2 = 180^\circ$ if one converter is operating in rectification mode then other converter must work in inversion mode

Advantage -



It gives high speed response if the ~~reversal~~ reversal of armature current is smooth during switching transition of converters.

Effect of Source Inductance (L_s) on one Pulse Converter

(136)

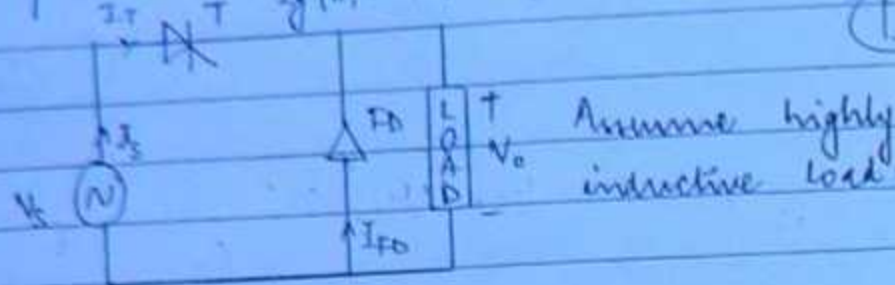

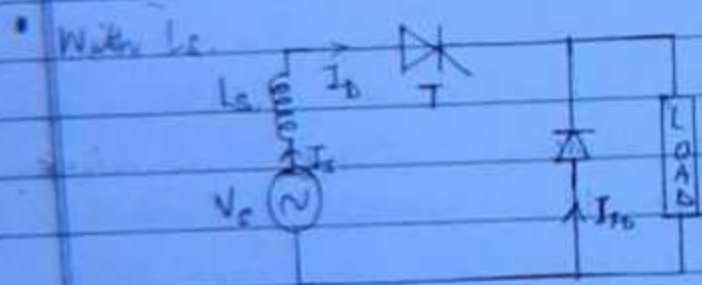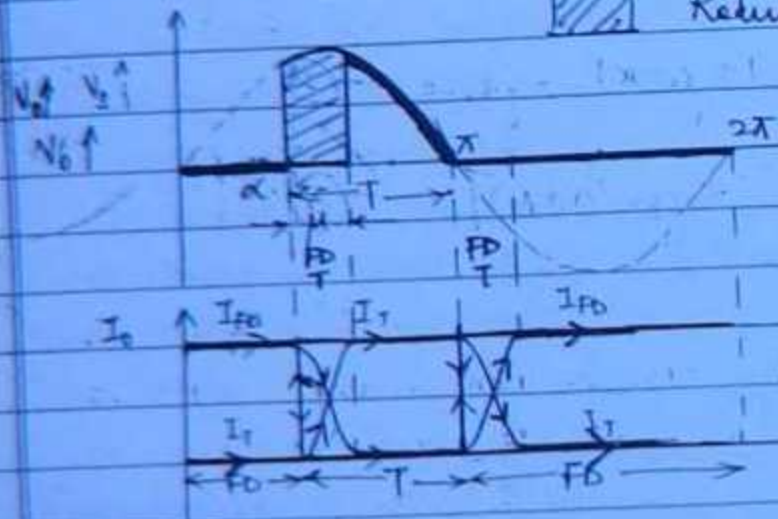Without $L_s \rightarrow V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$
 Reduction in v_l due to L_s



$\mu = \text{overlap period}$

During overlap period both T & FD are on
 exchanging load current I_{s0} $v_l = 0$

During Overlap $\Rightarrow$ FD & T $\rightarrow$ ON $V_o = 0$
 $V_s = L_s \frac{dI_s}{dt}$

$\alpha + \mu$ I_0

$$\frac{V_m [\cos \alpha - \cos (\alpha + \mu)]}{2} = \frac{\omega L_s I_o}{2}$$

$$(131)$$

divide to give
avg reduction
in vlg.

$$\Delta V_{do} = \frac{V_m [\cos \alpha - \cos (\alpha + \mu)]}{2\pi} = \frac{\omega L_s I_o}{2\pi} = f L_s I_o \quad \text{--- (1)}$$

ΔV_{do} = Avg reduction in V_o due to L_s

$$V_o = \frac{V_m (1 + \cos \alpha)}{2\pi} - f L_s I_o \quad \text{--- (2)}$$

$$V_o = \frac{V_m [1 + \cos (\alpha + \mu)]}{2\pi} \quad \text{--- (3)}$$

* * Overlap angle μ depends on firing angle α but avg reduction in vlg due to source inductance i.e. ΔV_{do} does not depend on firing angle α .


* Avg reduction in vlg due to source inductance depends upon frequency, L_s & I_o

* If $f \uparrow$ or $L_s \uparrow$ or $I_o \uparrow$ w/o changing V_s & α then μ also $\uparrow$.

If $V_s \uparrow$ w/o changing f , L_s , I_o & α then $\mu \downarrow$ but due to $\uparrow$ in V_s height of pulse $\uparrow$. To maintain same area ΔV_{do} the width $\downarrow$. Thus $\mu \downarrow$


Effect of Source Inductance for Two Pulse Converter.

(132)

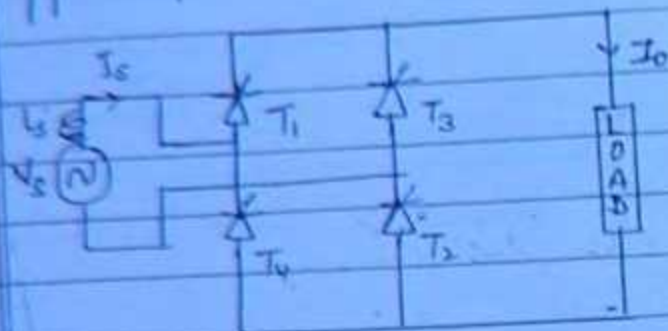

$$V_{do} = \frac{\alpha V_m}{\pi} \quad (\text{max dc o/p v/g})$$

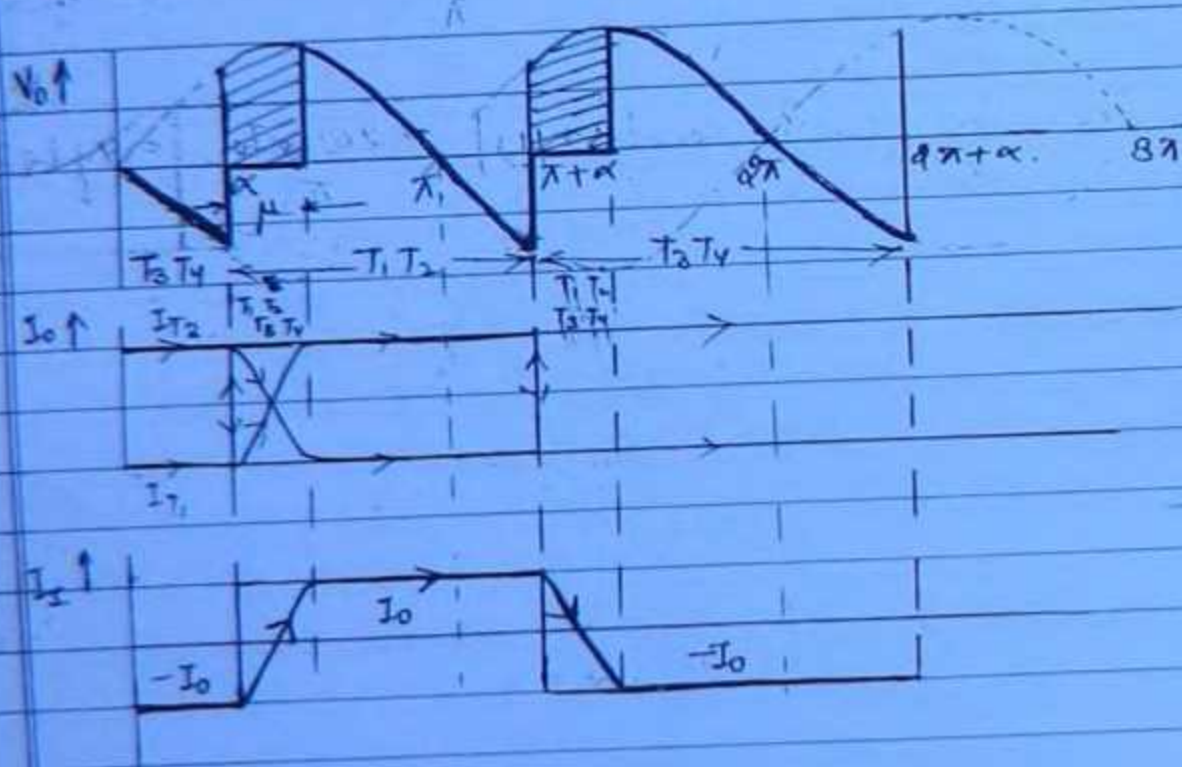Without $L_s \rightarrow V_o = V_{do} \cos \alpha$



$$\begin{aligned} T_1 T_2 &\rightarrow \text{ON} & I_{T1} &= I_{T2} = I_o \\ T_3 T_4 &\rightarrow \text{ON} & I_{T3} &= I_{T4} = I_o \end{aligned}$$

With L_s

During the overlap period v_{fg} is 0 as all thyristors are conducting ~~conducting~~ $\therefore v_{fg}$ is 0.

During μ T_1, T_2 & $T_3, T_4 \rightarrow ON$ So $V_o = 0$

(133)

$$V_o = L_s \frac{dI_o}{dt}$$

$$\int_{\alpha}^{\alpha+\mu} V_m \sin \omega t \, d(\omega t) = \omega L_s \int_{-I_o}^{+I_o} dI_o$$

Wrong P.S.E.

$$\frac{V_m [\cos \alpha - \cos(\alpha + \mu)]}{\pi} = \frac{2\omega L_s I_o}{\pi}$$

$$\Delta V_{do} = \frac{V_m [\cos \alpha - \cos(\alpha + \mu)]}{\pi} = \frac{2\omega L_s I_o}{\pi} = 4f L_s I_o \quad (1)$$

$$V_{do} = \frac{V_m}{\pi} \Rightarrow \frac{V_{do}}{2} = \frac{V_m}{\pi}$$

$$\Delta V_{do} = V_{do} [\cos \alpha - \cos(\alpha + \mu)] = \frac{2\omega L_s I_o}{\pi}$$

$$V_o = V_{do} \cos \alpha - 4f L_s I_o \quad (2)$$

$$V_o = \frac{V_{do}}{2} [\cos \alpha + \cos(\alpha + \mu)] \quad (3)$$

From (1)

$$V_m [\cos \alpha - \cos(\alpha + \mu)] = 2\omega L_s I_o$$

$$I_o = \frac{V_m}{2\omega L_s} [\cos \alpha - \cos(\alpha + \mu)]$$

$$I_o = \cos \alpha - \cos(\alpha + \mu) \quad (4)$$

Inductive Voltage Regulation -

Measure of reduction in vlg due to the source inductance.

$$\Delta V_{do}$$

$$= \frac{V_{do}}{2} [\cos \alpha - \cos(\alpha + \mu)]$$

$$= \frac{V_{do}}{2} [\cos \alpha - \cos(\alpha + \mu)]$$

ΔV_{do} does not depend on α .

At $\alpha = 0$ let $\mu = \mu_0$

$$\text{Inductive Vlg Reg} = \frac{\cos 0 - \cos(0 + \mu_0)}{2}$$

$$= \frac{1 - \cos \mu_0}{2}$$

Effect of L_s on the performance of converter -

* Reduces avg output vlg of the converter

* It limits the range of α

$$\alpha_{max} = 180 - (\omega t_d + \mu_0)$$

t_d = device turn off time

Disadv

$$* \text{PF} = \cos\left(\frac{\alpha + \mu}{2}\right)$$

due to L_s

Adv * $\uparrow g$ = gives smoothness of waveform towards sine wave,


so $\uparrow g$ waveform approaches towards sine wave

$\therefore$ with L_s , $g \uparrow$ THD $\downarrow$

on AC side of converter.

Here the $\uparrow$ in g value is dominating the $\downarrow$ in PDF . i.e. the PF is slightly $\uparrow$ (135)

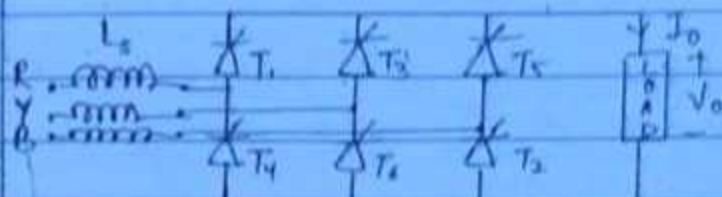
Effect of Source Inductance $\rightarrow$ 6 pulse converter



Without L_s

With L_s

Reduction in V_o due to L_s

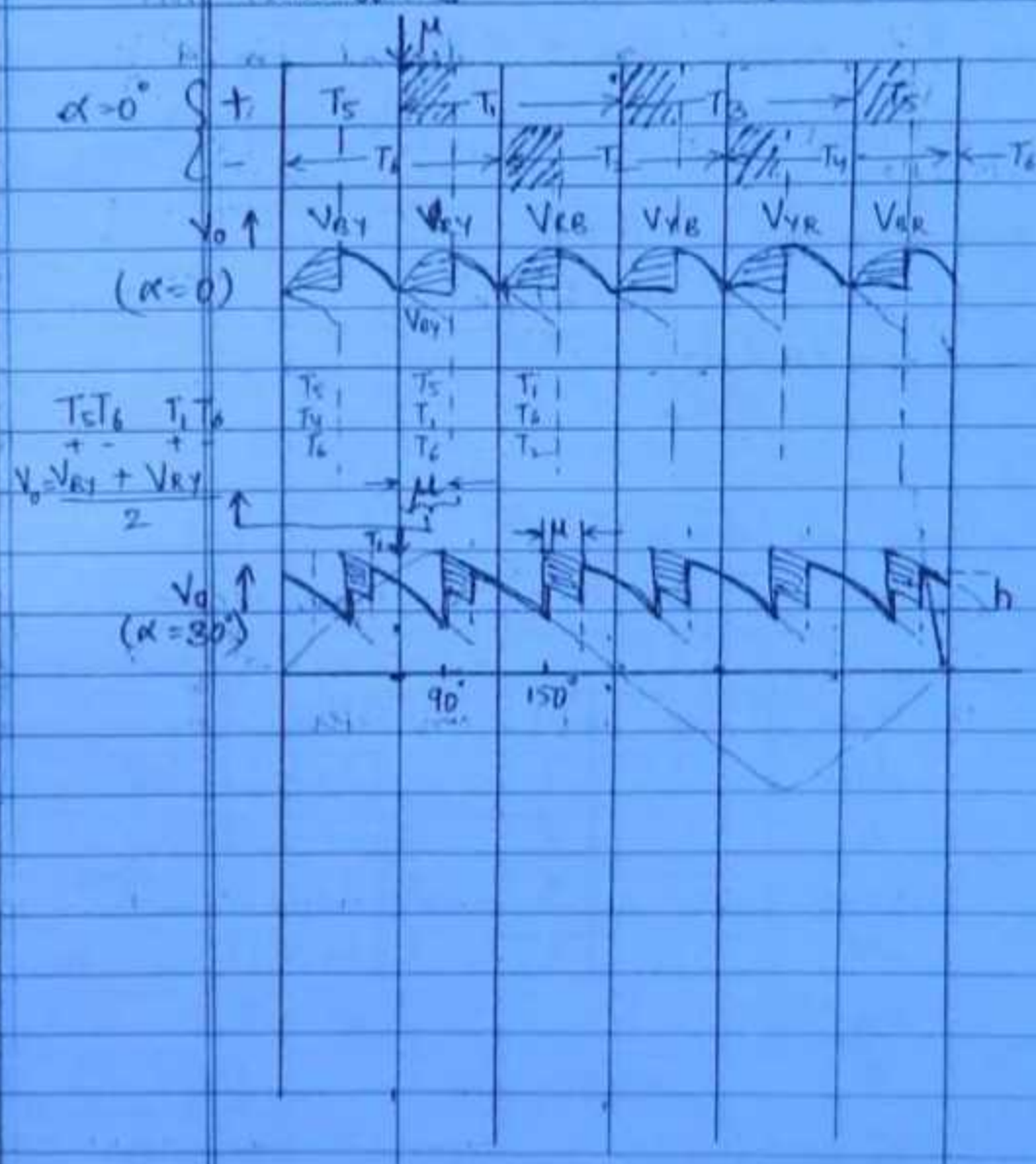

$\alpha = 0-90$

$\alpha \uparrow$ ripple $\uparrow$ $h \uparrow$

$\therefore \mu \downarrow$ to maintain same area

[max ripple $\rightarrow$ at 90°]

[min μ $\rightarrow$ at 90°]

$$\Delta V_{do} = \frac{V_{do}}{2} (\cos \alpha - \cos (\alpha + \mu)) = 6 f L_s I_o \quad \text{--- (1)}$$

(136)

* We get minimum μ at $\alpha = 90^\circ$ cuz we get maximum ripple

* We get maximum μ at $\alpha = 0^\circ$ cuz ripple is minimum

$\Rightarrow$ When other parameters are ~~at~~ ^{held} constant
 $\mu \downarrow$ ripple $\uparrow$ when $0 \leq \alpha \leq 90^\circ$

* for $\alpha > 90^\circ$ $\alpha \uparrow \mu \uparrow$ --- estimated option = $\mu \downarrow \uparrow$

$$V_o = V_{do} \cos \alpha - 6 f L_s I_o \quad \text{--- (2)}$$

$$V_o = \frac{V_{do}}{2} [\cos \alpha + \cos (\alpha + \mu)] \quad \text{--- (3)}$$

$$I_o = \frac{V_{mL}}{2 \omega L_s} [\cos \alpha - \cos (\alpha + \mu)] \quad \text{--- (4)}$$

m	V_{do}
2	$2 V_m$
	π
3	$3 V_{mL}$
	2π
6	$\frac{3 V_{mL}}{\pi}$

m	ΔV_{do}
1	$f L_s I_o$
2	$4 f L_s I_o$
3	$8 f L_s I_o$
6	$6 f L_s I_o$

$\int_{-I_o}^{I_o}$

INVERTERS

137


Fixed DC $\rightarrow$ Variable AC
(V_o f_o)

Classification of Inverters -

- $\rightarrow$ Voltage Source Inverters (VSI) $\rightarrow$ i waveform depends on load, vlg waveform is independent of load
- $\rightarrow$ Current Source Inverters (CSI) $\rightarrow$ app of VSI

VSI

a) 1ϕ Half Bridge Inverter -

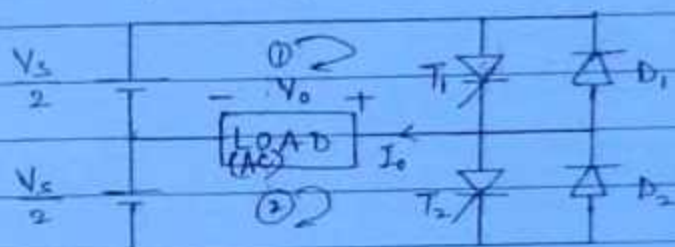


$$T_1 \rightarrow ON \\ V_o = \frac{V_s}{2}$$

$$T_2 \rightarrow ON \\ V_o = -\frac{V_s}{2}$$

$I_g \uparrow$


$I_g \uparrow$

$V_o \uparrow$
(Any Load)

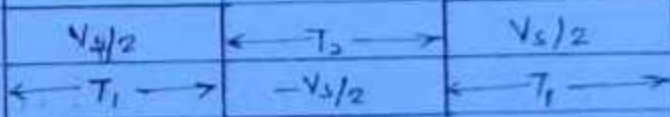

$I_o \uparrow$

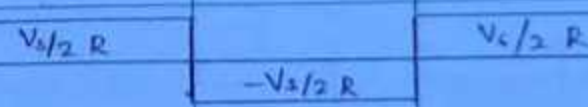(R Load)
Feedback diodes
will not conduct



$\rightarrow$ Forced commutation is required

$$V_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4}{n\pi} \left(\frac{V_s}{2} \right) \sin n\omega t$$

138

$$\Rightarrow V_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_s}{n\pi} \sin n\omega t$$

$$\Rightarrow V_{en} = \frac{2V_s}{n\pi} \sin n\omega t$$


$$(V_{en})_{rms} = \frac{\sqrt{2} V_s}{n\pi}$$

$$(V_{o1})_{rms} = \frac{\sqrt{2} V_s}{\pi}$$

$$g = \frac{(V_{o1})_{rms}}{V_{en}} = \frac{\frac{\sqrt{2} V_s}{\pi}}{\frac{V_s}{2}} = \frac{2\sqrt{2}}{\pi}$$

$$THD = 48.34\%$$

b) 1 ϕ Full Bridge Inverter

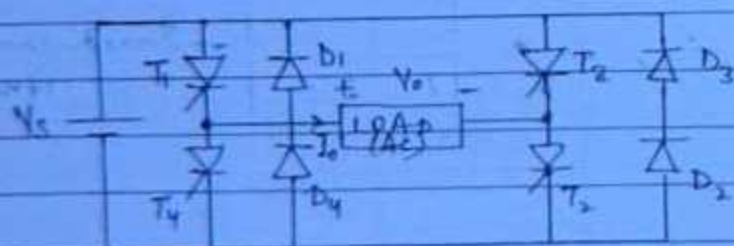

$T_1, T_2 \rightarrow ON$


$T_3, T_4 \rightarrow ON$

$V_o = V_s$

$V_o = -V_s$

$I_g, I_g \uparrow$

$I_g, I_g \uparrow$

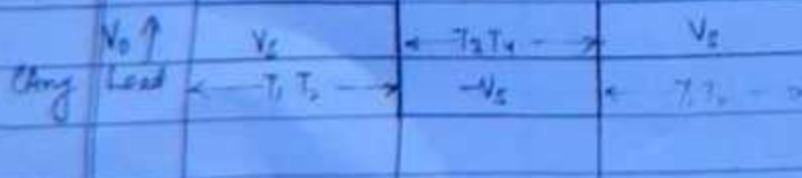

$$V_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi} \sin n\omega t$$

139

$$V_{on} = \frac{4V_s}{n\pi} \sin n\omega t$$

$$(V_{on})_{rms} = \frac{2\sqrt{2}}{n\pi} V_s$$

$$(V_o)_{rms} = \frac{2\sqrt{2}}{\pi} V_s$$

$$g = \frac{(V_o)_{rms}}{V_{on}} = \frac{2\sqrt{2}}{\pi} \frac{V_s}{V_s} = \frac{2\sqrt{2}}{\pi}$$

$$THD = 48.34\%$$

1 ϕ Half Bridge Inverter (Various Loads)

$V_o \uparrow$


$V_s/2$

$V_s/2$

$-V_s/2$

RL Load


$I_o \uparrow$

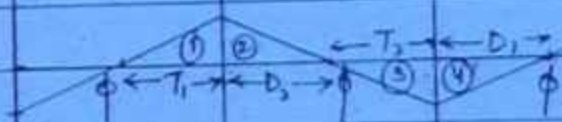

→ Forced commutation is required

RLC Load (Overdamped)


$I_o \uparrow$

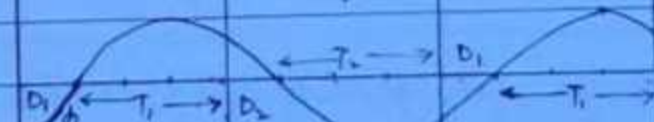

→ Forced commutation is required

RLC Load (Underdamped)

$I_o \uparrow$

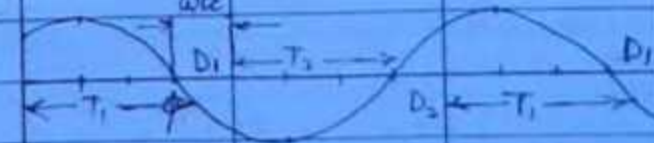

→ Forced commutation is not required (load comm occurs)
for load comm ($X_L > X_C$)

Switching logic for 1 quadrant converter

- ① $T \rightarrow ON$ $P+$
- ② $D \rightarrow ON$ $P-$
- ③ $(T, D) \rightarrow ON$ V_o+
- ④ $(T, D) \rightarrow ON$ V_o-


classmate
Date _____
Page _____

I RL Load -

After reaching steady state

$$I_o \text{ lags } V_o \text{ by } \phi = \tan^{-1} \frac{\omega L}{R}$$

140
V

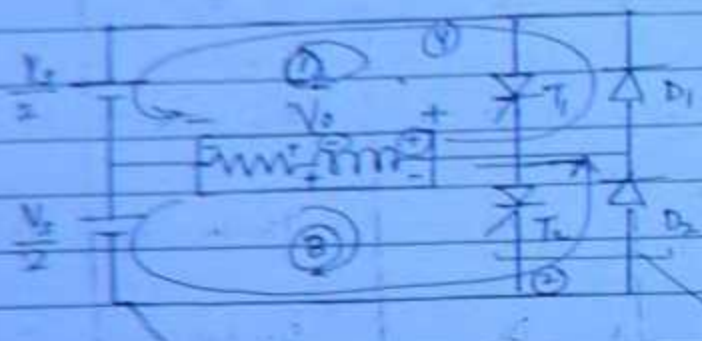

① $T_1 \rightarrow ON$

$$V_o = V_s \text{ i.e. } V_o + I_o R$$

$P_{source} \rightarrow P_{load}$

$$\left(I_o^2 R + \frac{1}{2} L I_o^2 \right)$$

Stores energy

② $D_2 \rightarrow ON$ $P-$

$$\frac{1}{2} L I_o^2 \rightarrow \text{source} + I_o^2 R$$

T (Releasing Energy)

of antiparallel devices cannot be ON at the same time.

e.g. D_2 when ON provides RB to T_2 so T_2 is OFF

③ $T_2 \rightarrow ON$

(D_2 releases reverse polarity thus T_2 starts conducting)

$$V_o = -V_s \text{ i.e. } V_o - I_o R$$

$P_{source} \rightarrow P_{load}$

$$\left(I_o^2 R + \frac{1}{2} L I_o^2 \right) \text{ Stores Energy}$$

④ $D_1 \rightarrow ON$

Inductor reduces its polarity to release energy searching for a favourable path which is achieved from D_1

$$\frac{1}{2} L I_o^2 \rightarrow \text{source} + I_o^2 R$$

(Releasing Energy)

* Forced commutation is required for RL Load

$\times$ $\times$ Switching Logic Table

141

Device (ON)

V_o	I_o	P	$\frac{1}{2}$ Bridge	Full Bridge
$T_1^+ D_1$	+	$T_1^+ T_2$	T_1	T_1, T_2
$T_1^+ D_1$	-	$D_1 D_2$	D_1	D_1, D_2
$T_2^+ D_2$	-	$T_1^+ T_2$	T_2	T_3, T_4
$T_2^+ D_2$	+	$D_1 D_2$	D_2	D_3, D_4

for all leading loads it starts with T

for all lagging loads it starts with D

II RLC (Overdamped)

$$X_L > X_C$$

$$I_o \text{ lags } V_o \text{ by } \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

III RLC (Underdamped)

$$X_C > X_L$$

$$I_o \text{ lags } V_o \text{ by } \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$\text{or } I_o \text{ leads } V_o \text{ by } \phi = \tan^{-1} \left(\frac{X_C - X_L}{R} \right)$$

$$\cot \phi = \frac{R}{X_C - X_L}$$

$$\tan \phi = \frac{X_C - X_L}{R}$$

* If $t_c < t_d$ then load commutation fails
($\therefore$ forced commutation is required)

$\rightarrow$ 4 for full bridge

$$V_{on} = \frac{2V_s \sin n\omega t}{n\pi} \quad (\text{Any Load})$$

(142)

Consider an RLC load

$$I_{on} = \frac{V_{on}}{Z_n}$$

$$Z_n = R + j(X_{Ln} - X_{Cn})$$

$$X_{Ln} = n\omega L$$

$$X_{Cn} = \frac{1}{n\omega C}$$

$\downarrow$
 n^{th} harmonic
inductive impedance

$\downarrow$
 n^{th} harmonic
capacitive impedance

$$Z_n = |Z_n| \angle \phi_n$$

$$|Z_n| = \sqrt{R^2 + (X_{Ln} - X_{Cn})^2}$$

$$\phi_n = \tan^{-1} \left(\frac{X_{Ln} - X_{Cn}}{R} \right)$$

$\downarrow$
 n^{th} harmonic
impedance angle
(or) displacement angle

$$I_{on} = \frac{V_{on}}{Z_n} = \frac{V_{on}}{|Z_n| \angle \phi_n} = \frac{V_{on}}{|Z_n|} \angle -\phi_n$$

$\rightarrow$ 4 for full bridge

$$I_{on} = \frac{2V_s \sin(n\omega t - \phi_n)}{n\pi |Z_n|}$$

$\rightarrow$ for RLC load

eg for pure inductive load

$$|Z_n| = n\omega L$$

$$\phi_n = 90^\circ$$

$$I_{on} = \frac{2V_s \sin(n\omega t - 90^\circ)}{n\pi |Z_n|} \neq I_{on} \propto \frac{1}{n^2}$$


If n^{th} harmonic is
inv. prop. to n^2 shape

3 ϕ VSI


a) 180 $^{\circ}$ MODE

+ T_1, T_3, T_5


143

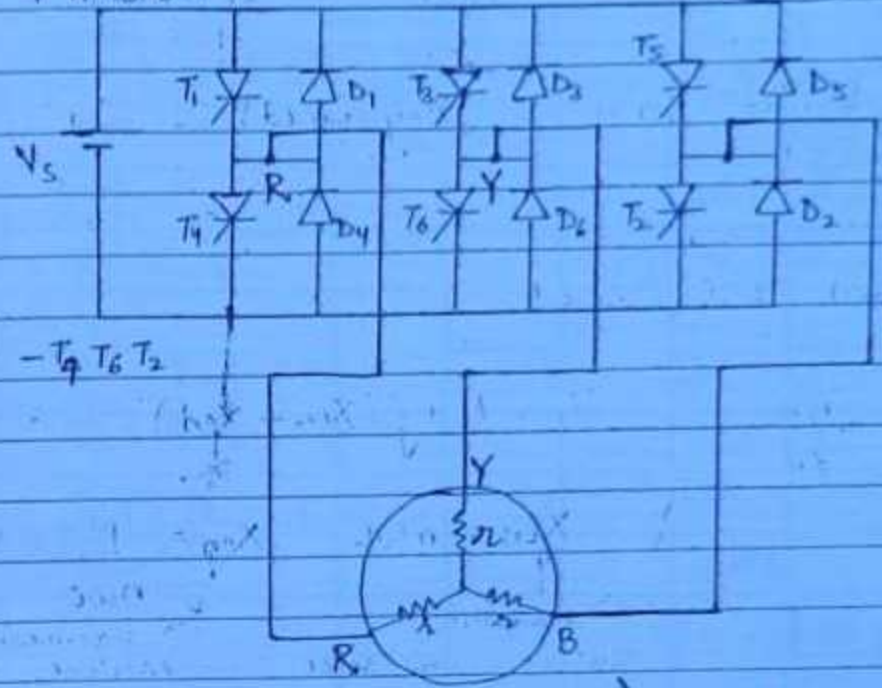

3 ϕ Y connected R Load

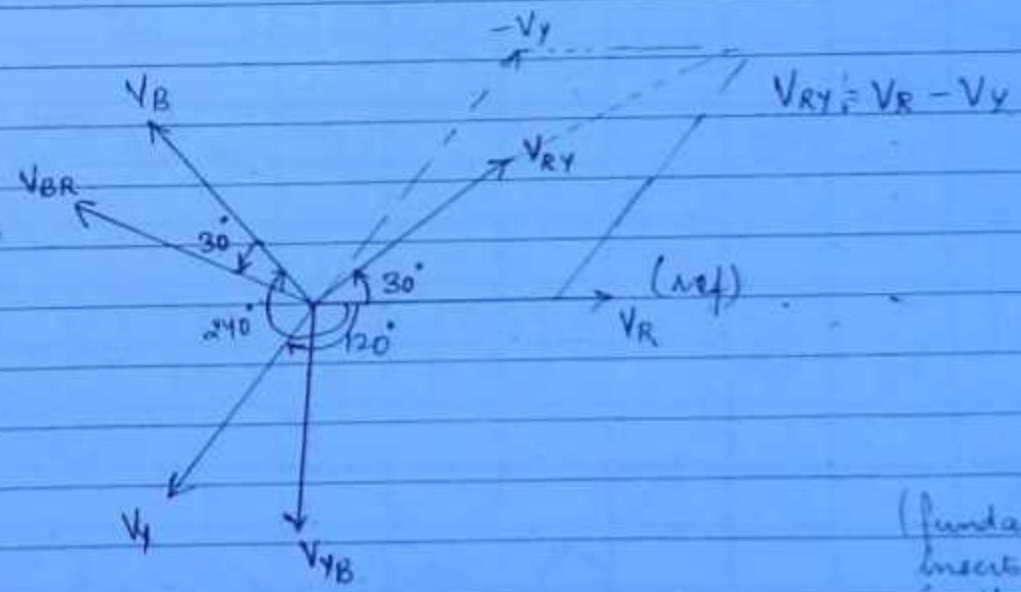

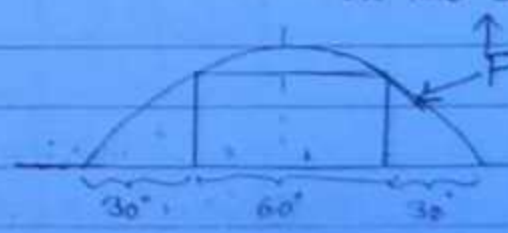(fundamental
inserts the pulse
in the centre)



$R[T_1, T_9] \leftarrow T_1 \rightarrow T_4 \rightarrow$
 $Y[T_2, T_8] \leftarrow T_6 \rightarrow T_3 \rightarrow T_6$
 $B[T_5, T_7] \leftarrow T_5 \rightarrow T_2 \rightarrow T_8 \rightarrow$
 $X_3 \quad 2A_3 \quad X \quad 4A_3 \quad 5A_3 \quad 2A$
 $212 \quad 123 \quad 239 \quad 345 \quad 456$
 561

$$V_R \uparrow \times \begin{array}{c|c|c|c|c|c} \frac{561}{-2} & \frac{212}{-2} & \frac{123}{-2} & \frac{239}{-2} & \frac{345}{-2} & \frac{456}{-2} \\ \hline & +2V_S & & & & \\ \hline +V_{2/3} & \frac{3}{3} & +V_{5/3} & & & \end{array}$$
 V_5
$$V_R - V_Y = V_{RY} \uparrow$$

天

The waveforms are same for any load Δ connected or Δ ^{connected} motor, induction motor etc.

$x = VSA$ v/o transformer is independent of load

561
+ - +

This -ve share
 current of 2 +ve
 phases
 so its double
 ie $Y \neq V$ of I
 no double of
 $R \neq S$
 since its -ve
 its polarity is -ve
 so $5 \rightarrow 6 \rightarrow +\frac{V_s}{2}$


$$\begin{array}{l} 6 \rightarrow Y \rightarrow -2V_s \\ 1 \rightarrow R \rightarrow +\frac{V_s}{3} \end{array}$$

144

$$0 \text{ to } \frac{\pi}{3} : T_5, T_6, T_1$$

$$\begin{array}{cc} T_1, T_6 & T_5, T_6 \\ + & - \end{array}$$

(145)

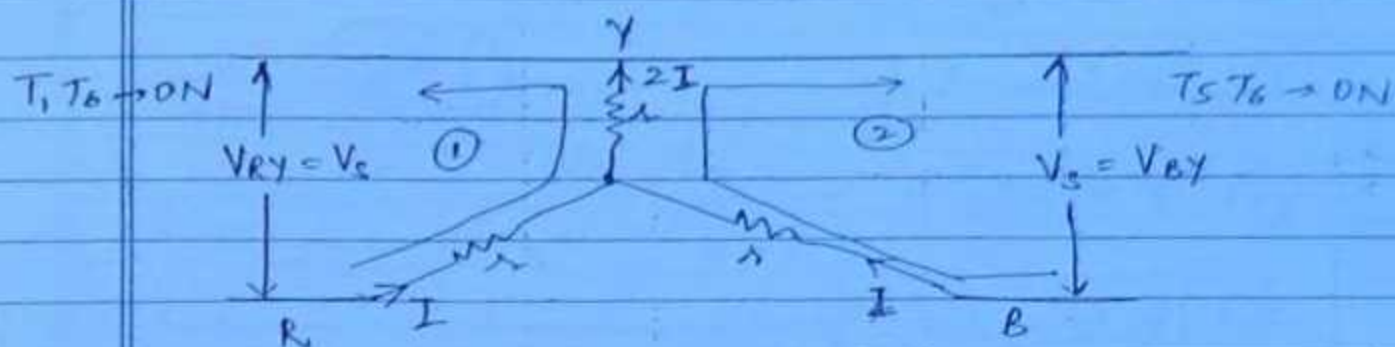

$$V_S = I\alpha + 2I\alpha$$

$$V_S = 3I\alpha$$

$$I\alpha = \frac{V_S}{3}$$

$$V_R = +I\alpha = +\frac{V_S}{3}$$

$$V_Y = -2I\alpha = -\frac{2}{3}V_S$$

$$V_B = +I\alpha = +\frac{V_S}{3}$$

$$V_{RY} = V_S \left(\frac{2\pi/3}{\pi} \right)^{1/2}$$

$$(V_L)_{rms} = V_S \sqrt{\frac{2}{3}}$$

$$V_R = \left\{ \frac{1}{\pi} \left[\left(\frac{V_S}{3} \right)^2 \frac{\pi}{3} + \left(\frac{2V_S}{3} \right)^2 \frac{\pi}{3} + \left(\frac{V_S}{3} \right)^2 \frac{\pi}{3} \right] \right\}$$

$$V_{ph} = \frac{\sqrt{2}}{3} V_S$$

$$I_L = I_{ph} = \frac{V_{ph}}{Z} = \frac{\sqrt{2} V_S}{3 Z}$$

$$(I_T)_{rms} = \frac{I_{ph}}{\sqrt{2}}$$

$$V_L = \sqrt{3} V_{ph}$$

$$(1) \quad V_{ph} = \frac{\sqrt{2}}{3} V_s$$

$$(2) \quad I_{ph} = \frac{V_{ph}}{Z}$$

$$(3) \quad (I_r)_{rms} = \frac{I_{ph}}{\sqrt{2}}$$

(46)

$$(4) \quad P = 3 I_{ph}^2 Z = 3 \frac{V_{ph}^2}{Z}$$

$$(5) \quad (V_L)_{rms} = \sqrt{3} V_{ph}$$

fourier series for Δ phase vlg waveform.

V_R

$$V_R = \sum_{n=6k \pm 1}^{\infty} \frac{a_n V_s}{n \pi} \sin n \omega t$$

NOTE: Even if triple harmonics are absent

$$V_{Rn} = \frac{a_n V_s}{n \pi} \sin n \omega t$$

$$(V_{Rn})_{rms} = \frac{\sqrt{2} V_s}{n \pi}$$

$$(V_{R1})_{rms} = \frac{\sqrt{2} V_s}{\pi}$$

$$g = \frac{V_{R1}}{V_R} = \frac{\frac{\sqrt{2} V_s}{\pi}}{\frac{\sqrt{2} V_s}{3}} = \frac{3}{\pi}$$

$$g = \frac{3}{\pi}$$

$$THD = 31\%$$

Let us consider, RLC load
in each phase.

$$V_{rn} = \frac{2V_s}{n\pi} \sin n\omega t$$

(147)

$$I_{rn} = \frac{V_{rn}}{Z_n} = \frac{V_{rn}}{|Z_n|/\phi_n}$$

$$I_{rn} = \frac{2V_s}{n\pi|Z_n|} \sin(n\omega t - \phi_n)$$

eg. I.M $|Z_n|$ per phase = $\sqrt{R_i^2 + (n\omega L_i)^2}$
 $\phi_n = \tan^{-1} \frac{X_{Ln}}{R}$

for $n=1$ (F)

Diode conducts for $\phi = \tan^{-1} \frac{X_L}{R}$ for RL load

if $\phi = \tan^{-1} \frac{X_C - X_L}{R}$ for RLC load

— x —

Line vlg.

$$V_{RY} = \sum_{\substack{n=1,3,5 \\ n=6k\pm 1}}^{\infty} \frac{4V_s}{n\pi} \sin \frac{n\pi}{3} \sin n\left(\omega t + \frac{\pi}{6}\right)$$

•

$$g = \frac{3}{\pi}$$

$$THD = 31\%$$

Disadvantage of 180° mode VSI

There is a possibility of S.C across the supply when incoming thyristor starts conducting before the outgoing thyristor belonging to the same phase stops conducting

b) 120° mode → In 120° mode VSI we are allotting a conduction angle of 120° for each thyristor & the last 60° is allotted for commutation



(148)

$V_R \uparrow$

$V_{s/2}$

$-V_{s/2}$

$V_Y \uparrow$

$V_{s/2}$

$-V_{s/2}$

$-V_{s/2}$

$V_B \uparrow$

$V_{s/2}$

$-V_{s/2}$

$V_{RY} \uparrow$

$= V_R - V_Y$

V_s

$V_{s/2}$

$-V_{s/2}$

for Δ connection

$V_{RY} \quad V_{YB} \quad V_{BR}$

→ displace this by 120° & 240° for V_{YB} & V_{BR}

$$(V_R)_{rms} = \frac{V_s}{2} \left(\frac{2\pi/3}{\pi} \right)^{1/2}$$

$$= \frac{V_s}{2} \sqrt{\frac{2}{3}}$$

$$(V_R)_{rms} = \frac{V_s}{\sqrt{6}} = V_{ph}$$

(149)

phase v/f $V_R = \sum_{\substack{n=6k+1 \\ n=1,3,5}}^{\infty} \frac{2V_s}{n\pi} \sin n \frac{\pi}{3} \sin n \left(\omega t + \frac{\pi}{6} \right)$

NOTE: Even & triple harmonics are absent

$$g = \frac{3}{\pi}$$

$$THD = 31\%$$

line v/f $V_{RY} = \sum_{n=6k+1}^{\infty} \frac{3V_s}{n\pi} \sin n \left(\omega t + \frac{\pi}{3} \right)$

NOTE: Even & triple harmonics are absent

$$g = \frac{3}{\pi}$$



$$THD = 31\%$$

For 120° & 180° mode

phase or line v/f

g & THD are same.

CSI

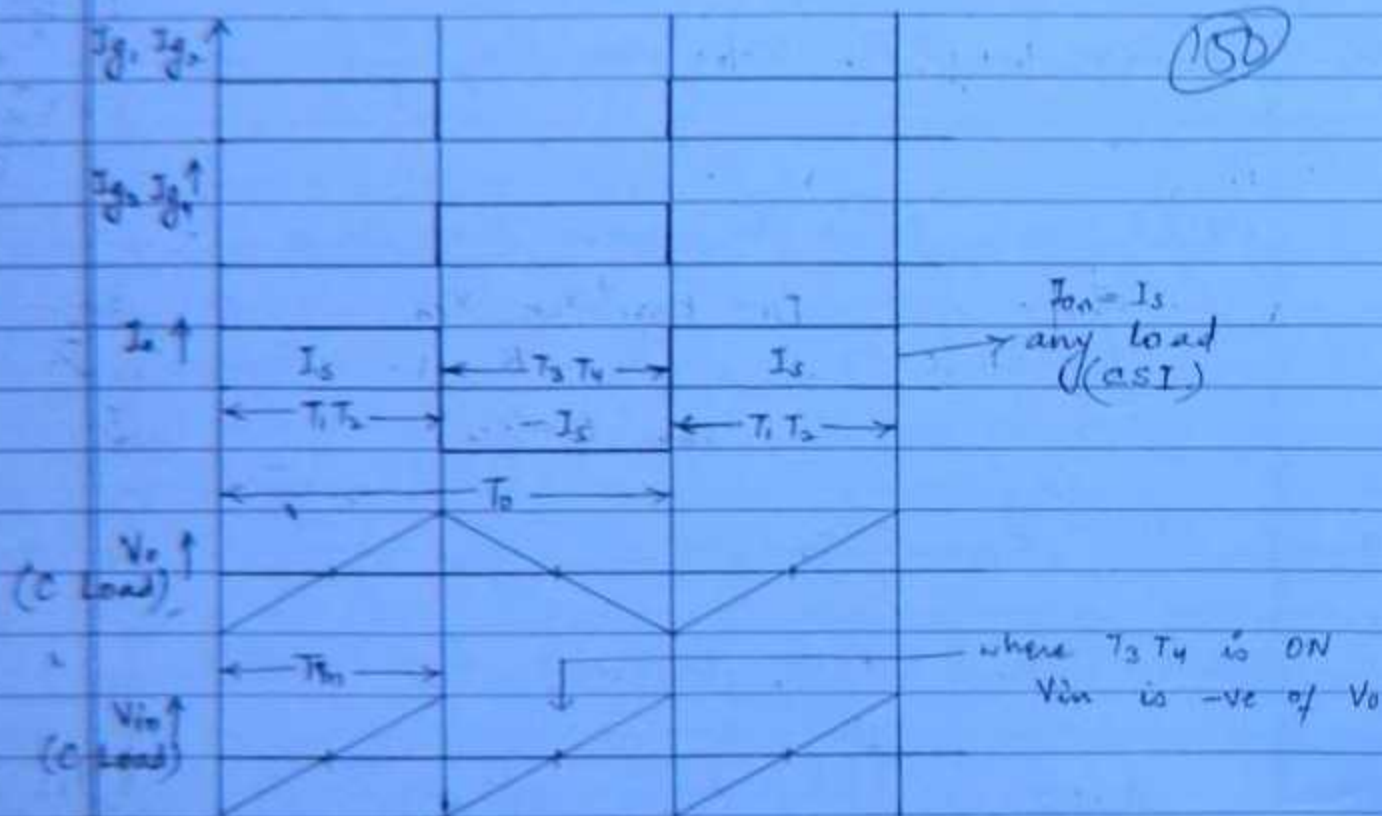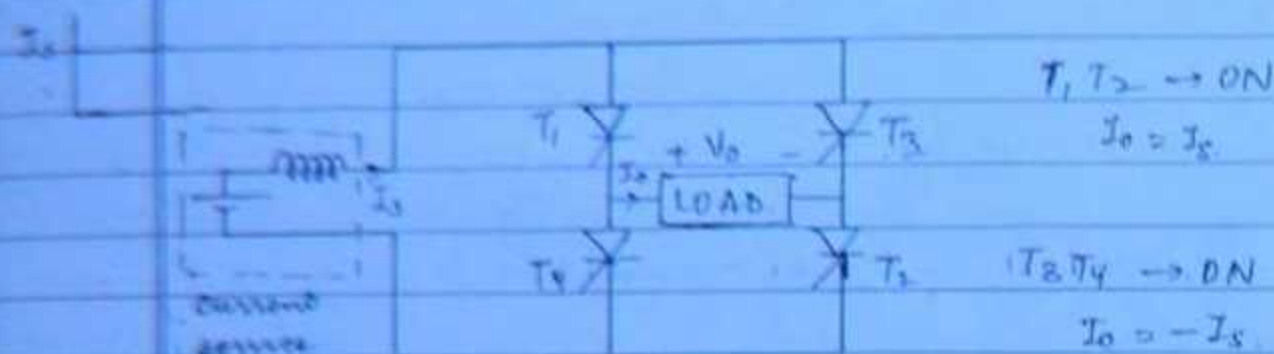

$$I_o = \sum_{n=1,3,5}^{\infty} \frac{4 I_s \sin n \omega t}{n \pi}$$

$$g = \frac{2\sqrt{2}}{\pi} \quad THD = 48.34\%$$

$$I_{om} = \frac{4 I_s}{\pi} \sin n \omega t \quad [\text{for any load}]$$

Let us consider an RLC load -

$$V_{on} = I_{on} Z_n$$
$$= I_{on} |Z_n| \angle \phi_n$$

(15)

$$V_{on} = \frac{4I_s}{n\pi} |Z_n| \sin(n\omega t + \phi_n)$$

$$Z_n = R + j(X_{Ln} - X_{Cn})$$

For C load

$$|Z_n| = \frac{1}{n\omega C}$$


$$\phi_n = \tan^{-1} \frac{X_{Ln} - X_{Cn}}{R}$$

$$= \tan^{-1} \frac{0 - X_{Cn}}{0}$$

$$\phi_n = -90^\circ$$

$$V_{on} = \frac{4I_s}{n\pi} \left(\frac{1}{n\omega C} \right) \sin(n\omega t - 90^\circ)$$

$$V_{on} \propto \frac{1}{n^2}$$

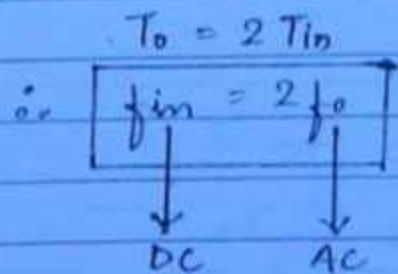


Advantages of CSI -

1. Feedback diodes are not required in CSI.
2. Commutation is simple.
3. For C loads there's a possibility of load commutation.
4. Inherently, there's a short-circuit protection for the source when the incoming thyristors are switched on before the outgoing thyristor becomes off due to the presence of high inductance.

Disadvantage of CSI -

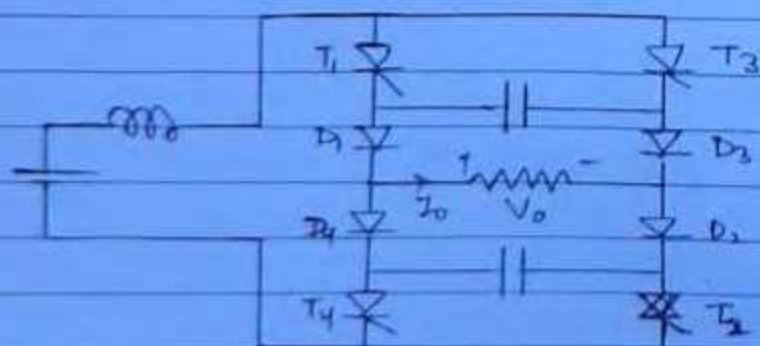1. The commutating element (along with the load) applies high reverse v/g across the power device used in CSI. i.e. the devices having low reverse v/g blocking capability such as GTO, IGBT or other transistors are not generally preferred in CSI. Here we prefer SCR because it has high reverse v/g blocking capability.
2. If commutating capacitor is directly connected across the load, then it will be continuously discharging through the load. To avoid it we must connect the diode as shown in figure.




(5) $\alpha = 60$ FDF = $\cos \alpha = \cos 60 = 0.5$
(IDF)

$$PF = g(FDF)$$

$$= \frac{3}{\pi} (\cos \alpha) = \frac{3}{\pi} \cos 60 = 0.476(c)$$

=

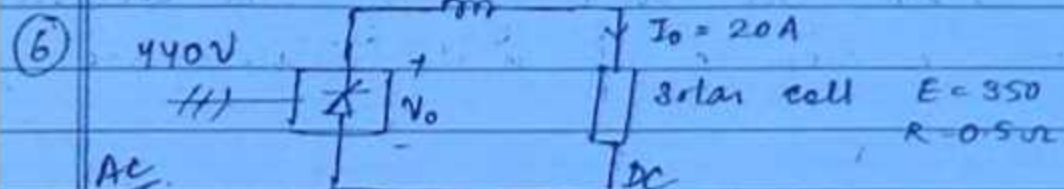

$$P_{AC} \leftarrow \frac{INV}{(\alpha > 90^\circ)} P_{DC}$$

$$V_o = -E + I_o R$$

$$= -350 + 10 = -340$$

$$\frac{3 V_{ML} \cos \alpha}{\pi} = -E + I_o R$$

$$\frac{3 \cdot 440 \sqrt{2} \cos \alpha}{\pi} = -340$$

$$\alpha = 125^\circ$$

for $\alpha > 60^\circ$ $\omega t_c = \pi - \alpha = 180 - 125^\circ$
 $= 55^\circ (d)$

(154)

10


(153)

$$\alpha = 60^\circ, \text{ FDF} = \cos \alpha$$

$$= \cos 60 = 0.5$$

$$\text{PF} = \frac{1}{\pi} (\text{FDF}) = \frac{3 \times 0.5}{\pi}$$

$$= 0.478$$

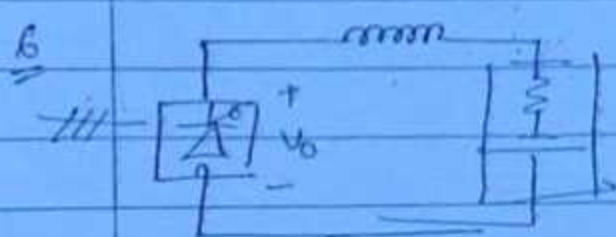

$P_{AC} < P_{DC}$
inversion
 $\alpha > 90^\circ$

$$V_o = -E + I_o R$$

$$\frac{\cos \alpha \cdot 3\sqrt{2} V_{ML}}{\pi \cos \alpha} = -3.50 + (20 \times 0.5)$$

$$\frac{3 \times 440 \sqrt{2} \cos \alpha}{\cos \pi} = -3.50 + 10$$

$$\cos \alpha \Rightarrow \alpha = 125^\circ$$

I $\alpha < 60^\circ, \omega t_c = 4\pi/3 - \alpha$

II $\alpha > 60^\circ, \omega t_c = \pi - \alpha/3$



$$= 180^\circ - 125^\circ$$

$$= 55^\circ$$

VOLTAGE Control of Inverter

ISL

I - External control

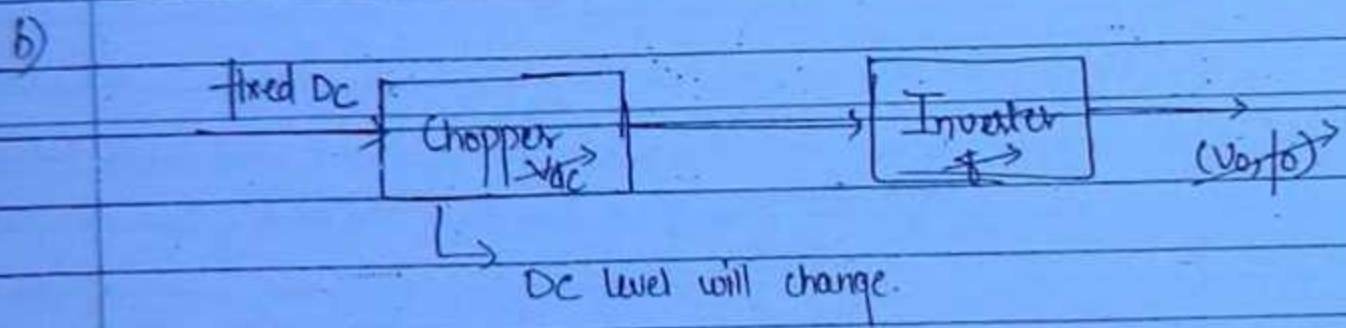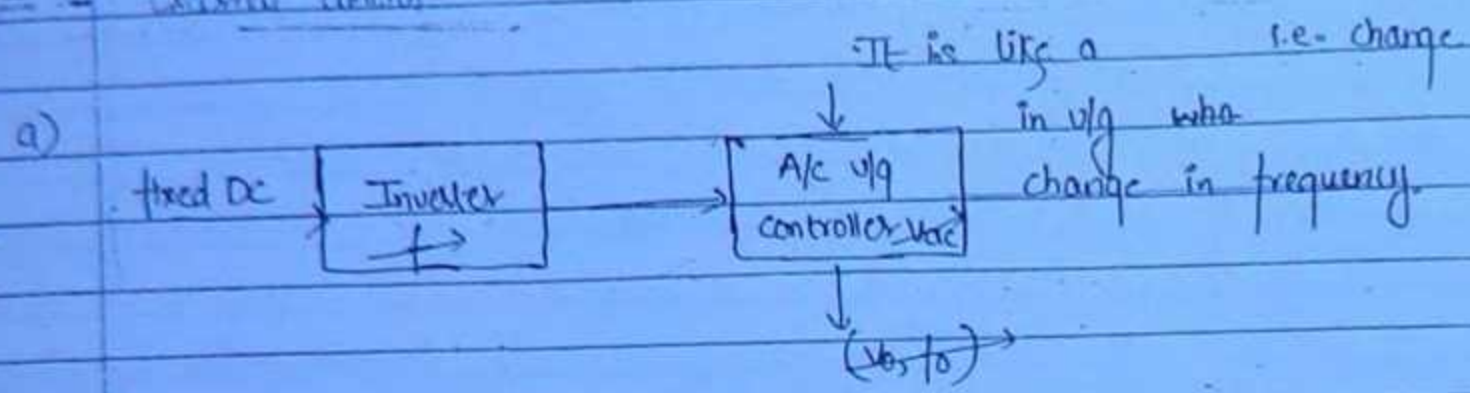

II Internal v/q control using PWM technique:-

(157)


Advantages of PWM technique:-


1. We can get variable v/q within the inverter without increasing no. of stages.
2. We can eliminate some of the lower order harmonics (higher order harmonics can be easily filtered).

Types of PWM techniques:-

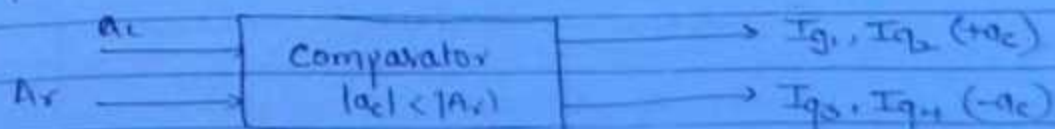1. Single PWM technique:-

Let us realise this modulation technique using full bridge inverter.



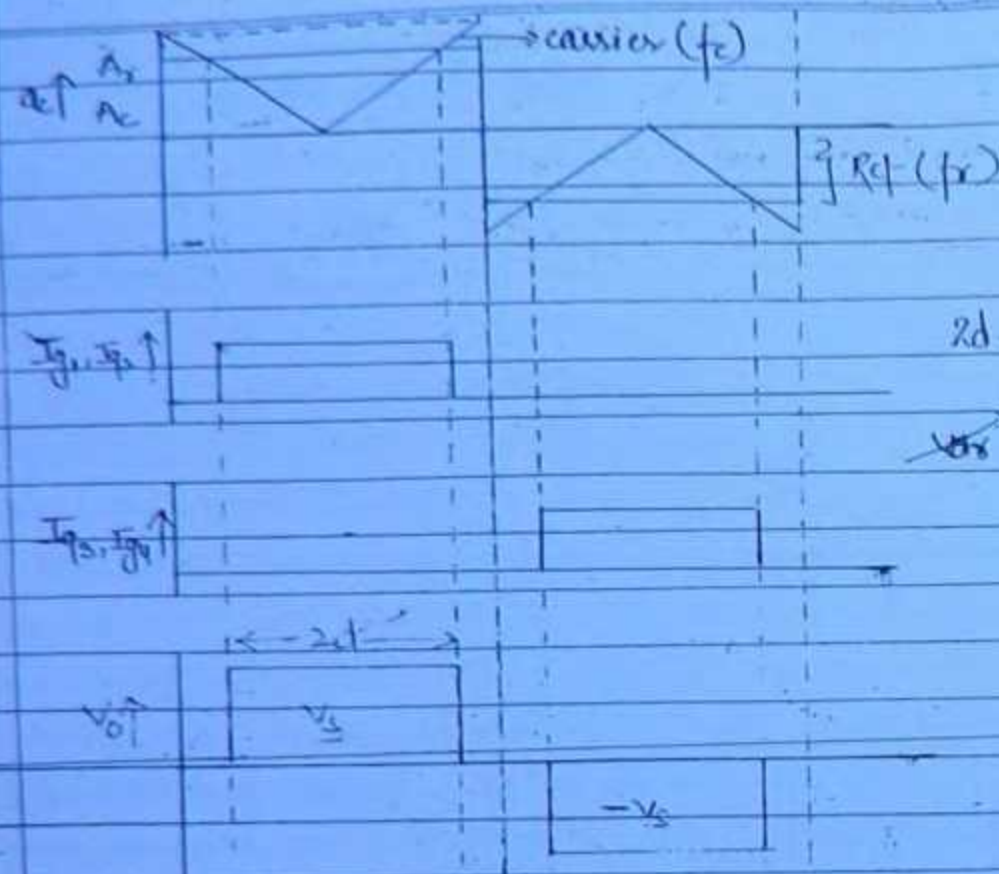

$2d \rightarrow$ Total pulse width

$$V_s = V_c \left(\frac{2d}{\pi} \right)^{1/2}$$

(158)

Fourier series for o/p vlg waveform:-

$$V_o = \sum_{n=1,3,5}^{\infty} \frac{4V_s}{n\pi} \sin n\omega t \cdot \sin n\pi \frac{2d}{\pi} \sin n\pi d$$

$$V_{on} = \frac{4V_s}{n\pi} \sin n\pi \frac{2d}{\pi} \cdot \sin n\pi d \cdot \sin n\omega t$$

$$V_{on} = 0 \quad \text{if } nd = \pi, 2\pi, 3\pi, \dots$$

$$d = \frac{\pi}{n}, \frac{2\pi}{n}, \frac{3\pi}{n}, \dots$$

$$\left[\begin{array}{l} 2d \neq \frac{2\pi}{n}, \frac{4\pi}{n}, \frac{6\pi}{n} \rightarrow \text{valid only if } 2d \leq \pi \\ \rightarrow \text{condition to eliminate } n\text{th harmonic} \end{array} \right]$$

To eliminate 3rd harmonic

$$2d = \frac{2\pi}{3}, \frac{4\pi}{3}, \frac{6\pi}{3}, \dots$$

$\therefore$ Since it is less than π

$$2d = \frac{2\pi}{3} = 120^\circ$$

(59)

To eliminate 5th harmonic

$$2d = \frac{2\pi}{5}, \frac{4\pi}{5}, \frac{6\pi}{5}, \dots$$

both less than π

$$2d = 72^\circ, 144^\circ$$

$$V_{on} = \frac{4V_s}{n\pi} \left| \sin\left(\frac{n\pi}{2}\right) \right| \sin nd \cdot \sin n\pi t$$

$\rightarrow$ for $n=1, 3, 5, \dots$ it is ± 1 , for rms value calculation it is always 1

$$(V_{on})_{rms} = \frac{4V_s}{n\pi} \frac{\sin nd}{\sqrt{2}} = \frac{2\sqrt{2}V_s \sin nd}{n\pi}$$

$$(V_{o1})_{rms} = \frac{2\sqrt{2}V_s \sin d}{\pi}$$

$$g = \frac{(V_{o1})_{rms}}{V_{or}} = \frac{2\sqrt{2}V_s \sin d}{V_s \left(\frac{2d}{\pi}\right)^{1/2}}$$

$$g = \frac{2\sqrt{2} \cdot \frac{1}{2} \sin d}{\sqrt{2d} \cdot \pi}$$

$$THD = \left(\frac{1}{g^2} - 1 \right)^{1/2}$$

Page 49

1

$$2d = \alpha = 120^\circ$$

$$V_s = 1V$$

$$(V_{o1})_{rms} = \frac{2\sqrt{2}V_s \cdot \sin d}{\pi}$$

$$= \frac{2\sqrt{2}}{\pi} \sin 60^\circ$$

$$= 0.78$$

166

2.

$$2d = 72^\circ \text{ or } 144^\circ$$

3

$$2d = 144^\circ$$

$$(V_{o3})_{rms} = \frac{2\sqrt{2}V_s \sin 3d}{3\pi}$$

$$(V_{o1})_{max} = \frac{2\sqrt{2}V_s}{\pi}$$

$$\frac{(V_{o3})_{rms}}{(V_{o1})_{max}} = \frac{\sin 3d}{3}$$

$$= 19.6\%$$

5

$$2d = 150^\circ$$

$$(V_{o1})_r = \frac{2\sqrt{2}V_s \sin d}{\pi}$$

$$g = \frac{2\sqrt{2} \cdot \sin d}{\sqrt{(2d) \cdot \pi}}$$


$$= 0.95$$

$$THD = 0.32$$

$$= 31.83\%$$

Multiple pulse PWM technique :-

(TGI)

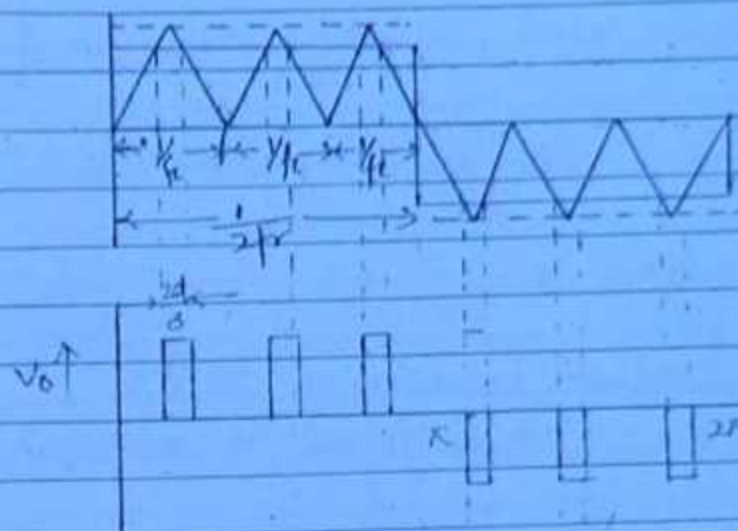

$$\frac{3}{f_c} = \frac{1}{2f_r}$$

$$3 = \frac{f_c}{2f_r}$$

$2d \rightarrow$ Total PW in each $\frac{1}{2}$ cycles

$$V_{or} = V_s \left(\frac{2d}{\pi} \right)^{1/2}$$

$$n = \frac{f_c}{2f_r}$$

$$\left| \begin{array}{l} \text{Pulse width} = \frac{2d}{N} = \left(\frac{1 - V_r}{V_c} \right) \frac{\pi}{N} \\ \text{(Pulse length)} \end{array} \right|$$

$\rightarrow$ Height of pulse is decided by supply, only by changing supply height of the pulse can be varied.

III.

Sinusoidal PWM technique



In sinusoidal PWM technique, the reference signal is taken as sine waveform.

There we've two cases:-

I case:- Peak value of carrier coincident with zero of Ref. signal

II case:- Zero of carrier coincident with zero of reference.

Case-1 :- $N = \frac{f_c}{2f_r}$, Case-2 :- $N = \frac{f_c}{2f_r} - 1$

(62)

NOTE:-

Dominant harmonics = $2N \pm 1$.

$N \rightarrow$ No. of pulses in each half cycle


for $N=3$, Dominant harmonic = $6 \pm 1 = 5, 7$ th.

for $N=9$, " " = $18 \pm 1 = 17, 19$ th.

$\rightarrow$ If Domination is chosen by lower order, it is difficult to filter them, we require big size filter to remove lower order harmonics.

$\rightarrow$ If Domination is chosen by higher order, we can easily filter them.

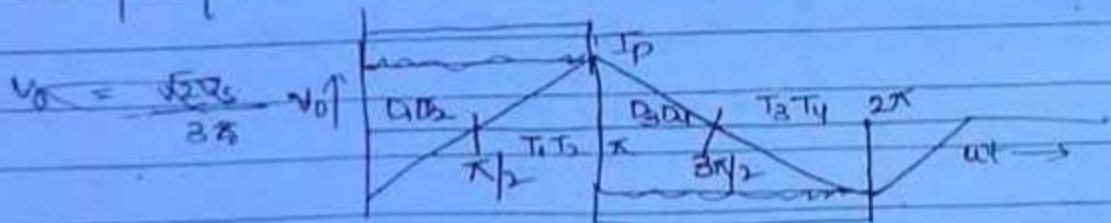In sinusoidal PWM tech, we $\uparrow$ the No. of pulses in each half cycle & $\uparrow$ the order of dominant harmonics so that they can be easily filtered.



$\frac{\pi}{2} \text{ to } \pi \rightarrow V_o = V_s = L \frac{di}{dt}$

$\omega di = \frac{V_s}{L} dt \quad \pi \rightarrow \omega di = \frac{V_s}{L} d(\omega t)$
 $\int_0^{\pi} di = \frac{V_s}{\omega L} \int_{\pi/2}^{\pi} d(\omega t)$

$$I_p = \frac{200 \angle \times \times}{100 \angle \times 0.1 \angle \times}$$

$$= 10A$$

(163)

13

Since, Inductor $\rightarrow \phi = 90^\circ$

$$\omega t_c = \phi$$

$$t_c = \frac{\phi}{\omega} = \frac{90^\circ/180^\circ \times \pi}{2\pi f} = 5ms$$

12

3 ϕ VSI

$\rightarrow$ pure inductive Load, $|Z_n| = n\omega L$

$$V_{on} = \alpha V_{oi} \quad (\alpha < 1)$$

$$I_{on} = \frac{\alpha V_{oi}}{|Z_n|} = \frac{\alpha n}{n} \frac{V_{oi}}{\omega L}$$

$$\frac{0.5 \times \pi}{2 \times \pi \times 50}$$

$$= \frac{\alpha n}{n} I_{oi}$$

1.

$$R = 3\Omega, X_L = 12\Omega, X_C = ?$$

$$f = \frac{10^3}{0.2} = \frac{10^3 \times 10}{2} = 5000 \text{ Hz}$$

$$t_g = 12 \times 10^{-6} \text{ s}, SF = 2$$

$$t_c = 12 \times 2 \times 10^{-6}$$

$$\phi = -\tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$\frac{12 \times 10^{-6} \times 2 \times \pi \times 5000 \times 180^\circ}{\pi} \tan^{-1} \left(\frac{12 - X_C}{3} \right)$$

$$X_C = X_L = 14.182$$

$$C = 2.15 \mu F$$


$$\frac{1}{\omega C} = X_C$$

CHOPPER


(164)

fixed DC $\rightarrow$ variable DC

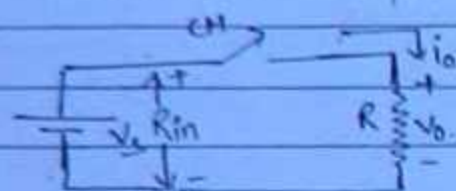1. Step-down Chopper :- ($V_o < V_s$) $\rightarrow$ without filter



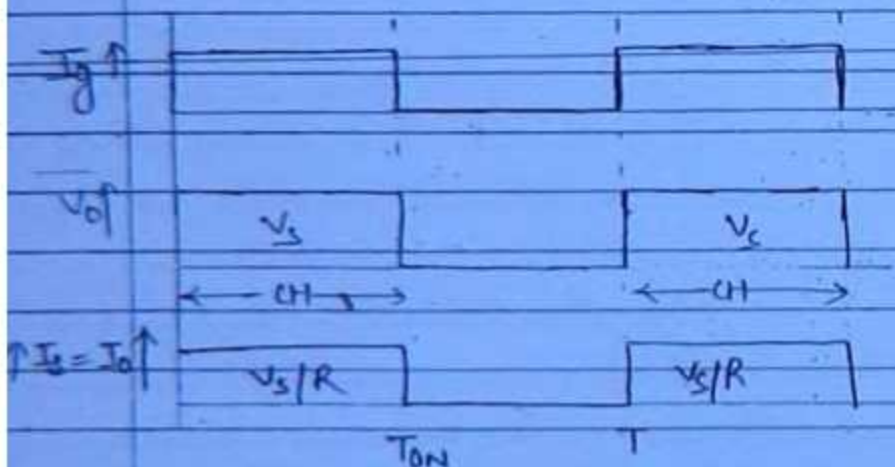Switch can be replaced by GTO or any power device for low power applⁿ but for high-power, it should be SCR with forced commutation.



$$\alpha = \frac{T_{ON}}{T}$$

= Duty cycle.

$$V_o = V_s \left(\frac{T_{ON}}{T} \right) = \alpha V_s$$

$$V_{rms} = \sqrt{\alpha} V_s$$

$$I_o = \frac{V_o}{R} = \frac{\alpha V_s}{R} = I_{s0}$$

$$R_{in} = \frac{V_s}{I_s} = \frac{V_s}{\alpha \frac{V_s}{R}} = \frac{R}{\alpha}$$

$$\boxed{R_{in} = \frac{R}{\alpha}}$$

$$V_o = \alpha V_s + \sum_{n=1}^{\infty} \frac{2V_s}{n\pi} \sin(n\omega t + \phi_n) \sin n\pi\alpha$$

$$\text{where } \phi_n = \tan^{-1} \left[\frac{\cos n\alpha}{\sin n\alpha} \right]$$

65

$$V_n = \frac{\alpha V_s}{n\pi} \sin n\alpha \cdot \sin(n\omega t + \phi_n)$$

$$V_n = 0 \text{ if } n\alpha = 1$$


$$\alpha = \frac{1}{n} \rightarrow \text{cond}^n \text{ to eliminate } n\text{th harmonic}$$

$$FF = \frac{V_{or}}{V_o} = \frac{\sqrt{\alpha} V_s}{\alpha V_s} = \frac{1}{\sqrt{\alpha}}$$

$$\downarrow VRF = \sqrt{FF^2 - 1} = \sqrt{\frac{1}{\alpha} - 1}$$

For High values of Duty cycle, harmonics are lesser.

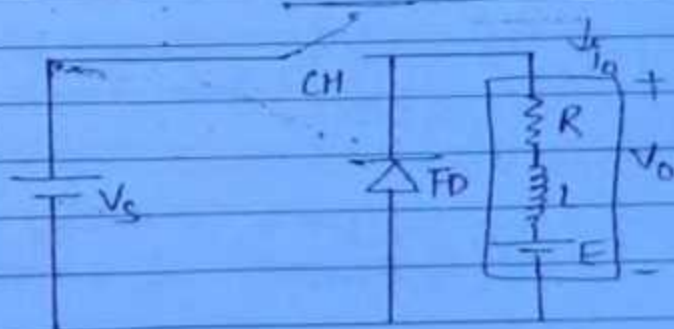
RLE Load $\rightarrow$ Cont. Conduction (waveform same for RL & RLE)



$$V_o = \alpha V_s$$

$$V_{or} = \sqrt{\alpha} V_s$$

$$I_o = \frac{\alpha V_s - E}{R}$$

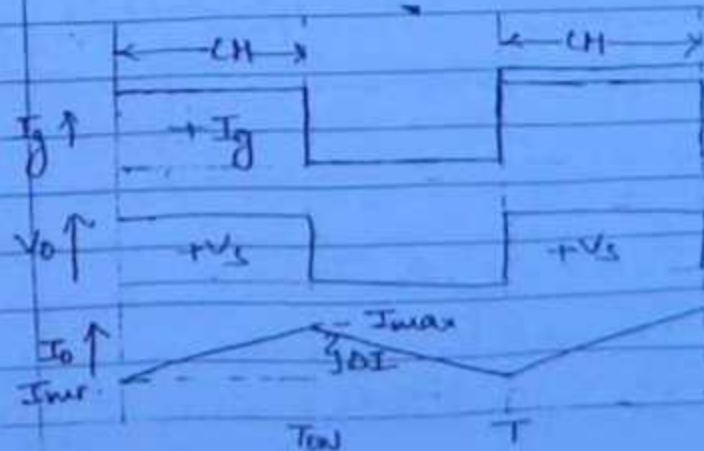

Avg. v/g will not depend on value of L but ripple will depend.

$$I_{\max} = \frac{V_s}{R_a} \left(\frac{1 - e^{-T_{\text{on}}/T_a}}{1 - e^{-T/T_a}} \right) - \frac{E_b}{R_a} \quad (1)$$

where $T_a = \frac{L_a}{R_a} \rightarrow$ w/c time const

(16)

$$I_{\min} = \frac{V_s}{R_a} \left[\frac{e^{-T_{\text{on}}/T_a} - 1}{e^{T/T_a} - 1} \right] - \frac{E_b}{R_a} \quad (2)$$

$$\begin{aligned} \text{Ripple current} = \Delta I_o &= I_{\max} - I_{\min} \\ &= \frac{V_s}{R_a} \left\{ \frac{(e^{T_{\text{on}}/T_a} - 1)}{(e^{T/T_a} - 1)} \left(\frac{e^{T/T_a}}{e^{T_{\text{on}}/T_a}} \right) - \left(\frac{e^{-T_{\text{on}}/T_a} - 1}{e^{T/T_a} - 1} \right) \right\} \\ &= \frac{V_s}{R_a} \left\{ \left(\frac{e^{T/T_a} - 1}{e^{T_{\text{on}}/T_a} - 1} \right) \left(\frac{e^{T_{\text{on}}/T_a} - 1}{e^{T/T_a} - 1} \right) \right\} \\ &= \frac{V_s}{R_a} \left[\frac{(1 - e^{-T_{\text{on}}/T_a})(1 - e^{-T_{\text{off}}/T_a})}{(1 - e^{-T/T_a})} \right] \end{aligned}$$

as α varies, ΔI_o varies.

$$T_{\text{on}} = \alpha T, \quad T_{\text{off}} = (1 - \alpha)T$$

$$\Delta I_o = \frac{V_s}{R_a} \left[\frac{(1 - e^{-\alpha T/T_a})(1 - e^{-(1-\alpha)T/T_a})}{(1 - e^{-T/T_a})} \right]$$

$$\frac{d \Delta I_o}{d \alpha} = 0 \Rightarrow \frac{V_s}{R_a} \left[\frac{(1 - e^{-\alpha T/T_a}) e^{-(1-\alpha)T/T_a} \times \frac{T}{T_a} + (1 - e^{-(1-\alpha)T/T_a}) e^{-\alpha T/T_a} \times \frac{T}{T_a}}{(1 - e^{-T/T_a})^2} \right]$$

$$\begin{aligned} &= \frac{(1 - e^{-\alpha T/T_a}) e^{-(1-\alpha)T/T_a}}{(1 - e^{-T/T_a})^2} - \frac{(1 - e^{-(1-\alpha)T/T_a}) e^{-\alpha T/T_a}}{(1 - e^{-T/T_a})^2} = 0 \\ &= \frac{e^{-(1-\alpha)T/T_a} - e^{-\alpha T/T_a}}{(1 - e^{-T/T_a})^2} \end{aligned}$$

$$\frac{(1 - \alpha)T}{T_a} = \frac{\alpha T}{T_a}$$

$$\alpha = 1 - \alpha \Rightarrow 2\alpha = 1$$

$$\boxed{\alpha = 0.5} \quad \Delta I_{o \max}$$

$$\Delta I_o|_{\max} = \frac{V_s}{R_a} \frac{(1 - e^{-0.5T/T_a})^2}{(1 - e^{-T/T_a})}$$

$$= \frac{V_s}{R_a} \tanh\left(\frac{T}{4T_a}\right) \quad (167)$$

$$\Delta I_o|_{\max} \approx \frac{V_s \times T}{R_a \times 4T_a} = \frac{V_s}{R_a} \times \frac{1}{f \times 4 \times \frac{L_a}{R_a}}$$

$\Delta I_o|_{\max} \approx \frac{V_s}{4fL_a}$

→ at $\alpha = 0.5$

from this Eqⁿ ↓ Ripple current $\propto \frac{1}{\uparrow f L_a \uparrow}$

for $L_a = \infty \Rightarrow \Delta I_o|_{\max} = 0$

i.e. for Highly inductive load → Const current.

for High frequency → Ripple will ↓ ∴ Chopper is being operated at very high frequency i.e. in range of KHz.

⇒ At very high switching frequency we can reduce the ripple in the current without ↑ size of filter. SMPS operates on the same chopper principle.

Reasons for Discont. conduction


Rectifier	Chopper
↑ α → firing angle.	↓ α → Duty cycle
↓ L	↓ L
↓ I_o	↓ I_o

[Signature]

RLE load $\rightarrow$ Discontinuous conduction

(168)

$T_n \rightarrow$ Extinction Time

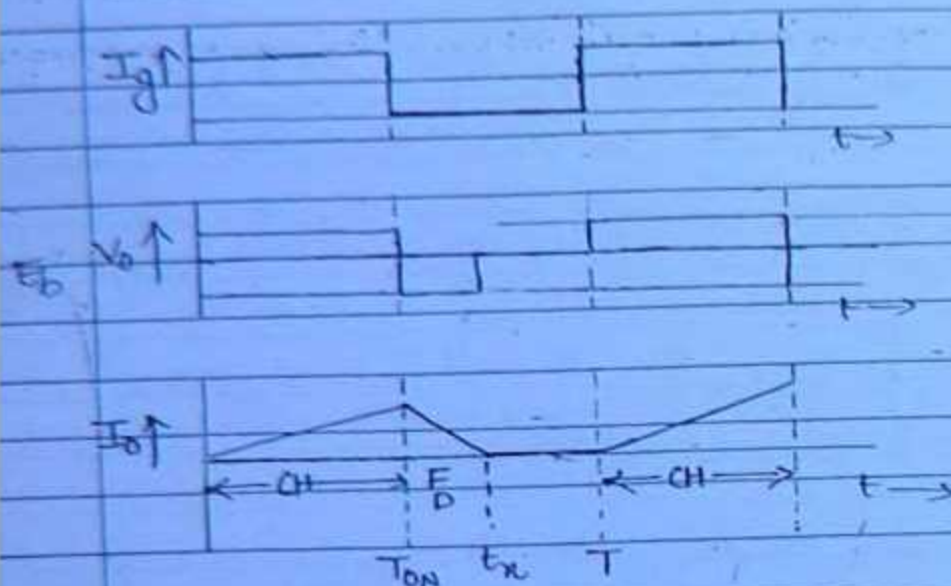

$$V_o = V_s \left(\frac{T_{on}}{T} \right) + E_b \left(\frac{T - t_n}{T} \right)$$

$$\Delta V_o = \alpha V_s + E_b \left(1 - \frac{t_n}{T} \right)$$

Duty cycle limit for continuous conduction :-

Let α' be the duty cycle at the boundary b/w continuous & discontinuous conduction.

at $t = T$, $I_{min} = 0$



$$I_{min} = \frac{V_s}{R} \left(\frac{e^{T_{on}/\tau_a} - 1}{e^{T/\tau_a} - 1} \right) - \frac{E_b}{R_a} = 0$$

$$\frac{e^{T_{on}/\tau_a} - 1}{e^{T/\tau_a} - 1} = \frac{E_b}{V_s}$$

at boundary, $e^{T_{on}/\tau_a} - 1 = \frac{E_b}{V_s} (e^{T/\tau_a} - 1)$

$$e^{T_{on}'/T_a} = \frac{E_b}{V_c} (e^{T/T_a} - 1) + 1 \quad (769)$$

$$T_{on}' = T_a \ln \left[\frac{E_b}{V_c} (e^{T/T_a} - 1) + 1 \right]$$


$$\alpha' = \frac{T_{on}'}{T} = \frac{T_a}{T} \ln \left[\frac{E_b}{V_c} (e^{T/T_a} - 1) + 1 \right]$$

$\alpha < \alpha' \longrightarrow$ Discontinuous conduction.

$\alpha > \alpha' \longrightarrow$ Continuous conduction.

Step-down chopper $\longrightarrow$ with filter
Buck Regulator

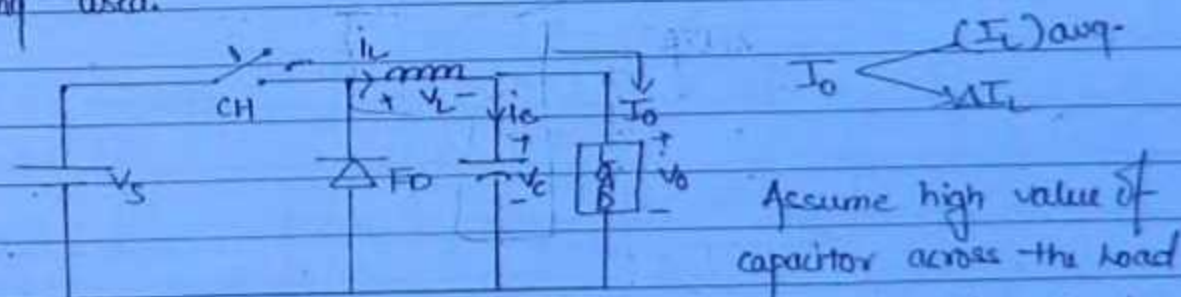In the step-down chopper, we could $\downarrow$ the ripple in current by $\uparrow L$ or f but Ripple in v_L was unaffected $\therefore$ to reduce Ripple in v_L , step-down chopper with filter is being used.




Assume high value of capacitor across the load

which maintains almost const v_L across the load.

$$(I_L)_{avg} \rightarrow \text{DC component} = I_o$$

$$\Delta I_L = \Delta I_c$$

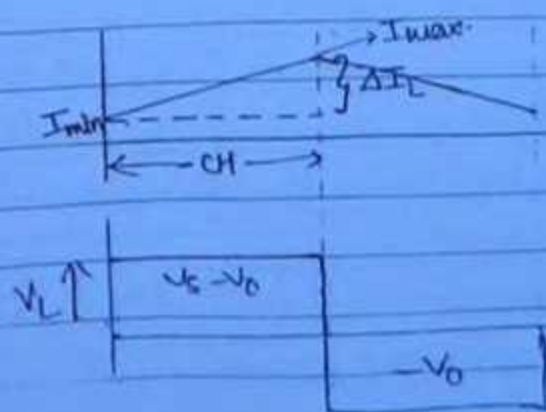

$$0 < t < T_{ON}$$

$$CH \rightarrow ON$$

$$-V_s + V_L + V_o = 0$$

$$V_L = V_s - V_o$$

$$L \frac{dI_L}{dt} = V_s - V_o$$

$$dI_L = \frac{V_s - V_o}{L} dt$$

$$\int_{I_{min}}^{I_{max}} dI_L = \frac{V_s - V_o}{L} \int_0^{T_{ON}} dt$$

$$(I_{max} - I_{min}) = \frac{(V_s - V_o) T_{ON}}{L}$$

$$\Delta I_L = \left(\frac{V_s - V_o}{L} \right) T_{ON}$$

$$= \frac{V_s (1 - \alpha) T_{ON}}{L}$$

$$\boxed{\Delta I_L = \frac{V_s (1 - \alpha) \alpha}{fL}}$$

$$\Delta I_L \propto \frac{1}{fL}$$

$$\frac{d\Delta I_L}{d\alpha} = \frac{V_s}{fL} (1 - 2\alpha) = 0$$

$$\alpha = 0.5 \text{ for } \Delta I_L|_{max}$$

$$\Delta I_L|_{max} = \frac{V_s}{4fL}$$

$$\boxed{I_s = I_{CH}}$$

$$II \quad T_{ON} < t < T$$

$$CH \rightarrow off, FD \rightarrow ON$$

$$+V_L + V_o = 0$$

$$\therefore V_L = -V_o$$

$$(V_L)_{avg} = 0$$

$$\text{Ar. of } (+ve \text{ spike}) = \text{Ar. of } (-ve \text{ spike})$$

$$(V_s - V_o) T_{ON} = V_o T_{OFF}$$

$$V_o (T_{OFF} + T_{ON}) = V_s T_{ON}$$

$$V_o T = V_s T_{ON}$$

$$V_o = \frac{V_s T_{ON}}{T}$$

$$\boxed{V_o = \alpha V_s}$$

Assuming No loss in chopper
I/p power = o/p power

$$V_o I_o = V_s I_s$$

$$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \alpha$$

CHOPPER works as DC transformer.


$$I_s = \alpha I_o$$

$$I_o = \frac{I_s}{\alpha}$$

$$\boxed{(I_{FD})_{avg} = (1 - \alpha) I_o}$$

Ripple in capacitor voltage ($\Delta V_c = \Delta V_o$)

(171)

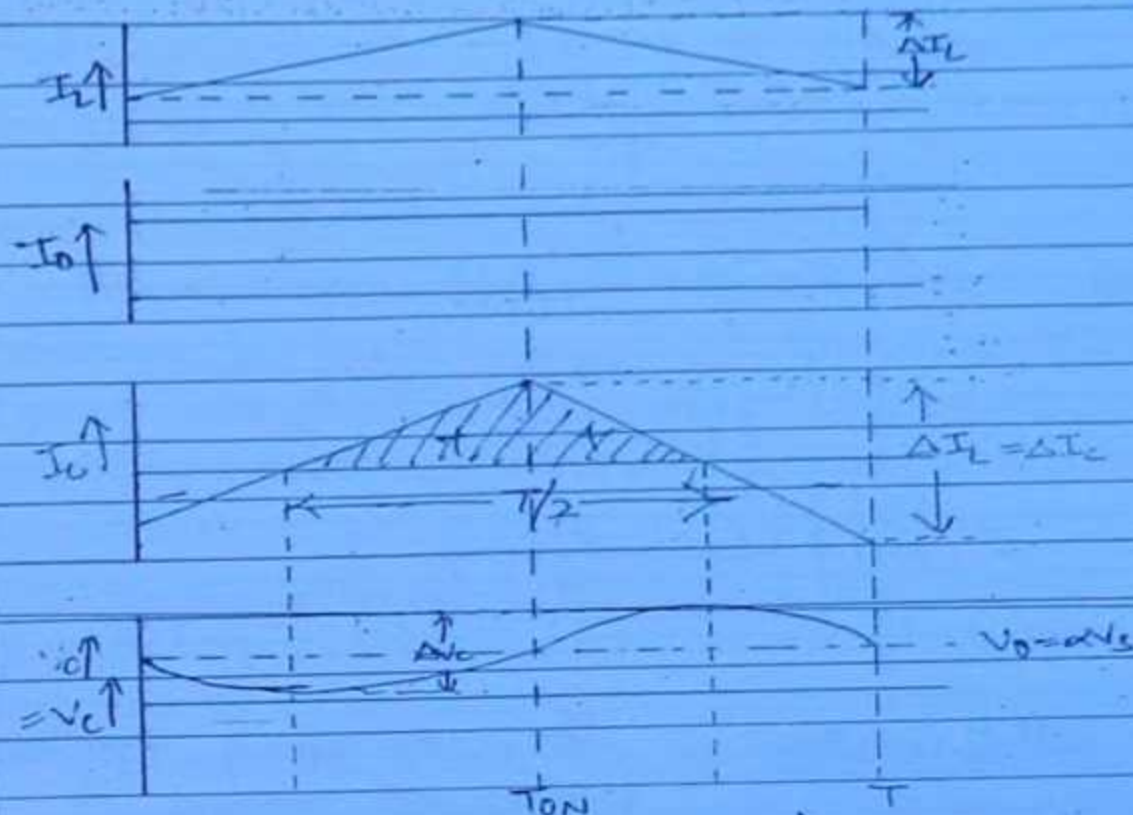

$$\Delta Q = C \Delta V_c \Rightarrow \Delta Q = \frac{\Delta I_L \times \frac{1}{2} \times \frac{T}{2}}{2} = \frac{\Delta I_L T}{8}$$

$$\Delta V_c = \frac{\Delta I_L}{8fC}$$

$$\Delta V_c \propto \frac{1}{fC}$$

$$\Delta V_c = \frac{\alpha(1-\alpha)V_s}{8f^2LC}$$

$$\Delta V_c|_{\max} \text{ at } \alpha=0.5 = \frac{V_s}{32f^2LC}$$

Critical Inductance :- It is the value of inductance at which the inductor current waveform is just continuous.

Symbol $\rightarrow L_c$

At the boundary b/w continuous & discontinuous conduction of I_c

$$I_0 = \frac{\Delta I_c}{2} = (I_c)_{avg}$$

(172)

$$I_0 = \frac{\alpha(1-\alpha)V_s}{2fL_c}$$

or

$$L_c = \frac{1}{2fI_0} \alpha(1-\alpha)V_s$$

$$L_c = \frac{1}{2f} \frac{\alpha V_s / R}{\alpha(1-\alpha)V_s} = \dots$$

$$L_c = \frac{(1-\alpha)R}{2f}$$

Critical Capacitance :- It is the value of capacitance at the boundary b/w continuous & discontinuous conduction for the capacitor v/g waveform.

At the boundary :- $V_0 = \frac{\Delta V_c}{2} = (V_c)_{avg}$

$$V_0 = \frac{\alpha(1-\alpha)V_s \times 1}{8f^2 L_c C_c} \times 2$$

$$\alpha V_s = \frac{\alpha(1-\alpha)V_s}{8f^2 L_c C_c} \times \frac{1}{2}$$

$$C_c = \frac{(1-\alpha)}{16f^2 L_c}$$

$\alpha = 0.5, \Delta I_c = 1.6, I_0 = 5A$


$$(I_L)_{\max} = (I_L)_{\min}$$

(173)

$$(I_L)_{\max} = I_{Lr} + \frac{\Delta I_L}{2}$$

$$= \frac{1.6}{2} + 5 = 5.8 \text{ Amp}$$

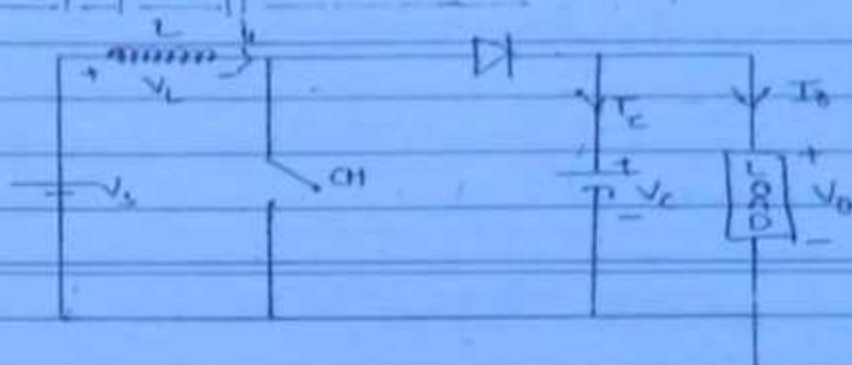3. Step-up chopper ($V_o > V_s$) (with filter) — Boost Regulator



(I) $0 \leq t \leq T_{on} \rightarrow I_c = -I_o$

CH $\rightarrow$ ON, D $\rightarrow$ OFF


$$V_L = V_s$$

$$L \frac{dI_L}{dt} = V_s$$

$$\int_{I_{\min}}^{I_{\max}} dt = \frac{V_s}{L} \int_0^{T_{on}} t$$

$$\Delta I_L = \frac{V_s}{L} T_{on}$$


$$\boxed{\Delta I_L = \frac{V_s}{fL}}$$

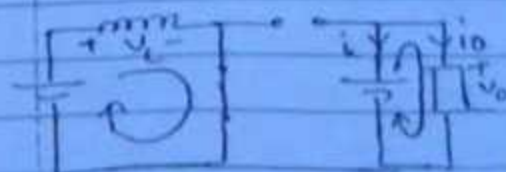

$$I_c = -I_o$$

II $T_{on} \leq t \leq T$

CH $\rightarrow$ OFF, D $\rightarrow$ ON

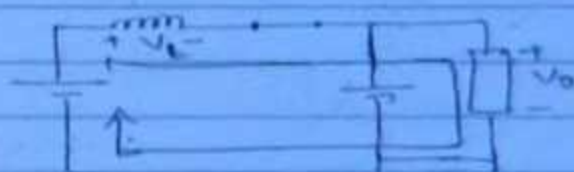

$$V_s = V_L + V_o$$

$$V_L = V_s - V_o = -(V_o - V_s)$$


Since it is step-up chopper,

$$V_o > V_s \Rightarrow V_L \rightarrow \text{+ve}$$

L is releasing energy

$$I_L = I_c + I_o$$

$$I_c = I_L - I_o$$

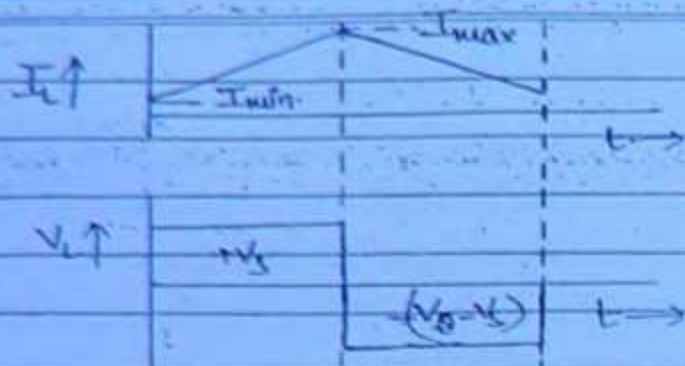

$$(V_C)_{avg} = 0$$

(124)

$$V_s T_{on} - (V_o - V_s) T_{off} = 0$$

$$V_s (T_{on} + T_{off}) = T_{off} V_o$$


$$V_s T = V_o T_{off}$$

$$V_s T = (1 - \alpha) V_o T_{off}$$

$$V_o = \frac{V_s}{1 - \alpha}$$

$$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \frac{1}{1 - \alpha}$$

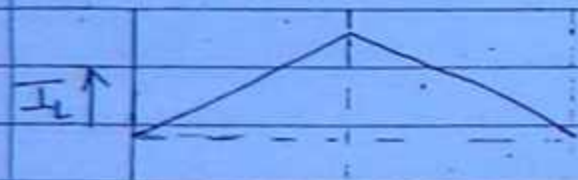Step in capacitor voltage :- $(\Delta V_C = \Delta V_o)$





$$\Delta V_C = \frac{\Delta Q}{C}$$

$$\Delta V_C = \frac{I_o T_{on}}{C}$$

I_o

$$\Delta V_C = \frac{\alpha I_o}{f_c}$$

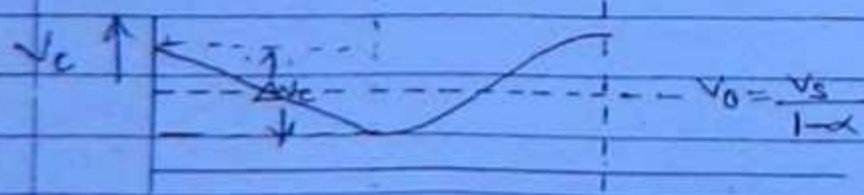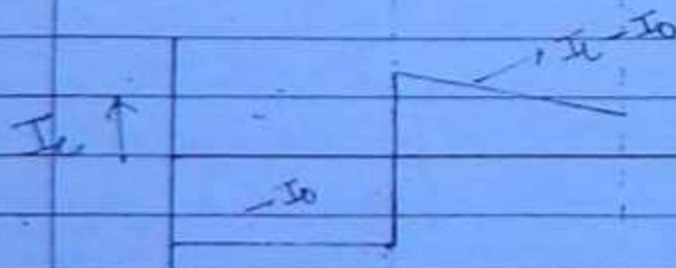

Critical Inductance (L_c):-

At the boundary condⁿ of I_L

$$I_0 = \frac{\Delta I_L}{2} = (I_L)_{av.}$$

(125)

$$\frac{V_s}{R(1-\alpha)} = \frac{\alpha V_c}{2fL_c}$$

$$L_c = \frac{R(1-\alpha)\alpha}{2f}$$

Critical Capacitance (C_c):-


At the boundary condⁿ of V_c waveform:

$$V_0 = \frac{\Delta V_c}{2} = (V_c)_{av.}$$

$$I_0 R = \frac{\alpha I_0}{2fC_c}$$

$$C_c = \frac{\alpha}{2fR}$$

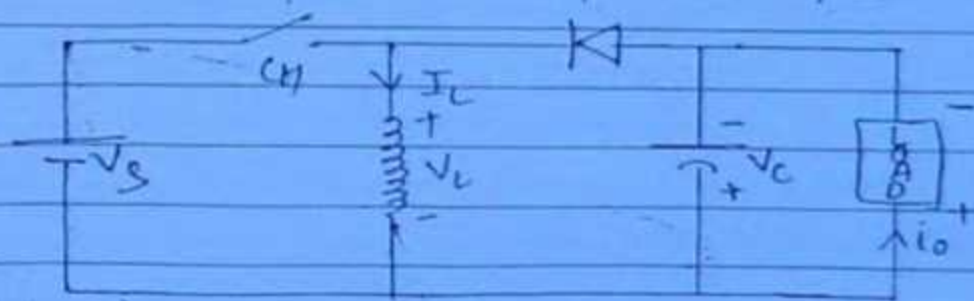
Buck-Boost Regulator (Step up / Step down chopper)



$\alpha > 0.5 \rightarrow$ step up
 $\alpha < 0.5 \rightarrow$ step down

Mode-I $0 \leq t < T_{on}$

Same as step-up chopper

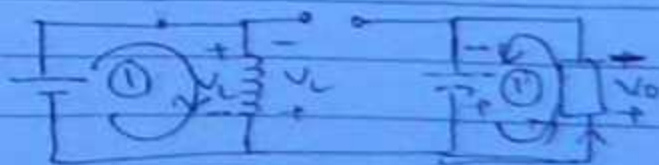

$$V_s = V_L$$


$$L \frac{di}{dt} = V_s$$

$$\int_{I_{min}}^{I_{max}} di = \frac{V_s}{L} \int_0^{T_{on}} dt$$

$$\Delta I_L = \frac{V_s T_{on}}{L}$$

$$\Delta I_L = \frac{\alpha V_s}{fL}$$

$$I_c = -I_o$$

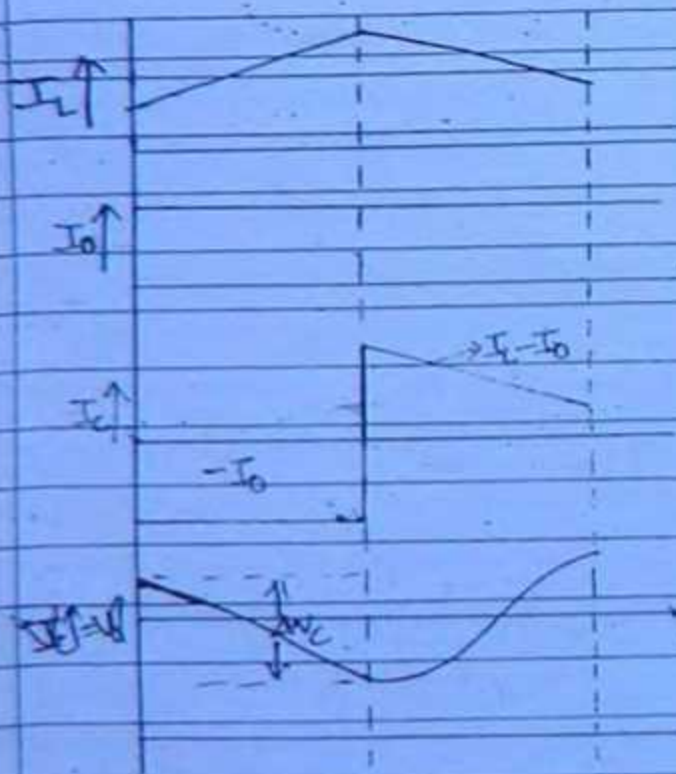

Mode-2 CH-OFF, D-ON $T_{on} \leq t \leq T$



$$+V_L + V_o = 0$$

$$\therefore V_L = -V_o$$

$$I_L = I_c + I_o$$

$$I_c = I_L - I_o$$

$$(\frac{dI_L}{dt})_{avg} = 0$$

$$V_s T_{on} - V_o T_{off} = 0$$

$$V_s T_{on} = V_o T_{off}$$

$$V_s \alpha T = V_o (1-\alpha) T$$

$$V_o = \frac{V_s \alpha}{1-\alpha}$$

$$\frac{V_o}{V_s} = \frac{I_c}{I_o} = \frac{\alpha}{1-\alpha}$$

$$\Delta V_L = \frac{\Delta Q}{C}$$

$$= \frac{I_o T_{on}}{C} = \frac{\alpha I_o}{fC}$$

Critical Inductance (L_c):-

$$I_o = \frac{\Delta I_L}{2}$$

$$\frac{\alpha V_s}{(1-\alpha)R} = \frac{\alpha V_s}{2fL_c}$$

$$L_c = \frac{(1-\alpha)R}{2f}$$

Critical Capacitance :-

$$V_o = \frac{\Delta V_c}{2}$$


(177)

$$\frac{\alpha V_s}{1-\alpha} = \frac{\alpha I_o}{2+C_c} = I_o R$$

$$C_c = \frac{\alpha}{2+R}$$

Classification of chopper based on quadrant operation

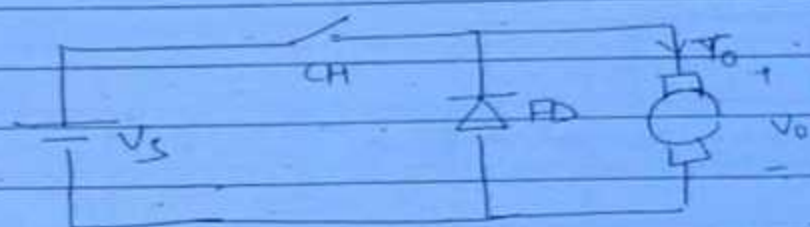I First quadrant chopper (Type A) - (Stepdown chopper)




(I) CH $\rightarrow$ ON, $V_o = V_s$

$\therefore V_o$ & I_o are E_b & I_a respectively

II CH $\rightarrow$ OFF

D $\rightarrow$ ON

V_o (Fwd)

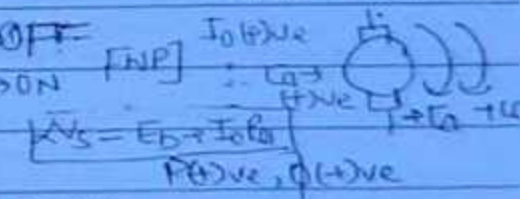


I_o (Fwd)

Second quadrant operation (Type B Chopper)

Regenerative Braking of Dc Motor :-


(17.8)

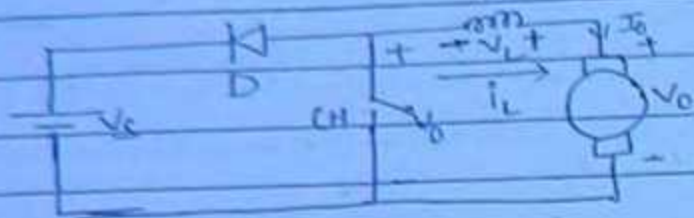

Assume that m/c is operating at rated speed b/t $T=0$ seconds

Mech Energy $= \frac{1}{2} J \omega^2 \rightarrow$ Brake Energy

$$I_0 = \frac{V_0 - E_b}{R_a}$$

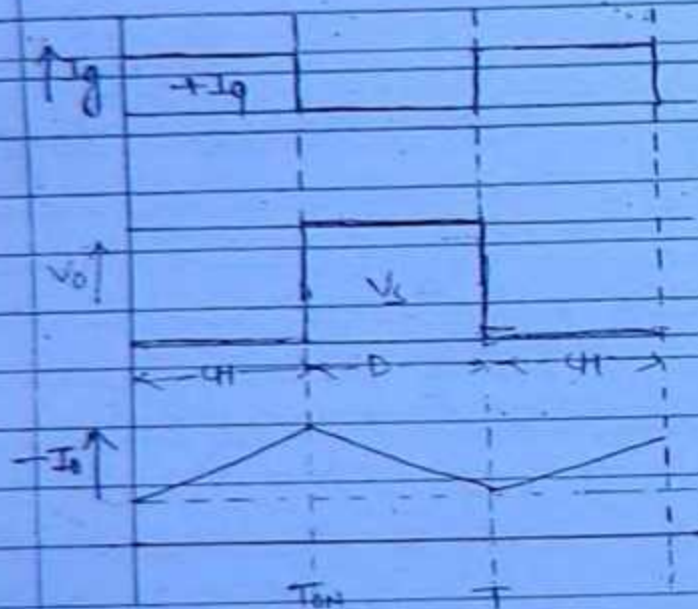


Mode-I

CH $\rightarrow$ ON, D $\rightarrow$ off


$0 < t < T_{on}$

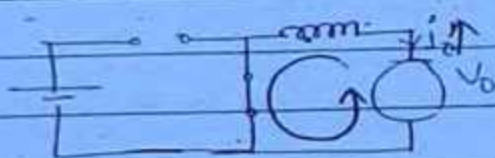$\therefore I_0 < 0$, $\therefore I_a \rightarrow \phi I_0$
 $t > 0$



$$\frac{1}{2} J \omega^2 \rightarrow \frac{1}{2} L I_a^2$$

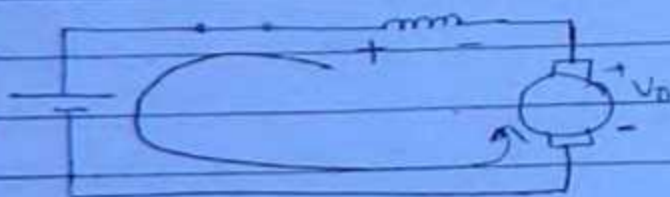
Mode-II, $T_{on} \leq t \leq T$, CH $\rightarrow$ OFF, D $\rightarrow$ ON



$$V_0 = V_s$$

$$\frac{1}{2} L I_a^2 \rightarrow \text{source}$$

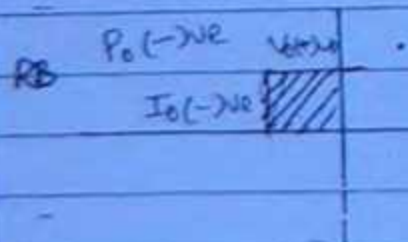Brake Energy to source
 Regenerative Braking




$$V_0 = V_s (T_{off}/T) = (1-\alpha) V_s$$

$$\begin{aligned} \text{Regenerated power} &= V_0 I_0 \\ &= V_s (1-\alpha) \cdot I_0 \end{aligned}$$

III → Two quadrant operation (Type C Chopper)

(179)

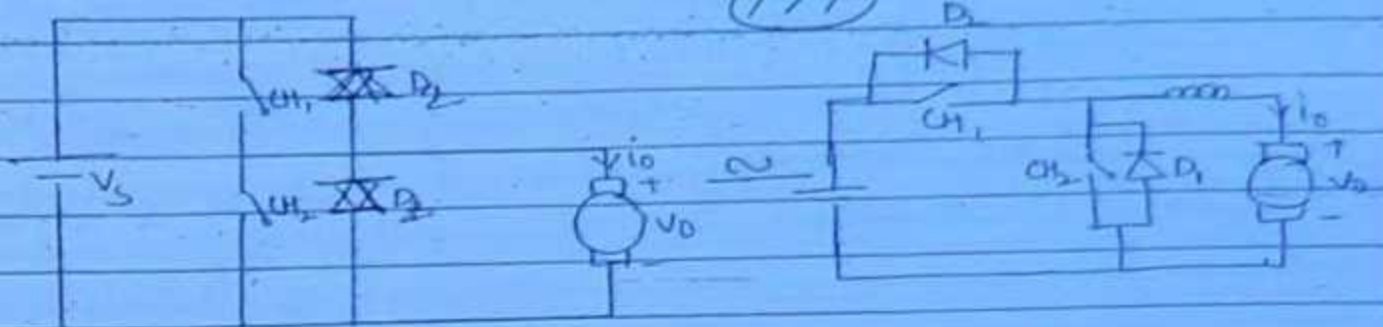

I $CH_1 \rightarrow ON$

$I_o \rightarrow +ve$, $E_a \rightarrow +ve$


$\frac{1}{2} I_o^2 R \rightarrow \frac{1}{2} L i^2$

II $CH_1 \rightarrow OFF$

$D_2 \rightarrow ON$

$\frac{1}{2} L i^2 \rightarrow \text{source}$

(RB)

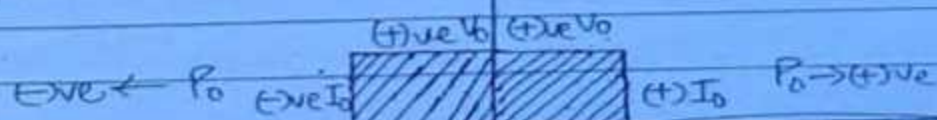


I $CH_1 \rightarrow ON$, $D_2 \rightarrow OFF$

$I_o \rightarrow +ve$, $V_o \rightarrow +ve$, $E_b \rightarrow +ve$, $T_a \rightarrow +ve$, active

II $CH_1 \rightarrow OFF$


$D_2 \rightarrow ON$ (FWD)

$V_o = E_b + I_o R_a$

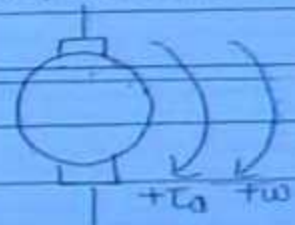

(FM)

IV → Four quadrant Chopper (Type-D)

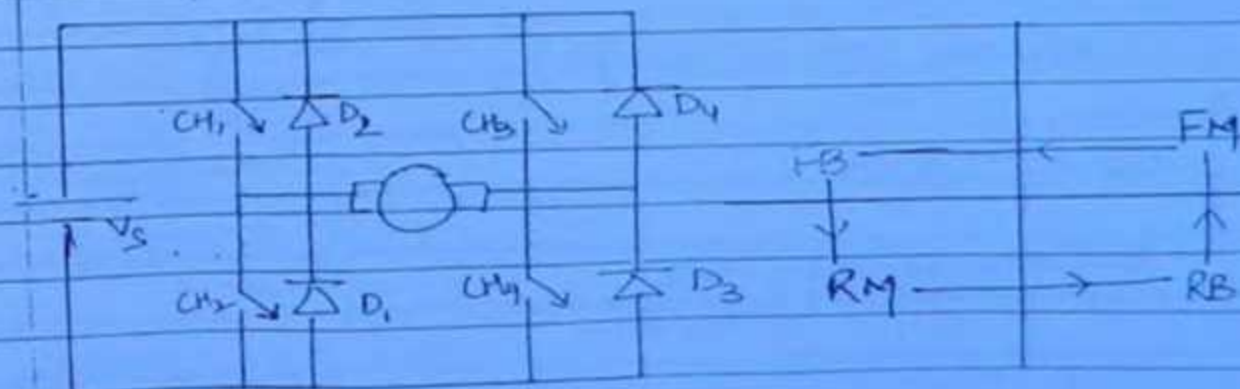

Ques 17

B-φ semi-converter

$$I_a \neq 0 \Rightarrow I_o \neq 0$$

$$I_o(\omega t) = 0$$

$$\text{at } \omega t = \pi, I_o(\omega t) = 0$$

i.e. it is discontinuous conduction.

During discontinuity,

$$\text{Load voltage} = \text{Back Emf}$$

$$18 \quad R_{\text{load}} = 100 \Omega, I_{\text{LD}} = 1 \text{mA}$$

Prp. $\rightarrow$ measure Av. value $\therefore$

It will measure DC vol only.

$$V_{do} = \frac{2V_m}{\pi} = I_f(100 + R_s)$$

$$\frac{2 \times 100\sqrt{2}}{\pi} = 10^3(100 + R_s)$$

$$R_s = 89.9 \text{ K}\Omega$$

19

$\alpha > 90^\circ \rightarrow$ Inversion mode

$$P_{AC} \leftarrow P_{DC}$$

$$V_o = -E + I_o R_s \quad \text{--- (1)}$$

$$\Delta V_{do} = 4f L_c I_o$$

$$V_o = V_{do} \cos \alpha - 4f L_c I_o$$

$$\frac{2V_o}{\pi} = \frac{2V_m}{\pi}$$

$$= \frac{2 \times 120\sqrt{2}}{\pi}$$

$$V_o = \frac{240\sqrt{2}}{\pi} \cos 110^\circ - \frac{4 \times 20 \times 10^{-3} \times I_o}{200}$$

$$-90 + I_o \times \frac{240\sqrt{2}}{\pi} \cos 110^\circ$$

$$I_o(1.2) = \frac{240\sqrt{2}}{\pi} \cos 110^\circ + 90$$

$$I_o = 85.87 \text{ A}$$

$$\Delta V_{do} = \frac{V_{do}}{2} [\cos(\alpha - \omega t) - \cos(\alpha + \omega t)] = 4f L_c I_o$$

$$\alpha = 8.35^\circ$$

$$\text{Rectification Efficiency} = \frac{V_o I_o}{V_{ar} I_{or}}$$

$$= 55.05 \%$$

20

Pulse No $\uparrow$ THD $\downarrow$

L filter, smoothing of waveform $\uparrow$
THD $\downarrow$

C filter, VRF $\downarrow$
but THD $\uparrow$

21

$$V_o = 50\% (V_o)_{\text{max}}$$

$(V_o)_{\text{max}}$ when $\alpha = 0^\circ$

$$(V_o)_{\text{max}} = V_{do} = \frac{2V_m}{\pi}$$

$$V_o = \frac{1}{2} \left[\frac{2V_m}{\pi} \right] (1 + \cos \alpha) \text{ rms}$$

$$V_o = V_{do} (1 + \cos \alpha)$$

$$\frac{1}{2} \left[\frac{2V_m}{\pi} \right] = \frac{2V_m}{\pi} (1 + \cos \alpha)$$

$$\frac{V_m}{\pi} - \frac{\sqrt{2} V_m}{2} = 1 = \cos(\alpha + 30^\circ)$$

$$\alpha = 61.7^\circ$$

$$I_o = \frac{V_o}{R} = 7.17 \text{ Amp.}$$

$$I_{or} = \frac{V_{or}}{R} = 10.48 \text{ Amp.}$$

$$\alpha_{max} = 180^\circ - (\omega t_q + \mu_0)$$

$\mu_0 \rightarrow$ overlap $\angle$ at $\alpha=0^\circ$

$$V_o = E_b + I_o R_a$$

$$V_o = V_m \cos \alpha - 3 f L_s I_o$$

$$E_b + I_o R_a = V_m \cos \alpha - 3 f L_s I_o$$

$$I_o = \frac{V_m \cos \alpha - E_b}{R_a + 3 f L_s}$$

$$V_{do} = \frac{3 V_m}{2\pi} = 202.5 \text{ V}$$

$$I_o = 14.77 \text{ A}$$

$$\frac{V_m (\cos \alpha - \cos(\alpha + \mu))}{2} = 3 f L_s I_o$$

$$\mu \big|_{\alpha=0^\circ} = 17^\circ$$

$$\omega t_q = \frac{2\pi f \cdot 250 \times 10^{-6} \cdot 180}{\pi} = 4.5^\circ$$

$$\alpha_{max} = 180 - 4.5 - 17^\circ = 158.5^\circ$$

$$\text{at } \alpha=0^\circ = \mu = 20^\circ$$

(781)

$$\frac{I_o}{I_{op}} = (\cos \alpha - \cos(\alpha + \mu))$$

$$I_{op} = 0.134$$

$$\text{at } \alpha=20^\circ$$

$$0.134 = \cos 20^\circ - \cos(20^\circ + \mu)$$

$$\mu = 12.94^\circ$$



$$\text{at } \alpha=60^\circ$$

$$0.134 = \cos 60^\circ - \cos(60^\circ + \mu)$$


$$\mu = 8.53^\circ$$

Choppers :-

1.

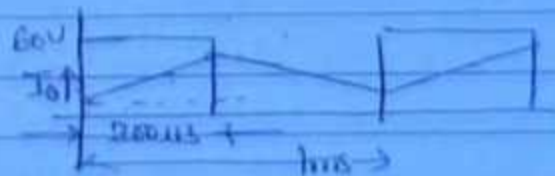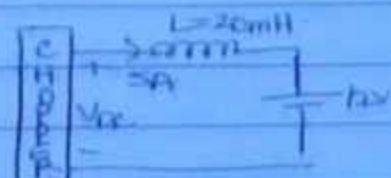
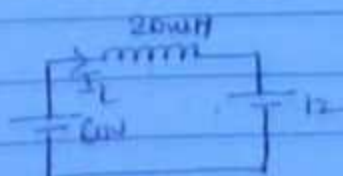
$$G_1 \rightarrow 60 \text{ V}, V_{dc} = 60 \text{ V}$$



$$60 - 12 = L \frac{di}{dt}$$

$$\Delta I_L = \frac{48}{20 \times 10^{-3}} \times T_{on}$$

$$\Delta I_L = \frac{48}{20 \times 10^{-3}} \times 200 \times 10^{-6}$$

$$= 480 \times 10^{-3} = 0.48 \text{ A}$$

$$V_s = 100V$$

$$\alpha = 0.8$$

$$(I_{FD}) = I_0 \frac{(T_{on})}{T}$$

$$= I_0 (1 - \alpha)$$

$$I_0 = \frac{\alpha V_s}{R}$$

$$= \frac{0.8 \times 100}{10} = 8$$

$$(I_{FD})_{av} = 8(1 - 0.8)$$

$$= 1.6A$$

3 CASS-D Commutation $\rightarrow$ v/q commutation

$$(T_{on})_{min} \text{ of chopper} = \pi \sqrt{LC}$$

$$= 140 \mu s$$

$$V_0 = V_s \left[\frac{T_{on} + 2t_{cm}}{T} \right]$$

$$(V_0)_{min} = 250 \left[\frac{140 \times 10^{-6} + 2t_{cm}}{T} \right] \times 10^3$$

$$t_{cm} = \frac{CV_s}{I_0} = \frac{10^{-6} \times 250}{10}$$

$$= 25 \times 10^{-6}$$

$$(V_0)_{min} = 47.5V$$

$$(I_{TM})_{peak} = I_0 + V_s \sqrt{\frac{C}{L}} = 10 + 250 \sqrt{\frac{10^{-6}}{10^{-3}}} = 10 + 250 \times 10^{-2} = 12A$$

$$(I_{TA})_{peak} = I_0 = 10A$$

Step-down Chopper $\rightarrow \alpha = 0.5$

$$I_0 = \frac{\alpha V_s}{R} = \frac{0.5 \times 60}{3} = 10A$$

Δv value will not depend on Inductance.

$$T_{on}' = T_A \ln \left[1 + \frac{I_0}{V_s} (e^{T/T_A} - 1) \right]$$

$$T_A = \frac{L}{R} = \frac{10^{-3}}{0.25} = 4 \times 10^{-3}$$

$$\frac{T}{T_A} = \frac{2.5 \times 10^{-3}}{4 \times 10^{-3}} = 0.625$$

$$T_{on}' = 332.5 \mu \text{ sec}$$

$$\underline{9} \quad \alpha = \frac{1}{5} \Rightarrow VRF = \sqrt{\frac{1}{\alpha} - 1} = \sqrt{5 - 1} = 2$$

183

$$T_{min} = \pi \sqrt{LC}$$

$$t_{max} = \pi \sqrt{LC} + \sqrt{LC} \sin^{-1} \left(\frac{I_0}{I_p} \right)$$

$$I_p = \frac{V_s \sqrt{C}}{\sqrt{L}} = \frac{230 \times \sqrt{10 \times 10^{-6}}}{\sqrt{25.29 \times 10^{-6}}} = 144.66$$

$$t_{max} \approx 75 \mu s$$

$$t_{min} = 50 \mu s$$

$$\underline{4} \quad L = 64 \mu H$$

$$(I_m)_{peak} = I_0 + \frac{V_s \sqrt{C}}{\sqrt{L}} = 70.7 + \frac{200 \sqrt{64 \times 10^{-6}}}{\sqrt{16 \times 10^{-6}}} = 170.7 A$$

$$\underline{1} \quad c) \quad t_{cm} = \frac{C V_s}{I_0} = \frac{50 \times 10^{-6} \times 220}{80} = 137.5 \mu sec$$


$$t_{ca} = \frac{\pi \sqrt{LC}}{2} = \frac{\pi \sqrt{20 \times 50} \times 10^{-6}}{2} = 49.67 \mu sec$$

$$a) \quad T_{on|effective} = T_{on} + 2t_{cm} = 800 + 2 \times 137.5 = 1075 \mu s$$

$$(I_{Im})_p = I_0 + \frac{V_s \sqrt{C}}{\sqrt{L}} = 427.85 \text{ Amp}$$

$$(I_{IA})_p = I_0 = 8 \text{ Amp}$$
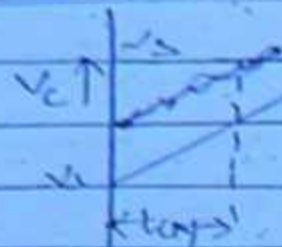
$$\text{Total Commutation Interval} = 2t_{cm} = 2 \times 137.5 = 275 \mu s$$



184



$$V_c = \frac{V_s}{t_{\text{avg}}} \cdot t = V_s \Rightarrow V_c = \frac{220}{137.5} \cdot 150 = 20V$$

AC VOLTAGE CONTROLLERS

(185)

fixed AC $\rightarrow$ variable AC (V_o , f_o)

I Phase Control Technique -

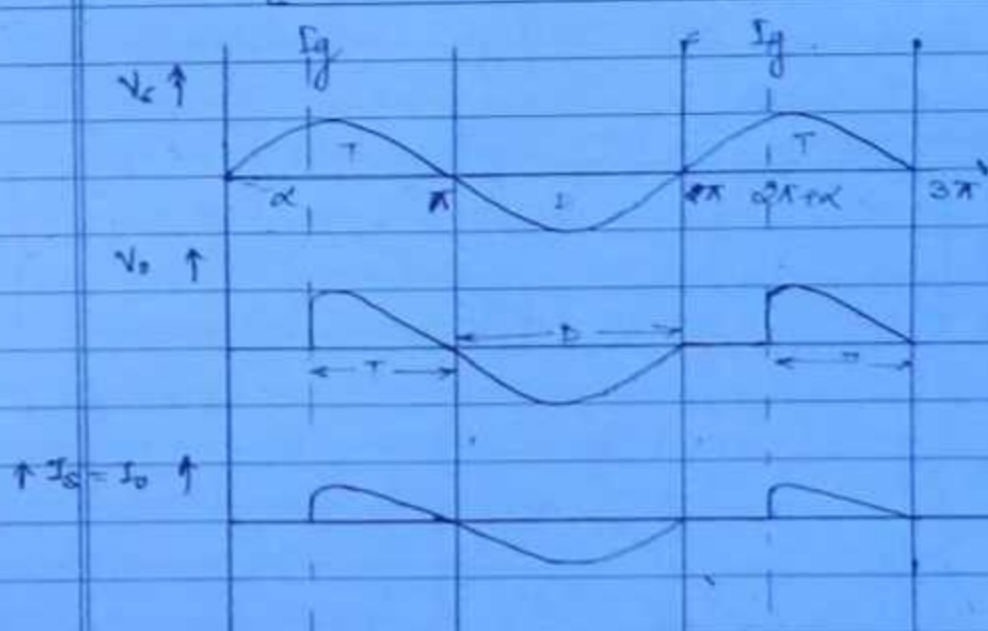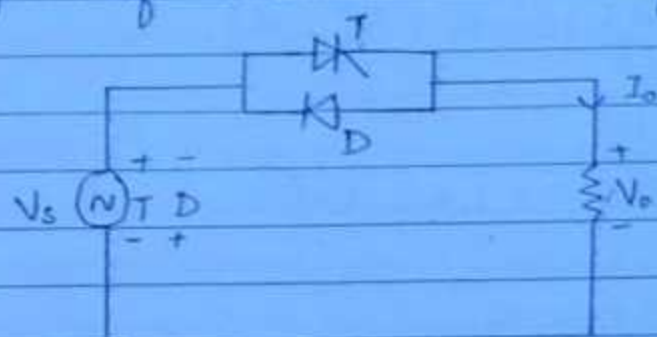a) 1- ϕ Half Controlled AC Voltage Controllers -

$$V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t) = \frac{V_m}{2\pi} (\cos \alpha - 1)$$

$$(I_s)_{avg} = I_o = \frac{V_m}{2\pi R} (\cos \alpha - 1)$$

DC component

Drawback -

Source current contains DC component & saturates the supply transformer core.

(186)



$$V_{or} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\pi+\alpha} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$PF = \frac{V_{or}}{V_{an}} = \frac{1}{\sqrt{2}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

(b) 1- ϕ Full Controlled AC Voltage Controller -

1. R Load

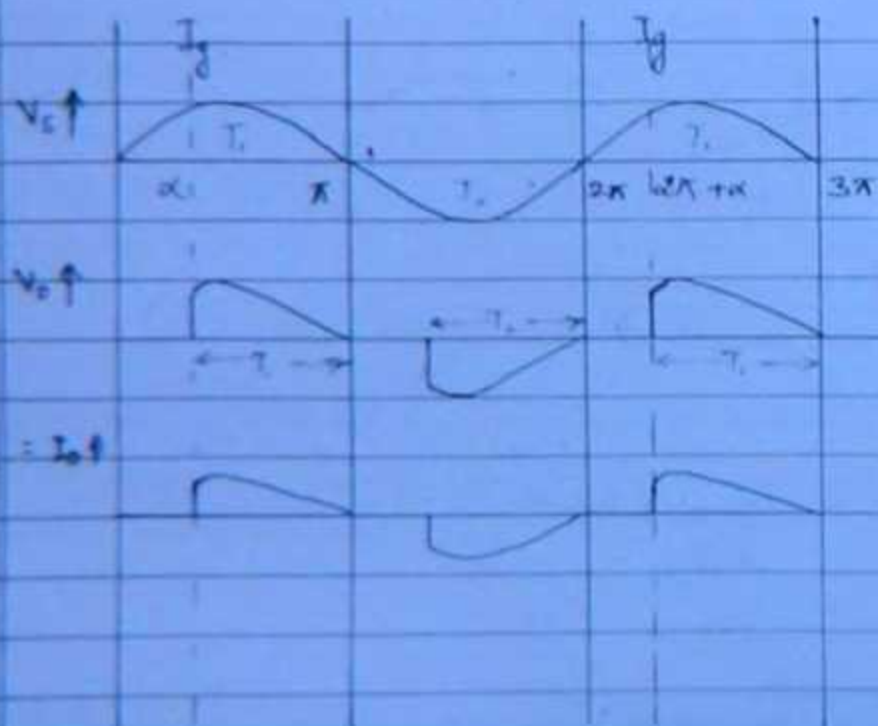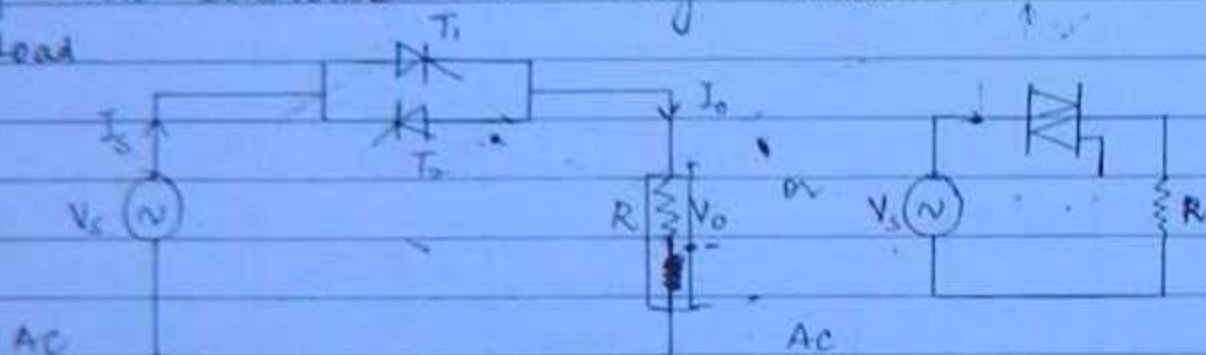



2. RL load.

After reaching steady state I_o lags V_o by $\phi = \tan^{-1} \frac{\omega L}{R}$

(I) $\alpha > \phi$, V_o is controlled

(II) $\alpha \leq \phi$, V_o is uncontrolled

(187)

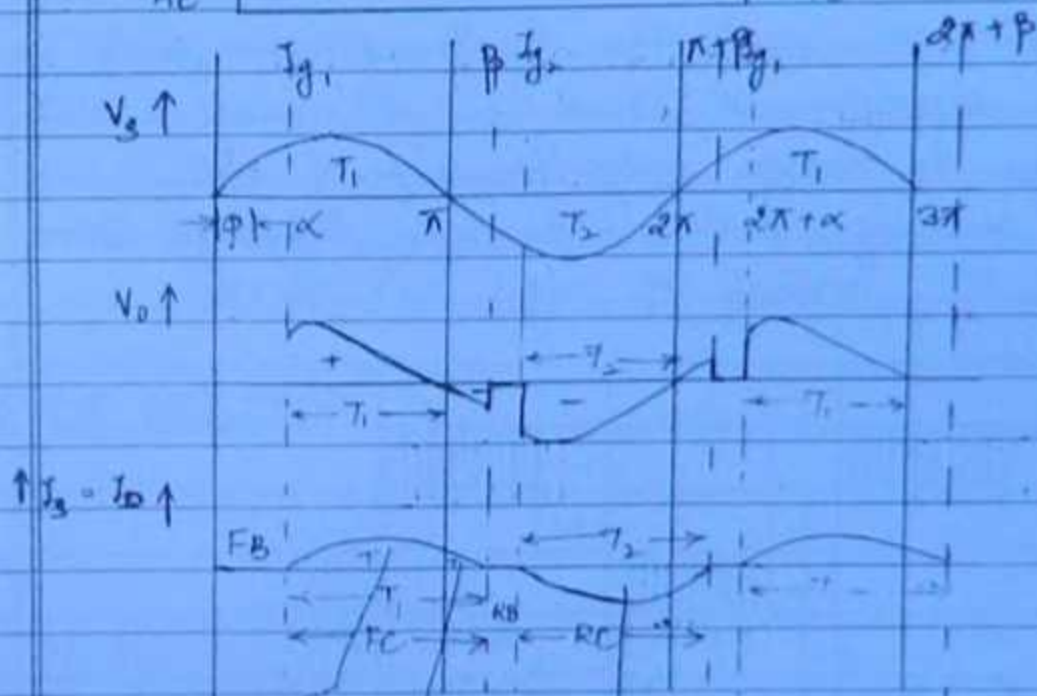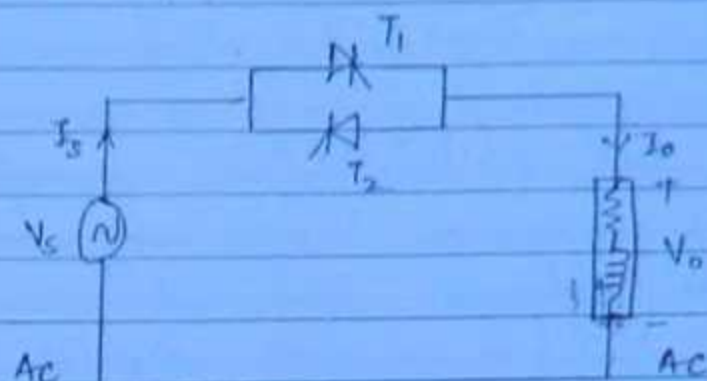

$P(+)$
power flows
from source to
load

(I) $\alpha > \phi$ V_o is controlled $\rightarrow$ (By α o/p vlg can be control)

$P(+)$
power again flows
from source to
load

$P(-)$
load $\rightarrow$ source (Inductor changes ϕ from ϕ)

$$V_{or} = \left\{ \frac{1}{\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t d(\omega t) \right\}^{1/2}$$

158

$$V_{or} = \frac{V_m}{\sqrt{2}\pi} \left[(\beta - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right]^{1/2}$$

II $\phi > \alpha$

$L \uparrow \quad T \uparrow \quad \beta \uparrow \quad (\beta > \pi + \alpha)$


$$\tan \phi = \frac{\omega L}{R}$$

continuous conduction of V_o occurs as β approaches $\pi + \alpha$

Only 2 modes available FC & RC

No blocking mode (SCRs are short circuited)

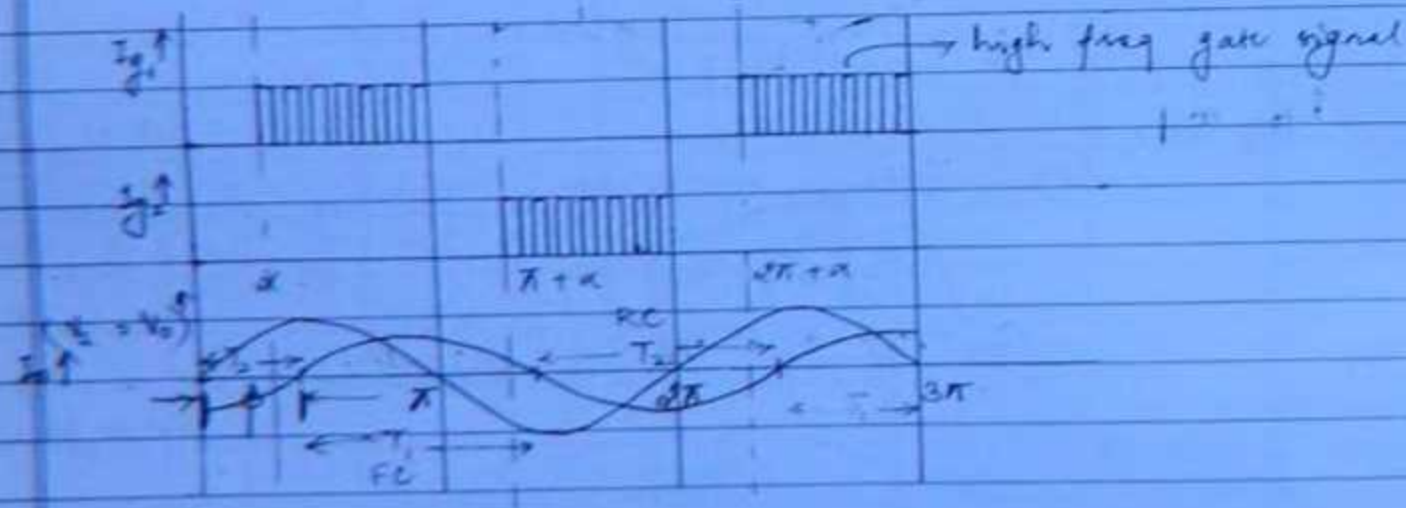$\therefore$ No control of $v_{gs} \therefore V_o = V_s$



When T_1 stops conducting, but there is no gate signal for T_2 (fig), T_2 fails to turn-on & it behaves as a rectifier.

To avoid this continuous gate signal is given but that $\uparrow$ power loss & also may saturate pulse T_{max}

We get max^m output v_g when its uncontrolled

$$(V_o)_{max} = (V_s)_{max} = \frac{V_m}{\sqrt{2}}$$

(189)


$$(I_{or})_{max} = I_{ss} = \frac{(V_o)_{max}}{|Z|}$$


$$|Z| = \sqrt{R^2 + (\omega L)^2}$$

NOTE

If pulse gate signal is given to AC v_g controller with inductive load, then it may behave as half wave rectifier because of one of the SCRs fails to turn-on due to the absence of gate signal at that instant. To avoid this problem we can give either continuous gate signal or high frequency gate signal.

c) Two stage AC v_g controller -

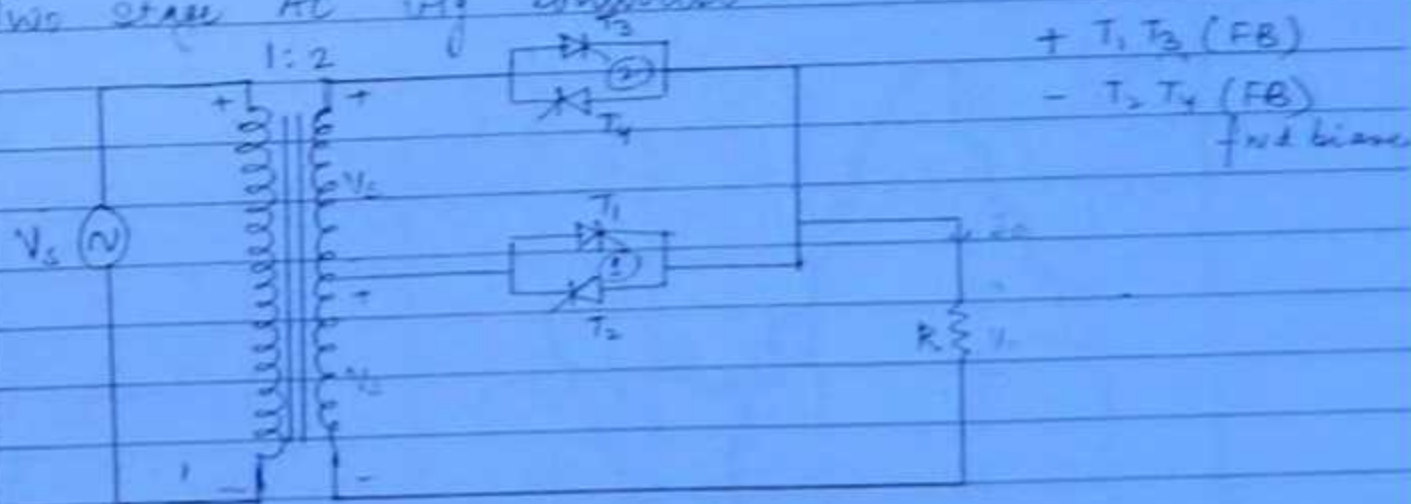

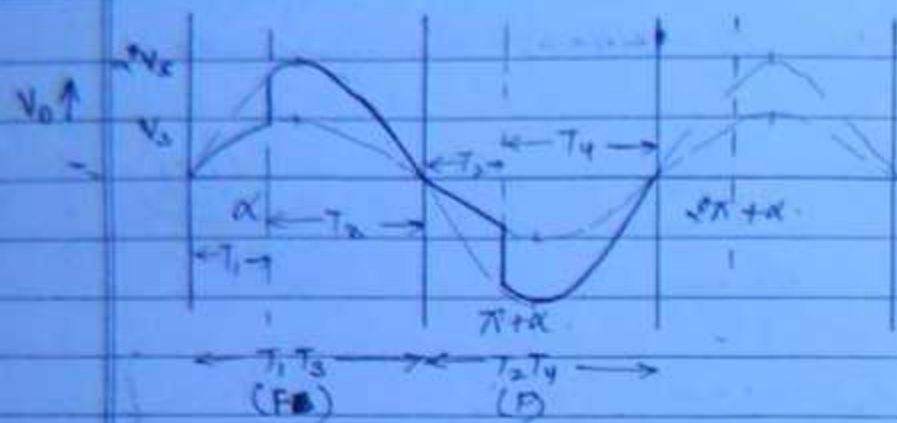


(90)

- (*) Since waveform is approaching sine wave, the smoothness $\uparrow$ with no. of stages
Thus harmonic distortion $\downarrow$.

$$V_{ox} = \left\{ \frac{1}{\pi} \left[\int_0^{\alpha} V_m^2 \sin^2 \omega t \, d(\omega t) + \int_{\alpha}^{\pi} 4V_m^2 \sin^2 \omega t \, d(\omega t) \right] \right\}^{\frac{1}{2}}$$


$$= \frac{V_m}{\sqrt{2}\pi} \left\{ \left[\alpha - \frac{1}{2} \sin 2\alpha \right] + 4 \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right] \right\}$$

d) Multistage Regulation -

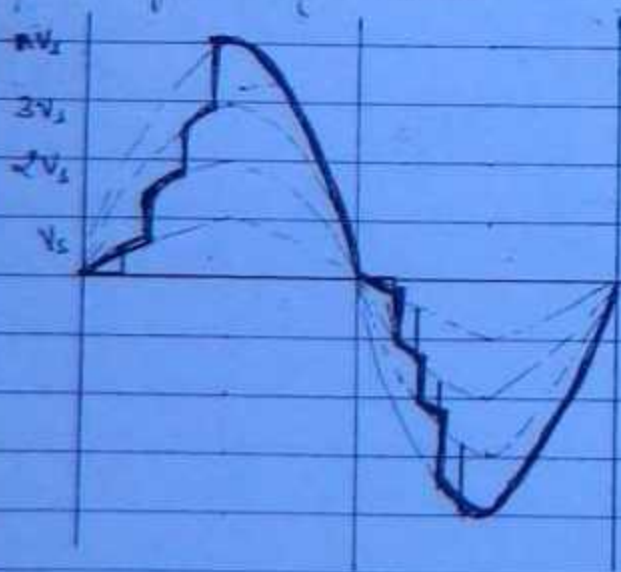

II Integral Cycle Control (ON/OFF)



(91)

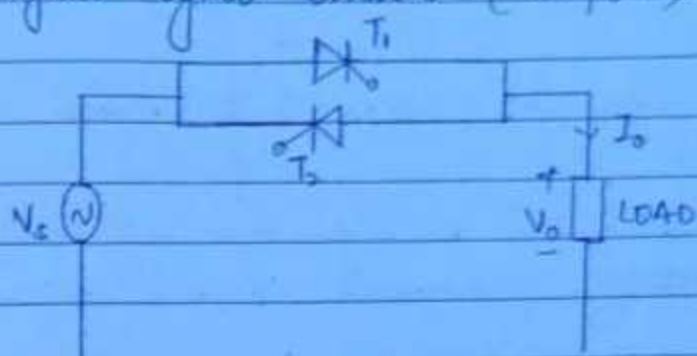

m cycles (ON) [$m=3$]
 n cycles (OFF) [$n=2$]

$I_g (0, 2\pi, 4\pi, \cancel{6\pi}, \cancel{8\pi}, 10\pi, 12\pi, 14\pi, \cancel{16\pi}, \cancel{18\pi}, \dots)$

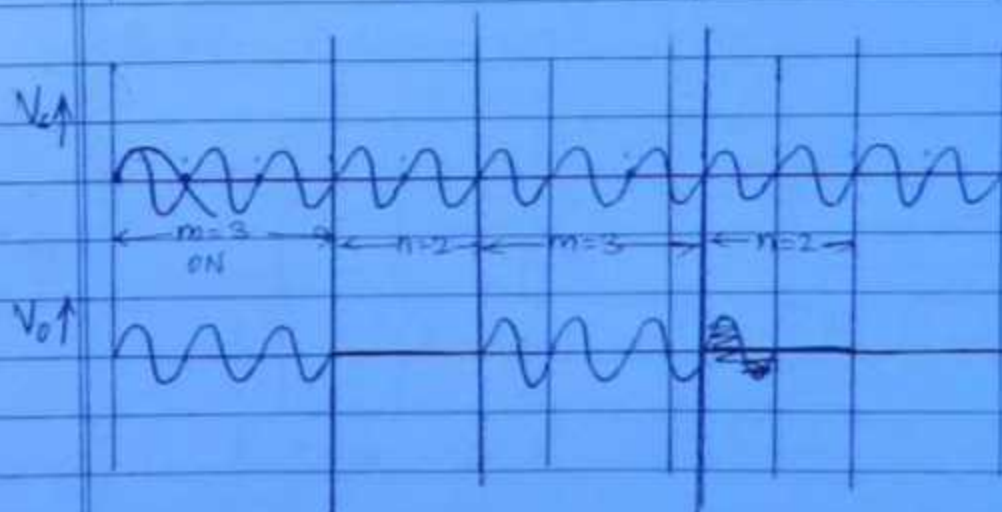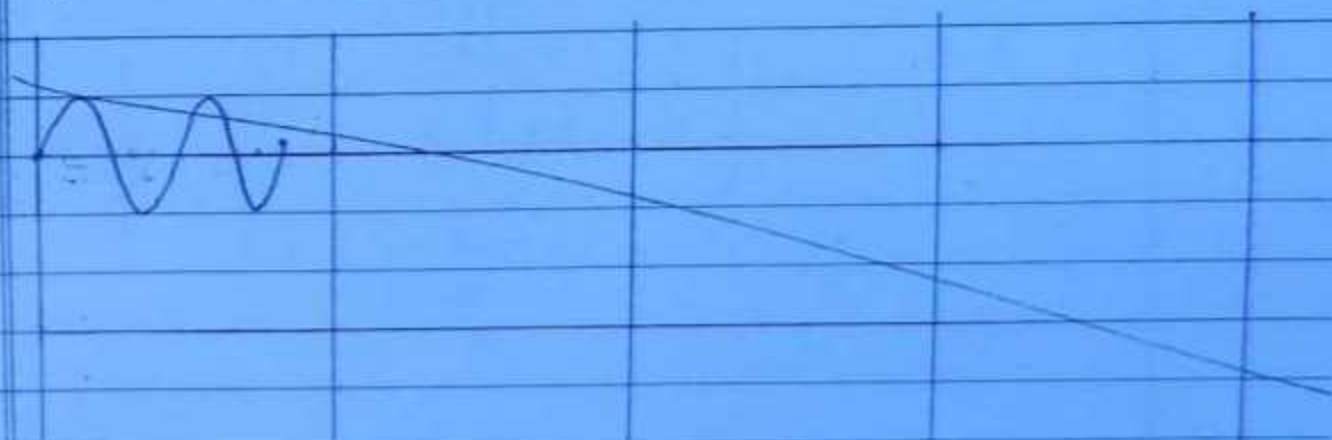$I_g (\pi, 3\pi, 5\pi, \cancel{7\pi}, \cancel{9\pi}, 11\pi, 13\pi, 15\pi, \cancel{17\pi}, \cancel{19\pi}, \dots)$



$$V_{or} = V_{cr} \left(\frac{m}{m+n} \right)^{1/2}$$

$$V_{or} = \sqrt{k} V_{cr} \quad \text{when} \quad k = \frac{m}{m+n}$$

Applications --

(92)

It can be used for AC loads with ~~low~~^{high} time constant.

eg. It can be used for a big size of motor with high MOI & mech time constant.

Limitations --

We cannot get wide range of control i.e. control is limited.

CYCLOCONVERTER


(93)

Fixed AC $\rightarrow$ Variable AC
 $(V_s, f_s) \rightarrow (V_o, f_o)$


$f_o < f_s \Rightarrow$ step-down cycloconverter

$f_o > f_s \Rightarrow$ step-up cycloconverter

Mid-Point Cycloconverter -

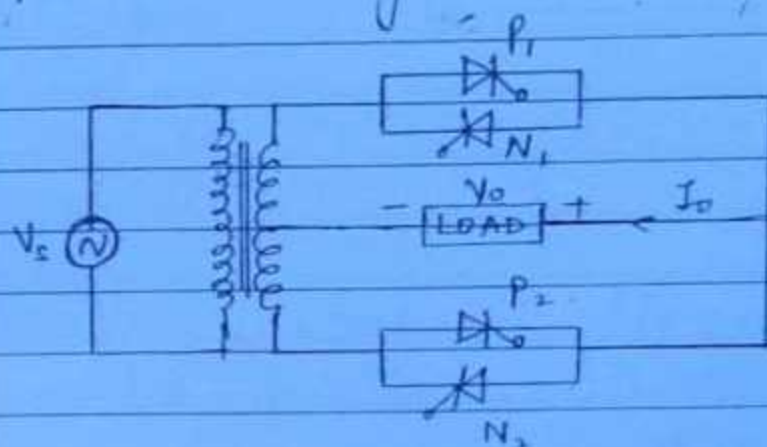

Bridge Cycloconverter

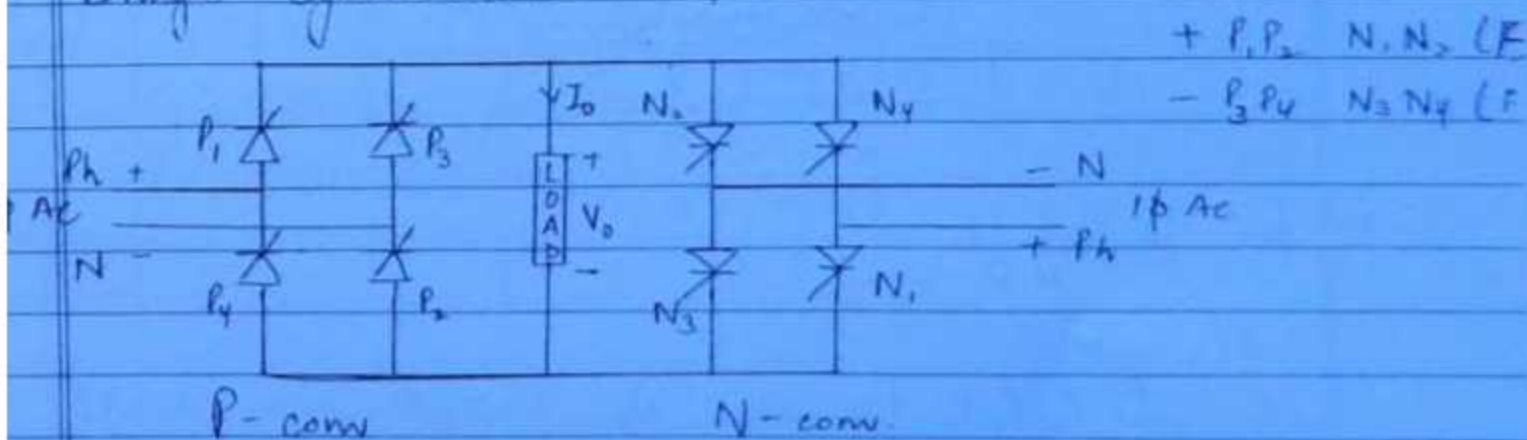

Step down cycloconverter ($f_o < f_s$)
let $f_o = \frac{1}{3} f_s$ $\therefore T_o = \frac{3}{8} T_s$

let $f_0 = \frac{1}{3} f$

$$\frac{V_c}{V_o} = \frac{V_s}{V_o} T_s$$

Here only frequency is varied α is kept 0 but if variation in both V_o & f_o is required, with this scheme vary α

(195)

R-load -


$$V_{oa} = \frac{V_m}{\sqrt{\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{\frac{1}{2}}$$

RL-load -

$$V_{or} = \frac{V_m}{\sqrt{\pi}} \left[(\pi - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\phi) \right]$$

Step Up Cycloconverter - ($f_o > f_s$)

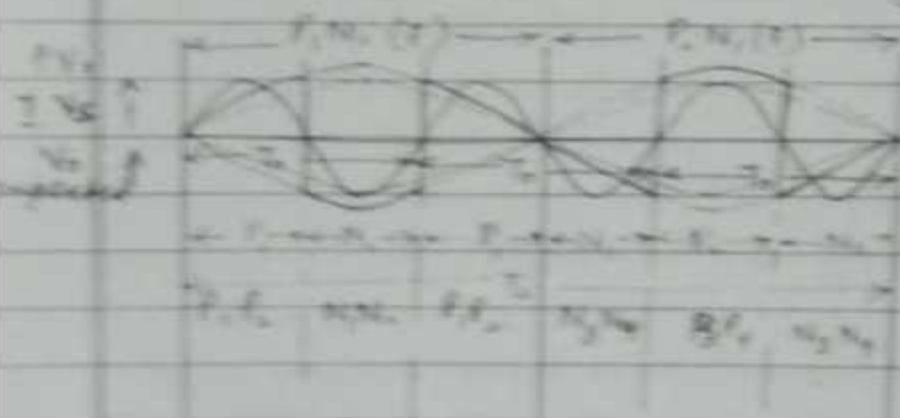Let $f_o = 3f_s$ $\therefore T_o = \frac{1}{3} T_s$ $\therefore T_o = 3 T_s$



- Load commutation is required in step up cycloconverters
- Harmonic distortion is more in cycloconverters than half wave rectifier


Applications -

(196)

Its used for high speed power, low speed and reversible AC drives
eg in S.F. I.M for controlling speed.

AC DRIVES -


1. Stator voltage control of I.M -

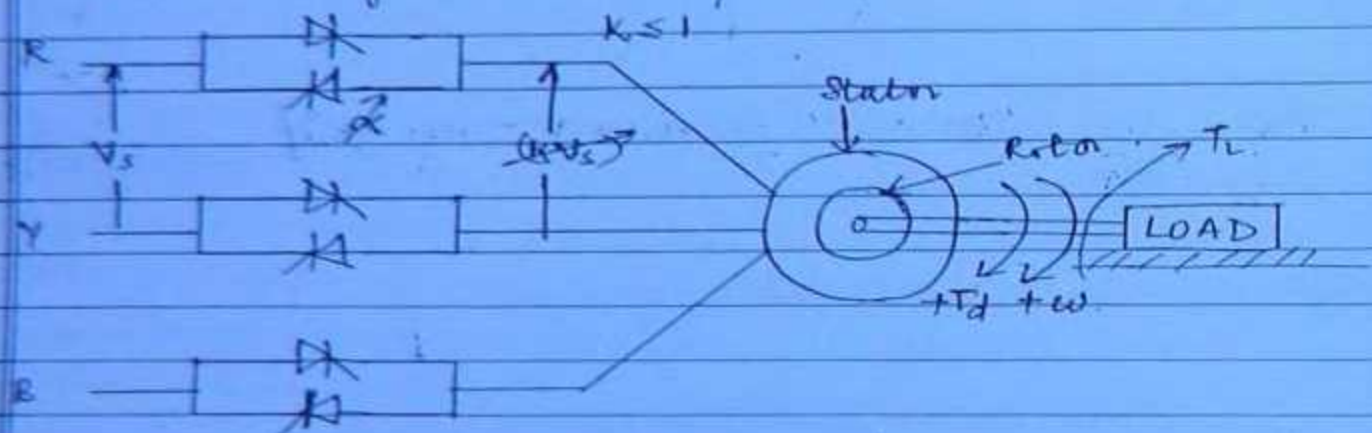

At starting $T_d > T_L$ $\omega \uparrow$

After reaching steady state speed $T_d = T_L$

$T_d < T_L$ $\omega \downarrow$

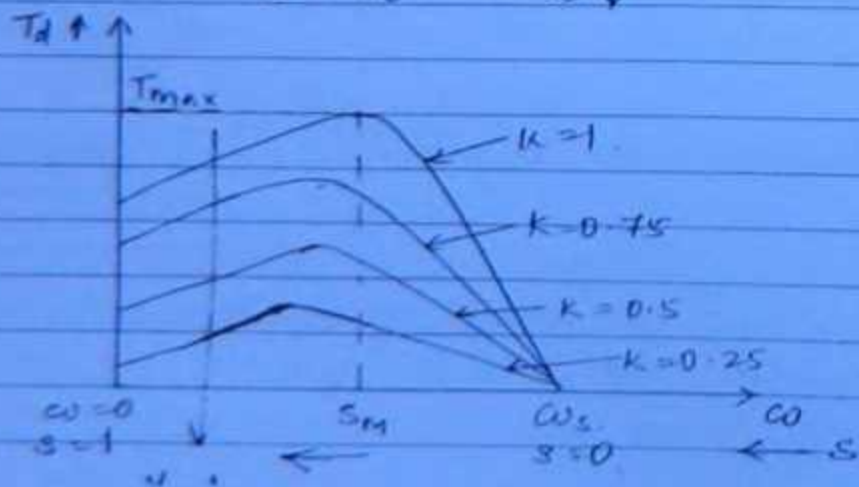

$$T_d = \frac{3}{\omega_s} \frac{(KV_s)^2 R'_s / s}{\left(R_s + \frac{R'_s}{s}\right)^2 + (X_s + X'_s)^2} \quad (197)$$

$$s = \frac{N_s - N}{N_s} = \frac{\omega_s - \omega}{\omega_s}$$

Mech. Loads -

1. $T_L = \text{const.}$
2. $T_L \propto \omega$
3. $T_L \propto \omega^2$
4. $T_L \propto \frac{1}{\omega}$

! $\Rightarrow$ Check whether constant load torque is suitable or not suitable for the given electrical drive

Let us consider the m/c is moving at rated speed

$$\therefore T_d = T_L$$

$$(KV_s) \downarrow, T_d \downarrow \quad (T_d < T_L)$$

$$\therefore \omega \downarrow, s \uparrow, I \uparrow \therefore T_d \uparrow$$

Here m/c will slow down if $\uparrow$ the T_d until it balances the constant T_L .

Here the m/c draws more current from the supply mains in order to $\uparrow$ the T_d for balancing the T_L . $\therefore$ m/c gets overheating

Hence this mech. load is not suitable for the drive.

$$T_e \propto \omega^2$$

$$(kV_e) \downarrow \quad T_d \downarrow \quad (T_d < T_e)$$

$$\omega \downarrow \quad T_e \downarrow$$

(198)

Here speed will slow down until the decreased T_e balances the T_d . Here the m/c will not draw more ^{current from} supply line.

This type of mech load is suitable for given electrical drive.

Applications -

Used where $T_e \propto \omega^2$

eg fan loads, reciprocating pumps, compressors etc.

2. Stator Frequency Control of I.M -

(a) V control ($\omega < \omega_n$)

To maintain const flux we go for V/f control.

If ϕ is not maintained const

overfluxing occurs

$\rightarrow I_m \uparrow$
 $\rightarrow$ harmonic distortion $\uparrow$
 $\rightarrow$ losses $\uparrow$
 $\rightarrow pf \downarrow$

$\rightarrow$ We can achieve V/f control by using cycloconverters but its used only for high power low speed. With cycloconverters the maximum speed is limited to 40% of rated speed.

- We can also realise the V/f control by using PWM inverters. With PWM inverters -
- smooth rotation is possible and some lower order harmonics can be eliminated.

(199)

(b) Constant V (for $\omega > \omega_n$)

At rated speed $V_s = V_{rated}$

$$V_s \propto \phi f \uparrow$$


$$N \uparrow \quad f \uparrow \quad \therefore \phi \downarrow$$

Now as $f \uparrow \Rightarrow \phi \downarrow$ because we cannot ~~exceed~~ $\uparrow$ the stator vlg beyond rated value. $\therefore$ stator vlg is fixed at rated value in this method.


We can realise this method by:

→ Square Wave Inverter

→ PWM Inverter

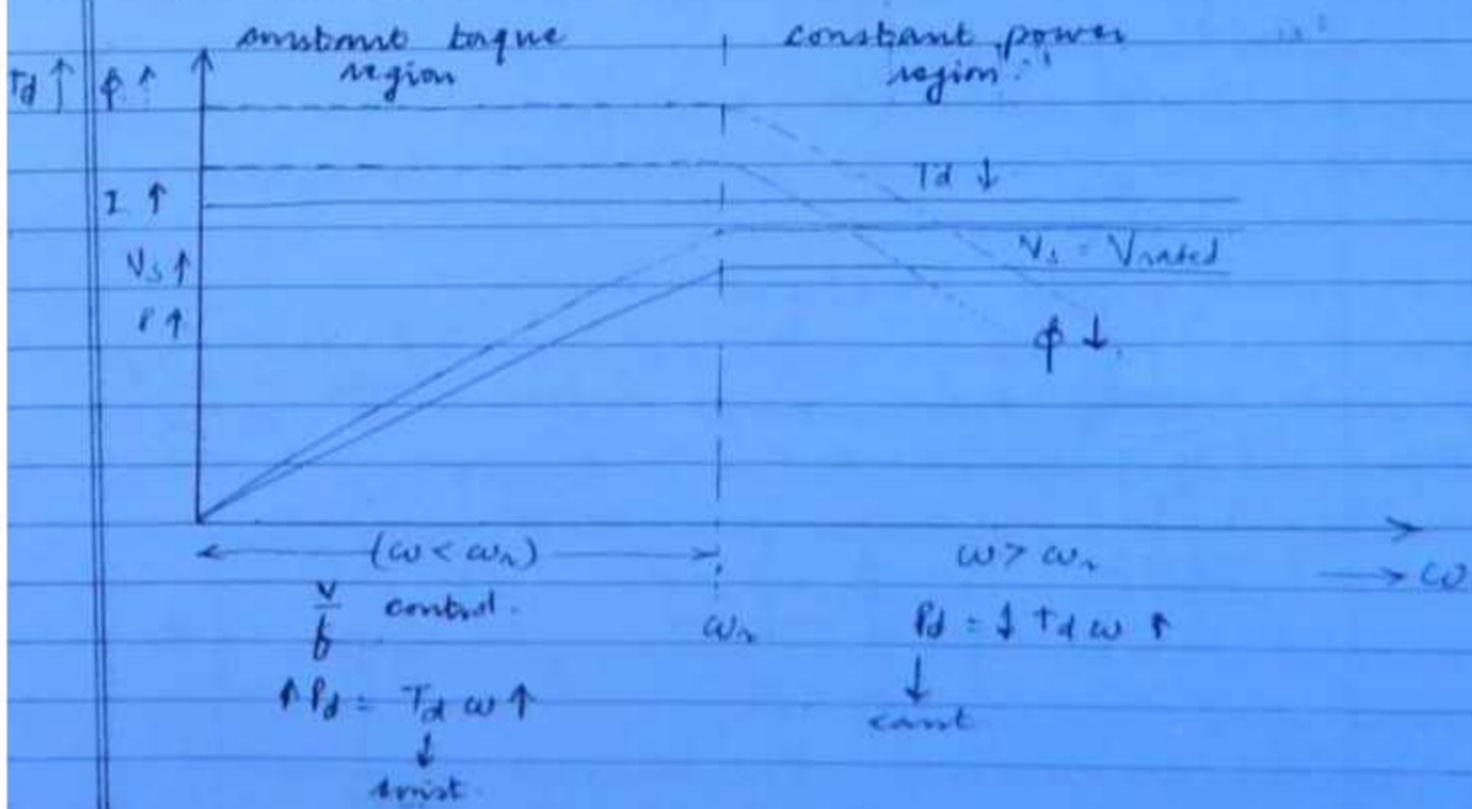

Rotor Resistance Control -

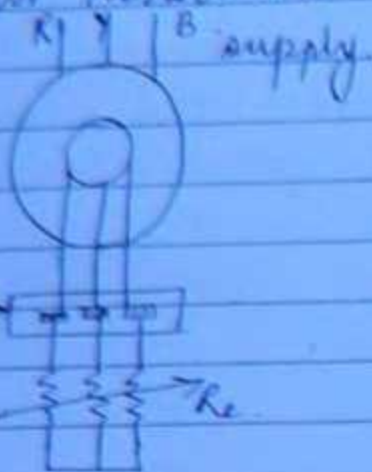


$$\text{Total Cu loss} = s I_g^2 R_r$$

$$3 I_N^2 [R_r + \uparrow R_e] = \uparrow s I_g^2 R_r$$

$$s \uparrow \therefore \omega \downarrow$$


200

Chopper Controlled Resistance -

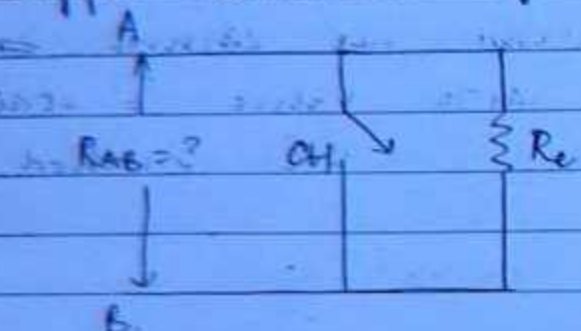

$$R_{AB} = R_e \left(\frac{T_{OFF}}{T} \right)$$

$$R_{AB} = R_e (1 - \alpha)$$

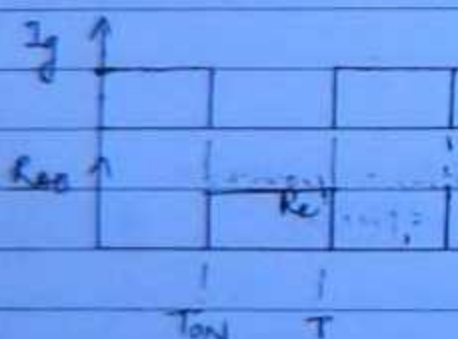

Stator Rotor Resistance Control



$$f_0 = 6.5 \text{ sfc}$$


$$s \downarrow \therefore f_0 \downarrow$$

$$\text{ripple in } I_d \uparrow$$

$$\therefore (SR) \uparrow$$

$$(SR) \uparrow$$

$$I_d$$

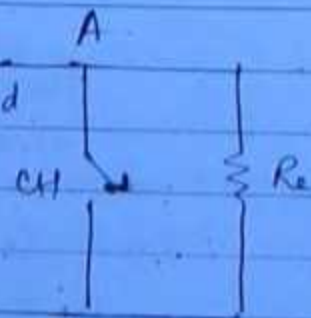

200

Q What is the effective resistance connected in series per phase with the rotor wdg per phase for the above system? (20)

$$\text{Total Cu loss} = s P_g$$

$$3 I_r^2 R_r + I_d^2 R_e (1 - \alpha) = s P_g$$

$$I_{cr} = I_o \sqrt{\frac{2}{3}} \Rightarrow I_r = I_d \sqrt{\frac{2}{3}}$$

$$I_d = I_r \sqrt{\frac{3}{2}}$$

$$\Rightarrow 3 I_r^2 R_r + \frac{3}{2} I_r^2 R_e (1 - \alpha) = s P_g$$

$$\Rightarrow 3 I_r^2 [R_r + 0.5 R_e (1 - \alpha)] = s P_g$$

$$\propto 3 I_r^2 [R_r + (C)]$$


eff resistance in series with rotor wdg per phase

This is not an efficient control cuz the slip power is dissipated in external resistance.

4. Slip Power Recovery

This is an efficient speed control method because the slip power can be utilised or given back to supply line.

a) Static Kramer Drive

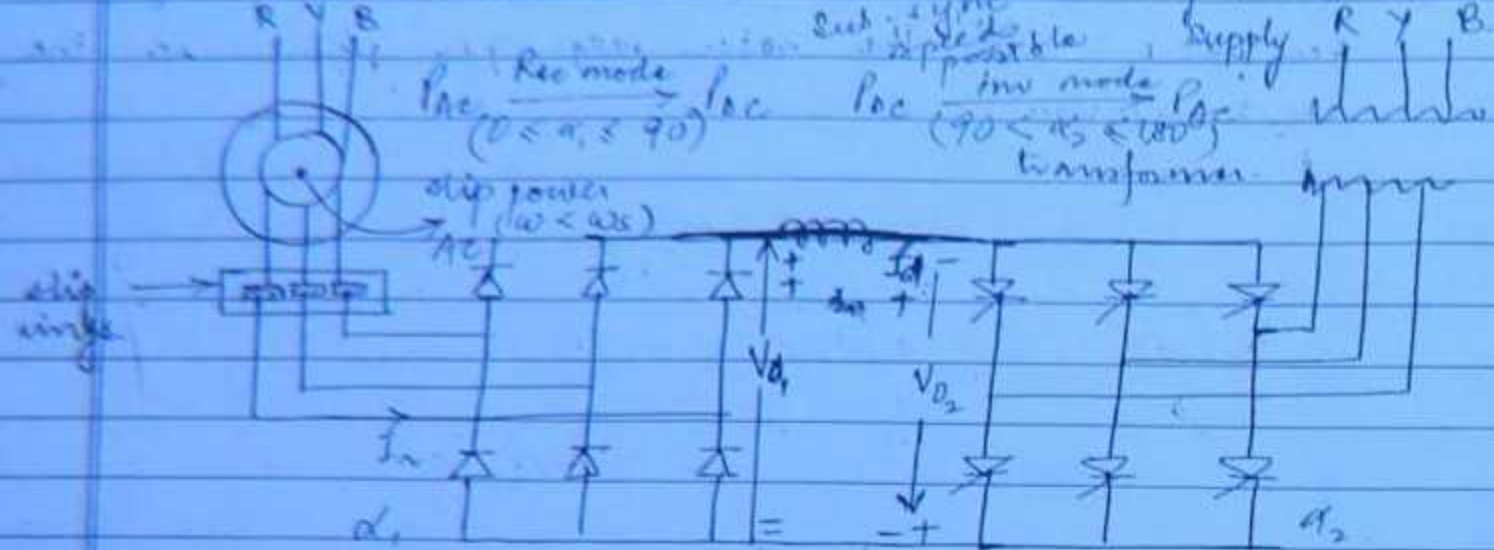

$\pm$ } Ref polarities of converter

(200)


$\pm$ } Actual polarities of converter.

$$V_d = \frac{3 V_{ML}}{\pi} \cos \alpha$$


$\alpha < 90^\circ$ $V_d +$ (Rec mode)

$\alpha > 90^\circ$ $V_d -$ (Inv mode)

b) Static Schenck Drive

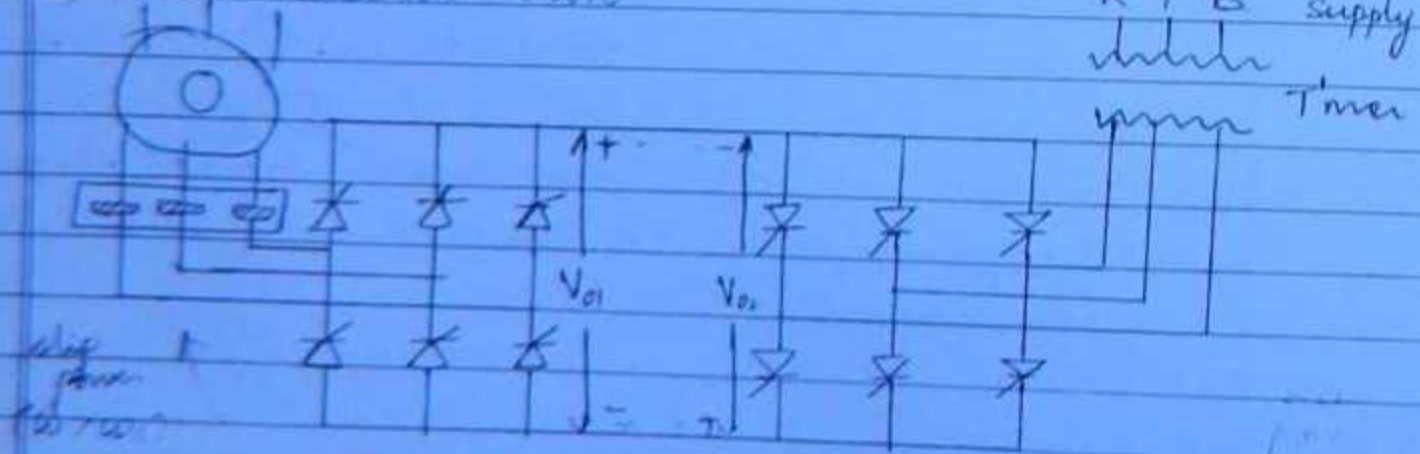

CWB chapter 5.

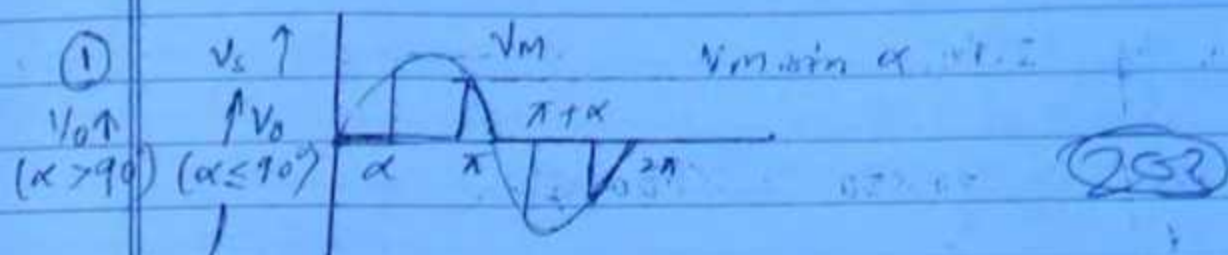

peak power = $\frac{V_m^2}{R} = \frac{(280\sqrt{2})^2}{R} = \frac{(280\sqrt{2})^2}{10}$

= 10580 W (d)

peak power $\Rightarrow \frac{(V_{m,avg} \alpha)^2}{R}$

② V_o is uncontrolled at $\alpha \leq \phi$

$\phi = \tan^{-1} \frac{\omega L}{R} \Rightarrow \phi = \tan^{-1} \frac{50}{50}$

= 45°

$0 \leq \alpha \leq 45^\circ$ (a)

③ ~~and~~ Per unit power = $\frac{P_o}{P_{max}}$

= $\frac{V_{or}^2/R}{V_{sr}^2/R}$

= $\left(\frac{V_{or}}{V_{sr}} \right)^2 = PF^2$

$PF = \sqrt{\text{per unit power}}$ (b)

Y control of I.M -

$$N_2 = \frac{100f}{f} = \frac{100 \times 50}{2} = 3000 \text{ rpm}$$

(204)

$$s = \frac{N_s - N_r}{N_s} = \frac{3000 - 2850}{3000}$$

$$s = 0.05$$


$N = ?$ at $\frac{1}{2} S_c$ $f = 90 \text{ Hz}$

$$N_2 = \frac{100 \times 90}{2} = 4500$$

$$0.025 = \frac{4500 - N_2'}{4500}$$

$$N_2' = 2890 \text{ rpm} \quad (c)$$

12. R_2 - in series with rotor

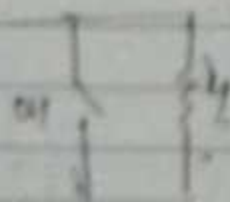

$$R_{eff} = R_2 + 0.5 R_1 (1 - \alpha)$$

$$= 2 + 0.5 \times 4 \left(1 - \frac{T_{off}}{T}\right)$$

$$= 2 + 0.5 \times 4 \left(1 - 4 \times 10^{-3} \times 9000\right)$$

$$= 18 \quad (c)$$

(14) PF at $\frac{1}{2} N_s$?

$$N_s = N_s$$

$$PF = \frac{V_o}{V_{max}}$$

At $\frac{1}{2} N_s$

$$PF = \frac{9}{\pi} \cos \alpha$$

$$V_o = I_L + I_o R_a$$

$$V_o = \frac{3 V_{mL} \cos \alpha}{\pi} = 60$$

$$\frac{3 V_{mL} \cos \alpha}{\pi} = \frac{440}{2}$$

$$\frac{3 \cdot 440 \sqrt{2} \cos \alpha}{\pi} = \frac{440}{2}$$

$$\cos \alpha = \frac{\pi}{2\sqrt{2}} \times \frac{1}{3}$$

$$PF = \frac{9}{\pi} \cos \alpha = \frac{1}{\sqrt{2}} = 0.354 \text{ (A)}$$

(15) As $\alpha \uparrow$ ripple $\uparrow$ smoothness $\downarrow$

At $\alpha \downarrow$ (smoothness of V_o waveform) $\uparrow$

$$\alpha \downarrow \quad V_o \uparrow \quad \omega \uparrow$$

high speed

(16) Regenerated power :


$$\begin{aligned}
 &= V_o I_o \\
 &= V_o (1 - \alpha) I_o \\
 &= 600 (1 - 0.7) 100 \\
 &= 18 \text{ kW (C)}
 \end{aligned}$$

TRENDS IN TRANSMISSION OF POWER


1. EHVAC

(206)

Features -

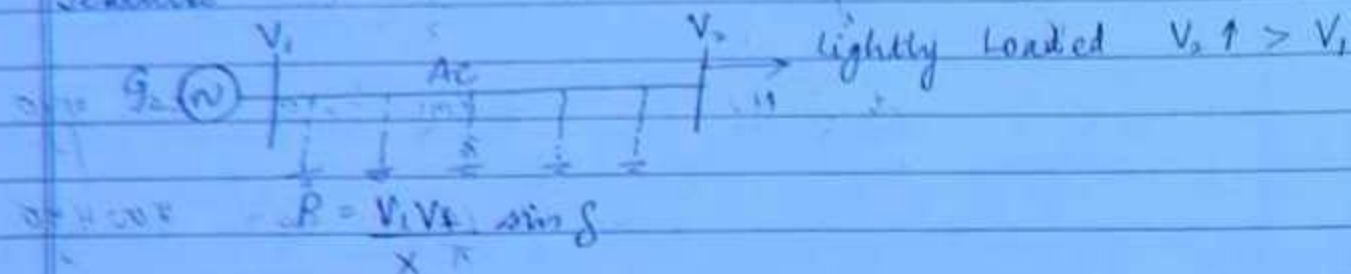

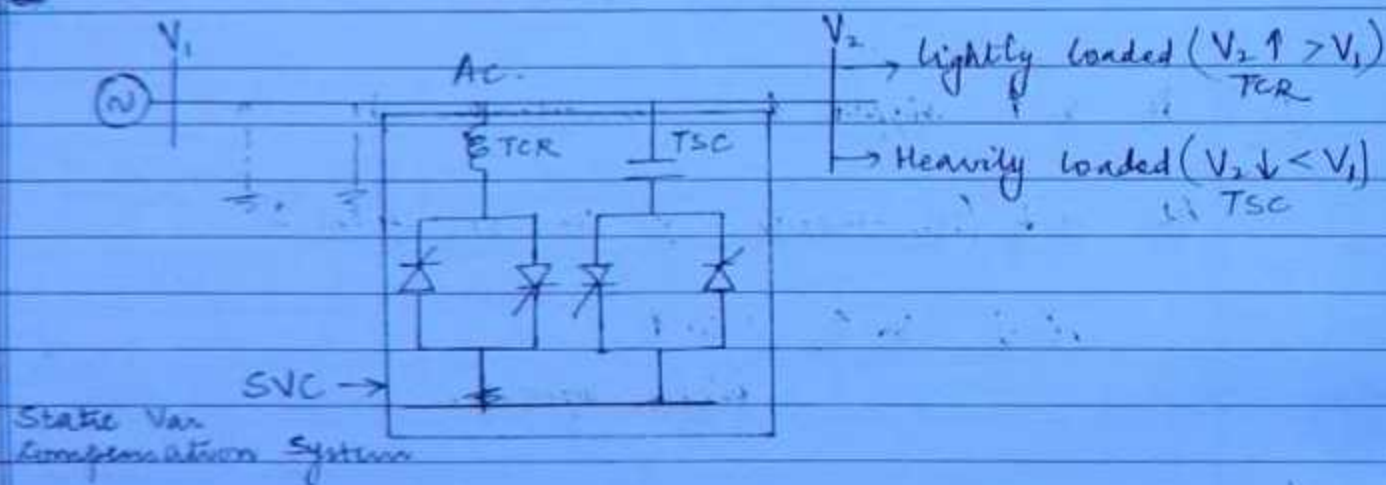- * $\rightarrow$ We cannot control the power flow magⁿ & dirⁿ quickly & easily



Thyristorised Controlled Reactor $\rightarrow$ TCR

Thyristorised 'Switched' Capacitance $\rightarrow$ TSC

- * $\rightarrow$ There is continuous variation of reactive power flow in the line & hence responsible for voltage fluctuations & additional power loss
- * $\rightarrow$ Intermediate substations are installed in the AC line for every 200-300 kms to compensate the


reactive power as per the requirement of reactive power in the line.


(207)

* → Other problems in the AC line is

→ Skin Effect

→ Corona loss

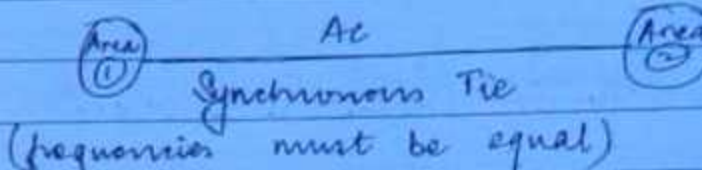* → 
(frequencies must be equal)

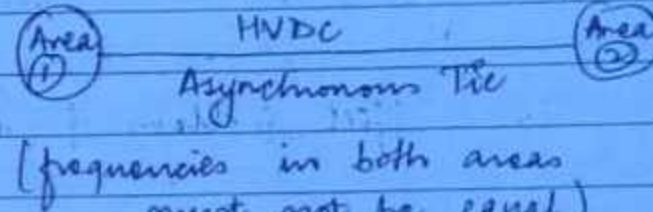
(frequencies in both areas must not be equal)

* → System disturbance in one of the area leads to power swings. If the power swings are unstable that may lead to cascaded tripping of alternators (if protection system fails)

* → With AC interconnection frequency disturbance is carried forward to other areas.

* → If multiple number of independent areas is interconnected by AC lines then the fault level of the system increases.

2. HVDC

* HVDC is economical to transmit large amount of power over long distance.

(208)

* Advantages -


1. The power flow magnitude & direction can be quickly and easily controlled.
2. The transient stability limit is improved.
3. We can fast clear the fault in HVDC line.
4. There is no Skin Effect problem & Corona loss is reduced.
5. HVDC can utilise Earth for its return path.
6. The phase to phase clearance, phase to ground clearance & tower height requirement is lesser in HVDC line.
7. Power handling capacity of a Bipolar HVDC line is almost twice that of 3 ϕ single circuit AC line.
8. We can interconnect independent areas at different frequencies because it is an asynchronous tie.
9. Frequency disturbance is not transferred to other independent areas, with HVDC interconnection.
10. If multiple no. of independent areas is

i interconnected by HVDC line the fault level of the system will not substantially increase (209)

ii HVDC is used for underground or submarine cables even for short distance because there is no continuous charging of DC cables.

* Types of HVDC

BIPOLAR

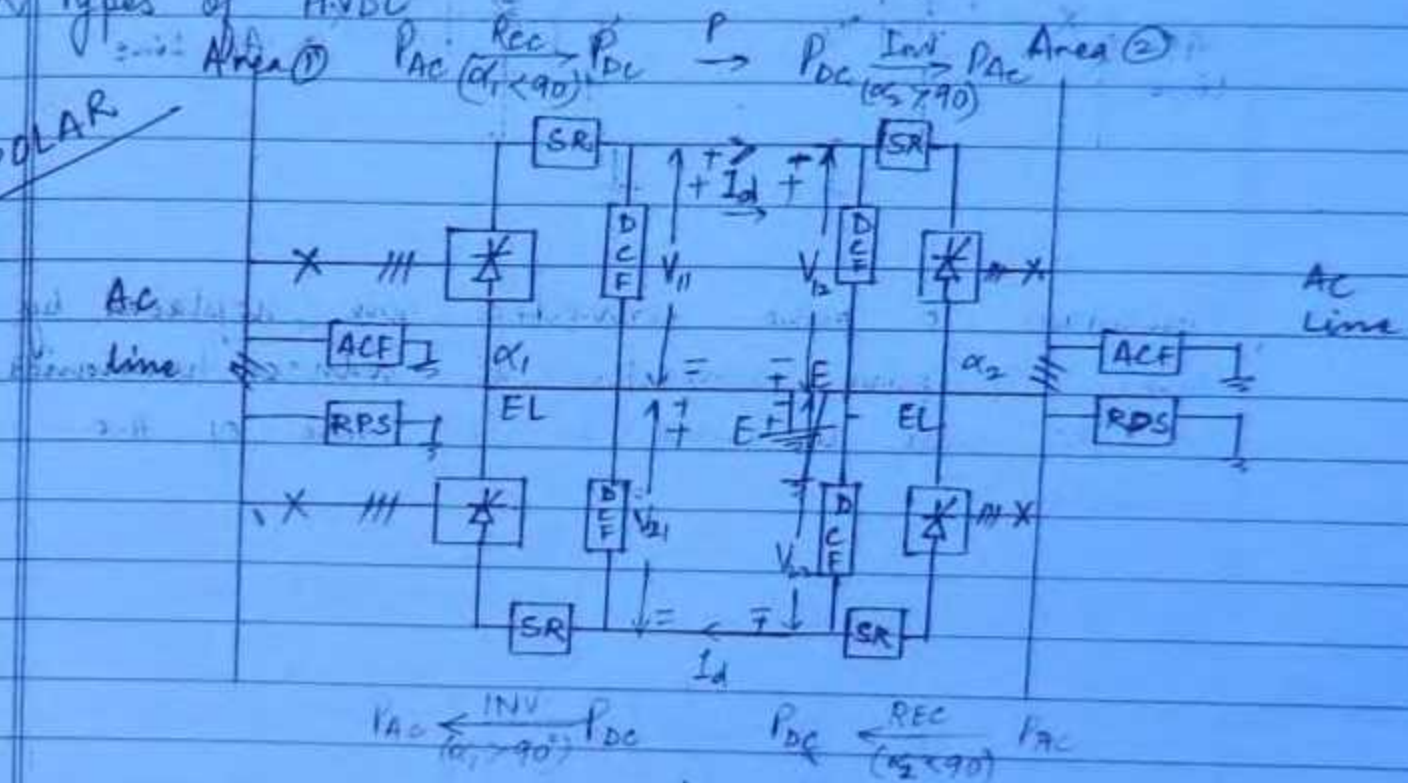

Smoothing Reactor (SR)

Used for smoothing

DC Filter (DCF)

Reduces harmonics on DC side of the converter (output side)

AC Filter (ACF)

Reduces harmonics on AC side of the converter


Reactive Power Source (RPS)

(216)

to compensate the reactive power required for converters

MONOPOLAR Area ①


Area ②

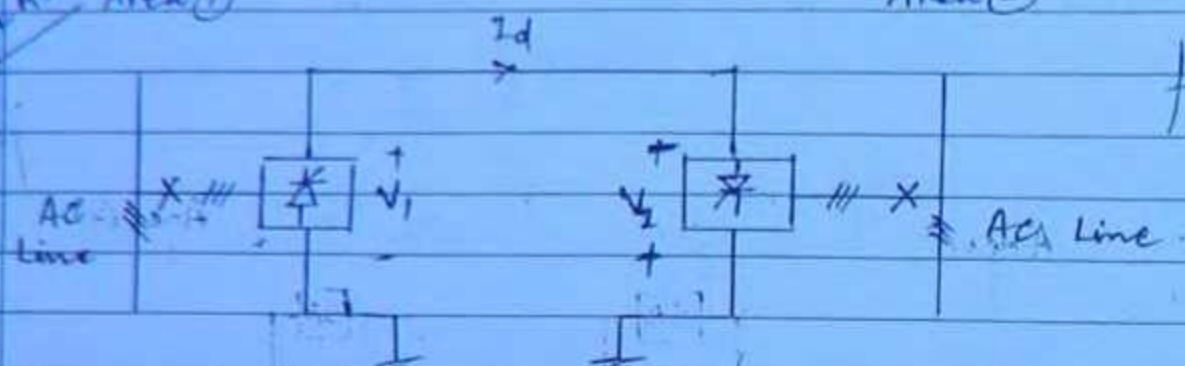




filters are understood

Nowadays 6 pulse converters are replaced by 12 pulse converters to reduce harmonics on AC side as well as DC side of the converter.

12 Pulse Converters -

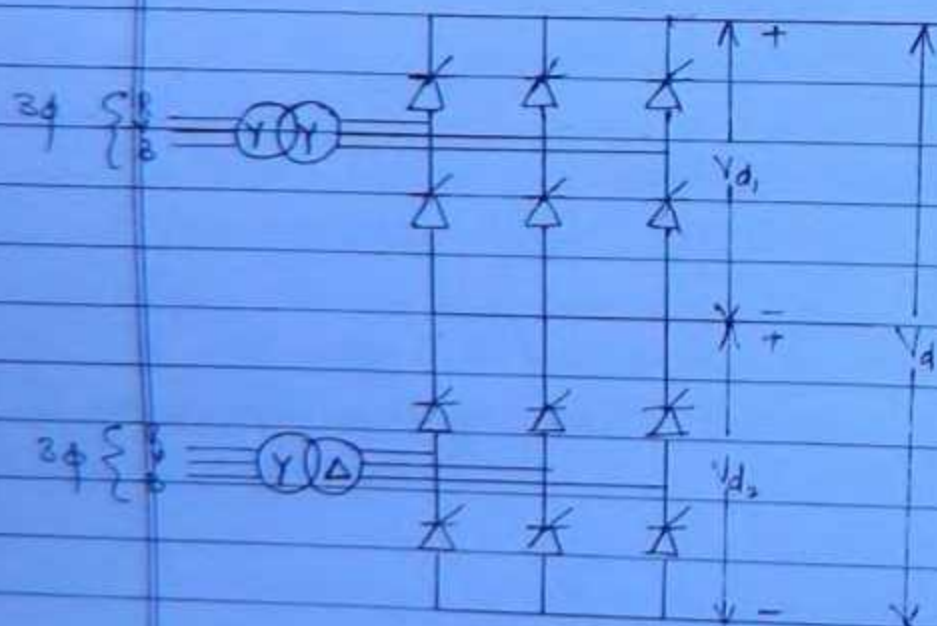

211

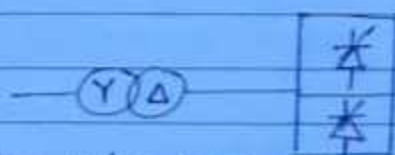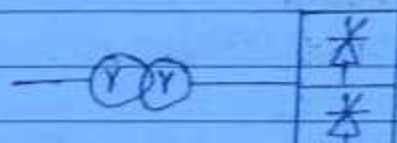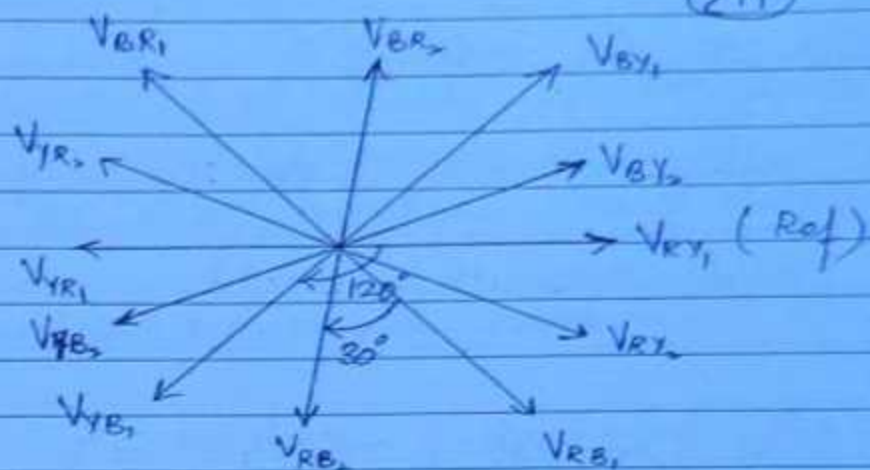

$$V_{RY1} = V_{ML} \sin \omega t$$

$$V_{RY2} = V_{ML} \sin(\omega t - 30^\circ)$$

$$V_{RY} = V_{RY1} + V_{RY2}$$

$$= V_{ML} [\sin \omega t + \sin(\omega t - 30^\circ)]$$

$$= V_{ML} [\sin(\omega t - 15^\circ)]$$

* Harmonics on AC side of δ

m pulse converter $\rightarrow mk \pm 1$

2 pulse converter $\rightarrow 2k \pm 1$
 $= 3, 5, 7, 9, 11, \dots$

6 pulse converter $\rightarrow 6k \pm 1$
 $= 5, 7, 11, 13, 17, 19, \dots$

12 pulse converter $\rightarrow 12k \pm 1$
 $= 11, 13, 23, 25, \dots$

* Harmonics on DC side of δ

m pulse converter $\rightarrow mk$

2 pulse converter $\rightarrow 2k$
 $= 2, 4, 6, 8, 10, 12, \dots$


6 pulse converter $\rightarrow 6k$
 $= 6, 12, 18, \dots$


12 pulse converter $\rightarrow 12k$
 $= 12, 24, 36, \dots$

- * SMPS provides good quality of DC power supply required for some applications like ICs, digital circuits & other sensitive circuit boards.
- * SMPS operates on chopper principle.
- * At very high switching frequency, the ripple is almost reduced.
- * At such a high frequency we can reduce the size of the filter as well as transformer.
- * In SMPS the transistor operates in the switched mode (Cut-off region is used for OFF state & Saturation region for ON state).
- * SMPS is more efficient & compact in size compared to linear power supplies. In linear power supplies transistor operates in the active region & hence Power loss is higher.

Types of SMPS -


1. The Buck Converter

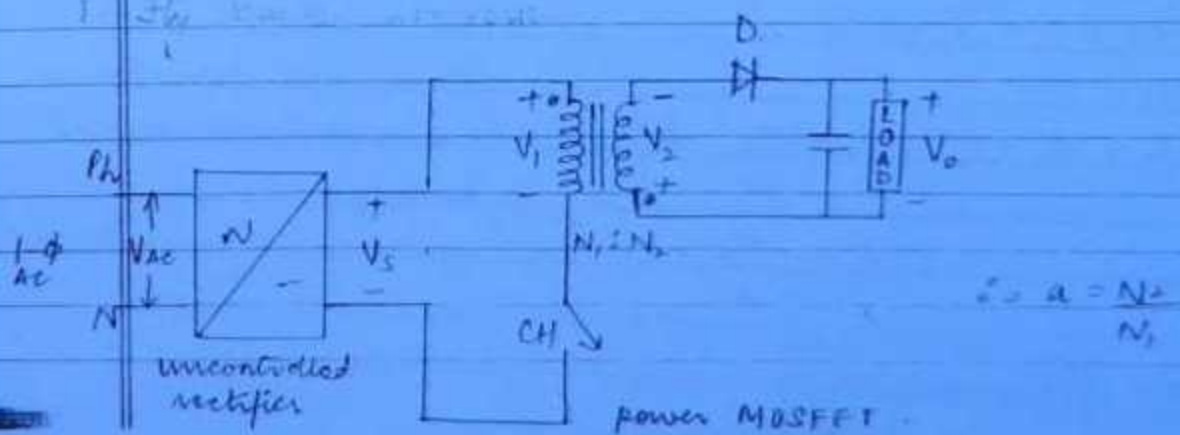

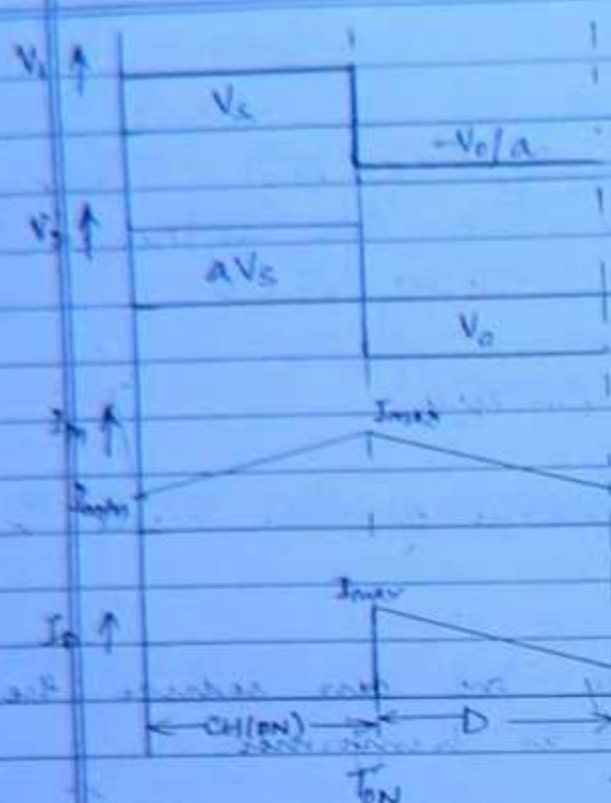

214

$$\alpha = \frac{T_{ON}}{T}$$

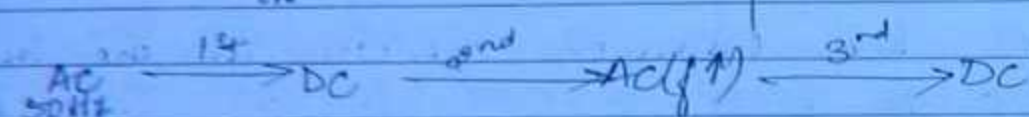

① $0 \leq t \leq T_{ON}$

CH $\rightarrow$ ON $V_1 = V_s$
 D $\rightarrow$ OFF $V_2 = \frac{N_2}{N_1} V_1$

$$V_2 = a V_1$$

Transformer stores energy $\therefore I_m \uparrow$
 CH is in ON state
 D is RD $\therefore I_D = 0$

② $T_{ON} \leq t \leq T$

CH $\rightarrow$ OFF $V_2 = -V_o$
 D $\rightarrow$ ON $V_1 = \frac{N_1}{N_2} V_2$
 $V_1 = -\frac{V_o}{a}$

Here the transformer releases the stored energy $\therefore I_m \downarrow$

Avg. $\Rightarrow V_o = a \frac{\alpha V_s}{1-\alpha}$

CWB chapter 7.

$$(4) \quad V_o = \frac{\alpha a \cdot V_s}{1 - \alpha}$$

(215)

$$= \frac{\alpha N_s}{N_1} \frac{T_{on}}{T_{off}} \quad (c)$$

Peak Forward Blocking Voltage of chopper module

$$= \frac{V_s + V_o}{a}$$

$$(3) \quad \text{PFB v/g} = \frac{V_s + V_o}{a}$$

$$= V_s + V_s \left(\frac{\alpha}{1 - \alpha} \right)$$

$$= V_s \left[1 + \frac{\alpha}{1 - \alpha} \right] = 115 \sqrt{2} \left[1 + \frac{0.3}{1 - 0.3} \right]$$

$$= 232.34 \text{ V} \quad (a)$$

Output dc v/g of front-end rectifier

→ with v/g doubling = V_m → peak AC i/p v/g


→ with v/g doubling = αV_m

(1) mark the highest freq given

2. Push-pull converter

216

3. Full Bridge Type -

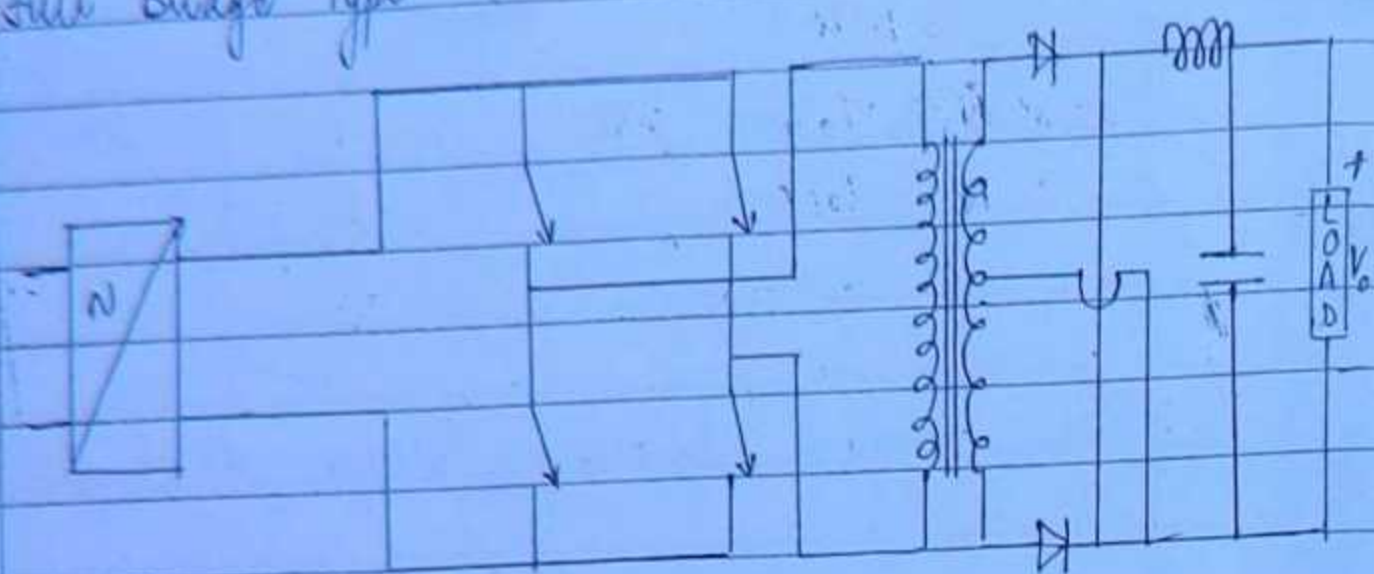

Remembering Formulas -

(217)

R_L - Load -

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha) \rightarrow 1 \text{ pulse}$$

cont. $V_o \propto \cos \alpha$
discont. $V_o \propto (1 + \cos \alpha)$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha) \rightarrow 2 \text{ pulse}$$

$$V_o = \frac{V_{mph}}{2\pi/3} [1 + \cos(\alpha + 30^\circ)] \rightarrow (\alpha > 30^\circ) \text{ 3 pulse.}$$

On 3 pulse
 $\rightarrow \alpha < 30^\circ$ cont.
 $\rightarrow \alpha > 30^\circ$ discont.

$$V_o = \frac{V_{mph}}{2\pi/6} [1 + \cos(\alpha + 60^\circ)] \rightarrow (\alpha > 60^\circ)$$

On 6 pulse.
 $\rightarrow \alpha < 60^\circ$ cont.
 $\rightarrow \alpha > 60^\circ$ discont.

$$V_o = \frac{V_{mL}}{\pi/6} [1 + \cos(\alpha + 60^\circ)] \rightarrow (\alpha > 60^\circ)$$